

Aero Has Short Wave Radio Telephone Transmitter

Surprising Distances Covered with Low Power
Sets Under Average Conditions

ATTRACTED to a recently opened new field of radio telephony on the higher frequencies, many broadcast listeners and those experimentally inclined are beginning to exhibit a great deal of interest in short wave radio phone transmission. Much of this interest is being fostered because of the fact the government has recently released a few short wave channels on which transmission by voice is allowed. In the past there were restrictions on voice transmission on the lower waves and all of the work which has been carried on has been by telegraphic means rather than telephonic.

Covers Great Distances

This field is naturally attractive because of the remarkable records that are being established by amateurs all over the world. To supply the demand created by this growing enthusiasm, several well known parts manufacturers have co-operated in the design of a short wave radio phone transmitter, which may be built for approximately the same cost and with the same facility as a good broadcast receiver. While this design is necessarily of a low power type, it has been repeatedly demonstrated that low power is sufficient to carry on conversation over surprising distances.

Built on Two Decks

Referring to the photograph in Figure 1, it will be noted that the manner of construction in this particular transmitter permits the isolation of all parts carrying radio frequency currents to the upper shelf, while all of the circuits associated with the power or voice currents are on the lower deck. This form of construction insures that the masses of metal contained in power devices such as transformers, condensers and other metallic objects will

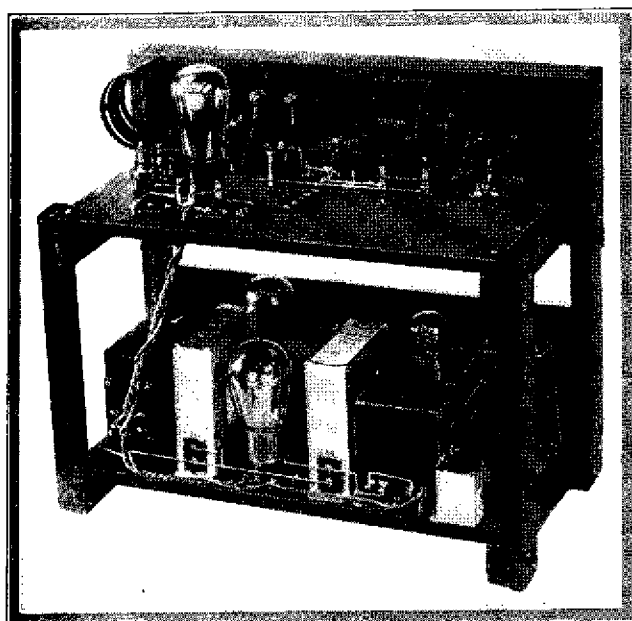


Figure 1. In this illustration is shown the rear view of the Aero short wave phone transmitter, which is built on two shelves, the power apparatus being on the lower and the actual transmitter itself on the upper

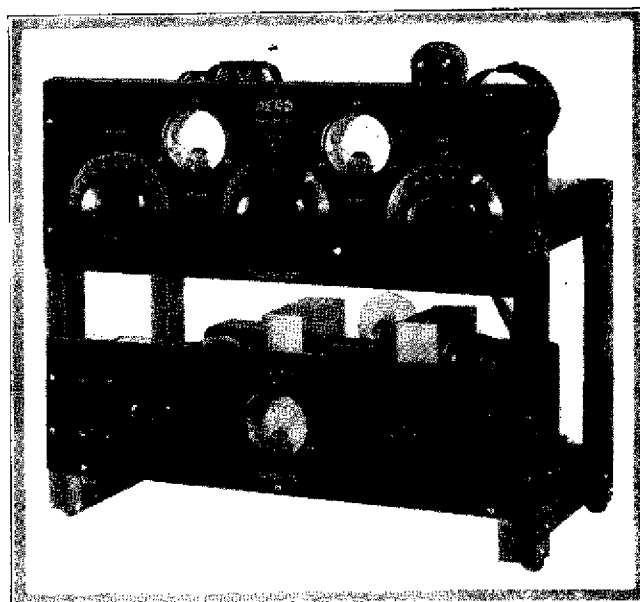


Figure 2. All controls of the short wave transmitter described in this article are grouped on the upper front panel so that tuning of the set is quite simple. The modulation indicator is located at the center of the lower panel

not be in the field of any of the radio frequency coils introducing losses therein. Corresponding to the arrangement of the circuits in decks, the front controls are also grouped. Thus on the upper front panel the reader will find controls for the tuning condensers and the antenna current meter, together with the plate current meter for the oscillator tube. On the lower deck will be found the plate current meter for the modulator tubes, the modulator C bias control, switch for changing from telegraphy to telephony and the necessary binding posts for the key, microphone and battery.

The circuit diagram is illustrated in Figure 3. The radio frequency portion of the circuit (on the upper deck) is the well known tuned-grid tuned-plate circuit that has been used for several years by amateurs, this preference being based on the fact that it is perhaps the simplest of all transmission circuits to tune and control. The only point of difference which might be noticed is the fact that where in most of the tuned-grid tuned-plate circuits the plate feed is in shunt, in this particular form of transmitter the series feed for the plate has been adopted in order to simplify the circuit and to prevent losses previously encountered in the choke coil when using shunt feed. On account of the high voltages developed between the plate coil and the ground by this method, it is necessary to use two condensers in series as a radio frequency bypass, these condensers being of .0005 mfd capacity.

The Power Supply

The power supply consists of a Silver-Marshall 328 transformer, which supplies the plate current, as well as lighting the filaments of the oscillator and modulator tubes. In order to secure a direct current, which is necessary for telephone operation, the high voltage of the 328 transformer is rectified by means of a No. 2721

(This transmitter constructed, tested and all illustrations made in our laboratory)

This manual is provided FREE OF CHARGE from the “BoatAnchor Manual Archive” as a service to the Boatanchor community.

It was uploaded by someone who wanted to help you repair and maintain your equipment.

If you paid anyone other than BAMA for this manual, you paid someone who is making a profit from the free labor of others without asking their permission.

You may pass on copies of this manual to anyone who needs it. But do it without charge.

Thousands of files are available without charge from BAMA. Visit us at <http://bama.sbc.edu>

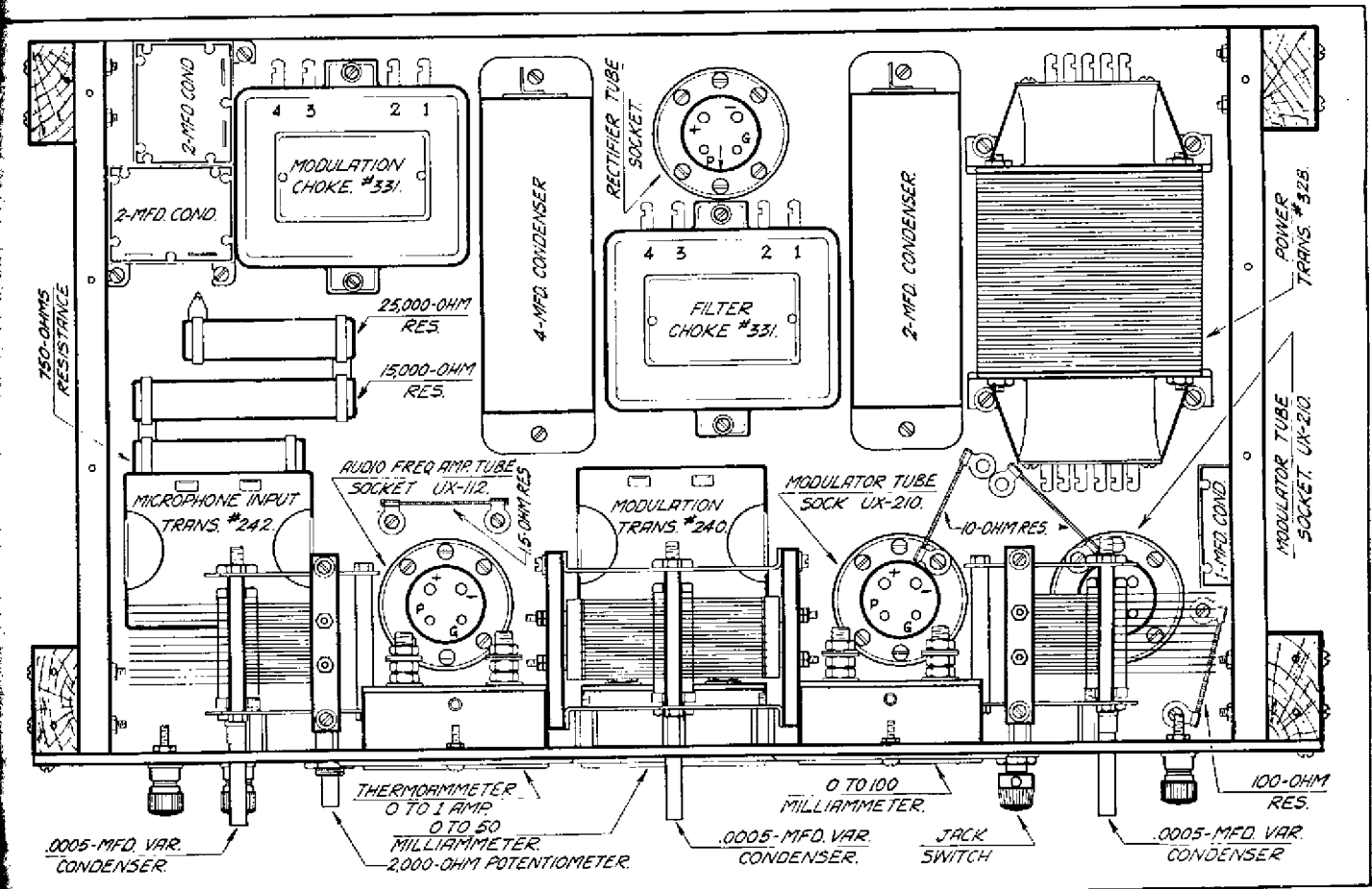


Figure 4. The baseboard layout shown above represents the manner in which parts should be placed on the lower shelf, where all of the power apparatus is located

On connecting an antenna and a counterpoise (or ground) and tuning the antenna condenser, this plate reading will be increased when resonance is established and at the same time some antenna current will be noted. If the coupling between the antenna coil and the plate coil is too close, the tuning of the antenna will have a tendency to stop the tube's oscillation.

Final tuning should always be done with a wavemeter in order that transmission may be within one of the bands licensed by the government for such transmission. One of the features of the transmitter described in this article is the fact that through the interchangeable coils made by Acro, the transmitter may be tuned

on any wave band between 18 and 180 meters, so that the set is not rendered unserviceable by any slight changes in the wavelengths granted by the government.

Need Government License

It should not be forgotten that the operation of such a transmitter in the United States requires a government license. Details regarding the license and the requirements for securing such a license may be obtained by writing to the Radio Supervisor at key cities such as New York City, Chicago, San Francisco, Atlanta, Washington, Boston, Seattle, Baltimore and New Orleans.

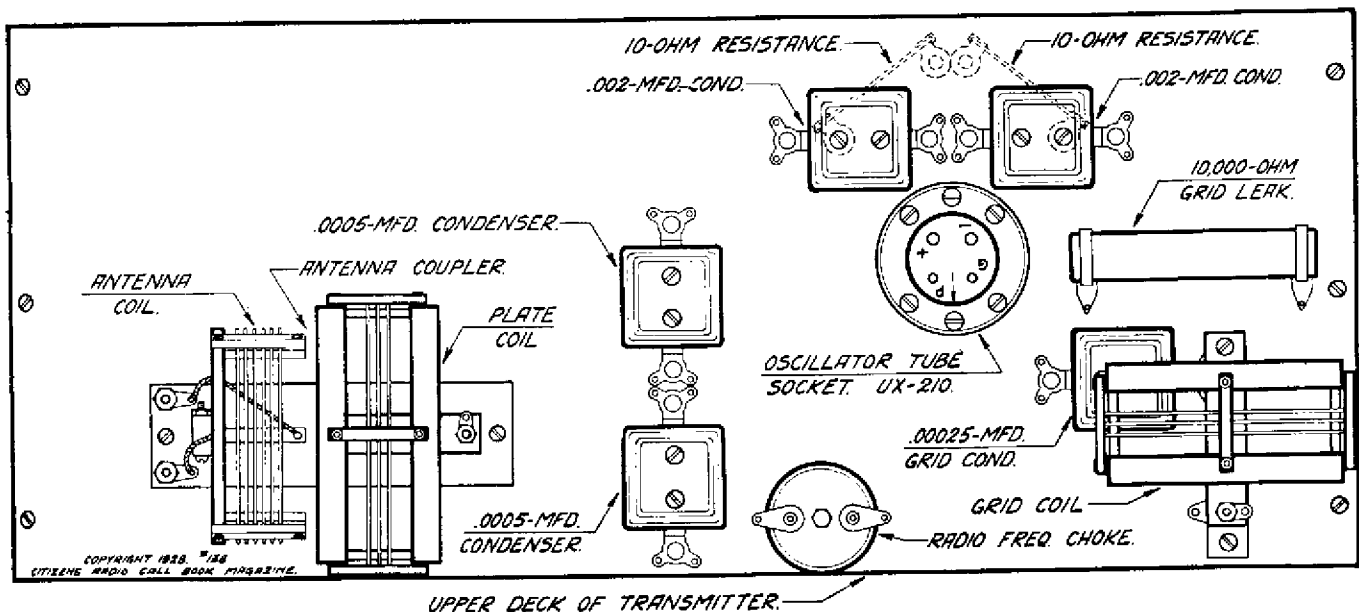


Figure 5. All apparatus involved in the oscillating circuit is placed on the top shelf in accordance with the layout illustrated above

Radiophone transmission is licensed by the government on the following bands: 4.69 to 5.35, 20.68 to 21.4 and 150 to 190 meters.

Little is yet known by the radio enthusiast of the unbounded daylight pleasures awaiting him in the diversion to twenty meter radiophone work. Not that the other wave bands have not their allurements, but the DX worker has always had to wait until after twilight to appease his appetite. This is no longer true when he takes up radiophone work and uses the twenty meter band, which has a wonderful daylight record to give him.

The Laboratories of Aero Products, Inc., report having held a two-hour-running telephone conversation with Syracuse, New York, on the afternoon of Saturday, January 28. The following Monday afternoon they talked over the telephone with Bristol, Connecticut, and got a signal rating of R-8.

Turning his attention to radiophone work, the DX enthusiast will find Saturday afternoons and Sundays the occasions of his greatest pleasures.

List of Parts

Parts necessary to duplicate this transmitter are as follows:

- | | |
|---|---|
| 1—Aero short wave transmitting kit, including r. f. inductances and r. f. choke | 1—Polymet .00025 mfd fixed condenser |
| 1—Aero transmitter foundation kit consisting of Micarta upper front panel, engraved lower front panel, frame kit for making stand | 2—Tobe 2 mfd 300 volt condensers |
| 3—SLC Cardwell .0005 mfd variable condensers | 1—Tobe 2 mfd 1000 volt condenser |
| 2—Polymet .002 mfd fixed condensers | 1—Tobe 4 mfd 1000 volt condenser |
| 2—Polymet .0005 mfd fixed condensers | 1—Tobe 1 mfd condenser |
| | 1—240 Silver-Marshall audio frequency transformer |
| | 1—328 Silver-Marshall power transformer |
| | 2—331 Silver-Marshall filter chokes |
| | 5—511 Silver-Marshall tube sockets |
| | 1—242 Silver-Marshall microphone transformer |
| | 4—810 Yaxley 10 ohm fixed resistors |
| | 1—2000 Yaxley 2000 ohm potentiometer |
| | 1—2L Yaxley 1½ ohm resistor |
| | 1—8100 Yaxley 100 ohm resistor |
| | 1—63 Yaxley 3-pole switch |
| | 1—10 watt Polymet 10,000 ohm resistor |
| | 1—10 watt Polymet 25,000 ohm resistor |
| | 1—10 watt Polymet 15,000 ohm resistor |
| | 1—10 watt Polymet 750 ohm resistor |
| | 8—Eby binding posts |
| | 3—Kurz-Kasch 4-inch plain dials |
| | 1—425 Weston thermo-ammeter 0-1 amp. |
| | 1—301 Weston milliammeter 0-100 mil. |
| | 1—301 Weston milliammeter 0-50 mil. |
| | 1—159 Frost desk microphone |
| | 40—Ft. Corwico braidite wire |
| | 1—Pkg. Kester radio solder |
| | Miscellaneous—lugs, nuts, screws, etc. |

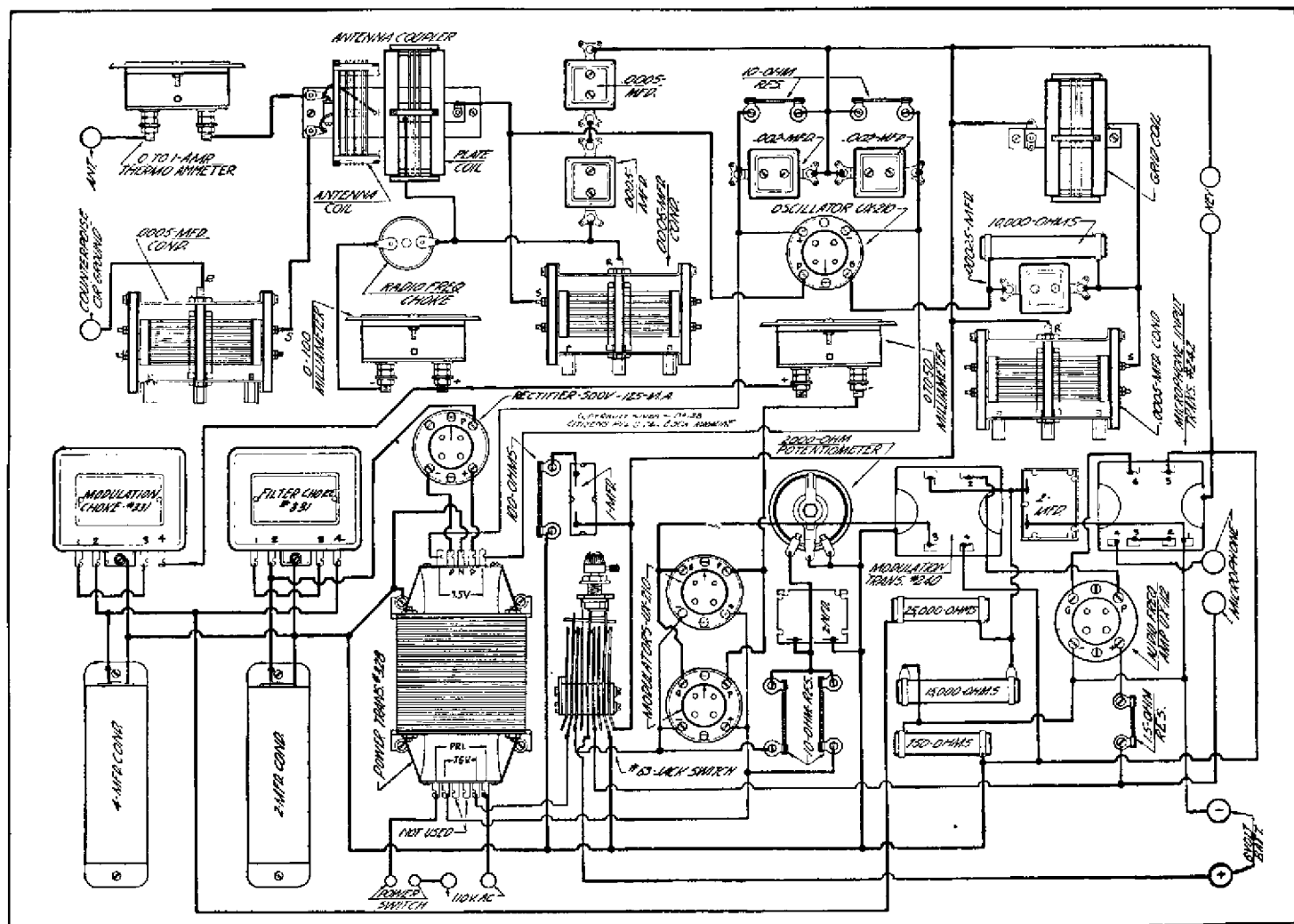


Figure 6. Every connection necessary for the completion of the short wave radio telephone set is shown in the graphic diagram. Parts should be placed in accordance with the layouts in Figures 4 and 5 and the wiring should be performed in accord with the above graphic

