

CIRCULATION OF THIS ISSUE OVER 400,000 COPIES

RADIO NEWS

REG. U.S. PAT. OFF.

25 Cents

DECEMBER

Over 200
Illustrations

Edited by HUGO GERNSBACH

GRANDMA'S X-MAS SHOPPING



RADIO'S GREATEST MAGAZINE

EXPERIMENTER PUBLISHING COMPANY, NEW YORK, PUBLISHERS OF

SCIENCE and INVENTION

THE EXPERIMENTER

MOTOR CAMPER & TOURIST

www.americanradiohistory.com

Christmas

---and the whole
world is young again

THE Air is a-quiver, the Ether crowded, with the Yule-tide Music. The carols, the simple songs, that carry us back to a rose-tinted childhood are beating . . . beating . . . beating . . . their soundless tattoos at our Hearth-Stones.

Radio is the Magic-Key that translates it all into vibrant glorious sound.

Only a Scrooge, untouched by the Christmas Spirit, will leave the Key unturned.

Of course, for the utmost in Radio enchantment, you will equip your set with tubes of the rarest scientific accuracy—

*Quality Plus Service
Since 1915*

Cummingham RADIO TUBES

PATENT SUIT: Cummingham tubes are covered by patents dated 2-15-09, 2-19-12, 2-20-11, 10-23-17, 10-25-17, and others issued and pending. Licensed only for anyone experimental and experimental use in radio communication. Any other use will be an infringement.

Cummingham 40-page data book fully describing care and operation of Radio Tubes now available by sending 10c in stamps to San Francisco Office.

Price the same on all five types
C-301A, C-299, C-300, C-11, C-12

A. J. Cummingham Inc.
182 Second St.
Home Office: SAN FRANCISCO CHICAGO NEW YORK



Tower's

Bring Christmas Cheer from far and near

Think of the little hearts that will beat the faster on Christmas morn on finding in their stocking a gift so pleasing.

If you only will — Old Santa himself from way up North will talk to the kiddies, and stories tell.

No Other Gift
Can Bring Such Cheer
A Gift to Last
Throughout the Year.

*A Merry Christmas
and a Happy New Year*

Tower's Scientific Headset

Every set tested and approved by Government Licensed Radio Operators.

Tower's Scientific Headsets are guaranteed to be made of the best materials money can buy — highest test enamel, insulated magnet wire, best grade five-foot tinsel cord, unbreakable cups, polished aluminum cases — using the famous scientific heat-tard construction for maximum comfort.

If your dealer cannot supply you, order direct by post card, and we will ship immediately Parcel Post, C. O. D., plus a few cents postage.

The Tower Mfg. Corp.
98 Brookline Ave., Dept. N., Boston, Mass.

Scientific



www.americanradiohistory.com



Synchrophase
with Battery base

GREBE SYNCHROPHASE

TRADE MARK



"Of what use is cleverness
of speech?"

—Confucius

Words, even though select-
ed and phrased with the
greatest deliberation, can-
not do full justice to the
Grebe Synchrophase—and
its performance.

Robert Taylor

IN THIS outstanding triumph of fif-
teen years of radio development,
a new type of fieldless "Binocular"
coil transformer—unaffected by
local interference—is used for tun-
ing the detector and two stages of
Balanced tuned radio frequency.

The settings for the various broad-
cast stations are equally spaced over
the dials. The S-L-F (straight line
frequency) condensers accomplish
this.

Write for literature

A. H. GREBE & COMPANY, INC.

Van Weyk Blvd., Richmond Hill, N. Y.

Western Branch: 443 So. San Pedro St., Los Angeles, Cal.




TRADE MARK
REG. U. S. PAT. OFF.

All Grebe apparatus is covered
by patents granted and pending.

Belden

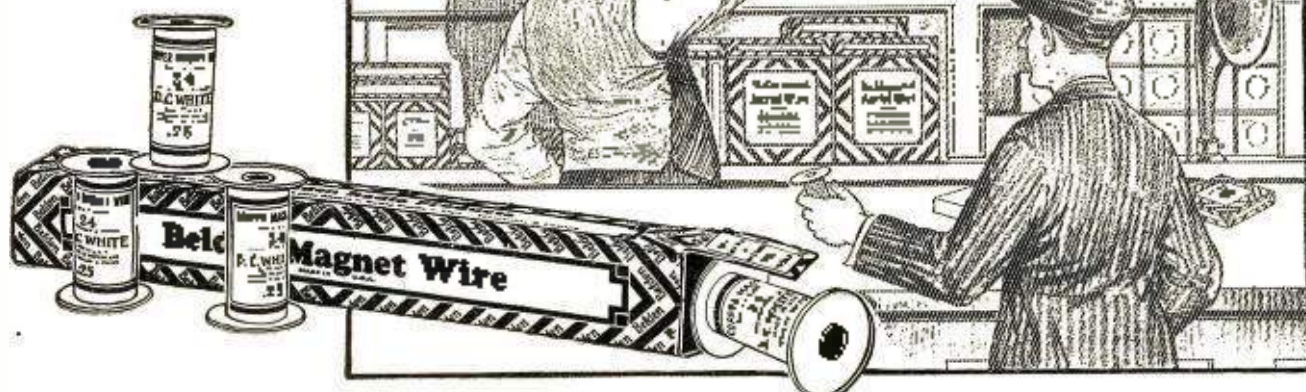Magnet Wire
Is known the world
over for its uniform-
ity and high quality.



Wind Your Own Coils for the New Hook-ups!

The joy of real accomplishment comes to the radio fan who tries the new hook-ups and succeeds in making new records of long distance reception. He leads—others follow!

This fascinating work calls for special coils of new specifications. The enterprising experimenter winds his own coils to save time and to be sure that the new set will operate at the highest efficiency. To him comes the thrill of true scientific discovery and research.

Belden Radio Magnet Wire has been used for many years by famous manufacturers of radio devices. They require wire of uniform gauge, carefully insulated with high grade cotton or silk insulation from one end of the spool to the other. You should insist on Belden Radio Magnet Wire for your own protection. Every spool is full weight, plainly marked, and of full gauge throughout. Be sure to get Belden Wire—it makes a world of difference!

Other Belden Radio Products

Our instructive booklet, "Helpful Hints for Radio Fans" describes many other Belden Radio Products, such as Enameled Aerial Wire, Loop and Link Wires, New Terminals, Sockets, and many other important items. Know all about these efficient radio products. Send for the booklet, now!

Radio Dealers

Belden Magnet Wire is merchandised in handy cartons of 5 spools each. Every spool is marked for weight, insulation and gauge. Send for complete dealer bulletin, by writing us on your business letterhead. Write, today.

Belden

Manufacturing Company

4634 West Van Buren Street
CHICAGO ILLINOIS

Send for this
Free Booklet!



Belden Manufacturing Company
4634 W. Van Buren St., Chicago, Ill.
I would like to know more about Magnet Wire.
Send me your latest booklet—Helpful Hints for
Radio Fans. Be sure to explain Link Wire, too.

Name _____

Address _____

RADIO NEWS READERS' BUREAU

Time and Postage Saver

IN every issue of RADIO NEWS you undoubtedly see numerous articles advertised about which you would like to have further information. To sit down and write an individual letter to each of these respective concerns, regarding the article on which you desire information, would be quite a task.

As a special service to our readers, we will write the letters for you, thus saving your time and money.

Just write the names of the products about which you want information, and to avoid error the addresses of the manufacturers, on the coupon below and mail it to us.

If the advertiser requires any money or stamps to be sent to pay the mailing charges on his catalogue or descriptive literature, please be sure to enclose the correct amount with the coupon.

We will transmit to the various advertisers your request for information on their products.

This service will appear regularly every month on this same page in RADIO NEWS.

If there is any Manufacturer not advertising in this month's issue of RADIO NEWS, from whom you would like to receive literature, write his name, address and the product in the special section of the coupon below.

TEAR ALONG THIS LINE

READERS' SERVICE BUREAU,

RN-12

Experimenter Publishing Co., Inc., 53 Park Place, New York, N. Y.

Please advise the firms listed below that I would like to receive detailed information on their product as advertised in the issue of RADIO NEWS.

NAME	ADDRESS (Street — City — State)	List here specific article on which you wish literature.	If Catalogue of complete line is wanted, check in this column
.....
.....
.....
.....
.....
.....
.....
.....

Do Not Use This Coupon for Technical Questions

Use this space if you desire information from a manufacturer whose advertisement does not appear in this month's issue.

NAME	ADDRESS (Street — City — State)
.....
.....
.....

Your own name here

☐ If you are dealer check here.

Address

City State

Earn \$5⁰⁰ to \$20⁰⁰ a Day in RADIO

You can! Hundreds of ambitious men are already earning thousands of dollars in this wonderful new industry—you, too, can get your share. Mail coupon below for Free Book which describes fully the amazing money-making opportunities in Radio and tells how YOU can earn from \$5,000 to over \$10,000 a year.

The astounding growth of Radio has created thousands of big money opportunities. Millions of dollars were spent during the past year on Radio, and thousands of young men are needed right now to meet the ever-increasing demand of work.

Men are needed to build, sell and install Radio sets—to design, test, repair—as radio engineers and executives—as operators at land stations and on ships traveling the world over—as operators at the hundreds of broadcasting stations. And these are just a few of the wonderful opportunities.

Easy to Learn Radio at Home in Spare Time

No matter if you know nothing about Radio now, you can quickly become a radio expert, by our marvelous new method of practical instruction—instruction which includes all the material for building the latest up-to-date radio apparatus.

Scores of young men who have

taken our course are already earning from \$75 to \$200 a week. Merle Wetzel of Chicago Heights, Ill., advanced from lineman to Radio Engineer, increasing his salary 100% even while taking our course! Emmet Welch, right after finishing his training, started earning \$300 a month and expenses. Another graduate is now an operator of a broadcasting station—PWX of Havana, Cuba, and earns \$250 a month. Still another graduate, only 16 years, is averaging \$70 a week in a radio store.

Wonderful Opportunities

Hardly a week goes by without our receiving urgent calls for our graduates. "We need the services of a competent Radio Engineer." "We want men with executive ability in addition to radio knowledge to become our local managers." "We require the services of several resident demonstrators"—these are just a few small indications of the great variety of opportunities open to our graduates.

Take advantage of our practical training and the unusual conditions in Radio to step into a big paying position in this wonderful new field. Radio offers you more money than you probably ever dreamed possible—fascinating easy work—a chance to travel and see the world if you care to or to take any one of the many radio positions all around you at home. And Radio offers you a glorious future!

The National Radio Institute is America's Pioneer Radio School—established in 1914. Our course is the absolutely complete one now being offered which qualifies for a government first-class commercial license. It gets you the bigger paying jobs in Radio.




Send for FREE RADIO BOOK

Learn more about this tremendous new field and its remarkable opportunities. Learn how you can quickly become a radio expert and make big money in radio.

We have just prepared a new 32-page booklet which gives a thorough outline of the field of Radio—and describes our amazing practical training in detail. This Free Book, "Rich Rewards in Radio," will be sent to you without the slightest obligation. Mail coupon for it now!

For a short time we are offering a reduced rate to those who enroll at once. Act promptly and save money.

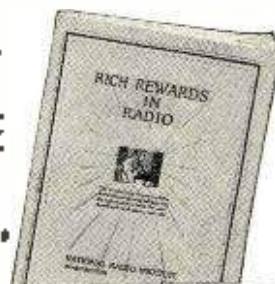**NATIONAL
RADIO
INSTITUTE**
DEPT. 13-MA
Washington,
D. C.



NATIONAL RADIO INSTITUTE
Dept. 13MA, Washington, D. C.

Please send me without the slightest obligation your Free Book, "Rich Rewards in Radio," and full details of your special offer and Free Employment Service. Please write plainly.

Name..... Age.....
Address.....
City..... State.....



PAY INCREASES OVER \$200 A MONTH
I am shipping anywhere from \$75 to \$100 a week. Last week I was getting \$200 a week. I would not consider \$100 a week much for the work I do. I signed the A. J. Jones, Greenburg, Pa.

DOUGLAS BALART
I am very much interested in the amount of money now that I am getting. I am now getting \$200 a week. I would not consider \$100 a week much for the work I do. I signed the A. J. Jones, Greenburg, Pa.

T. Winder
131 Madison Ave.
Grand Central Station, N.Y.



FROM \$15 TO \$20 A WEEK
I have just finished with you. I was making \$15 a week. Now I am making \$20 a week. I am now getting \$200 a week. I would not consider \$100 a week much for the work I do. I signed the A. J. Jones, Greenburg, Pa.



FROM \$15 TO \$20 A WEEK
I have just finished with you. I was making \$15 a week. Now I am making \$20 a week. I am now getting \$200 a week. I would not consider \$100 a week much for the work I do. I signed the A. J. Jones, Greenburg, Pa.



"The
Stradivarius
of Radio"

\$1250

Black finish

FROST-RADIO

Pan-Tab Jacks.

3 in. port; desired type. Prices
from 70c. to \$1.00.



FROST-RADIO

No. 140 Plug.

A 2-Fone Plug at a
ruby price, 60c.




FROST-RADIO

No. 622 Toggle

Switch, 110V. 50c.

FROST-RADIO

No. 651 Bakelite Vernier Rheostat

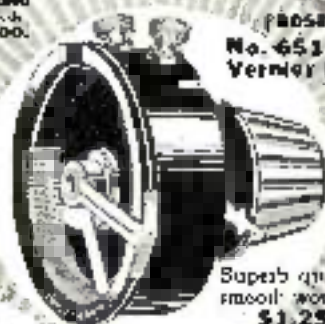

Superb quality,
smooth working.
\$1.25.



FROST-RADIO

No. 607-610 Tube Control Unit

Combines channel
with control and
potentiometer.
\$1.75.



FROST-RADIO No. 602

Metal Frame Vernier Rheostat

A remarkable value
in metal frame type.
assembled 80c.

FROST- Ask Your

A complete line of

FOR the broadcast listener **FROST-RADIO** offers the only complete line of parts and accessories of nation-wide reputation.

If you plan to build a receiving set you will find **FROST-RADIO** parts the most dependable you can buy, as well as the most value for your money, and fully guaranteed.

Should you already own a receiving set you will find a number of **FROST-RADIO** Accessories that will improve its operation or increase its service and satisfaction to you. Among these items are **FROST-RADIO** Musette, and Musette Phonograph Attachment, **FROST-FONES**, **FROST-RADIO** Jac-Boxes, Extension Cords, Switches, Adapters, Protectors and Ground Clamps, to mention only a few.

HERBERT H.
154 WEST LAKE STREET
NEW YORK CITY KANSAS CITY

RADIO

Neighbor

parts and accessories

Go to your local radio dealer today and ask him to show you the complete line of **FROST-RADIO**. This now includes **FROST-RADIO** Musette, "The Stradivarius of Radio," Musette Phonograph Attachment, **FROST-FONES**, **FROST-RADIO** Plugs, Standard and Pan-Tab Jacks, Jack Switches, Moulded Bakelite and Metal Frame Rheostats, Potentiometers and Tube Control Units, Jac-Boxes, Extension Cords, Shock Absorber and plain Sockets in moulded Bakelite, both single and in gangs of three, Moulded Bakelite Adapters, as well as **FROST-RADIO** Protectors, Ground Clamps, and the famous Musselman Selective Antenna.

A POST CARD
brings 44 page cat-
alog free.



FROST-FONES

\$4 \$5 \$6

No. 101 Alluminum Shell
FROST-FONES \$5.00

No. 173 Alluminum Shell
FROST-FONES \$5.00

No. 172 Bakelite
FROST-FONES \$6.00




Musette Phonograph
Unit \$5.50



FROST-RADIO
Pan-Tab Jack
Switch. Works
with any set
made. \$1.00 to
\$1.50



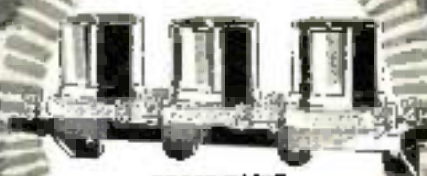FROST-RADIO Jac-
Box, complete
in stock. \$2.50.



FROST-RADIO
No. 619 3-Gang Shock
Absorber Socket, Moulded
Bakelite, \$3.25.



FROST-RADIO
Extension Cord,
10 feet. \$2.50



FROST-RADIO
No. 614 Bakelite
Socket, 100 Watts
Type 85c.



FROST-RADIO
No. 611 Bakelite
Adapter, 100 Watts
Type 50c.

FROST, Inc.
CHICAGO. ILLINOIS.
CLEVELAND LOS ANGELES

Build the Neutro-Reflex—

Complete
Set
\$15.00



The Wonder Circuit

The new Neutro-Reflex circuit makes three tubes do the work of five. Why build a neutrodyne when the Neutro-Reflex does the same work on practically half the number of tubes?

A complete kit for building the Neutro-Reflex is shown here. With this kit comes a complete instruction booklet. It describes every step in the construction of this marvelous circuit. You can't go wrong if you follow this instruction book.

This circuit gets the results on local stations, brings in distance that is surprising, and gives the same volume as the neutrodyne. It is a distinct advance in radio receiving set construction.

By means of this Tuned Radio Frequency outfit you can also build the following: A five tube Neutrodyne receiver; a tuned crystal receiver; a five tube Radio Frequency receiver; a one tube Regenerative receiver; a balanced wave trap.

FREE We will send you the booklet "All About Tuned Radio Frequency" free of charge on receipt of a postcard from you.

If your dealer cannot supply you use the coupon below

"RICO" Straight Line Condenser

New manufactured in three types, to replace 43 plates, 25 plates and 13 plates.

No. 450 "Rico" Condenser .001 mfd. (43 plate capacity)

\$1.25

No. 423 "Rico" Condenser .0005 mfd. (25 plate capacity)

\$1.25

No. 411 "Rico" Condenser .00025 mfd. (13 plate capacity)

\$1.75

All above types without dial

\$1.50

THREE STYLES
.001 mfd. 43 Pl.
.0005 mfd. 25 Pl.
.00025 mfd. 13 Pl.



This Replaces This



This condenser marks a revolution in condenser building. It is the simplest and most practical type of condenser as yet developed for broadcast and amateur work. This condenser has been developed by our engineers after considerable research work and has been pronounced perfect by experts.

The "Rico" condenser weighs 6 oz.

The old style weighs 15 oz.

"Rico" vernier type has only one dial.

Old type requires difficult mechanism.

IF YOUR DEALER CANNOT SUPPLY YOU USE THE COUPON BELOW

Radio Industries Corp.,
133 Duane Street, N. Y. City.

Gentlemen:

As my dealer cannot supply me, kindly ship me the following material for which I will pay postman on delivery.

Name

Address

City

State

133 Duane Street

New York City

SPECIAL ANNOUNCEMENT "Rico" No. '6' Headset Now \$2.95

GUARANTEED
FOR
ONE YEAR

FAMOUS
TRI-POLE
PULL



Finest pair of Headsets made—DON'T PAY MORE
INSIST ON "RICO"

Our large Production enables us to give you the full benefit of this unusually low price

**RADIO
INDUSTRIES
CORPORATION**

The Tropadyne Super Radio Outfit

Greatest Distance, Superior Volume, No Distortion. Positively Non-Radiating, Six Tubes Do the Work of Eight—The Only Super Radio Set with Tuned Intermediate Transformers

Kit
No. 350
PRICE
\$28.75



\$6.75

No. 351 (Patent Pending)

The TROPAFORMER here illustrated is the only scientific balanced intermediate Super-Heterodyne transformer. It combines transformer and condenser, and enables the transformer to be tuned to the very finest degree. Once tuned it need not be touched again. Built entirely of hard rubber.

The Tropafomer does away with special input couplers, staggered, fixed by-pass condensers and inefficient, broadly tuned transformers. It may be tuned to any wave-length from 2500 to 30,000 meters, thus the advantages of either low or high intermediate frequency can be had.

In the August, 1924, issue the Editor of Radio News has this to say about the TROPADYNE circuit:

"Here is a remarkable Super-Heterodyne circuit, which we warmly recommend to our readers. It has several new and unusual features. In the first place only six tubes are used giving as much volume as the average 8 tube Super-Heterodyne. The selectivity of this set is unusual. Unequalities of the intermediate transformers have now been done away with by tuning each transformer. After the transformer has been tuned it can be left this way, no further tuning being necessary. This system makes for maximum simplicity and maximum volume. Another outstanding point of superiority of the Tropadyne circuit is that it practically does not radiate, thereby not interfering with other nearby receiving stations. Most Super-Heterodyne circuits, as is well known, are powerful radiators."

It is now possible to build a real Super-Heterodyne that not only exceeds them all, but is the only Super-Heterodyne scientifically balanced. Heterodyne when building a Super-Heterodyne you either made or bought the intermediate transformers. These were matched as it is impossible to make two windings exactly electrically alike.

While some firms are advertising matched or balanced transformers this is a misleading statement because even though they are balanced ever so well, when placing them in the circuit they become unbalanced automatically due to inductive effects between transformers, lead wires, etc.

The TROPAFORMERS built according to the inventor's—Mr. C. Fitch—specifications can be scientifically balanced by anyone. Each transformer is equipped with one of our well known condensers which is shunted across the secondary of the transformer. This is the big secret of the TROPADYNE circuit and accounts for its wonderful work. Once the TROPAFORMERS are tuned by means of the tuning condensers they need not be touched again; the balancing is permanent.

Any other technical information will be gladly supplied by us. We offer to the trade and those interested in building their own TROPADYNE Super-Heterodyne the following:

- No. 350 Kit containing four TROPAFORMERS with tuning condensers, tuner and one oscillator coil. Price complete with booklet giving full directions
- No. 351 Tropafomer, each
- No. 352 Tropadyne Bakelite Tuner, each
- No. 353 Tropadyne Bakelite Oscillator Coil, each

\$28.75
6.75
1.25
1.50

IF YOUR DEALER CANNOT SUPPLY YOU USE THE COUPON BELOW

**RADIO
INDUSTRIES
CORPORATION**

133 Duane Street

New York City


Radio Industries Corp.,
133 Duane Street, N. Y. City.

RM12

Gentlemen:

As my dealer cannot supply me, kindly ship me the following material for which I will pay postman on delivery.

Name
Address City State

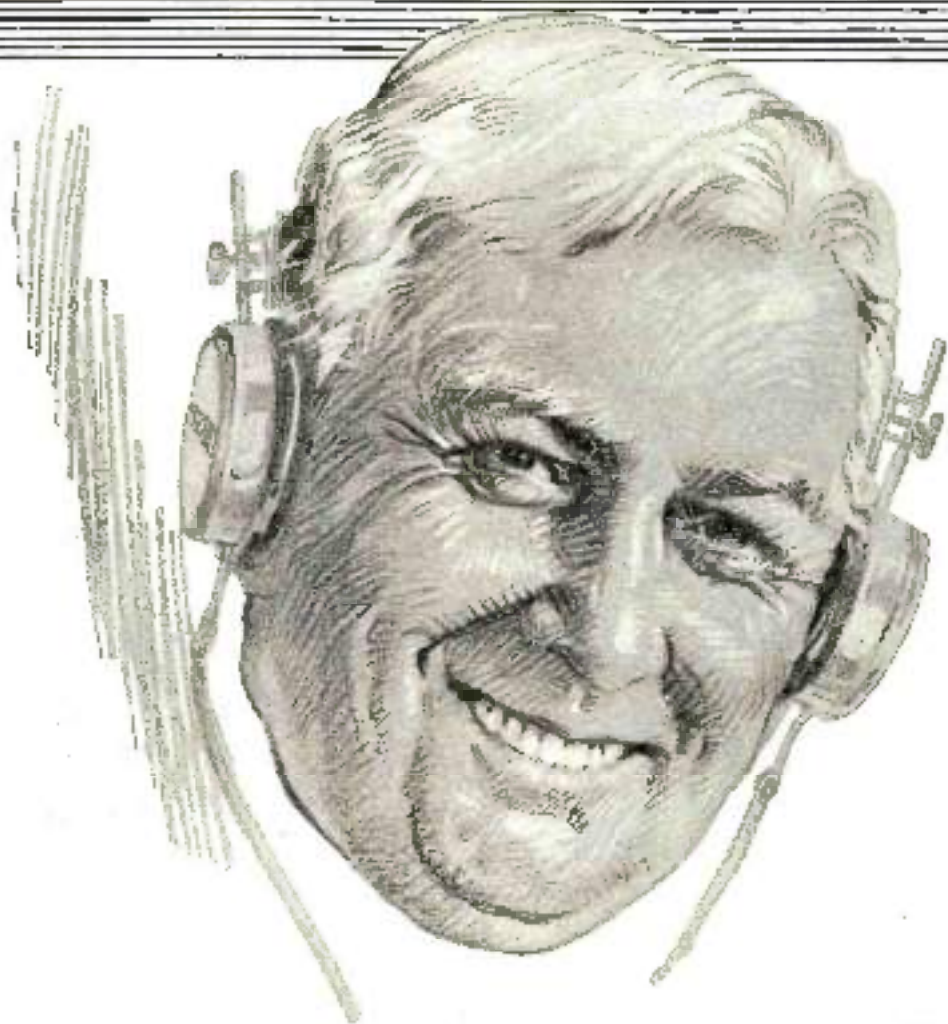

Of Course It's
a CROSLEY
 Better—Costs Less
 Radio

*Crosley
 Head Phones
 Better—Cost Less
 \$3.75*

TO COMBINE the two most desirable things in radio—distant clear reception at the lowest possible price—there is only one radio receiver for you. That is a Crosley.

When you listen in on a Crosley—no matter what the price—you wonder, as thousands of others have, that such exceptional results can be obtained, and so reasonably.

The answer is simple—quality radio receivers built in quantity production. During the past twelve months, we believe Crosley made and sold more sets than any other manufacturer in the world. This is self-evident proof of Crosley Quality and Crosley Performance. Combined with Crosley excellence are such additional advantages as selectivity, ease of tuning, simplicity and beauty—all at the lowest radio cost.

THE CROSLEY RADIO CORPORATION

1222 All-ied Street
 Powell Crosley, Jr., President
 Cincinnati, O.
 Crosley Sales and Operator Broadcasting Station WEN



Crosley Teirdyn Newport, \$100.00
 With tubes and Crosley Phones \$115.75

CROSLLEY has made it possible for everyone to own a radio receiver. You can start with the one tube Armstrong Regenerative Receiver at \$14.50, without accessories—\$22.25 with tube and head phones—the lowest priced regenerative set on the market, and equivalent in reception to many two tube receivers. Then as more volume is desired, you can add to it at a very low cost.

Or, you can purchase the three tube Crosley Trirdyn Regular, which has come through the summer period of comparatively poor reception with colors flying—for only \$65. In Special Mahogany cabinet to house necessary accessories—\$75, or the beautiful new Crosley Trirdyn Newport as shown herewith, \$100. The combination of one stage of tuned radio frequency, with regenerative detector and reflexed amplification, has proven beyond a doubt that the features of selectivity, volume and ease of operation can be obtained with three tubes better than heretofore has been possible with five tubes. We believe that no other set on the market combines these features so well incorporated in the Trirdyn.

In addition there are the Crosley 51, the two tube Armstrong Regenerative Receiver that became the biggest seller in the world in just 24 days, price \$18.50. This set will at all times bring in local stations on the loud speaker and distant stations under fair receiving conditions. Distant stations can at all times be heard with ear phones. The three tube Armstrong Regenerative Receiver Crosley 52, that brings in distant stations with loud speaker volume under practically all conditions, price \$30; and the Crosley 50 and 51 set in portable cabinets at \$19 and \$25. These receivers, each in its own class, though assuring you as good or better reception than any other instrument of the same number of tubes, are by far the least expensive ever offered to the public.

Before You Buy—Compare Your Choice Will Be a Crosley
For Sale By Good Dealers Everywhere

Write for Complete Catalog

The CROSLLEY RADIO CORPORATION

Powell Crosley, Jr., President

1222 ALFRED STREET

CINCINNATI, OHIO

Crosley Sales and Operating Broadcasting Station W. J. W.




Crosley One Tube Model 50, \$14.50
With tube and Crosley Phones \$22.25



Crosley Two Tube Model 51, \$18.50
With tubes and Crosley Phones \$30.75



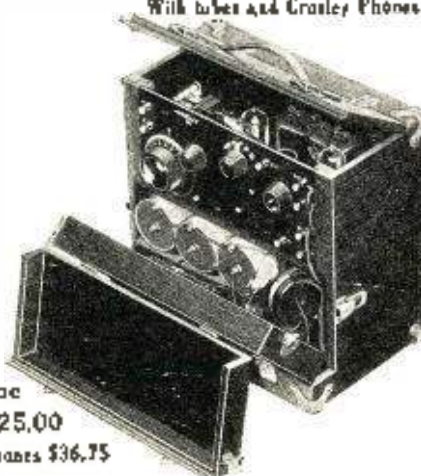Crosley Three Tube Model 52, \$30.00
With tubes and Crosley Phones \$45.75



Crosley Two Tube Model 51-P, \$25.00
With tubes and Crosley Phones \$36.75



Crosley Trirdyn Regular, \$65.00
With tubes and Crosley Phones \$80.75

Crosley Regenerative Receivers are licensed under Armstrong U. S. Patents 1,115,149. Prices West of the Rockies add 10%.



Crosley Trirdyn Special, \$75.00
With tubes and Crosley Phones \$90.75

Mail
This
Coupon
At Once

The Crosley
Radio Corp'n.
1222 Alfred St.
Cincinnati, O.

Mail me, free of
charge, your catalog
of Crosley receivers
and parts with booklet
entitled "The Simplicity
of Radio"

Name _____

Address _____

Every one of the C-H Radio products—the famous Rheostats, Grid Leak, Potentiometer, Radio Switch and Socket—was designed by these engineers whose successes in electrical design are acknowledged throughout the world.



A Moments Care in Buying Assures Hours of Better Reception

Your set starts with the first instrument you buy. It and every other part you put behind your panel determines the results you obtain for the money you spend.

In radio, because of its very nature, the receiving set is only as good as its weakest part. One instrument of poor design or improper construction limits the efficiency of the entire circuit.

Because of this the man who builds

his set and buys with care can be assured of maximum receiving pleasure at the lowest net cost. He can buy each part with understanding and combine in his set the cream of the engineering knowledge of the entire world.

For the delicate parts of your circuits—where the feeble energy received *must* be conserved—the Cutler-Hammer engineers, world famous for more than a quarter of a century as the master builders of all electrical control,



CUTLER-



Know What You're Buying ~for instance~

have safeguarded the radio buyer with a trade mark that allows the most inexperienced enthusiast to buy with the confidence of seasoned engineers.

In their rheostats, grid leak, potentiometer and other radio parts, they have provided a degree of precision that means added miles of range and hours of clear, enjoyable reception. When you start to build, start right—the dealer is glad to recommend C-H parts—this trade mark is his protection and yours too.

THE CUTLER-HAMMER MFG. CO.

Member Radio Section, Associated Manufacturers
of Electrical Supplies

MILWAUKEE, WISCONSIN

Disproof cover of C-H Radio
Switch removed to show
unique mechanism.



The C-H Radio Socket is a marvel of electrical efficiency. One piece, no-joint contact plated with genuine silver—not nickel. And they are spaced wide—true low loss construction. The shell is real Bakelite and the base genuine Thermoplex. No "molded mud" or other poor construction in this socket. Prove it by holding a match to the base—it can't burn. But, be sure you see the C-H trade mark first—the dealer won't let you do that to most sockets.



Before you buy a radio switch ask regarding its mechanism. You can now get many switches that provide the convenience of the original C-H "one up" mounting—and buttons that make them look like the C-H switch from the panel front. But no switch can give you the quiet reception, and positive operation that you get with the C-H patented fluting, contactor construction. Know the mechanism and you will know why all the leading set manufacturers are using it as standard equipment—and why there are almost a million in use today.

HAMMER

How many radio miles did you go last night?

HOW many radio miles did you travel last night—that's the up-to-the-minute question. Did you voyage from New York to Chicago? Did you look in on Boston fifty seconds after, and on Philadelphia half-a-minute after that? If you didn't, why didn't you? There's fun and excitement, too, in a De Forest Radio—and it's ready to "get to work" five minutes after it enters your home.

Here is a Radiophone so astonishingly simple for the work it does that it's your best introduction to the marvels of radio space. Here is one so perfectly developed that it invites graduation from other less efficient instruments.

Here is a receiving set sponsored by the very genius who made radio, as we know it, possible—an instrument which offers a really remarkable demonstration in radio performance at a price far less than any instrument whose achievements compare with it. Here is a practical, a modern Radiophone, depending upon no out-strung wire to obtain results, but which, with a simple loop the size of a picture frame, opens to you a far-flung range of concert, speech and lecture—and all with a tonal purity, a sensitiveness of choice that is rare to any but De Forest users.



DE FOREST RADIOPHONE

~ D-12 REFLEX ~

For Beauty and Clear Reproduction




Use the De Forest Loud Speaker. It reproduces naturally, brilliantly, without distortion. The adjustment of the reproducing unit assures uniform response over entire range of audible frequencies. Its horn is shaped to retain the full brilliancy of the original sound, and also to

add volume. The complete unit is free from rattles. No rattles can ever develop. Every De Forest Loud Speaker is thoroughly tested and is guaranteed free from defects.

Sold by authorized De Forest dealers only. Price, with 6 feet of cord, \$25.00.

The De Forest Radiophone is a complete four-tube receiver, built on the best reflex principle. Its four tubes and crystal detector do the work of seven tubes with four-tube economy of operation.

We could be extremely technical in telling you how the four tubes do the work of seven and why the crystal detector gives both power and economy to this instrument. If you are technically inclined we shall be glad to do so if you will write us. Technical or not, however, know this: You can get splendid results from a De Forest D-12 Radiophone. Its upkeep is low. Its tone is clear and pure. It can be moved easily from room to room.

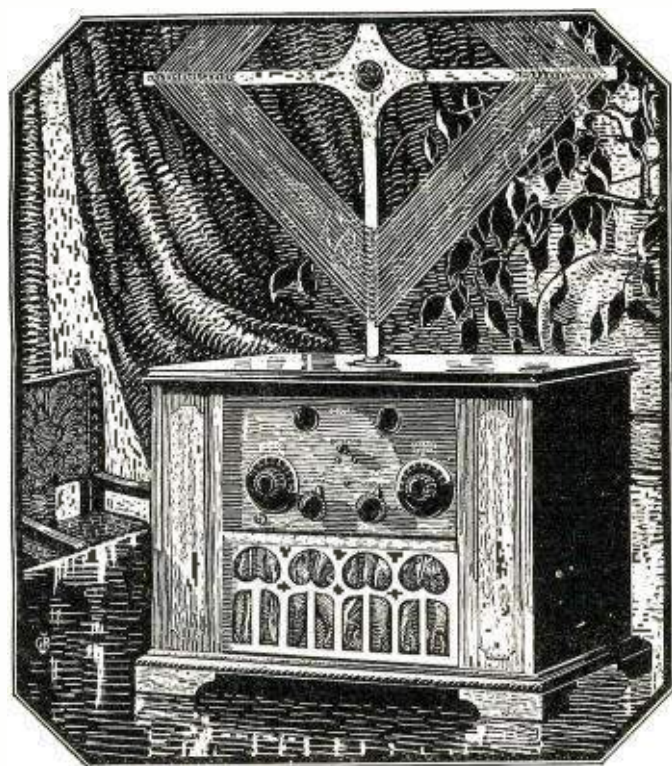

DE FOREST D-12 RADIOPHONE
Seven-tube efficiency with four-tube economy.
Ask the De Forest agent to demonstrate.

Why it pays to look for the De Forest agent

De Forest from first to last stands for all that is substantial and thorough and fundamentally right in radio. De Forest agents are qualified to give you sound and practical advice and help in radio. When you find a De Forest agent you find a man who knows radio—a man who has given us his word that he will see that every instrument he sells is thoroughly inspected and properly serviced after the sale. He has been carefully picked and schooled in the operation and care of De Forest Radiophones. He will install your instrument and explain to you simply how to get the fullest satisfaction and enjoyment from it.

Avail yourself fully of his help. You will find it valuable.

Prices on De Forest D-12 Radiophones

COMPLETE

Including loop, self-contained loud speaker, four De Forest tubes, A and B batteries, and all equipment ready to operate.

With Dry Batteries

In two-tone gray and black Fabrikoid cabinet	\$161.20
In two-tone Mahogany cabinet	176.20

With Storage Batteries

In two-tone gray and black Fabrikoid cabinet	180.00
In two-tone Mahogany cabinet	195.00

De Forest D-14 Radiophone

In burl walnut cabinet with loop and loud speaker built in. Price, including five DV-2 tubes, four B batteries, and storage batteries.	371.50
--	--------

DE FOREST RADIO COMPANY
Jersey City, N. J.

DE FOREST RADIOPHONE

D-12 REFLEX

Your Set Deserves De Forest Tubes

The original De Forest three-electrode vacuum tube was the first of many millions of De Forest tubes that have never been excelled in quality of workmanship, or performance. Today, as in the past, De Forest tubes are unsurpassed for giving volume and beauty of tone.

They are non-microphonic. They can be used with all standard circuits. The DV-3 is for use with dry batteries, the DV-2 with storage batteries. They are guaranteed against defects in material and workmanship. Sold only by authorized De Forest dealers. Price, \$4.00 each.

De Forest
DV-3 Tube
for use with
Dry Cell
Batteries



De Forest
DV-2 Tube
for use with
Storage
Batteries





RADIO NEWS

H. GERNSBACK, Editor and Publisher
ROBERT E. LACAUT, Associate Editor

EDITORIAL AND GENERAL OFFICES, 65 PARK PLACE, NEW YORK

Vol. 6

DECEMBER, 1924

No. 6

Your Boy and Radio

By HUGO GERNSBACK

The following is an editorial published by the writer in 1914:
A SERMON TO PARENTS
"Keep Your Boy at Home"

THE strongest ties in life are the home ties. It makes a lot of difference, both to you—his parents—and to him too, when a young man grows up whether his thoughts dwell with sweet pleasure upon his old homestead, or whether the remembrance of his home and his past home-life is painful to him.

How many well-meaning, fond American parents develop the home idea in the young boy? Are you not a bit to blame if your boy, when still in his teens, is seen too much in questionable company and in questionable resorts? Your boy is not naturally inclined to stay away from his home and his family. He is usually forced out, for want of something to keep his growing, inquisitive mind occupied; it's the something that he can't find at his home that forces him out. So out he goes. He drifts on, away from you,—the heartstrings loosen more and more, you—his parents—wonder and wonder and the boy becomes a stranger before you realize it.

Then It Is Usually Too Late to Amend

This is—alas—only too true a picture of the average American youth. And it is so easy to keep your boy at home. He doesn't want much, just something to dabble, to tinker, to experiment with and to keep his inborn insatiable curiosity satisfied.

You know your boy likes nothing better than this, he was born for it; are you going to club it out of him?

He has the right idea—the home idea; somewhere in him is a spark alive that needs but proper fanning to create a future Edison, a coming Marconi.

Electricity, especially Wireless, are positively the strongest home-magnets today. His workshop, his small electric laboratory or his Wireless Den are the most powerful home attractions for the 20th Century Boy.

Electricity and Wireless are the coming, undreamed of, world-moving forces. Don't tell the electric spark is your boy. It costs little to keep it going, and some fine day it will pay you and your boy handsome dividends.

Only one boy in 300 is interested in Electricity and Wireless. Your boy has the electric "bug." Thank the stars for the fact that he is so deeply interested in the greatest art the world has ever known. It's a distinction, besides:

"It Keeps Your Boy at Home."

THE views expressed therein are just as true today as they were 10 years ago with the exception that at that time the message was intended to reach only 100,000 where the same message today concerns literally many millions of young men, not only in this country but throughout the world.

It is true that today millions of boys and young men all over the world are experimenting with radio, and it is also true that it would be a still greater boon if many more millions were to take it up. To the uninitiated, to the layman, and to most parents, radio today is still a big enigma. Many people still look upon it with a feeling of trepidation; stranger yet, many parents view it with apprehension when their bright off-spring begins spending their hard earned money on radio paraphernalia. There are still many people who have the idea that radio is only a fad which will disappear sooner or later. To these good people we wish to say that radio today is a vast industry which stands 34th on the list of all the industries in this country. It is an industry already greater than that of railway car building. It also already rivals in dollars and cents the ship-building industry which, as everyone knows, is of considerable size.

The writer's message years ago to the parents of the young men then was that radio kept their boys at home, off the streets and away

from bad influences. This is just as true today as it was then. The modern boy easily becomes bored at home. He has the adventurous spirit and it is a matter of vital importance for him to use his surplus energy. For that reason, as a rule, he seeks amusement away from home, whereas it is quite a simple matter to cultivate the home ties if the parents go about it in the right way. If the young man becomes interested in radio he will soon forget the pool room, the corner hangout and the questionable "gang" he was getting to know so well—too well. He will be so busy at home trying out the latest hook-ups that it becomes somewhat of a problem to get him away from his radio. Of the two evils this seems to be the lesser, for, as long as he is at home, at least the chance of his going wrong is more remote.

But this is not the important consideration. The far greater and vital point is that we know of nothing that sharpens one's wits more effectively than the intricacies of radio. Not every boy has the brain or the inclination to ferret out the mass of radio circuits and technique. It takes real brains and stick-to-it-iveness to build a radio outfit and make it work.

If the young man shows an inclination toward radio he should be encouraged with all possible means. The expense in no case is very great and the educational value derived by the boy can never be figured in dollars and cents. Impressions upon the mind are strongest in youth as we all know. What is learned and learned well in youth is hardly ever forgotten. The boy experimenter of today may be the radio magnate of tomorrow. The radio industry which today has already reached tremendous proportions will probably be one of the leading industries ten years hence, and those who get their feet firmly implanted in that industry will surely grow up with it.

If Edison had not been an experimenter in his boyhood he would not have attained his present success. If Henry Ford had not been mechanically inclined in his childhood the world might not have a reasonably priced car today. The list could be continued indefinitely. In radio it is all-important that when a six or an eight year old boy shows any leaning towards it, the spark should be fanned with all possible zeal.


Radio is vastly more complicated than the electrical and mechanical arts just now. Important changes occur almost every month. It takes many years of hard work and training to become a radio engineer. Too many "radio engineers" today masquerade under that name, some of them have been at it but a short time, while many boys of 26 have been at it since they were eight years old and probably know more about the new art than many self-styled radio engineers. It is a fact that when radio became a big thing in 1921, practically every radio amateur was immediately drawn into the new industry and a great many of them today are in some commanding position. Even if the radio enthusiast who has been at it a number of years should find it necessary tomorrow to go into some other line of endeavor the writer still maintains that the radio training will leave its mark upon him during the remainder of his life.

The radio mind is always keen and sharp, and whether this thinking is applied to the radio or the banking business makes little difference. It is a valuable acquisition that will probably grow more valuable as the years go by. Radio to the young man today is a valuable college education. It not only trains the mind to useful and careful thinking, but it trains the young man manually as well. In building a number of radio sets he becomes well versed in the handling of tools and the handling of a surprisingly large amount of materials. He comes into close contact not only with a vast number of various metals which he must not only know thoroughly but also various kinds of woods, hard rubber, bakelite, cottons, silks, and many other products. He soon learns to appreciate values in a business sense because he is quickly trained where to buy his materials and how to buy them at the lowest price. This is an education in itself.

Radio to the youth is the best possible foundation of the future self-made man.

The Behavior of Radio Waves and the Heaviside Layer

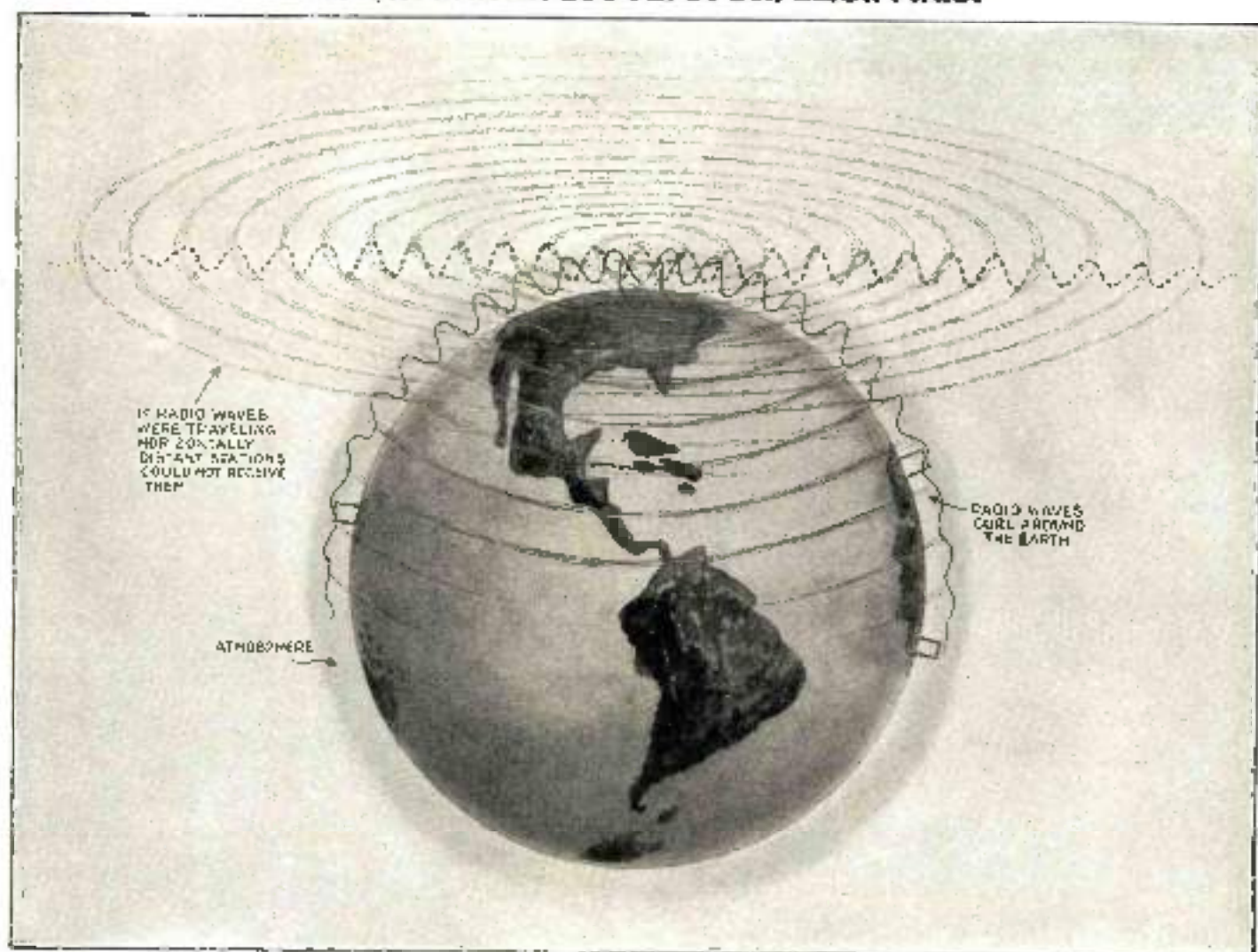By SIR OLIVER LODGE, D. Sc., LL.D., F.R.S.



THE surprising fact that electric waves travel around the earth instead of spreading out in straight lines like the rays of ordinary light, has set a problem to mathematicians, which many have taken up and found to be of considerable difficulty. It is known that waves can be guided along conductors under certain conditions; in fact, that is how ordinary telegraph signals are conveyed, whether by land wire, or by cable they travel through the insulation, but are guided by the conductor. Conductors are opaque to waves, they cannot be penetrated, at least the better the conductor the more opaque it is. But a conductor can reflect waves. If they establish a footing on its surface, they can creep, or rather flash along it, with great ease, leaving a little energy behind them if the conductor is imperfect, and becoming thereby somewhat distorted, but traveling almost free from distortion if the conduction is nearly perfect.

One way, therefore, of treating the problem of long distance transmission mathematically, is to imagine the earth a perfectly conducting sphere, and find out what would happen in that case. After solving this difficult problem, the data may then be modified so as to introduce a certain amount of resistance making the earth an imperfectly conducting sphere, as if for instance it were totally covered by sea-water. A third attempt, hardly one tractable mathematically, can aim at distributing land and water into continents and oceans, and seeing what happens then. This, however, is one of the empirical problems that can only be approximated.

This graphic representation of wave propagation shows that if the energy of a radio wave were radiated horizontally, distant stations would not be able to receive the signal. The waves, according to scientists, are either reflected on the Heaviside layer or follow the curvature of the earth.

Illustration showing the propagation of radio waves around the Earth.


On the right the photograph of high frequency discharge shows that the currents of very high frequency do not follow the shortest path.

Illustration showing the propagation of radio waves around the Earth.



Another plan is to treat the subject optically, not electrically at all, and to think of waves curling round an obstacle by what is called diffraction. The laws of diffraction for small obstacles are pretty well known; and if the earth could be treated as a small body in comparison to the size of the waves—that is, if the waves were as big as the sun or the solar system,—then diffraction would be efficient; and there might be a focus or concentration of such waves at the

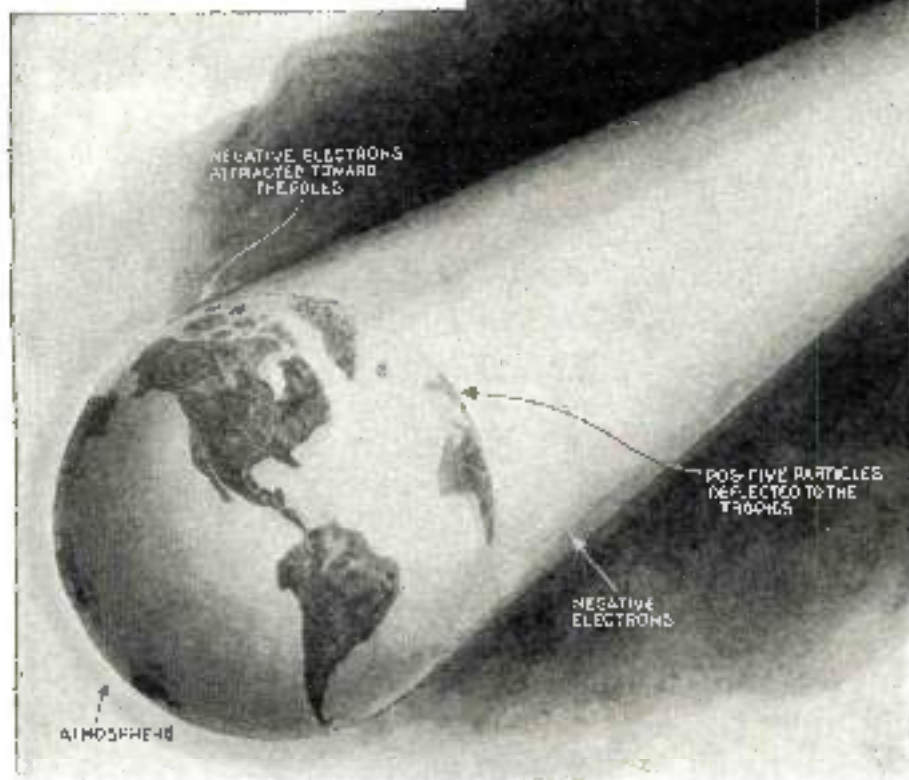According to Arrhenius, the earth's magnetism separates the positive particles and the negative electrons from the sunlight, the electrons being attracted toward the poles and the positive particles to the equator.



angles. But that is a quite different notion from anything appropriate to radio telegraphy. Diffraction will not account for the curling round of ordinary ether waves. Nor is earth conduction very satisfactory.


And yet the waves do curl round, and easily reach Europe. Whereas if they were in straight lines, they would be going far overhead, even for that distance. And now Mr. Marconi appears to find that even short waves, or comparatively short waves, travel enormous distances, under favorable conditions. What are these favorable conditions? If they were due to earth conduction, they would not be so likely to vary as they do. The fact that they are capricious and dependent on sunlight and other causes, shows that the conditions must be partly regulated by the atmosphere. And as is well known, Mr. Oliver Heaviside attributed the curling round of the waves to the influence of a good conducting layer in the atmosphere overhead, acting concentrically perhaps with the salt water below, so that the waves were enclosed in a stratum between two conducting surfaces, the air effect on the whole being more efficient than the earth conduction.

Everyone who has worked with vacuum tubes, with an air-pump, knows that at a certain stage of exhaustion, the residual air is conducting, or at least leaks down very easily, conveying a current and lighting up at very small voltage. Whereas, when the air is at high pressure, or very low pressure, great voltage is needed to drive a current through it. But at the best conducting vacuum, a very small voltage suffices.

Now as we ascend through the atmosphere, we pass from ordinary atmospheric pressure to zero. Consequently a best conducting layer must exist. But a stratum of that kind is so gradual that it is unlikely to be able to serve as the layer postulated by Mr. Heaviside, even if it were sufficiently conducting. But it is well known that air can be made conductive by various means, notably by X-rays, and even by ultra violet light, also by combustion, as by flames; and by various kinds of physical or chemical action, even by splashing water. These agents are said to ionize the air, that is, to eject electrons from atoms so that electric charges are free in the air for a time, and are able to conduct, as they do in metals, where for another reason they are extremely free.

The chief ionizing factor in the atmosphere is probably the solar rays. What we get down here of sunshine has been filtered by the atmosphere. But the upper layers of the air have to stand a bombardment of the unfiltered sunlight. By ascending a very high mountain or going up in a balloon, we may experience the sunlight only partially filtered. The result is that we get first bronzed and then blistered! There can be little doubt that the really unfiltered sun-

(Continued on page 1046)

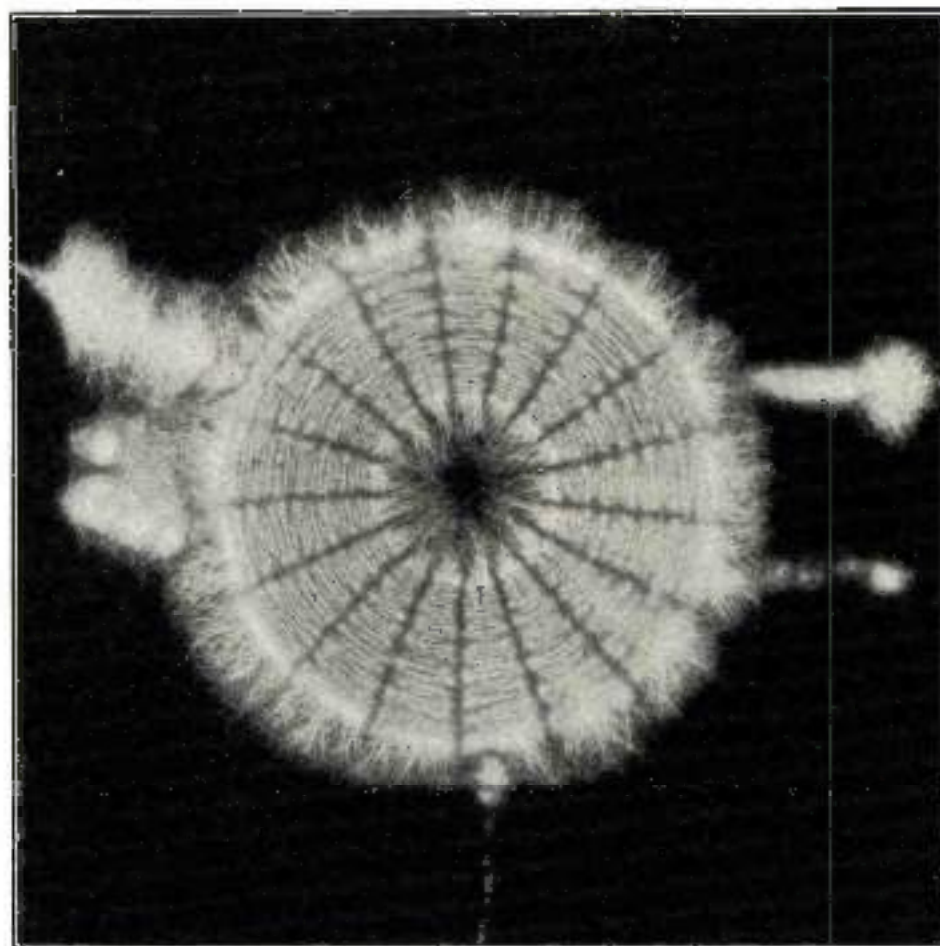


This photograph shows the distribution of high frequency current in a spider-web pattern. It spreads on the outside of the conductor, but follows it the same there probably happens around the earth.

"We Will Now Give the Official Weather Forecast"

By FRANCIS DASHIELL, M. I.R.E.

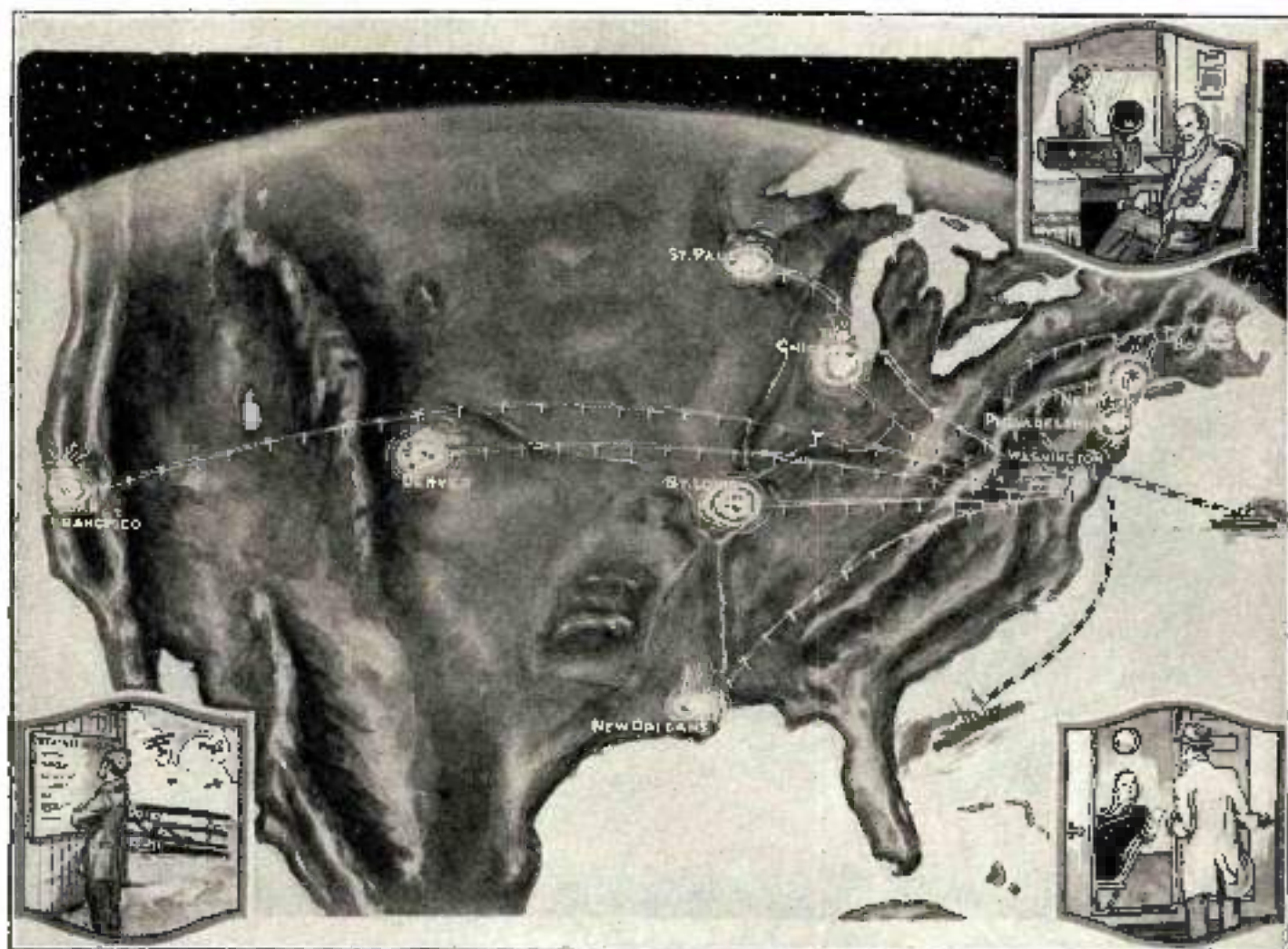Describing how weather reports are compiled and broadcast.



This map illustrates how the local weather conditions from all parts of the United States and from the ocean are sent to the weather Bureau at Washington, D. C., and how these reports are transmitted to the various broadcast stations by telegraph, from where they are broadcast.


It is quite safe to assume that practically every radio broadcast listener has heard some announcer say, "We will now give the official weather forecasts." A simple statement, yes true, and the time it takes to broadcast it is very short, but how many listeners realize just what is behind the forecast, from whence does it come, and what is the use and extent of its distribution?

The United States Weather Bureau at Washington is, without exception, the greatest scientific agency ever established for the study of meteorology and the distribution of weather forecasts throughout the world. It issues official forecasts of expected weather conditions, storms and hurricanes, under the specific authority of Congress, which established the Bureau about 50 years ago. Any weather forecasts which may be issued as coming from the Federal Bureau are a violation of the law. Therefore, as will be seen later, the forecasts which you may hear over the radio and credit to the Weather Bureau are official, and can be counted upon to prove correct time and time out of time, according to actual verification figures.

The radio station broadcasting weather forecasts are specially licensed by the Department of Commerce, after a complete investigation by the Weather Bureau at Washington. It is a violation of the Federal radio regulations for a station to broadcast any Government weather forecasts without this license. This prevents spurious forecasts

from being broadcast to millions of listeners who would become aroused at some radical and incorrect forecast. In order to receive

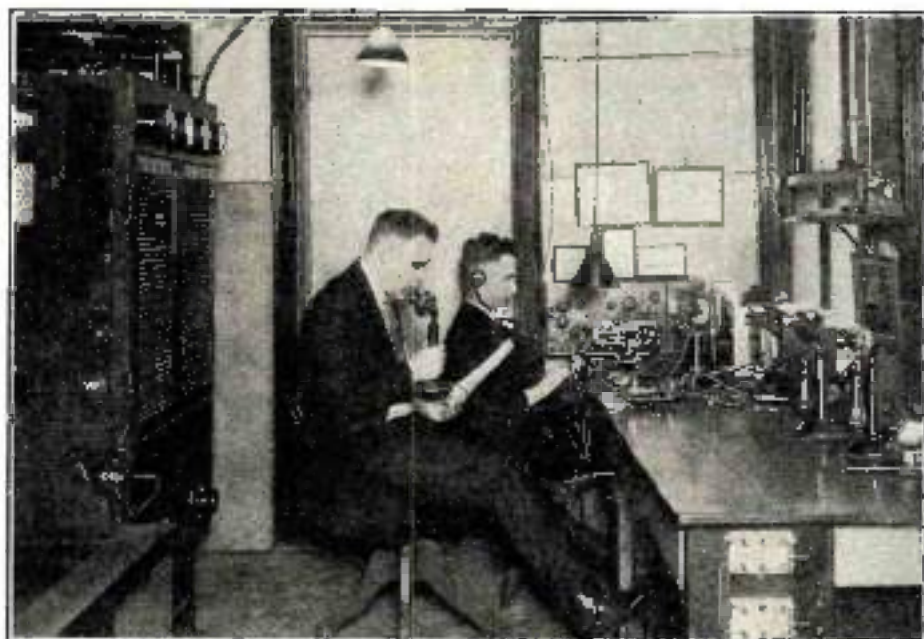a recommendation from the Weather Bureau for a weather broadcasting license, a station (Continued on page 1151).



Broadcasting weather forecasts from station KYW, Chicago, Ill. The operator sees the window is receiving the forecasts by radio, in code and on a long wave. The complete information, on a typewritten sheet is passed to the other operator who transmits it over the radiophone.

¹Observer, United States Weather Bureau.

Third Radio Conference Makes for Better Radio Service

By CARL H. BUTMAN

THE third annual radio conference held Oct. 11 at Washington, D. C., and the clean-up squad of supervisors and technical experts has finished its work reorganizing stations and reallocation wave-lengths. Practically everything went through and, in general, the radio public and industry will be better served in the future.

The first report of the Conference was made by Mr. W. D. Turrell, Chief Supervisor of Radio of the Department of Commerce, who is chairman of the sub-committee on general allocation of frequency or wave-length bands. The allocation for marine communication allows ship communication between 600 and 1,651 meters with wave bands provided for radio compass stations at 800 meters and radio beacons at 1,700 meters, with suitable protecting bands on either side. It was recommended that ships be no longer required to maintain the 300 meter adjustment as required by international regulations. The wave band reserved for marine telephone, colleges and Government use from 1,054 to 1,579 was continued. Wave bands from 1,579 to 1,817 meters were assigned to point to point and marine use for spark, CW and LCW, and 1,817 to 1,910 meters for use of point to point and marine, CW, and LCW. Non-exclusive 1,910 to 2,500 meter length is reserved for the exclusive use of marine communication on CW and LCW. The band for Government use between 2,500 and 3,150 meters as fixed by the previous Conference, was left unchanged. The band for broadcast purposes was extended to include 200 to 545 meters and cleared from all other types of service thereby permitting it exclusive use for broadcasting.

The radio amateurs were allowed to retain the wave bands previously assigned, with slight changes. They were assigned 150 to 200 meters; 25 to 36.6 meters; 37.5 to 32.8 meters; 33.7 to 24.2 meters; 44 to 5.3 meters. These allocations were made for CW and LCW and telephone operation only.

Dr. George K. Burgess, Director of the Bureau of Standards, reported as chairman of the sub-committee on allocation of frequencies to broadcast stations. This allocation does not differ except in degree from the allocation now in force. The extension of the broadcasting service to 200 meters allows a large number of simultaneous, non-interfering communication channels in this class. It was recommended that the present Class C licenses be discontinued after November 15, 1924. This will make available several new channels for Class B broadcasting and will eliminate one of the most important causes for congestion in the broadcasting band. It is also recommended



Hon. Herbert Hoover, Secretary of Commerce, opening the Third National Radio Conference with an important talk on the vital problems of radio. © Henry Miller News Picture Service, Inc.

that the frequency assignments on the Atlantic coast be repeated on the Pacific coast. This has been shown to be practical in the experience of the Department. The zoning system of the United States was, therefore, changed in such degrees to take care of this alteration and allows a large number of frequencies for the congested areas. This new allocation makes possible 61 Class B channels, 12 Class A channels and a new class is created and given five channels. This latter class includes all low-power stations having a power of 1,000 watts or less. It is proposed that instead of designating stations as Class B and Class A, the three classes be designated as Class 1, now Class B; Class 2, now Class A and Class 3, which are local low power stations. The plan retains all of the principles of the present Class B assignments, that is, the 50 kilocycle separation in each zone and maximum of 40 kilocycles separated in adjacent zones. It is further recommended that in a given locality not more than two Class 1, now Class B, stations be licensed on a given frequency. Any additional applicants should be temporarily assigned to frequencies in the Class 2, now Class A band, until a frequency is available. Thus, there would be a possible maximum of 126 Class 1 stations. These changes in the allocation of frequencies in broadcast stations require that several alterations be made in existing assignments. Such changes are inevitable, but the assignments could be made. It is recommended that a special committee be designated by the Conference to remain in Washington and collaborate with radio supervisors in a re-assignment of the broadcast station frequencies in accordance with the recommendations of this Committee.

General George O. Snider, formerly Chief Signal Officer of the United States Army, reported that the work of Subcommittee No. 1 on general problems of radio broadcasting was practically completed after three extended sessions. This group states that due consideration has been given to the class of programs broadcast from various stations.

(Continued on page 1166)



President Coolidge addressing delegates at the Third National Radio Conference. He said the Federal Government would stand for no monopoly of the air. © P. H. A. Press.



Dr. J. H. Dellinger, Chief of the Radio Laboratory of the Bureau of Standards.

VACUUM tubes of increased efficiency, transmitting stations with correspondingly greater power, and the elimination of batteries and antennas! These are among the radio developments foreshadowed by Dr. J. H. Dellinger, Chief of the Radio Laboratory of the Bureau of Standards, in an interview with the writer. The progressive changes outlined, according to his version, will also be attended by a greatly increased popularity of this medium of communication—that is, radio receiving sets will be as common as telephones and automobiles, and the number in use in the United States is likely to approach 12,000,000.

"In the next few months we shall doubtless see the beginning of a steady development of cheaper, simpler, and better receiving sets," predicts Doctor Dellinger, with the added comment that this is already being accomplished. "Radio sets are now in the same stage as the early automobile when they had a whipsocket on the dash board. Ten years from now it will be hard to believe that the complicated instruments we now call receiving sets were used at all."

"We shall certainly see the elimination of batteries and antennas. Perhaps even the electron tubes will go, and crystal detectors come back, if broadcasting is distributed from a sufficient number of stations. These stations will be linked together, so as to send out the same material simultaneously. The stations will be connected by one of three methods, namely, wire telephone distribution, radio relaying, and the carrier-current system. The receiving sets will be kept at the pressing of a button will adjust the set to bring in the particular material desired. One thing about radio sets that now appears certain is that practically everybody will have one."

"Is the present trend toward the use of radio receiving instruments with a great number of tubes, or will the one- and two-tube sets be the popular type of the future?" the doctor was asked.

"Certainly there will not be an increase in the number of vacuum tubes used," he replied. "Distant reception is not always due to the sensitivity of a receiving set or

The Progress of Radio

By S. R. WINTERS

to the power of the transmitting station," he added. "Favorable atmospheric conditions and the absence of electrical disturbances occasionally make possible long-distance reception, this accounting for the freak records reported. On the other hand, static, electrical interference and other limiting factors operate against the full possibilities of a receiving set."

Pertinent to this conclusion are the results of a two-year study recently completed by the Bureau of Standards. About 50,000 observations were made with respect to the distance ranges of broadcast reception and the effects of varying conditions such as atmospheric disturbances, fading, interference from other transmitting stations, radiating receiving sets and weather characteristics. The results, which are now being tabulated, indicate that the major obstacles to radio reception are other broadcast stations, atmospheric disturbances, and fading. These forms of interference are stated in the order of their relative extent. These tests were participated in by 200 voluntary observers, located at varying distances up to 1,000 miles from the broadcast stations whose signals were under study.

"The necessity for fewer tubes ties in with the assurance of an increased use of power at the transmitting stations," indicates the Chief of the Radio Laboratory of the Bureau of Standards. Already there are instances in the United States and Canada where transmitting stations have increased appreciably their consumption of electric energy for broadcasting purposes.

HIGH POWERED STATIONS MUST MOVE

With the general use of high-powered stations, according to Doctor Dellinger, there

will arise a demand for their locations to be removed from the congested centers of population. That is to say, as the stations increase their powers, there will be a tendency to erect them in the country or open spaces, thus reducing interference. A notable instance of this was the removal of a powerful broadcast station from the suburbs of London, England, to a point 30 or 40 miles from the city.


The commercial development of a 3-electrode vacuum tube with a flame heated by alternating current, according to Doctor Dellinger, is indicative of the trend toward greater efficiency and more power in the path of transmitting and receiving work. Outdoor antennae will gradually be eliminated and the electric light socket will become both the tube power supply and antenna.

The use of increased power by transmitting stations will necessitate that they adhere accurately to the wave length or frequency assigned them. In this connection, it has been discovered that small pieces of quartz crystal, one or two inches long, have a natural frequency of the same order as the frequencies of currents used in radio communications. It has been found too that the frequency of the crystals is surprisingly constant, and are thus extremely useful in establishing and maintaining radio standards.

QUARTZ CRYSTALS

"The quartz crystal may be used in numerous ways," comments Doctor Dellinger. "In one method, it forms an auxiliary condenser in a resonance circuit and when the current in the circuit is made to have a frequency equal to that of the natural vibra-

(Continued on page 1050)

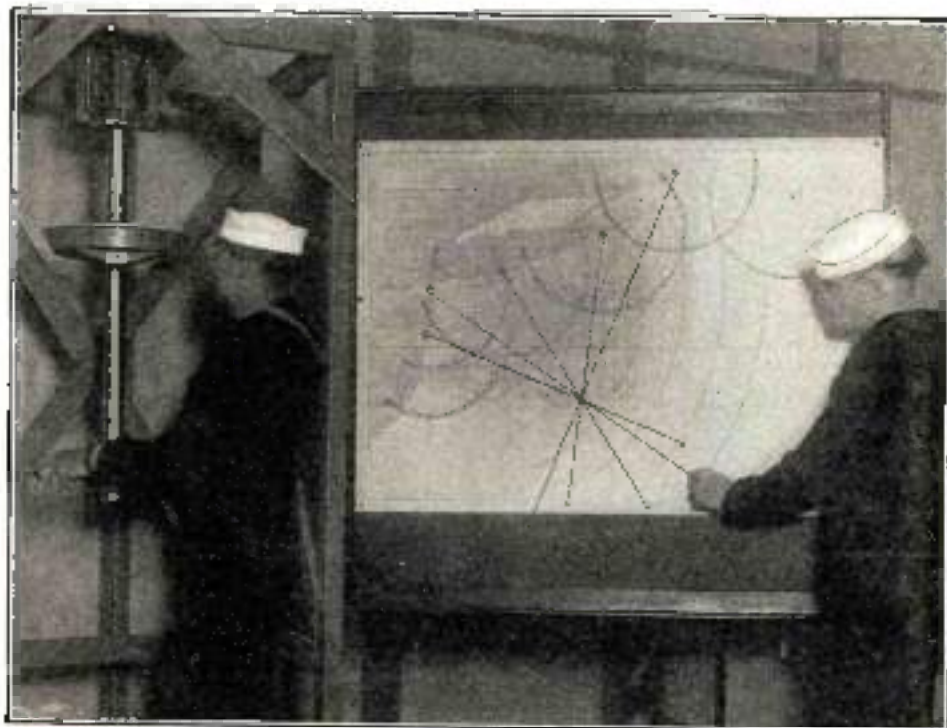

One of the many U. S. Radio Compass Stations, the original system was improved upon by the radio laboratory staff of the Bureau of Standards. A ship's bearing is determined by the combined angle readings obtained at a number of compass stations, and plotted on the map in the manner shown. Where the strings intersect is the position of the ship.

© Felt-Tapia, Inc.

Will Radio Make Our Railroads Safe?

By HOWARD S. PYLE,
A.M.I.R.E.



Showing how the mediator circuit gives radio frequency energy to the rails through intermediate coupling circuits. A change of frequency at the mediator, accomplished automatically by the block signals, affects either one of the two pickup loops on the locomotive. These loops may be seen under the cow catcher.

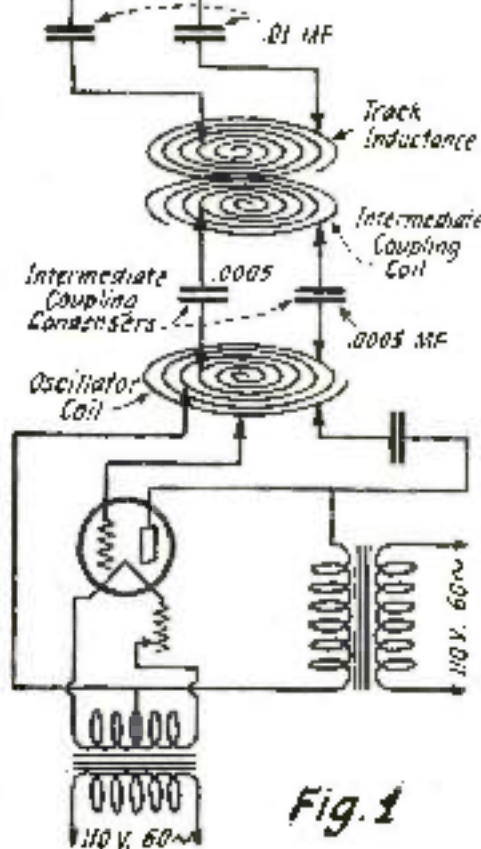


Fig. 1

TO you who have accepted radio as a household necessity, a medium of education and entertainment, it has possibly not occurred that radio is being developed in other ways to provide enormous benefit to the public, probably to a degree of far greater importance than radio broadcasting, for its application to train control work involves the protection of human life and property.

It was not so very many years ago that the present efficient block signal system in use on practically all our railroads today,

was almost unknown. Signals were then looked on by many veteran engineers as a nuisance and they resented the installation of the now familiar semaphore arms at fixed points along the right-of-way. Perhaps the feeling was somewhat similar to that of many old salts—captains of the world's vessels, who objected strenuously to the installation of radio telegraphic equipment on their vessels or the grounds that it took the supreme control of their ship out of their hands, enabling the owners to control the vessel's movements through the medium of a bit of wired apparatus manned by a smug-faced youngster. Although that feeling still is present to some extent among old mariners, this does not hold true in the railroad sense.

In talking with a veteran engineer the other day, the writer questioned him regarding his resentment against signals, which was so unanimous among the old engineers, and he said, "Resent them? Why, man, I consider it is just the difference between life and death for me as well as my passengers to have the security of

block signal protection, and I think you'll find a pretty large majority feel the same." They do; further inquiry developed that, just a few days ago, while the writer was engaged in experimental work along the Pere Marquette right-of-way, his attention was attracted by several short, sharp blasts from a locomotive whistle just outside the experimental station. Catching my inquiring glance, the engineer called, "What's the matter up ahead? I haven't any signal" and glancing at the signal lights, I noted that they were out. It developed that a house was being moved across the rails, temporarily interrupting the system, but the engineer was lost—helpless, without his indication.

Present methods of block signaling are developed to an amazing degree, and with the recent installation of three-color lights, rather than the more common type of semaphore arm, the Pere Marquette Railway has what is considered the most modern and up-to-date signal system today. It has just one fault, a weakness that is evident in all

(Continued on page 1101)


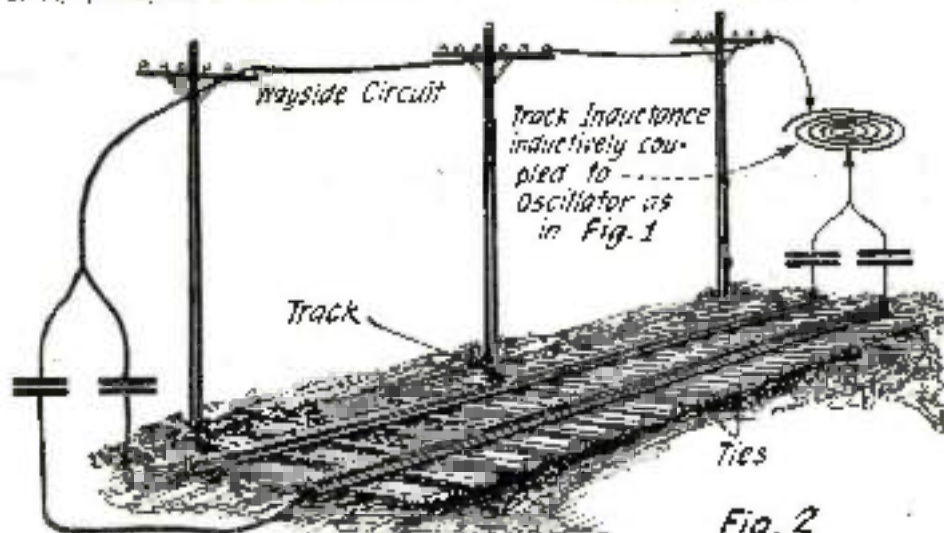


Fig. 2

Leakage from rail to rail through the ties is eliminated by employing a separate return circuit and connecting the two rails in parallel.

Radiophone Serves Power Company

By S. R. WINTERS

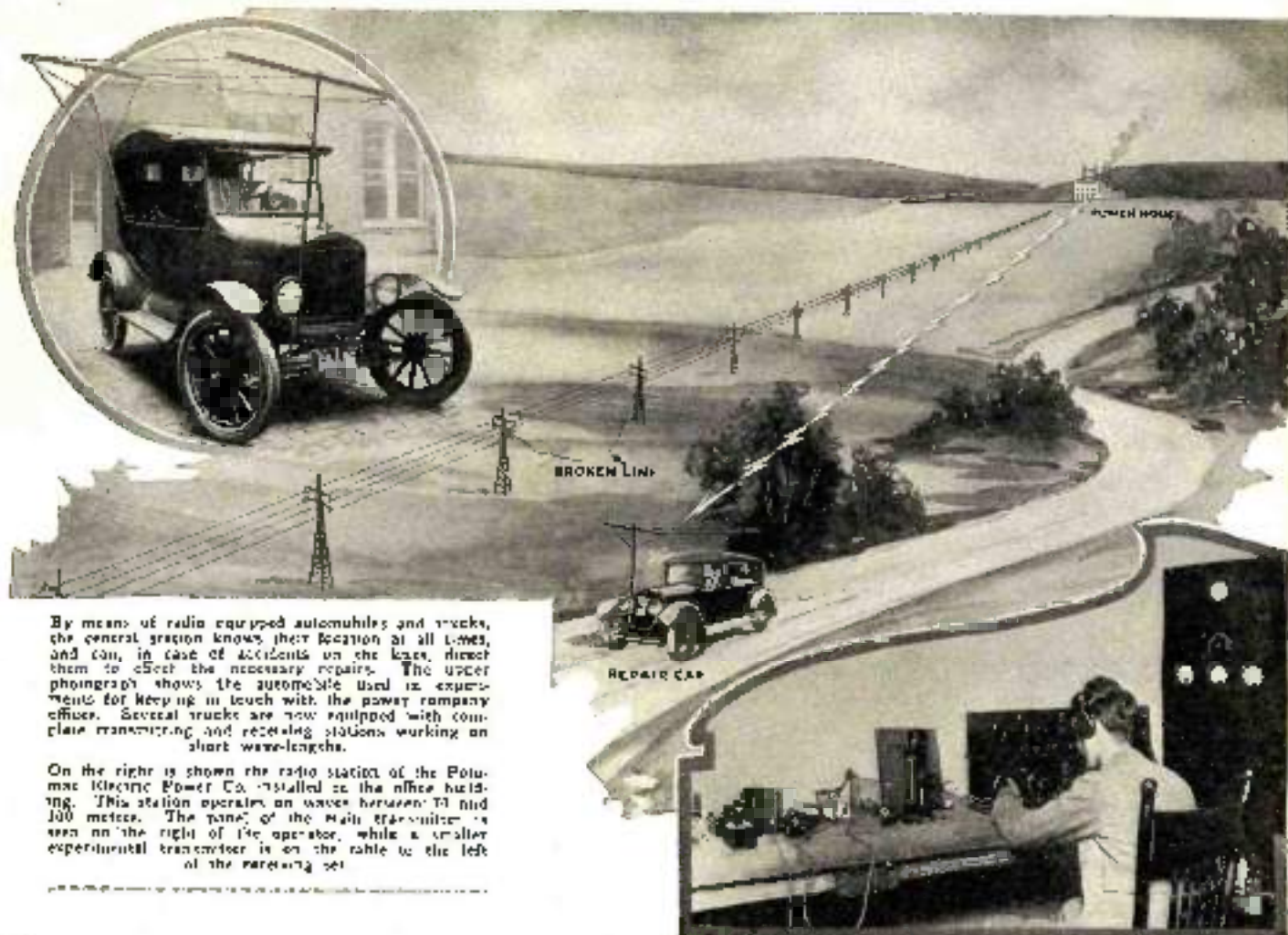

By means of radio equipped automobiles and trucks, the central station knows their location at all times, and can, in case of accidents on the line, direct them to effect the necessary repairs. The upper photograph shows the automobile used in experiments for keeping in touch with the power company office. Several trucks are now equipped with complete transmitting and receiving stations working on short wave-lengths.

On the right is shown the radio station of the Potomac Electric Power Co. installed in the office building. This station operates on waves between 70 and 100 meters. The panel of the main transmitter is seen on the right of the operator, while a smaller experimental transmitter is on the table to the left of the receiving set.

It was only a short while ago that the Radio Laboratory of the Bureau of Standards conducted experiments in the transmission and reception of radio telephone communications by means of short wave-lengths—between 10 and 105 meters. Now, short wave-lengths or high frequencies for radio telephone communication have been introduced in practical service.

The Potomac Electric Power Co. of Washington, D. C., has equipped two radio transmitting and receiving stations for dispatching messages between the main office in Washington and the power plant on the outskirts of the District of Columbia. This traffic will be negotiated on wave-lengths between 100 and 200 meters, a band of frequencies sufficiently removed from those allocated to popular broadcast stations as to cause little or no interference.

The local electric power transmission company will not only use radio as a means of communication between headquarters and its power plant, but will keep in touch with repair trucks through this method. This involves the departure of equipping about 12 repair trucks with radio receiving sets whereby signals may be intercepted from the transmitting station at headquarters. In operation this plan means that the foreman of each repair truck will listen for signals the first 15 minutes of each hour. Thus, the main office will be enabled to issue instructions and direct the movements of repair trucks in the field without the necessity of their returning to headquarters.

This is a novel use of the radio telephone. However, this more novelty should not overshadow the significant thing of utilizing short

wave-lengths or high frequencies in commercial traffic. It means that the increasing use of wave-lengths around or below 100 meters will serve to eliminate some of the

IMPORTANT NEWS

A LONG the well-established policy of RADIO NEWS to give its readers only the best, we are pleased to announce that beginning with the January issue we shall begin a new serial entitled:

"The Inventions of Reginald A. Fessenden"

Dr. Fessenden needs no introduction to the radio fraternity. He is one of the outstanding figures in the radio world today. He is the original inventor of the modern radio telephone. His was the first experiment to send the human voice and music through space without wires—the forerunner of the present day radio telephone. He is also the inventor and patentee of the Heterodyne principle, now used in all of the Super-Heterodyne radio sets.

In addition to this he is the inventor of almost one hundred important radio and electrical inventions.

An author and experimenter of note, he will give RADIO NEWS readers the benefit of his many years of experimentation. The serial will run in RADIO NEWS for the next year and will be published exclusively and for the first time in RADIO NEWS.

—EDITOR

interference encountered in broadcast reception. The point is, the Bureau of Standards emphasizes this very point as one of the chief advantages in employing high frequencies. The wave-lengths between 200 and 600 meters are already congested by

increasing allocations to broadcast stations.

The transmitter at each of the two sending stations of the Potomac Electric Power Co. consists of a 50-watt oscillator and a 50-watt modulator. Signals from the radio telephone station, operating on a band of wave-lengths between 70 and 100 meters, have been heard by amateurs in a middle western state. The feasibility of repair trucks picking up signals from the station at headquarters has already been determined by the experimental use of a Ford automobile equipped with a portable receiving outfit.

COLD WEATHER AIDS RADIO TRANSMISSION

A new natural phenomenon in the form of cold waves improves radio transmission especially at a distance of between 150 to 180 miles, radio engineers of the Bureau of Standards at Washington state. In daylight, cold waves affect the radio transmission of long wave signals from trans-Atlantic stations at New Brunswick and Tuckerton, N. J., a preliminary report from the Bureau points out.

The signal strength varied and the apparent direction of the station deviated, according to the observation. From a moderate distance the signal strength was found to be quite uniform during most of the year, but with the coming of cold waves in January, the signals increased to more than twice their normal strength. At the same period there were deviations of many degrees in the apparent directions of the transmission.


(Continued on page 1055)



Kadel & Herbert.

The First Radio World's Fair

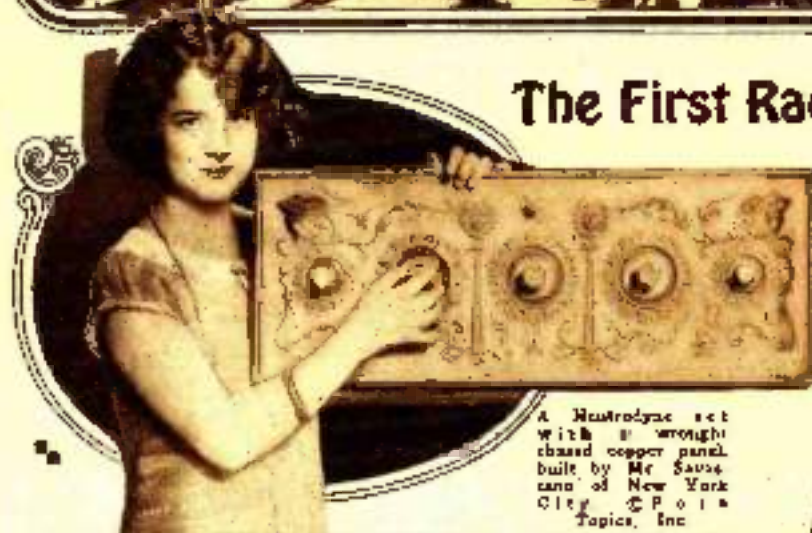One of the greatest Radio Exhibits ever undertaken



A Neutrodyne set with a wrought brass copper panel built by Mr. Sausage, of New York City. C.P.O. 111 Topics, Inc.

Radio World's Fair Great Success

The First Radio World's Fair was a great success from a number of standpoints. The attendance was far greater than was expected, in fact a few of the nights during the exhibition it was found necessary to close the doors at both Madison Square Garden and the 69th Regiment Armory as early as 8:30 o'clock because the crowds were so great. It has been estimated that 175,000 people saw the exhibits. Special details of police were required to maintain law and order. But the success of the Fair was not in the record attendance, but in the volume of business transacted during this period. Eight European countries were represented in the special foreign section and it is understood that their wares were given favorable notice, which of course means business with the United States. Practically every American manufacturer of radio apparatus was represented and many new and novel devices were exhibited for the first time. Neutrodyne sets predominated in the showing of complete receivers and there are so many good ones it is hard for a person to make a final selection of the one he would want.

Any number of contests were held, one of the most interesting being the Homestead Set contest. Some very ingenious and decidedly original outfits were entered. It has been suggested that manufacturers would do well to follow a few points of design incorporated in some of them.




Truly, this is a really good loud speaker, regardless of the fact that the young lady has her hand to her ear. Kadel & Herbert.

Seen at



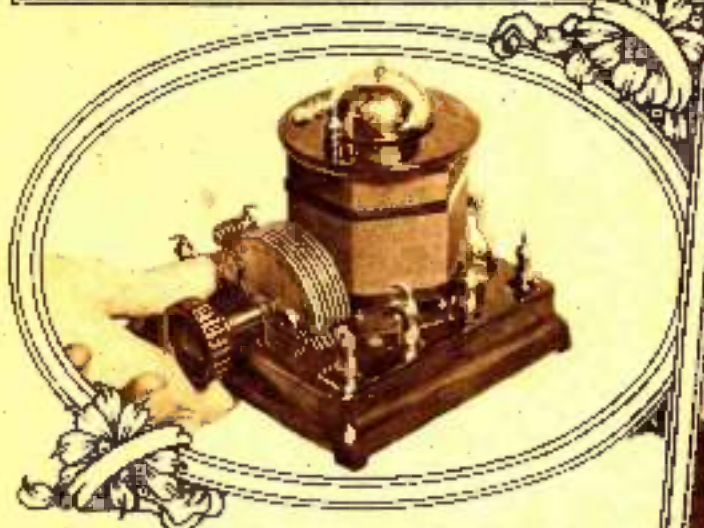A HAMMERED COPPER PANEL is the novel feature of this Super-Heterodyne receiver built by Alfred Savareno, of New York City, who is shown beside it. The panel is made of hammered chased copper and is a thing of rare beauty. It seems an effective shielding. © Kadel & Herbert



JUST A HANDFUL. This miniature 1-4-ga tube regenerative set of unusual construction works as well as its big brothers. Note the scale engraved on the foremost rotary plate of the variable condenser. The pointer is mahogany. © Kadel & Herbert



CRYSTAL SET OPERATES LOUD SPEAKER, but a special attachment is necessary. The special apparatus is seen attached to the turn table of the phonograph. The volume obtained on local broadcasting is equal to ordinary phonograph volume. What more could one want? © Kadel & Herbert.



A **MINIATURE LOOP ANTENNA** of singular construction was one of the many interesting exhibits. The frame is moulded out of pyradialin, a compound similar to bakelite, and the method of winding the turns gives a low distributed capacity. © Kadel & Herbert.

the Radio World's Fair



THE 50th REGIMENT ARMORY, New York City, where a portion of the Radio World's Fair was located. © Kadel & Harberg.




THE LARGEST RADIO INSULATOR in the world; one of the many insulators designed particularly for the high powered short radio stations of the U. S. Navy, exhibited at the Radio World's Fair. How about a couple of these for your aerial? © Kadel & Harberg.




NEW NAVY TRANSMITTER with a power of 200 watts. It employs twelve 50 watt tubes and can be used for C.W., J.C.W. or Radiopneum. It was designed especially for use on the Man o' war. Chief Gunner F. C. Hantz and John Cox are shown demonstrating it at the Radio World's Fair. © Kadel & Harberg.

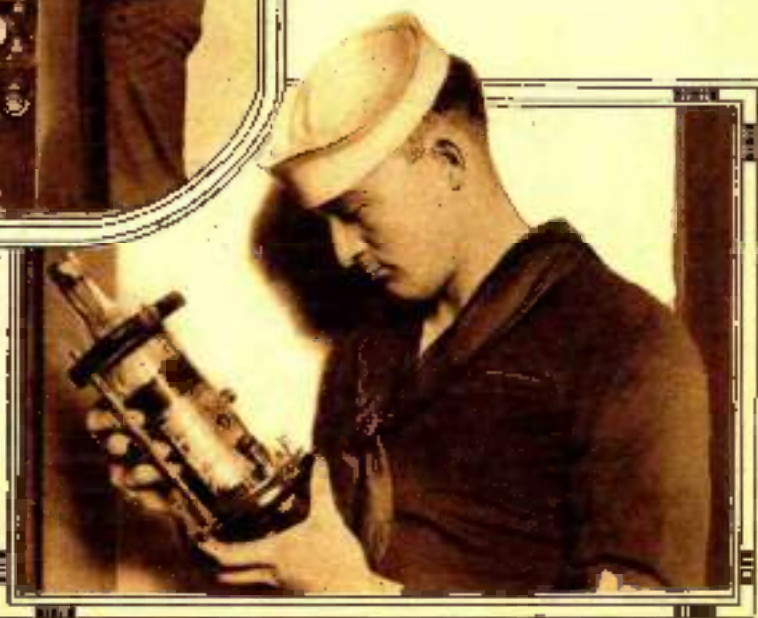A WINK BOTTLE RADIO SET, exhibited at the Radio World's Fair. This interesting two tube vacuum coil crystal set is made out of a German wine bottle that has seen better days but judging from its naval employment it still has one or two kicks left for the owner. © Kadel & Harberg.



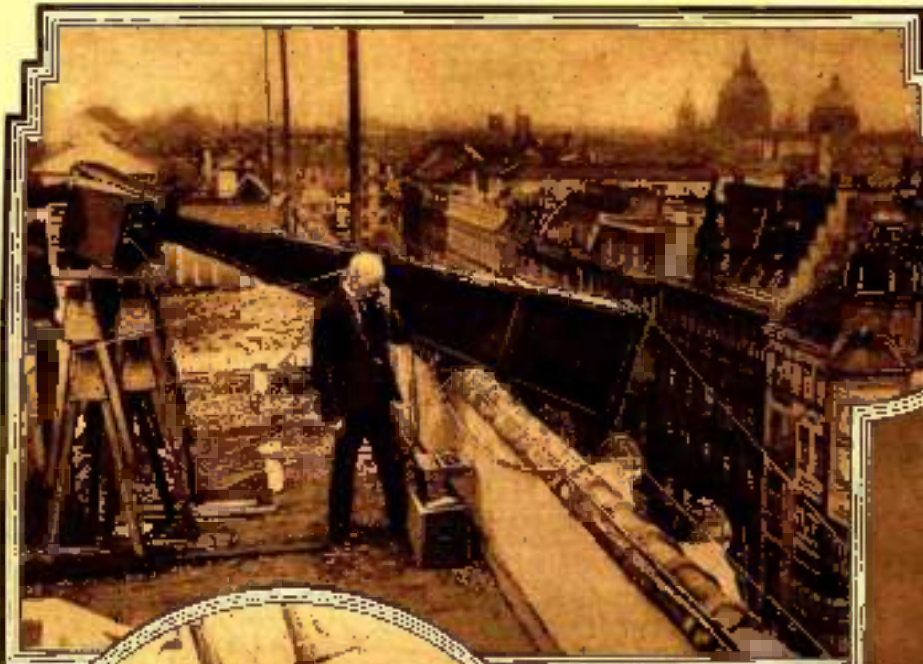
WAVE MUSIC TO THE CROWD BELOW The apex of a Berlin merchant who desired a novel form of advertisement. A huge loud speaker was placed on the roof of the building and the best of German broadcasting led to it, through a power amplifier. There is a public park below where the people gather to listen to the program. (Kadel & Herbert)



RADIO IN A TEA-POT. What an ideal! How sweet! And the damsel in the picture none other than the nationally known dealer—Gilda Gray. This receiving set was entered in the prize contest for a series of amazing construction at the Radio Exposition. (Kadel & Herbert)



CAPTAIN DONALD G. MACMILLAN RETURNS FROM THE FAR NORTH: the Bowdoin anchored at Wiscasset, Maine, after her trip to the Arctic. Radio WNP, the "Bowdoin" was almost constantly in touch with the "outside world" through amateur stations in the United States and Canada. Donald Mac, the operator of WNP, is to be given credit for his excellent work during the absence of the "Bowdoin" from civilization. (Fido Tapira, Inc.)

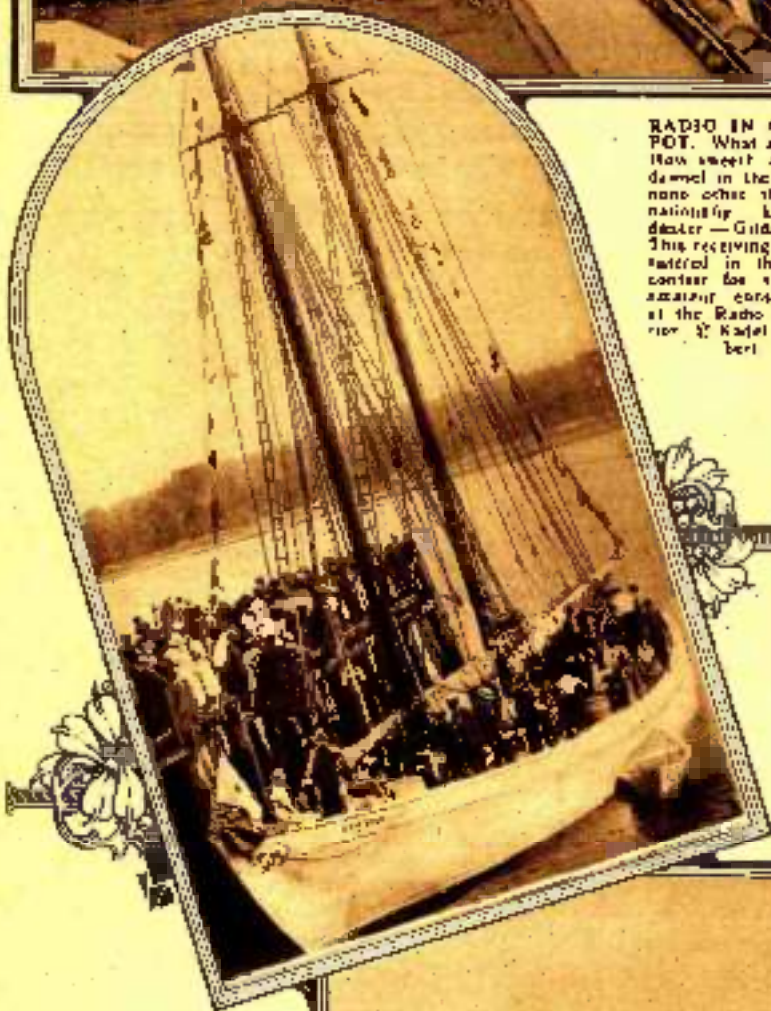

SET YOUR CLOCK BY RADIO. The photo shows the apparatus which does the trick. This is the result of recent experiments carried out by experts of the U. S. Bureau of Standards. The stunt is accomplished by the use of a standard form of radio receiver and a series of induction relays. One of these days, no doubt, it will be a little easier to wake that will wake you in the morning—by waking off your alarm. (Kadel & Herbert)





A SINGING ARC OF OLD was one of the novel attractions at the Radio World's Fair. This queer looking machine is an old singing arc radio-telephone transmitter, a relic of bygone days; it was built in 1917 by P. E. Butler, who is shown on the screen right, demonstrating it to a group of interested amateurs. © Kadel & Herbert

BOTTOM - RIGHT



DONALD E. MACMILLAN TELLS THE WORLD of his trip to and from the Arctic, near the radio. He is shown here speaking into the microphone at station WABG, Richmond Hill, L. I. He had with him his favorite Eskimo dog, which also gave a short talk on "The Call of the North." © Ymagina, N. Y.



TOP - LEFT

GENERAL PERSHING'S FAREWELL SPEECH to his comrades at arms was delivered through the medium of the radio, his words being carried over thousands of miles of telephone wires from coast to coast and border to border as they entered a microphone at the War Department. His message was relayed through 38 broadcast stations. This was the most wonderful piece of work ever accomplished in the art of broadcasting. © Henry Miller News Picture Service, Inc.


LOPEZ AND DEMPSEY. Yeah, Vincent is explaining the mysteries of radio to Jack while sitting in on his own orchestra. You see, Jack visited Vincent. He said, "I learned about jazz from Vin.; but Vin. didn't learn anything about the art of tuning." © Foto Topics, Inc.





TO SCHOOL WITH THE RADIO is Master James Scull's idea of real fun, but he doesn't let it interfere with his lessons. He agreed to leave his radio set all day so he rigged up this three tube reflex on his bike and listens in at lunch time and on his way to and from school. *A. Athletic Bone Service.*

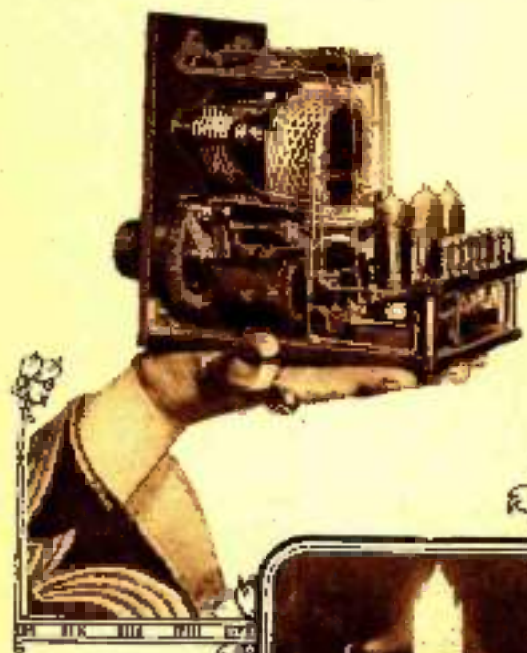THE FORGOTTEN APPLE. A typical case of radio fever. Master Herbert Roy Fox is so taken with a radio program that he has entirely forgotten about the beautiful apple mother gave him. Radio fever affects the young as well as the old in some.



A MIDGET THREE TUBE SET said to be the smallest of its type in existence. It is 3 1/2 inches long and 3 1/2 inches high. All the apparatus is standard except the vacuum tube sockets. It employs a regenerative circuit and a two stage audio frequency amplifier. The set was built by D. F. McQuire, Baltimore, N. J. *Photograms, N. Y.*



COLONEL GREEN in his radio laboratory at Round Hill, Mass., surrounded by a number of embryo inventors employed by him to work for the advancement of radio. At present they are experimenting with a radio station picture system. *C. Photograms, N. Y.*



YOU CAN'T HELP BUT SEE THEM day or night. The two antenna towers supporting the antennas of station WHO, Des Moines, Iowa, as they appear at night. They are illuminated by search lights and each tower has a beacon light on its top. *J. Kadel & Herbert.*

La Presse


CKAC
Montreal, Canada



THE STUDIO OF CKAC is unsurpassed in its beauty—the interior decorator was truly inspired. Note the microphone and stand in the foreground.





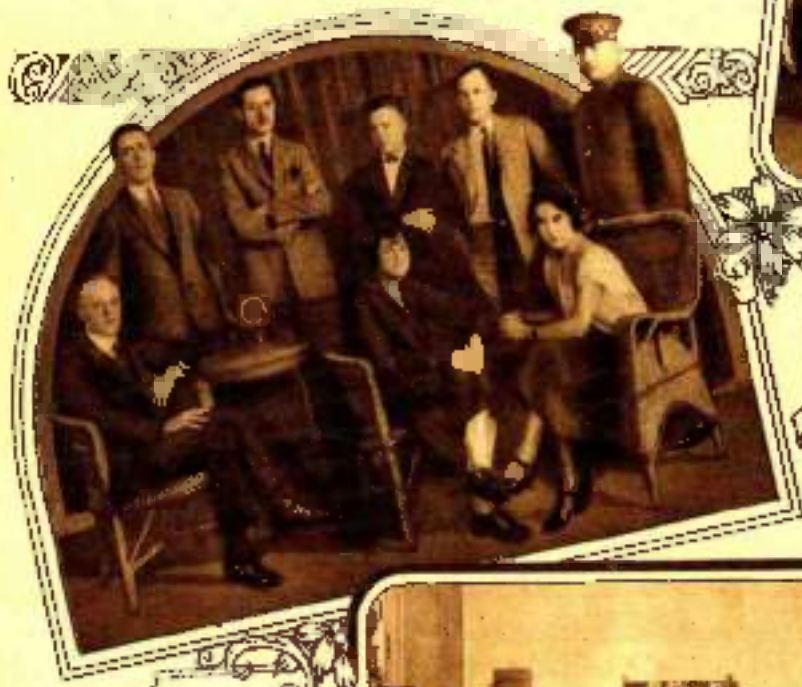THE STUDIO ORGAN is a work of art in itself. Its rich tones are picked up by the microphone in the foreground and reproduced perfectly for critical ears.



AN ALL BILINGUAL PERSONNEL is the staff of CKAC La Presse. We introduce, from left to right, standing, Arthur Dupont, Assistant Announcer; Adrian Aresed, Radio Editor; Leonard Spruce, Technical Assistant; J. N. Gosselin, Director and Chief Announcer; A. Lebel, Master of Ceremonies; and sitting, J. P. Collin, known to kiddies as Father Radio; Mary Brennan and Norah O'Donnell, typists and stenographers.

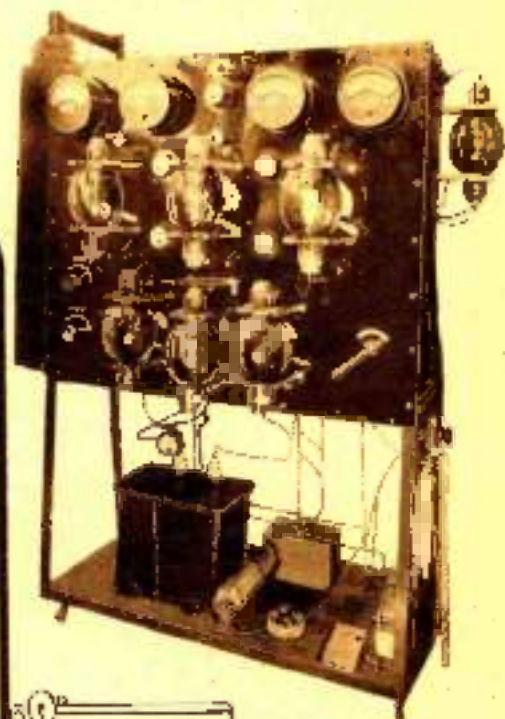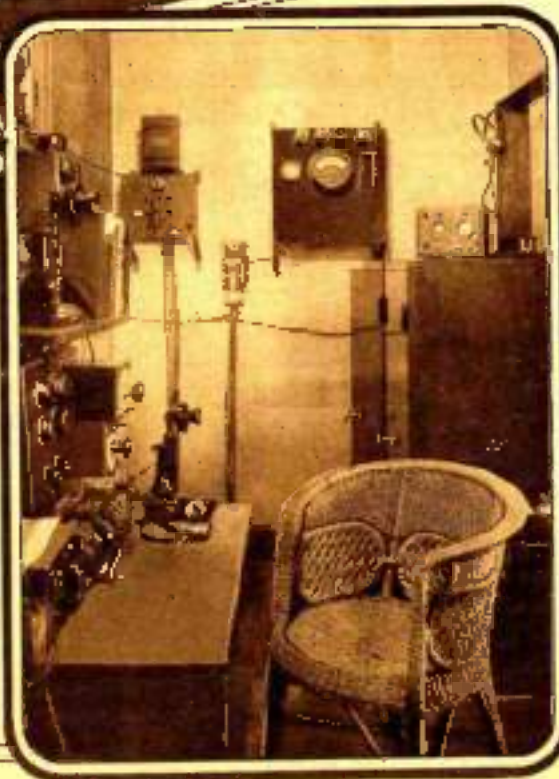THE CONTROL ROOM is shown in the photo to the right. From this point the "be" transmitter is made to "do its stuff" and so it is a wonder to your home. It is carefully trafficked on the 475 meter wave and is not allowed to roam. Over-modulation is never allowed.



THIS IS THE TRANSMITTER and it is a new one, with a power of 7½ kilowatts! See the nice big tubes! It is so sturdy that they are worked hard, but when they are let loose there is no telling how loudly CKAC will be heard in Europe.



The Life and Work of Lee De Forest



PART III

THE day was a warm one in Spring. The laziness of late June was announced by the drone of insects and the gentle rustle of leaves. The tall stately elms of Yale stood in the heaviest of verdure keeping a lazy watch over the campus against the return of the hordes in search of knowledge. Commencement was just over, the last of the stragglers had just seen their trunks and luggage hauled off to the station in the town's disreputable express vans and the stragglers themselves stood about smoking a last pipe while they prolonged a good-bye until train time.

The walks and campus greens were deserted in a few days. Summer had settled down over New Haven in its fullest sense. A young man strolled leisurely up to Jackson's restaurant. He had a couple of books under his arm and was holding a paper with his free hand. Evidently he had come from the railroad station and was in search of some one. In the restaurant he went to one of the tables in the rear, after speaking to the waitress, sat down and ordered a cup of coffee. He asked after his friend Barbour. He hadn't, the waitress said, been in that day, but she added that the day was yet young.

CONTEMPLATES POST GRADUATE WORK

Immediately the young man pushed his paper to one side and opened the larger of the two books, which was a heavy treatise by an Englishman named Maxwell who had done, it seemed, a great deal of experimenting with electricity and had developed several theories concerning the magnetic properties of coils through which electric currents were passed. The young man was extremely interested in his book for he had, less than a week before, graduated from the Sheffield Scientific School of Yale University in the class of '20. Nevertheless, he was already contemplating three years of post graduate work looking toward a degree of Ph. D. and he chose to make investigations along the line of those in the Maxwell volume, except of course, experiments would go further than those delineated in the heavy book. He was also extremely interested in the wave motions which seemed to postulate themselves more and more prominently as the underlying principles of electricity became better known.

The diploma which the young man had recently received, and which he still placed on his bureau to gaze upon each night before retiring, was given, according to the Latin inscription upon it, to one Lee De Forest.


From time to time as he sat pouring over the pages of fine print he took a drink of the coffee before him. When the coffee was all gone, he paid for it out of a well worn wallet and walked slowly out to the street and up toward the campus, his two books under his arm. As he started to take a short-cut up toward one of the dormitories, a decided expression came over his face. He looked around, seemingly as if he were trying to find himself in some strange surroundings. Then he bowed his head a little and hastened his speed. Near the dormitory he looked up and gazed "Oh, Barbour"

"Ye ho" came the answer and a touselled head thrust itself out of one of the upper windows. A few minutes later Barbour came down the last flight and asked DeForest if he had had lunch. DeForest had, so they decided to walk to the lake.

"OLD GRADS," BOTH

As they left the campus, both looked fondly and sadly around at the buildings, the ivy and the arching trees. They reminded each other of the good old times represented at each of the crannies about the buildings. They convalesced themselves as having passed the under graduate days and being at last lonely "old grads."

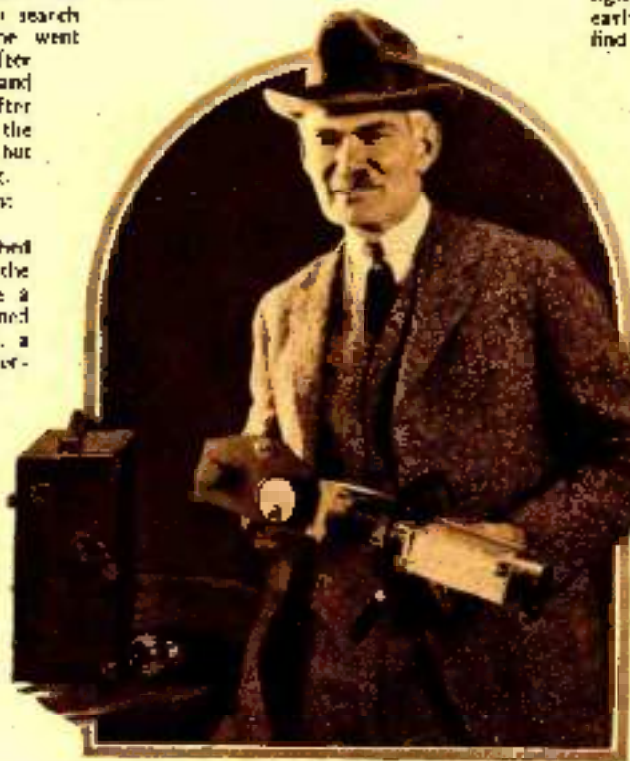They were sad. Every man who has left an Alma Mater after four wonderful years understands the feeling. With such a sentimental person as DeForest it is not unusual that this feeling should run to the highest pitch.



Dr. Lee De Forest holding the Phonofilm recording device, one of his latest inventions.

Once away from the campus, however, their talk turned to other subjects. With the last of the summer came the great Presidential election and the first race made by William Jennings Bryan. It was the first election in which either of the young men could take a part, both having just recently become of age. They had long talks as they walked, and covered the whole field of politics from the theoretical limitations of the state to the comparative honesty of the two chief candidates.

From politics the two young philosophers would pass on to the inevitable dream of youth—a Utopia. Hour after hour they would devote to the specifications of their perfect state, dealing in details of the wonderful organization down to the mechanics of the Public Health system. This latter point always obscured on account of the very bad and ever debated sewage system

of New Haven. From their Utopia they would pass on to some engineering problem of the time. It was DeForest's general procedure to name some great want of the country such as electrification of the railroads and then proceed to plan ways and means for doing it. They would spend hours on the problem at hand and having exhausted themselves with their labors, return late to town, go to Jackson's for an omelette or a very thin steak and a cup of coffee, thus closing an enjoyable day.

At other times Barbour could not go and DeForest would start out by himself. Some new creek or small river would catch his fancy. He would make a long exploration trip in search of a fairy-like spot in which to sit and contemplate the woes of the world and the beauties of Nature. Sometimes he would find a particularly soothing place and would return home with the light of a Thoreau converted in his eye. The early hours of the following morning would find the light still burning in his room and Lee sitting at a table laboriously pouring forth his soul on paper, attempting to put the beauty of the past evening into his diary.

As the summer moved on, DeForest spent more and more of his time in the country around New Haven. For the first time in years, much to his disgust and chagrin, he had little to do. He could find no work during vacation time, so most of his time was spent to suit himself. During the bright days he roamed the fields and took hikes. In the evening he returned home to his books, the reading of Maxwell and Hertz occupying most of his time. Toward the latter part of the summer he discovered Emerson and immediately became a slavish disciple of the Boston sage. For recreation from his studies he read the poems and tales of Poe—for the fourth time. He obtained odd jobs with various companies around New Haven. He spent a few days reading meters for the gas company and did some work for older post graduate students in the laboratories.

BEGINS POST GRADUATE WORK

The beginning of the school year in September brought back the old accustomed rush of activity. His course consisted of higher mathematics, with particular relation

to vector analysis and analytical equations, alternating currents, theories and history of electricity, and advanced mechanics. For his laboratory work, he was given a place in one of the laboratories under Prof. Chas. Hastings. The first couple of months in the school year were spent entirely in lectures and reading. His first actual experimenting along original lines was begun in the autumn of 1904, in November or that year to be exact. His first step upon being assigned to a division of the laboratory was to select the various instruments and calibrate them. He spent numerous unpleasant hours at his work since a veritable flood of logarithms occupied his hours while he was calculating the constants of the various measuring instruments. He ate

and dreamed logarithms for a week at a stretch. He almost considered memorizing the tables in order to save the time necessitated in looking them up.

The work was so entirely new to him and the professors were proceeding at such a rate he had little time for anything else. The first break in his routine after the beginning of the work was the death of his grandfather, just at Christmas time.


Coming just 11 months after the death of his father, the blow was exaggerated. He felt it not so much from a sense of personal loss as from the effect it had upon his mother. She had not yet fully recovered from her husband's tragic death. Then, too, it was mid-winter and the family was in dire financial straits. The Christmas had promised to be a sad one—the year had been the hardest in the history of the family. And to add to the already great load of sadness, a few hours after the arrival of the telegram announcing the tragedy, the postman brought a letter to each member of the family written by the old man just a few hours before his death. Each one contained a new dollar bill as a gift of the season.

THE PROM AND HELEN

However, such sloughs of despondency never held him entirely for long. About that time he had decided upon inviting his beautiful Boston cousin to the annual Junior Prom. He had already broached the subject to her in letters and as the time for it drew near he pressed his invitation. After posting the letter in which he urged her acceptance, he immediately was brought back into the old pit of torture. His conscience troubled him for days. And to make it worse, the return of his mother from Iowa was delayed a few days, and the acceptance from Helen, his cousin, was in his hands before his mother returned.

The situation came to more pleasant results than he expected, however. His mother was compliant; in fact, she was more or less in favor of the visit. The Prom was set for a few weeks after Christmas. Preceding Helen's arrival on the scene, the house was decorated and the rooms rearranged. Lee was a victim of himself. Having the best room in the house he was forced out of it in order to make room for his visitor.

She arrived. There was a pleasant day of walks about the campus and the favorite haunts of the students. Then the big night. Dressed as he had never been before, he hired a cab, weeks before he had, with four other social climbers of Yale, bought a box at the Prom and was prepared for the most enjoyable evening of his academic year. All went well at the start, but one can never forecast events. Before the evening was over, a combination of pride and jealousy arose to take the keen edge from his happiness. Helen was dancing with a great number of other men. Lee was self-

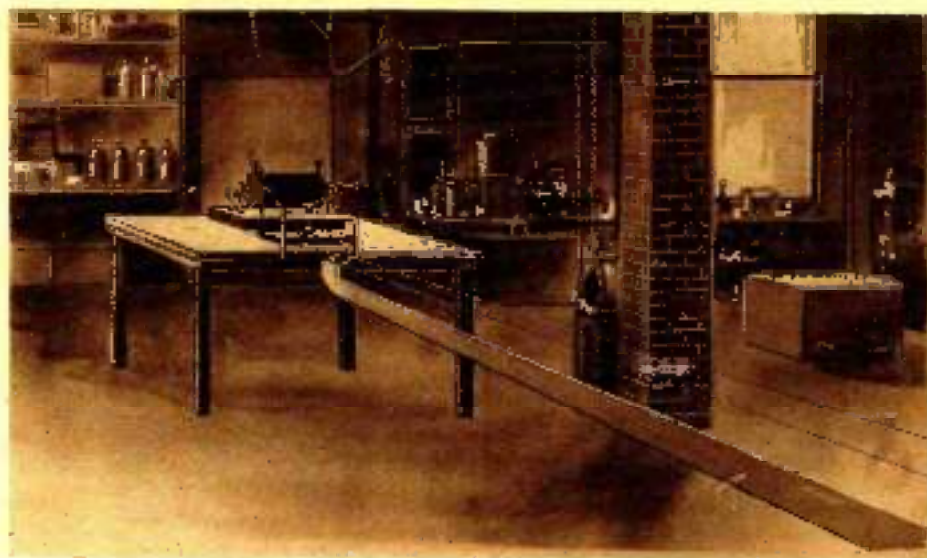

Some of the busiest days of DeForest's life were spent in the laboratory shown in the above picture. It was here he made his first acquaintance with ether waves.

appraised as to his abilities on the dance floor. But he did not think that this slight defect in his social equipment was sufficient to warrant the coolness in his cousin toward him, which he accused her of showing. The evening was not totally spoiled. There were many pretty girls and the atmosphere was one of gaiety and abandon. By comparison to his general routine it was a Bacchanalian revel.

LOVE ATTEMPTS TO ENTER

At four o'clock in the morning, with an air of the Gay Dog, Lee held his arm for his lady, hailed one of the cabs standing by, with a bit more of a flourish than was actually necessary to call the cabby's attention, helped Helen into the dark recesses of the musky-smelling vehicle, took his own seat and gave the man on the box the address. As the street lamps temporarily lighted up the interior of the cab, a young man might have been seen gazing with a discernible bit of worship in his face at the very tired and sleepy, though happy young girl beside him.

As with most such cases of young love there is an anticlimax, and it usually is surprisingly humorous and often pathetic to the onlooker. At the house, the two revellers slipped into the parlor and doiled their wraps. Lee showed Helen to her room and on the stairs dared to mention his extreme happiness at having her as his guest to the greatest of Yale's annual functions.

Now it has been mentioned that the young lady made her home in Boston and it is a generally known fact that Harvard is situated almost within a stone's throw of that town. And, one may conclude from the

fact that the young lady was pretty, well bred and of good family, that she knew a much larger number of Harvard men than students from Yale. All these young men, in justice to their alma mater, had told her of the virtues of their own institution as opposed to the vices and shortcomings of their opponents, Yale. The volume of evidence decided the issue. At heart, Helen was loyal to Harvard. As the hour was very late and a drowsy hack ride had just been concluded, the young lady's reaction was more natural than studied. She repeated some chance remark that one of her Harvard friends had made. The result was instantaneous. Lee resented the fact that she should make so obvious her preference to a rival, may a hated university, and said so.

Helen ended the incident with hauteur.

HELEN IS TAKEN ILL

The following morning found the young lady dangerously ill with appendicitis. After three days passed with a growing seriousness in her condition, her mother was called to the bedside and a medical consultation was called. The girl was too ill to be moved and the doctors declared that an immediate operation was necessary. She was taken to a local hospital where the operation was performed. Lee paid her a visit every day while her condition was serious. Sometimes he would send flowers.

He had announced himself in several places in his diary as being "upon the verge of falling in love with Helen." He still held this idea even after the Prom episode. The visits to the hospital were sometimes tender and charming. After a long and perilous convalescence Helen was able to return with her mother to her home. "Poor little Prom girl," Lee wrote in his diary in closing this sad episode.

All the while, he was continuing his work in the laboratory and keeping constantly at his reading in electricity and mathematics. It was shortly after the beginning of 1897 that he made his first real acquaintance with the electric condenser, that is, he began some experiments with it. Immediately, thousands of possible uses for this device thrust themselves into his consciousness. Of them he wrote in his diary, "It flashed across me today—my special first field of electrical enterprise—the condenser half brother to the transformer, more efficient, cheaper, lighter—to develop it. Make it take the transformer's place both for phase alternation and also for step up and down—superseded everywhere—Millions! Then find

(Continued on page 1087)



As DeForest looked during his Spanish American War experiences. He was fond of riding and loved his horse.

The Latest Radio Swindle

By HUGO GERNSBACH

Member American Physical Society

Every new industry or a rule is explained by legitimate business as well as by "business" that is neither legitimate nor anything else. Attempts are often made to delude the innocent public by pseudo-scientific means. One of the most flagrant recent swindles is here described.



Right: "Feeding the nerves with Transmission." Another caption under the same photograph taken from Dr. Rogers' pamphlet. If we can believe Dr. Rogers, by means of this bakum, box position—hook-up—we can "test the capacity and inductance of the brain and the chiropressor will know the degree of INTEREST. FERENCE in the flow of life force." Said to relax, squelch, we do not believe Dr. Rogers.

Abuse: "Determining the capacity and inductance of the brain. Absolutely no electricity gets to the patient." So reads the highly interesting yet nonsensical caption printed underneath this picture in Dr. Rogers' pamphlet.

SINCE radio became popular, the general public has pounced upon it as the marvel of the age, which truly it is. The non-technical man, if told of any new and seemingly impossible wonder that has been performed by radio is not at all incredulous, but willing to believe anything and everything, as long as the magic word of radio is connected with the new wonder. If it were to be announced tomorrow by some experimenter that by means of a new radio outfit we could live to be a hundred, there would be a huge sale for such an outfit. Indeed, there is very little the public will not believe that cannot be accomplished by means of the marvelous radio.

We had occasion before to mention through the columns of Radio News a new crop of unscrupulous exploiters who have sprung up of late to take advantage of the public belief in radio in order to make huge sums of money. In our June, 1924, issue we showed some of the taking which has already been carried out. It seems that only the fullest and widest publicity can eradicate the new evil with which radio is threatened. In the non-technical man, we give this warning—IF AT ANY TIME YOU ARE APPROACHED BY A SO-CALLED "DOCTOR" OR PRACTITIONER TO UNDERGO A PHYSICAL TREATMENT IN WHICH A REGULAR RADIO OUTFIT IS USED—SHUN HIM AS YOU WOULD SHUN A BURGLAR. Both operate on the same principle, namely, to extract money from you, with the difference that the burglar should get the benefit of the doubt—at

\$1,000 Reward

RADIO NEWS challenges Dr. George D. Rogers, D. C., Ph. C., the manufacturer of the NEUROPHONOMETER, to come to New York City and demonstrate his NEUROPHONOMETER before a body of twelve scientists, composed of six physicians and six scientists, all of good repute and standing. If these independent twelve men decide that the claims put forth for the NEUROPHONOMETER by Dr. Rogers are founded upon scientific truth, RADIO NEWS will pay over to Dr. Rogers the sum of ONE THOUSAND DOLLARS (\$1,000) plus HIS TRANSPORTATION TO AND FROM NEW YORK.

THIS OFFER WILL BE OPEN FOR SIX (6) MONTHS.

least he is fair minded about it and does not deprive you of your hard earned money under false pretences.

We have to do with the Wonder (?) of the Age—THE NEUROPHONOMETER, manufactured by one George D.



Rogers, D. C., Ph. C., former Dean of the Texas Chiropractic College, 1715 Main Avenue, San Antonio, Texas.

We give Dr. Rogers full publicity so the Neurophonometer so that any individual who desires to know all about the "conductivity of his nerves" can buy this \$50 radio outfit masquerading under the high-sounding name of neurophonometer, for the small sum of \$500—CASH, as advertised by Rogers.

The Neurophonometer, as our illustrations show, is a regular radio outfit thinly disguised. On the front panel there is a vacuum tube for some reason or other not very clear to anyone and a Baldwin phone. The outfit looks very formidable, to say the least, and the poor victim who is to undergo treatment must certainly be inspired by the sight of the variegated knobs, voltmeter, dials and other paraphernalia which are soon to help cure him.

The Neurophonometer is of course never sold to private individuals. It is sold to certain practitioners who fall for the humbug and who in turn tickle their prospective victim's spine by means of a "iron" electrode supposed to carry the radio current.

The following paragraphs are taken from Dr. Rogers' pamphlet.

"The Neurophonometer is a highly sensitive electric instrument constructed to measure the exact conductivity of the nerves of the entire body. The Neurophonometer does not measure the conductivity by a hypothetical point called normal, BUT IT DETERMINES THE VARIANCE FROM THE CAPACITY AND INDUCTANCE OF THE BRAIN (DYNAMO) WHICH GENERATES THE LIFE FORCE OF THE BODY. THE RATE OF THE GENERATION IS THE RATE OF CONDUCTIVITY. IF THE NERVE IS FREE FROM PRES-SURE. If there is interference with the flow of life force, the Neurophonometer will register the degree. Surface temperature does not alter the efficiency of the Neurophonometer, because IT IS ACTUALLY DETERMINING THE CONDUCTIVITY OF THE NERVE. This was determined by locating an impinged nerve with the Neurophonometer under ordinary conditions, then heat was applied over the

one being tested, then the instrument showed that the heat increased the conductivity of the nerve about one fourth of a unit, an ice pack was then applied over the same nerve, and the instrument showed that the interference is increased by the cold one third of a unit. BY ELECTRICAL LAWS HIS TEST PROVES THAT THE NEUROPHONOMETER ACTUALLY MEASURED THE CONDUCTIVITY OF THE NERVE.

"Probably the most important feature of the Neurophonometer is the establishment of the positive normal conductivity of the nerves. This is important, BECAUSE EVERYONE HAS A DIFFERENT FREQUENCY, therefore, it would be very difficult to determine an average, even then the test would not be specific. BUT BY DETERMINING WHAT THE INDIVIDUAL PATIENT'S FREQUENCY is, then test the nerves by comparison, THE TEST IS ABSOLUTELY SPECIFIC AND SCIENTIFIC.


"AFTER THE CAPACITY AND INDUCTANCE OF THE BRAIN HAS BEEN DETERMINED, the free electrode is placed over the nerve to be tested. If this nerve is free from pressure, IT WILL TEST IN RESONANCE WITH THE BRAIN, but if there is pressure it will test BELOW THE CAPACITY AND INDUCTANCE OF THE BRAIN, and the chiropractor will know the degree of interference to the flow of life force.

"The tests are made with an oscillating circuit that is made audible by means of radio principles. Therefore, the test is an audible test, which is six times as sensitive as the most sensitive galvanometer. This, of course, increases the efficiency of the instrument in locating nerve impingements.

"The Neurophonometer is so constructed that the technique is easily and easily mastered, but of course, experience increases your efficiency. Its wearing parts are only three, and they are expensive to replace and your local electrician or radio man can make all necessary repairs or adjustments. You can learn to operate it in a short while, all practice makes perfect.

"Should you buy one, you will be instructed in its use. Its value or worth cannot be estimated in dollars and cents, however, we have decided upon a fair price which will always remain at a minimum of \$500 cash. Labor conditions and supplies may make it go

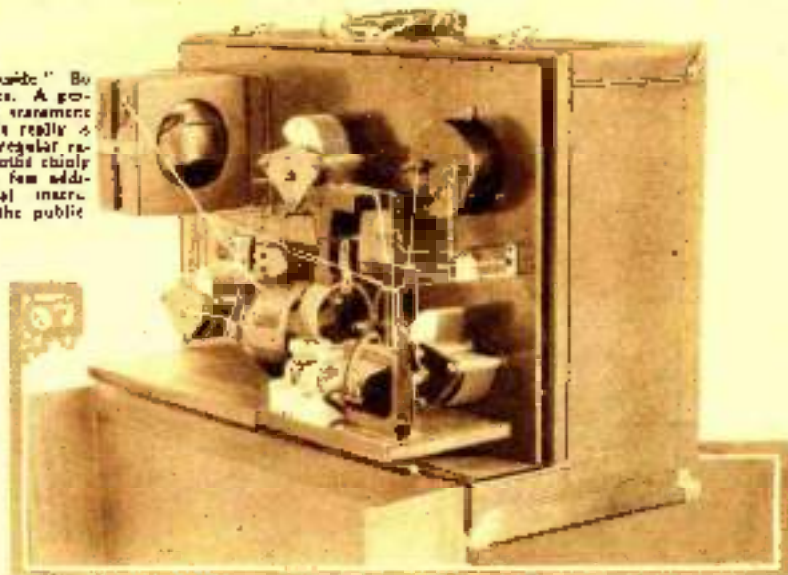"This is the inside." Says Dr. Rogers. A perfectly mechanical instrument in this case. It really is the inside of a regular radio receiver with a few additional electrical instruments to fool the public.



higher, but there is little possibility that it will ever be cheaper.

"Don't be afraid you cannot be supplied."

"We guarantee delivery in thirty days. There is no hurry.

"You have until tomorrow to decide, and should you want advice, seek it. Good advice is always desirable.

"The Neurophonometer is constructed and operated by POSITIVE LAWS OF PHYSICS. It will be opened up at any time for inspection by electrical experts, and its every part explained in detail. It can stand the test—it is so constructed.

"The Neurophonometer has been in the process of making for over a year, and it has proved its value to Chiropractic to the entire satisfaction of everyone who has seen the demonstration. The alarmist, the skeptic and the non-believer have all had their fling at this instrument and, as strange as it may seem, THE LITTLE VOICE OF INNATE SPEAKS THROUGH THE TRANSMITTER just the same and tells the Chiropractor THE EXACT POINT OF INTERFERENCE WITH THE TRANSMISSION OF VIBRATORY LIFE FORCE.

"Don't discard your X-ray, it may mean dollars and cents to you sometime in a malpractice suit.

QUESTIONS ANSWERED BY DR. ROGERS

"Q. How does the Neurophonometer

differ from other instruments announced?"

"A. We have not seen the other instruments. The Neurophonometer is A PROVEN SCIENTIFIC INSTRUMENT, WHICH REGISTERS THE LIFE FORCE being carried by a nerve.

"Q. Is the Neurophonometer difficult to operate?"

"A. No. The instructions furnished are sufficient to learn to operate this instrument. You will improve continually as you use and operate the instrument, the same as driving a car. It is operated similar to a radio receiver, BUT MORE SIMPLE.

"Q. How long does it take to make a reading or analysis of the spine?"

"A. Average, ten minutes.

"Q. Does the patient feel any shock?"

"A. Absolutely none.

"First, the Neurophonometer is not a mere finder of hot-boxes. In fact, its functioning does not depend upon surface heat at all. What the Neurophonometer really MEASURES IS THE ELECTRICAL CONDUCTIVITY OF THE NERVE, and inasmuch as science has virtually established the fact that the transmission of impulses over nerve is essentially electrical in nature, THIS MEASUREMENT OF ELECTRICAL CONDUCTIVITY CONSTITUTES A DIRECT INDICATION OF THE ABILITY OF THE NERVE TO TRANSMIT MENTAL IMPULSES. Here we have a direct means of determining the degree of impingement on any nerve.

"The second great advantage of the Neurophonometer is that in getting a reading the operator is guided by his ear. With receivers clamped over his ears, he adjusts the dials so as to get the maximum sound. Such a method is regarded by workers in the exact sciences as being at least ten times as sensitive as any recording device and is resorted to whenever great precision is desired and the nature of the work permits of its use."

The parts which have been capitalized by us show the silly nonsense that is being paraded before unsuspecting buyers. If Dr. Rogers sells many of these \$500 outfits for \$500 he should soon grow rich, but it is particularly the crass nonsense of the technical verbiage that Mr. Rogers uses which is so offensive to the man of science. For instance, the sentence—"After the capacity and inductance of the brain has been determined, the free electrode is placed over the nerve to be tested. If this nerve is free from


(Continued on page 1085)



Meet the latest radio wonder—the Neurophonometer, shown here in all its glory. In addition to being a regular radio outfit it also possesses an extra bulb in front of the panel, also a telephone receiver shown to the left of the meter. Nifty contraption, we say. It will positively determine the capacity and inductance of the brain.—NOT

A First Night With a First Set

By JASON C. GRANT

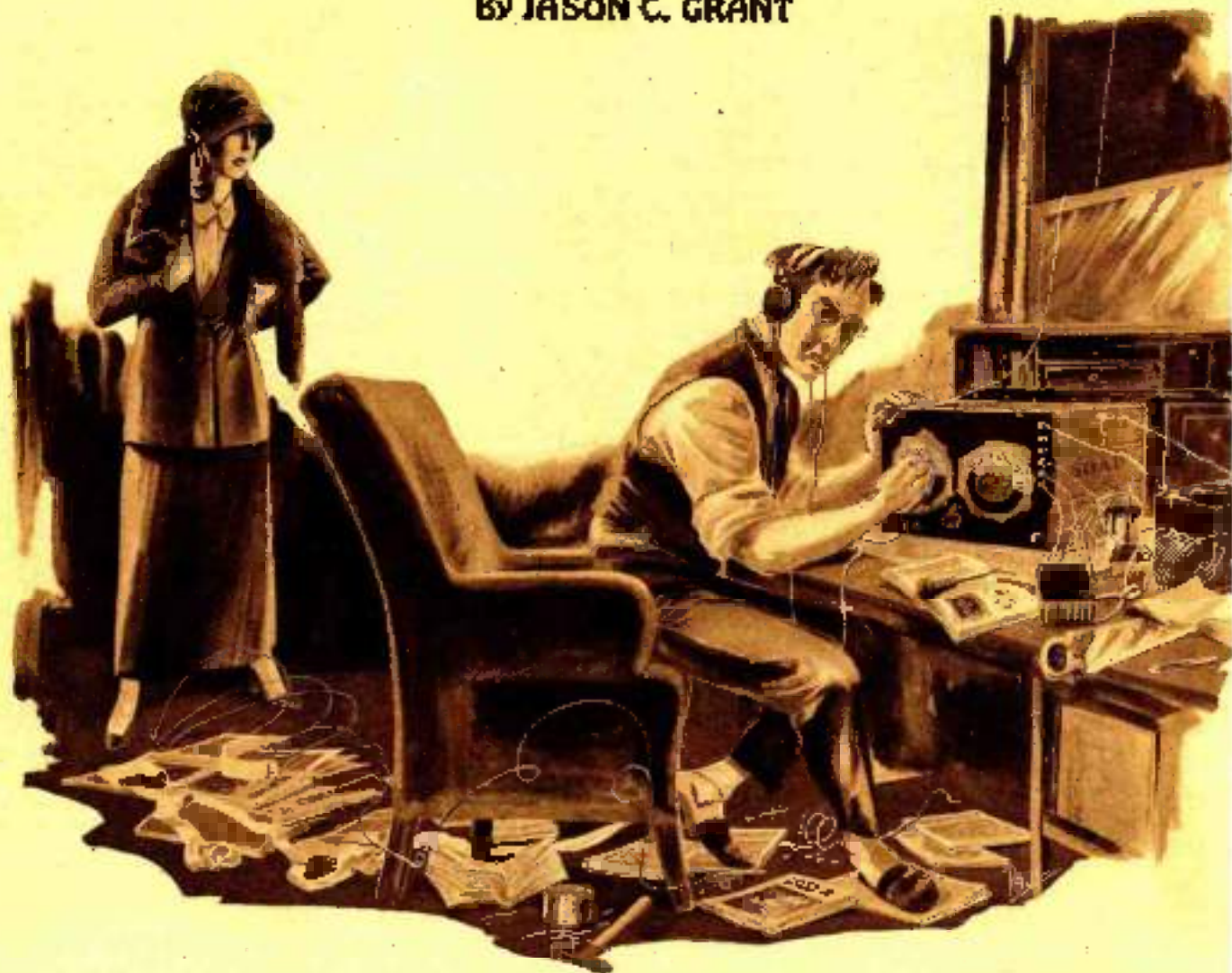

She stepped forward so heavily that the floor scruffs shook, and began in a high pitched voice the barangue to which I had resigned myself.
 "Bill Gaskins! Are you a fool? Do you mean— She never got a syllable farther.

I DIDN'T know much about radio in those days back in the summer of 1922 (I don't know much about it now.) I had never even seen a receiving set except in pictures. What one looked like on the inside was both a puzzle and a mystery. Nevertheless the articles on radio, the reports of people who had successfully built "their own," the pictures in the advertisements, not only aroused in me an interest in the subject but fanned it into a zealous desire to make a set.

"Why not?" I asked myself. Even kids were getting a thousand miles on sets they had built.

I felt hard. I use these terms not because I have any regrets to offer, for I have none, but there is one incident in my career as a fan which came near ending in a manner which would call for regrets. It is this incident that I am about to relate.

As mentioned above, I fell completely for the game. I decided to build a radio set, although I had never used a saw except on cord wood. I had a purely imaginary conception of a breast-drill, a bushing, a binding post and a tension spring. Of course variocoupler, variometer, condenser, grid leak and rheostat meant absolutely nothing to me. And then there were EMF, DPDT, mfd., D.C.C., D.S.C., and a whole host of symbols, abbreviations, and equations which

rendered, with rare exceptions, the technical articles on radio enigmatical to me.

And still I was mystified. But one writer had said, "Anybody with common sense can —." I had common sense, or, at least I thought so, and I jumped into the thing without knowing just where I'd come out, or even whether I'd come out or not.

The trouble started when I got my first box from the grocery store. I had selected it with great care,—all of the boards were whole, and so I carried it home with a fine feeling that I had started well. Then came thoughts of the panel and the baseboard I could make out of it after I had knucked it down, dressed the boards with someone's plane, yet to be borrowed, and sawed them into the proper lengths. I was quite in another world. When I arrived home, I hid the box under the back porch, returned to the front door, and entered in the usual manner. Two days later I discovered the box filled with ashes and rubbish of all kinds. There was no use saying anything about it, no use arguing: I could get another. The only thing I regretted was that I had asked my wife where the box was before I found it, for she attached significance to my asking and, by going through an elaborate process of reasoning, reached the conclusion that the box had something to do with radio. In a word, she

sensed just what I was planning.

She didn't mind my being interested in radio, but she did mind my making a set out of the salary of a common clerk and she did mind the mess I had already made about the house and would make. I thought I should be doing the house cleaning, house patching, and numerous other things she had on her list for me to do during my vacation. All of this gleaned from her answers to questions relating in radio that I had put at various times when the psychological moment seemed to be at hand.

But I had gone too far to be stopped. I stood the strain as long as I could and then decided one Friday afternoon to buy some of the parts that were listed in a how-make-it article. I made my mind up in a moment. I would make a variocoupler. Straightway I went downtown to a hardware store,—I didn't know there were the regular radio stores in the little town. But by I went into the store, affected a ratt careless, know-all-about-it attitude, and asked with indifference for the article I desired.

"A pound of No. 24 direct current cops wire, please."

"You want what?" inquired the clerk, little puzzled.

(Continued on page 993)

Oscillations

By WILLARD WILSON

Editor of Radio News, which are not condenser of high-spoilage ideas, kinks and other useful pieces of radio wisdom.

Hon. Sir—

Recently, huge re-radiation have been sent in literary world of radio by many regulations, laws, etc., concerning dealers, amateurs, commercial operators and other inhabitants of radio world. The laws for such are being made so fast, Hon. Sir, I desire to insert plea for laws concerning other peopl. connected in radio, namely, men which sell radio parts, sets, etc.

My reason for such highly simplified de- are as following:

Great while ago I became painfully interested in radio, and also consumed with fire to possess receiver yet to pluck radio from set. Thudly I went to neighboring garage man which have become im-empire dealer in radio parts.

"Oh," he squawk featurally, "you wish to I your own, yes?"

I desire to do such," I refab timidly. "I are to have small diagram of hook-up for set."

"Blah!" he snort with nose wrinkle no attempt. "Such set can hear but small thing. You shall buy nice box of parts quite hyper-super-dome. Such are easily preferable to cheap crystal set."

"Maybe yes," I gargle back uneasily, "but have small amt of cash at present for di set. It will be too strained for me." "Ah," he squirt pitifully, "then I will re you small one-tube receptor for night- at sum of 80 hecres."

"Klik!" I squeal pitifully. "But I have by ten for in-vature in set at present!"

"Ten?" he pass uneasily. "Oh! I will



"Ten?" he typed uneasily. "Oh! I will give you small piece of nice enamelled wire, one spiderfoot coil and small paper condenser for this sum."

give you small piece of nice enamelled wire, one spiderfoot coil, and small paper condenser for that sum."

With protests of good-will I flee from clutches of such dealer, Hon. Sir, and slink into my humming back door of such.

Those, Hon. Sir, were my first experience with robber-thiefs under disguise of garage radio dealers. Since then I have become skunked by such in more deals than are castrail to relate. I have emptied pockets of week's wages to receive, in return, small, crippled battery of uncertain volting! I have paid converted bicycle man—who now rides in limousine and sells radio parts—great pile of cash for worthless Mazda lamps under name of V. T.

After great amount of earbreaking experiences, Hon. Sir, I have become forced to admit to myself, also wife, that many radio dealers, make wealthy foreign brokers (of pawn variety) look like generous philanthropists.

Do not understand such talk from me. At present I am no more skunked of huge amounts of cash, for reason that I have become acquainted with decent and honest radio dealer which are not trained as lux mechanic. There are such, Hon. Ed., if one are able to find them. There are also more cheap, better parts, which are able to be bought at standard prices.

Such radio dealers, however, which are (Continued on page 1924)

A Guess Evermore

(As Poe might have written it.)

By WARREN W. SCHULTZ

NCE upon a midnight dreary, while I pondered weak and weary,

Before the dial which I had purchased lately from a Radio store;

Suddenly there came a rapping, as of someone gently rapping,

Rapping at the speaker's core.

Is some static then I muttered rapping at the speaker's core,

Or this and nothing more.

It could not be I had blundered, yet the good loud speaker thundered,

For the tapping, growling tapping, moved the dog outside the door.

Quickly out the door he lumbered, and he neither slept nor slumbered.

While the good loud speaker thundered, thundered at its very core,

For he joined the wailing howling, sometimes barking, sometimes growling.

As he'd never done before. Only this and nothing more.

Now this rapping set me thinking, for I know I'd not been drinking,

Thinking evil thoughts about the man in our own Radio store.

Then I wanted to start asking, just like married people fussing,

But I dared not do a thing that I had never done before.

Instant within me I enquire, that all Radio men are liars.

That the frobs of course are bovers, and it made me very sure,

And that next day I'd consult him, use the noose and big tree on him,

Or knock him down upon the floor. Only this and nothing more.

Quiet, quiet, awful quiet, as in some great Chinese dore;

For the tubes which glowed so brightly now were silent evermore.

All the air rushed from my sails, and not as slow as gait of snails;

So I stayed inside the door, still on the rack reclines my hat, for I mistook "B" for "A" bar,

Which I shall do necevermore. Only this and nothing more.

MORAL

If you blame anyone for anything, first be sure you are not to blame yourself.



How Your Ear Helps Out Your Loud Speaker

By PAUL B. FINDLEY, E. E.*

Did you know that your ears have the habit of fooling you at times? Much to the credit of the loud speaker, Mr. Findley explains how and why the ear does it



Dr. J. C. Semmler adjusting a vacuum tube amplifier which will produce a pure musical tone of any pitch. Note the various dials under the table.

WHEN radio broadcasting started, the fan who had any sort of a set drew gasps of wonder from his friends when they heard some local station grunting out phonograph music. A year later, and the craze was for long-distance records. Then came loud speakers whose raucous hearings were an insult to the public's musical good taste.

Developed by men of brief experience in the art, having little or no knowledge of the acoustic principles involved, many of the early loud speakers were merely glorified telephone receivers, fitted to a horn and designed "by guess, and by gosh." Now that radio is settling down to a means of entertainment that must stand on its own merits in competition with other forms, the public is demanding a quality and volume of reproduction so faithful to the original that the listener can close his eyes and believe himself in the studio or concert hall.

Such faithful transmission and reproduction of a radio program is possible only when every link in the chain is carefully designed and skillfully operated.


The system must not fail to transmit the full range of tones; it must not add any tones of its own, recognized as "blur" or

"fuzz," caused by overloading one or more elements; it must not introduce noise, and it must give enough volume for comfort, yet not so much as to make the lower tones "heavy."

RESEARCH NECESSARY

To avoid these troubles, "cut and try" methods with the human ear and memory as

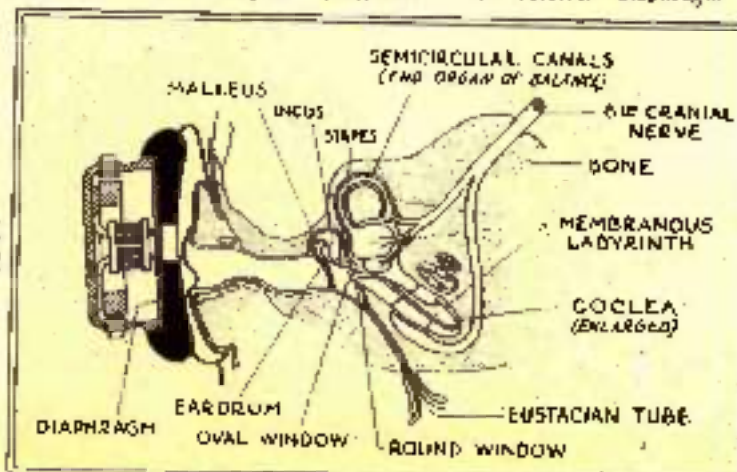A schematic representation of the human ear. Note the numerous organs necessary for our hearing.



guides will not serve. Present-day achievements have been possible only because measurement methods and standards rest on fundamental researches extending a more than a generation. The high-quality carbon microphone of today is a direct descendant of the granular carbon transfer on which Bell System engineers were working as early as 1886.

In the great research laboratories engineers are constantly studying every element in telephonic transmission, from speaker's voice to the listener's ear. So fascinating stories could be written of the things these engineers are doing; of them, perhaps the most important to the radio listener, deals with his own ears: how they interpret the air-waves in terms of sound. This work has been carried on by a group of scientists headed by Dr. Harry Fletcher of the Western Electric Co.

Sound is carried from the loud speaker to the listener's ear by air-waves. "Frequency," that term which recurs so often in radio literature, means the number of waves per second that pass a given point. The ear can hear—that is, translate the air-motion into sound—frequencies from about 20 to 20,000 waves per second, the range from 100 to 5,000 is the one it must be considered for good broadcasting.

The human ear itself is a fascinating study.

Beginning with the ear-drum, which is this membrane stretched across the end of the canal from the open air, the parts are as follows:

FIVE PARTS OF THE EAR

The drum, which converts the air-wave to mechanical vibrations.

A chain of three small bones—hammer and stirrup—follow. The last goes into the oval window, an opening in the cochlea. This is a spiral chamber like a snail shell, which is filled with a fluid. Down its center is a curtain called the basilar membrane, dividing the cochlea into two parts. From one side of this membrane emerge a lot of fine hairs. The roots of these hairs are in little sacs connected to the auditory nerve.

What happens when you listen to a radio program? The receiver diaphragm

*Member of the Western Electric Staff, associated with Dr. Fletcher

ates sending off air-waves. These in turn set the ear drum into vibration, passing a motion along through the three little bones to the oval window. The vibrations travel down one side of the winding curtain in the cochlea to a point determined by air frequency (number of waves per second). Here it becomes easier for them to go through the curtain and start back up the other side than to keep on down the original passage. Slow vibrations may go the length of the cochlea; higher pitches can go only a short distance. Where the vibrations pass through the curtain they make it move, and as it moves the fine hairs growing out of it first in turn excite the auditory nerve, and the brain gets the sensation of sound.

WHEN SOUND BECOMES FEELING

If the air-waves come in at less than about 20 per second, the whole fluid in the cochlea is moved back and forth, and the sensation is of "feeling" rather than of sound. This is what happens to some people when the lowest of organ notes are played; they feel a heavy fluttering sensation rather than a musical tone. And when the sound waves come in at 20,000 per second and up, the moving parts of the ear offer so much impedance that practically nothing gets into the cochlea.

Within the range of pitch that can be heard there are definite limits to the useful range, or loudness, of the sound. Beyond the upper limit sounds are felt, and are unpleasant if not even painful; below the lower limit they are not heard at all. The limit is lowest for sounds pitched about three octaves above middle C. Taking the louder normal sounds of an average voice as the speaker's lips as a very rough standard, the upper limit is 10 times as loud, while the lower limit for people of good hearing is one ten-billionth as loud. The range of loudness from the most intense sound to the weakest consonant in ordinary speech is about one million to one. The range of sensation is shortened as the air waves grow weaker and to a partially deaf person they fade out sooner. This comes a serious matter when the victim can no longer follow a conversation, for



By the use of this table full of apparatus, Dr. Haverly Fletcher (right) can imitate the vocal sounds of the human voice. This is accomplished with the aid of vacuum tube oscillators. © Knickerbocker Photo Service.

speech is our most powerful social instrument. So every year has seen new kinds of hearing aids, from the tin trumpet to the vacuum tube amplifier. Eager to re-establish communication with their fellowmen, hopeful sufferers have purchased according to their means and sometimes beyond, and have all too often been sadly disappointed at the results. For the plain truth is that, beyond a certain point, hearing cannot be restored by amplification. If your deaf friend cannot understand when you talk directly into his ear in a loud voice, then probably no hearing aid can be of much use to him.

THE DECEITFUL EAR

But how does your ear help out the loud speaker? An experiment of Dr. Fletcher's throws light on this subject. He arranged 10 separate vacuum tube oscillators so that they produced an electric current from 100 cycles per second up to 1,000 at intervals of 100 cycles. These were connected through switches to a special telephone receiver. When all were connected a full tone was heard which had a pitch corresponding to 100 cycles. Switching off the 100-cycle tone had no noticeable effect on the pitch, nor did the pitch change when the first seven tones were cut off and only the 800, 900 and 1,000

cycle currents reached the receiver. In fact, any three consecutive currents gave the sensation of a pitch corresponding to 100 cycles, while with any four consecutive currents the apparent 100-cycle note was very prominent.


Where did the ear pick up the 100-cycle note if it wasn't sounded by the receiver? To tell the truth, the ear "made it out of whole cloth," just as some men make up a breakfast-table story of what they did the preceding night. In justice to the ear, however, it must be said that it must have something to work with, and what it does is to combine the sounds that enter it and make up a new tone from them. The action is strictly analogous to that of the vacuum tube detector, which makes an audio frequency current out of the difference of two radio frequencies. The air waves of frequencies 500, 600, 700 and 800 cycles have a common difference in tone which gives us the sensation of hearing it.

BRAIN NOT ALWAYS FOOLED


"From the results which have been described," says Dr. Fletcher, "one might conclude that the pitch of a musical tone was determined by the common difference in the frequency of the harmonics, rather than by the frequency of the lowest component. This suggested trying a combination of frequencies which are separated by a common difference, but which are not necessarily multiples of this common difference. For instance, 100, 300, 500, 700, 900—the common difference is 200, but none of these are multiples of 200. What happened? Just a noise; and the same thing happened for 100, 400, 700, 1,000; and for 100, 500 and 900. So the brain shows its suspicion of the ear and its tricky ways, and won't allow itself to be imposed on too far."

These experiments were on putting tones together. In many practical radio and loud speaker systems actual tones are cut apart. So Dr. Fletcher took his high-quality experimental telephone system, one which transmitted faithfully all tones from 100 cycles to 5,000 cycles—and inserted an elec-

(Continued on page 1006)

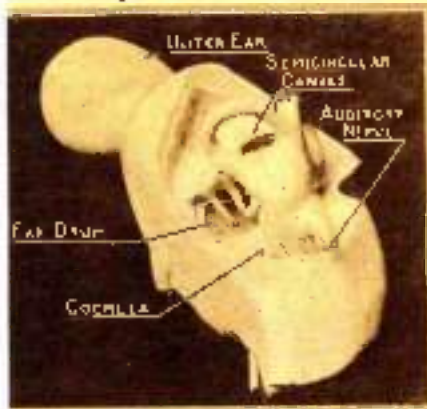

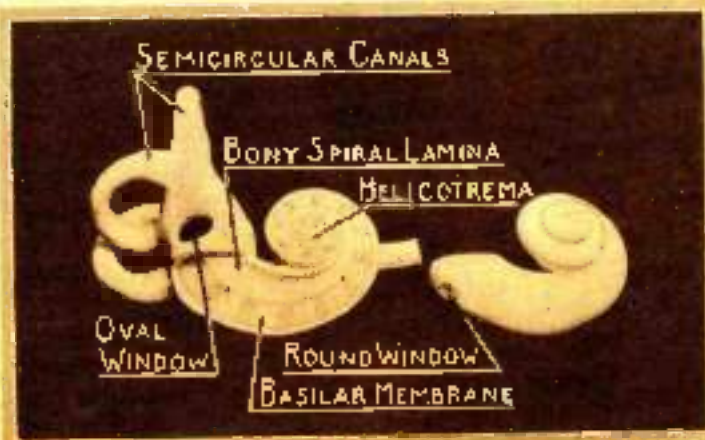Two views of a plaster model of the ear made by Dr. Fletcher for demonstration purposes. By comparing these with the diagram one may have a good idea of the exact shape of each organ.





Interior of 2COW showing one of the campers operating the radiophone transmitter. Note how the wavemeter is suspended above the transmitter.

A De Luxe Amateur Station 2COW, New Paltz, N. Y.

COINCIDENT with the call, 2COW is located in the heart of the Hudson Valley dairy country on Camp Wallkill, New Paltz, N. Y. The station has been in operation for two seasons and has been logged many times in every district.



2COW was erected at a cost of many thousands of dollars and for its complete equipment can only be compared with 3ZD or 2H3JH.

It is ideally located on the top of a hill commanding a wide view of the entire Wallkill valley. Two steel towers, each 75 feet high, support a beautifully made cage aerial about 70 feet above the six-wire counterpoise suspended directly beneath the antenna proper.

A miniature cage lead-in drops in a straight line to the porcelain insulated lightning switch mounted outside one of the operating room windows. One-half inch copper tubing connects this switch with the ground on the apparatus.

The main transmitter, once installed at old 2LH, has won several prizes, and despite the fact that it was built nearly three years ago it never fails to arouse the admiration of those who see it. Two 50-watt tubes are used in a Hartley circuit. A small double-pole double-throw switch mounted on the panel connects the tubes in parallel for C.W., or in a Heising modulation arrangement for voice transmission. Two 5-watt speech am-

(Continued on page 106)

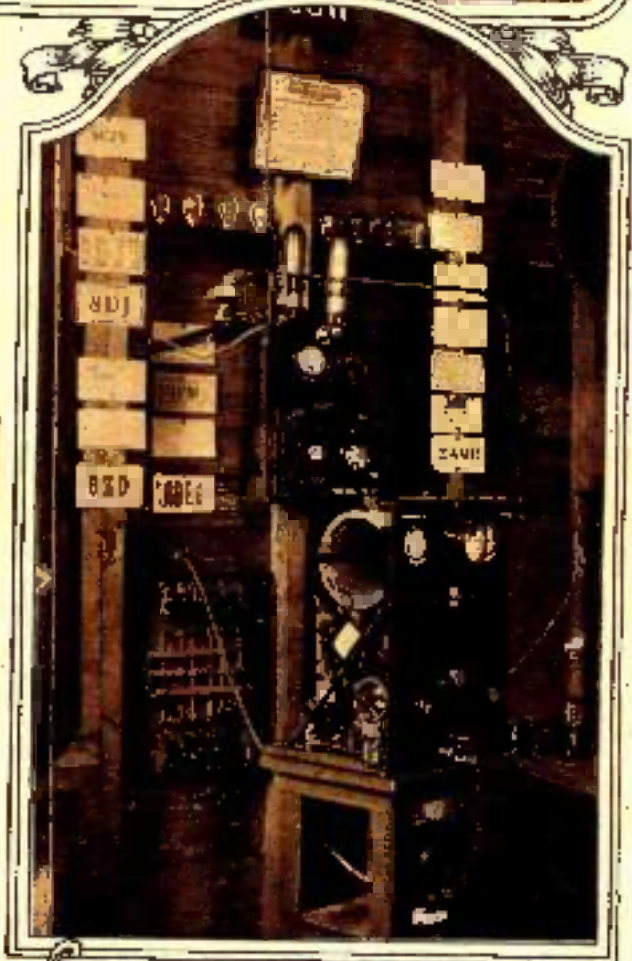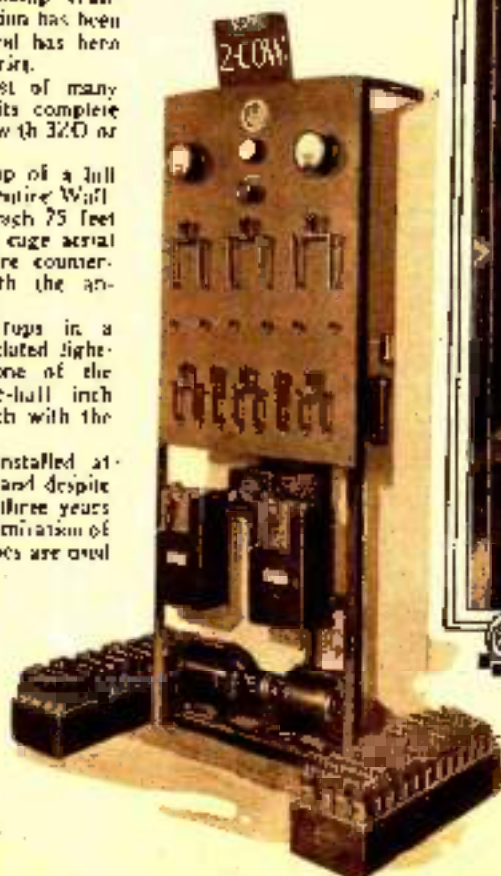

Above: The main transmitter at 2COW. A duplicate of the famous transmitter used at old 2LH. Note the copper tube lead-in. This photo affords a better view of the wavemeter and its position in relation to the transmitter.

Right: The switchboard, motor generator and section of the storage "B" battery used for transmission.

Hamitorial

Experimental Technique

SEVEN different transmitting hook-ups in a month and no one of them thoroughly tried is the record of experimentation, with one Ham we know. And the sad part of this tale of woe is that the same procedure is followed by many of the fraternity, though possibly not in so virulent a form.

Not that the diligence in the search for the ultimate Non-Doggett transmitter is to be derided. Nay and again nay. That is not the point. The point is, as George Ade says, "if you are hasty in your drinking you may pass up a good cocktail." Which is to say, sloppy, superficial experimentation results in little more than piling slips on the traffic hook and generally securing a reputation for not being dependable.

The whole idea underlying experimentation is to search out the best, and the best means that which is most efficient under all conditions and under all circumstances. The only way to test a set for such qualities is to try it under all conditions. And three nights' work does not constitute all conditions. As a matter of fact, with the proper precautions almost that time is consumed in getting a new circuit tuned, particularly if it happens to be one embodying a major change in the arrangement of the apparatus. After the first preliminaries it is always necessary for the operator to become acquainted with a new arrangement—he must learn what to expect of it, where to look for idiosyncracies, what usually constitutes a mechanical stomach ache or electrical indigestion.

The usual custom—the custom, at least, with far too many Hams—is nothing more nor less than a system of untidy initial habits. He finds a promising new line of research. After thinking it over for a few days and finding the ten dollar bill he forgot

complete erection of the set—for an artificial mouse.

Well, the set wasn't so wonderful, anyhow. Down it comes and the old one punches the sigs. across the change-over the following week.


The Ham's experience spoken of in the beginning of this spleen may prove a far-shot guide. He has tried several circuits at least three times in his various radio gyrations because he has not kept competent notes on his work—not that they would

Of course, there are the stations with complete logs covering every possible scientific contingency in connection with tests, but they are the exception and not the rule.

Just suppose some diligent brass pounder were to notice a change in the operating efficiency of his set in working two stations equally distant and in the same direction. What would he do about it? Usually he would not even make a note of the fact under the night's entry in the log—*if he kept one.*



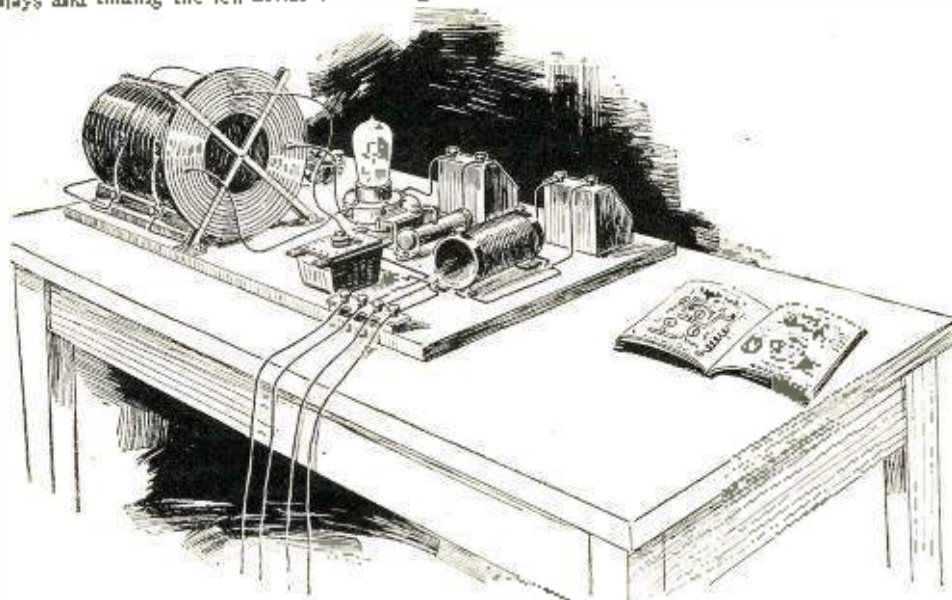Slipshod methods result in inaccurate conclusions by the experimenter. Likewise methodical and orderly procedure results in accurate conclusions worthy of a place in your note book. Glance at these layouts.



and left in last year's vest pocket, he buys a new tube and proceeds to take another chance. Down comes the whole lay-out and up goes the new. The chase is on again.

The set may prove promising at first but before the completion of the preliminary tests a condenser, hooked up with a couple of pieces of loose No. 14, slips over and smashes the improvised antenna inductance with the result that the tuning clips all fall to the floor. Several days pass on account of a bit of extra work at the office. Upon the resumption of experiments it turns out that the cat has used the original hook-up—with some slight changes made before the

ever frighten the world as posthumous investigations if they were kept—and as a consequence he can never give absolutely accurate dope regarding any circuit.

Why, oh why, will the Hams not cultivate habits of a respectable scientist? They have given radio as much or more than any other group of experimenters and yet they continue in the old careless ways. What would they have done if a little care had been taken and inexplicable demonstrations which they encountered fully noted for further investigation; if some line of research were followed to its end; if there were competent records including notes on conditions, etc.?

With every deviation from normal, there is a possibility of discovering a new and perhaps fruitful line of investigation that may turn up—Jupiter knows what.

Why not keep a record of such instances, ready for reference when some explanation presents itself? The only way one may make a journey across the sea is by charting a course. The only way a Ham can hope to make any progress in the more or less unknown field of research is by keeping some sort of record of the journey.

Also, the only way a course may be taken is by observation, very careful observation. No Captain ever sets his course on our petty through the sextant. He makes many of them in order to be sure of getting accurate results. With a new vessel he must take a long time with her before he is perfectly sure in his knowledge as to how she will behave in a Nor'wester in mid-winter, or how she will carry herself with an empty forehold.

Likewise it is necessary for the Ham, not only to keep careful records as to his observations, but it is equally important that he make his observations with due care and over a sufficiently broad range of circumstances to warrant accurate and complete final results.


A search through the history of abstract science will show you obviously that all the details of a seeming deviation from natural laws may be important in analyzing the reason for the deviation. How is the experimenter to know that his deviation is a mistake or a bona fide demonstration of some new idea unless he has the dope complete for comparison?

It's old stuff, but like certain merchandise very popular, although quite sparse at present, it's better for the age, this platitude, that most of the world's discoveries were accidents.

Urgo, put your accidents in a book. You
(Continued on page 1083)

Station 2XNA of the College of the City of New York

By SIDNEY FISHBERG, 2AHT

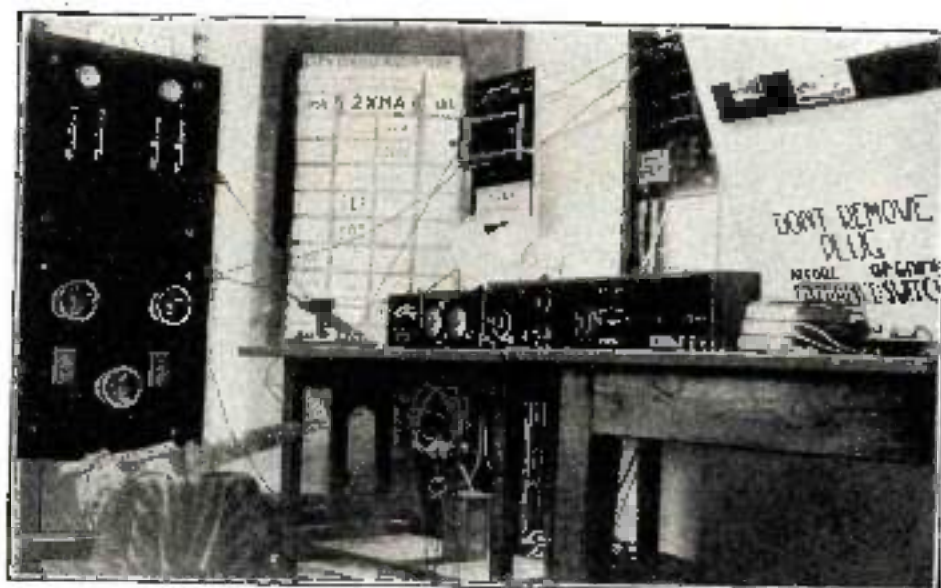

Interior view of amateur station 2XNA of the College of the City of New York. Some of the best second district amateurs are operators of this station, probably the most well known is 2BRR, who is chief operator.

STATION 2XNA is located at the College of the City of New York, St. Nicholas Terrace and 143rd Street. The station is owned and operated by the City College Radio Club. Through the kindness of the faculty, one of the towers on the main building has been set aside for the use of the Radio Club. The operating room is located in a deck house on top of this tower, 110 feet above the ground. Since the College itself is on the highest point in Manhattan, 2XNA enjoys an excellent location.

The transmitter was designed by the famous 2BRR, with the aid and advice of Prof. A. N. Goldsmith of the Radio Corporation of America. It consists of a 200-watt Hartley set, and may be used for CW or 1 CW. Only direct current is available in the tower, consequently a motor-generator is used. This consists of a 1/2-horsepower 220-volt compound wound motor driving a 600-watt, 1,000 volt double commutator generator. In order to supply filament current, the motor has been equipped with slip rings which turn out 30 cycle, 154-volt alternating current. A special transformer steps this down to 12 volts. The two meters on top of the panel are plate current and antenna current meters. The filament voltmeter is placed on the operating table, so as to be in easy view of the operator; it may be seen on the extreme left in the picture. The four switches below the meters control the filament supply to the tubes. The top rheostat on the left is the generator field rheostat, that on the right is the filament rheostat, and the one in the center is the motor starter. There is a special contact on this rheostat which automatically turns on the filament before the motor can be started. A small cam switch on the left side of the transmitter starts the chopper motor. The chopper gives a 300-cycle note which carries very well. The two tubes on top of the panel are defunct navy 50-watt tubes which died gloriously at their post, and were placed in their present position by a member who had just come from an art lecture.

Two receivers are in use: an amateur set going from 50 to 220 meters, and a broadcast and commercial receiver, the range of which is 220 to 880 meters. Both of these sets are of the low-loss type and give excellent results. English stations have been

heard often on the Ham receiver, while KGO can be received any good night on the broadcast set. In the picture, the amateur receiver is on the left, next to the filament voltmeter. The set next to it is the old variometer set now hidden in a closet. Next is a two step amplifier to actuate a loud speaker. This amplifier uses 220 volts from the power line, and gives plenty of pep to the signals. In the far right a loud speaker is installed in the student concourse, and the World Series and the collegiate football games are reproduced in a howling, carrying mob of frenzied students.

The antenna at 2XNA is one to put, yes in the heart of a city ham. As has been said

before, the operating room is on top of a 110 foot tower which is high above the surrounding country. The mast is 40 feet high and supports an 80-foot six-wire cage. It is supported at the other end by a wire which runs to the main tower of the building. The counterpoise consists of a seven-wire fan, five feet above the roof and 50 feet below the antenna. At 180 meters an antenna current of 2.5 amperes is obtained with 450 watts in the antenna. This current is not continuously low, for the fundamental is 235 meters.

All the apparatus at 2XNA was donated by Dr. A. N. Goldsmith who is also a professor of engineering at the College. Dr. Goldsmith has given liberally his time, and technical advice as well, and has done much toward getting the station to its present state of excellence.

Station 2XNA is on the air every night of the school year, and handles traffic directly to all parts of the United States. The station is operated by the following men:

2BRR "EG", Chief Operator, 2ABN "DW", 2ABW "DC", 2AHT "AC", 2AVY "EK", 2NOP "BL", 2CBJ "ES", 2CRC "HD", 2CRB "IG".

Calls Heard

2WZ, BROOKLYN, N. Y.

CW U. S. A.
(140), 144, 145, 146, 999, 1000.

(Continued on page 1057)



Station 9BPT, owned and operated by Harry D. Clingenpeel, Flora, Ind. The transmitter is a 100-watt C.W. and a 10-watt phone set. The Hartley circuit is used and the (300 prior to Ray-don 1,000-volt A.C. motor generator. Plate current is 250 milliamperes. The receiving circuit consists of a Grebe CR-3 and a 1BGF short wave low loss tuner. The aerial is a wire cage 22 feet long and 30 feet and 25 feet high with lead-in or low end. The counterpoise is fan type, and extends radially beneath the cage for 20 feet.

A New Oscillator for Very Short Waves

By ROSS GUNN, B.S., E.E., M.S.



Due to the fact that the Department of Commerce has presented the amateur with some choice short wave bands he will no doubt wish to take advantage of them. Mr. Gunn's short wave oscillator opens the field well. It is decidedly superior to the average oscillator circuit.



THE new range of wave-lengths assigned for experimental and amateur work opens up an interesting field for experiment. For wave-lengths down to perhaps 25 meters the usual methods apply, such as the standard Hartley circuit, but for wave-lengths from 2 to 25 meters, special care and different methods become necessary.

The writer recently devised a new circuit for these very short waves that is far above anything else he has seen for reliability and power output. This circuit oscillates freely and works every time if one or two precautions are taken in selecting the tubes and properly arranging the various parts. The circuit is essentially a Colpitts type and makes use of the internal capacity of the tube to couple the plate and grid circuits. The circuit is novel in that there is no

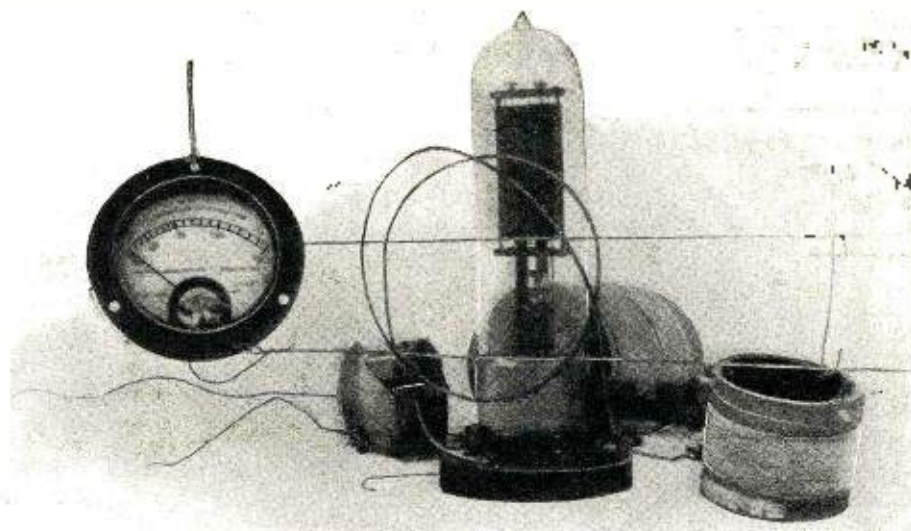


Fig. 1. This shows the tube used in a standard socket. The meter, the two parallel wires and the slide (antenna right) are used to measure the wave-length of the oscillator.


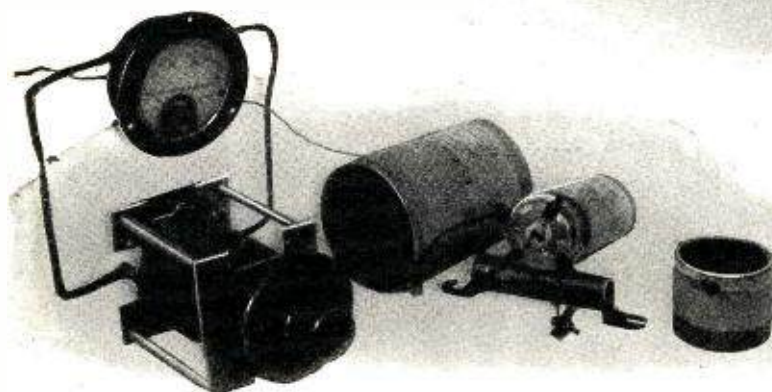


Fig. 4. Another view of the tube with its base removed, resting on the grid leak. Note the R.F. chokes on either side of the tube. The wavemeter is in the foreground.

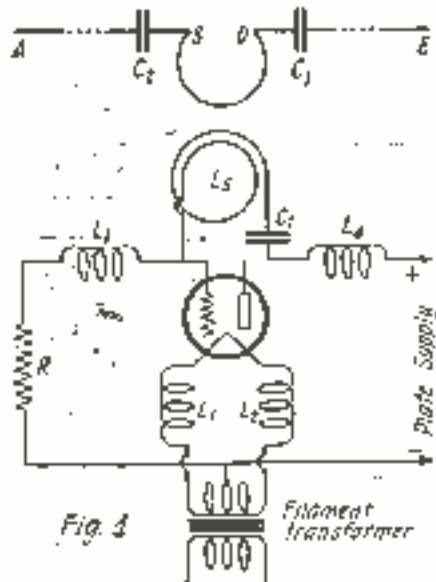

- Fig. 1**
- | Symbol | Description |
|---------|---|
| L1 - L2 | Choke No. 20 D.C.C. in parallel - 50 turns on 3-inch form. |
| L3 - L4 | Choke No. 20 D.C.C. - 125 turns - 7-inch form. |
| L5 | Oscillating circuit inductance, 1/2 to 1 1/2 turns 4 1/2 inches in diameter. |
| C1 | Stopping condenser. Either fixed or variable. Value .002 mfd. to .0002 mfd. |
| C2 | Adjustable tuning condenser made of two copper disks 3 inches in diameter soldered to antenna tubing. |
| R | Grid leak 5,000 to 10,000 ohms. |
| | Lengths A-B-C-D-E in meters should be from 50 per cent. to 75 per cent. of the working wave-length. |

external connection between the filament and the oscillating circuit and, therefore, would not be expected to oscillate. By drawing the Standard Colpitts circuit and replacing the coupling condensers by the tube capacities, the action is readily understood.

Fairly large tubes may be made to oscillate satisfactorily at these short waves if this new circuit is employed. The writer has succeeded in securing wave-lengths as low as three meters from a standard Western Electric 30-watt tube. In using this circuit the tube is first isolated, as far as high frequency is concerned, from every

thing else by placing suitable chokes in all the leads to the tube. The oscillating circuit then consists of a turn or two of wire and a mica stopping condenser together with the internal capacity of the tube. The wire L_5 and the stopping condenser C_1 are connected between the plate and grid terminals, as shown in Fig. 1. The output or antenna circuit ABCDE with a hot wire ammeter in series is connected inductively to L_2 . The plate and grid chokes L_1 and L_2 should be made by winding at least 125 turns of No. 27 D.C.C. to No. 30 D.C.C. wire on a cardboard tube 2 inches in diameter. The filament chokes L_3 and L_4 are conveniently made by winding at least 50 turns of No. 20 D.C.C. (two wires in parallel) in a single layer on a cardboard tube 3 inches in diameter. Under no circumstances should a jumble winding or hodgepodge coil be used, as these are inefficient chokes at short wave-lengths. The grid resistance R has a resistance of from 4,000 to 10,000 ohms, the exact value being determined by experiment. The condenser C_1 is a mica stopping

(Continued on page 1072)

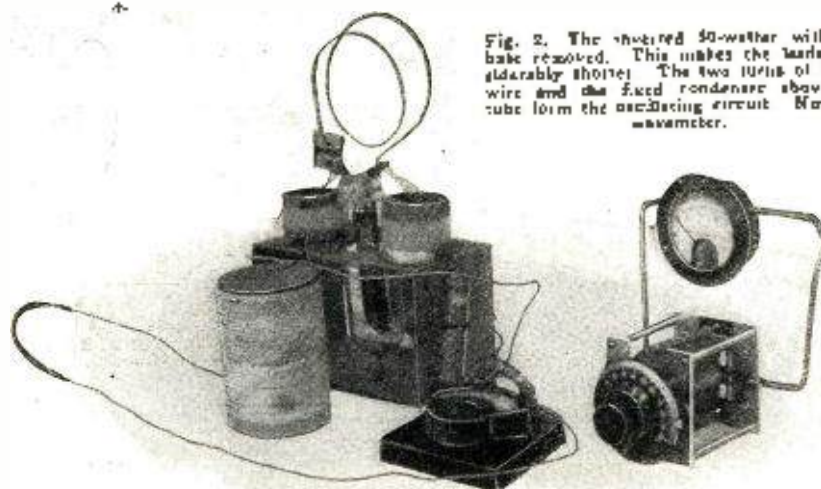



Fig. 2. The vacuum 30-watt tube with the base removed. This makes the leads considerably shorter. The two turns of heavy wire and the fixed condenser about the tube form the oscillating circuit. Note the wavemeter.

A Short Wave Adapter for the Broadcast Receiver

By J. L. CASSELL



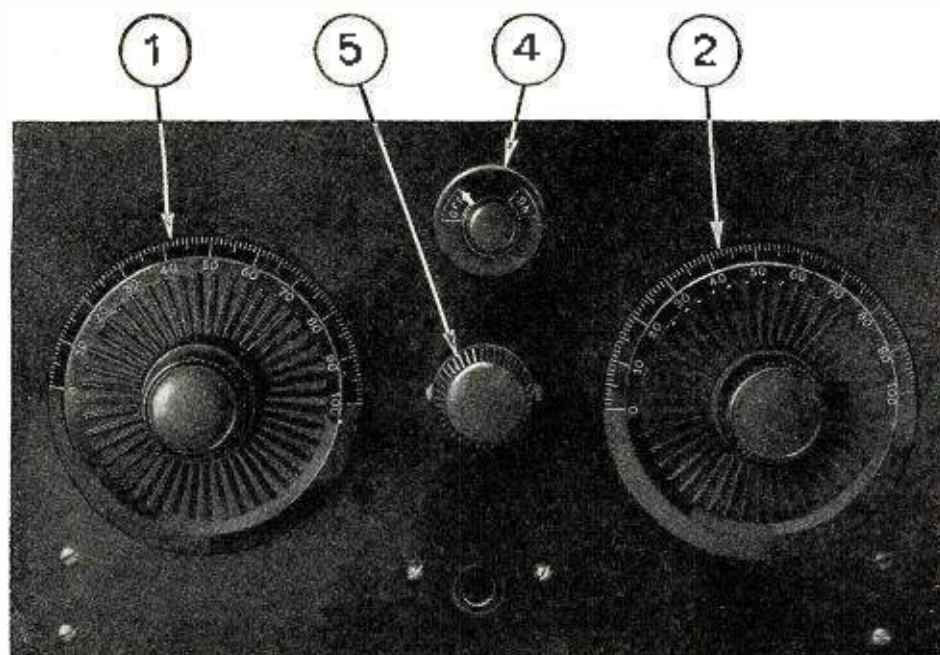The popularity of broadcasting on short wave-lengths below 100 meters has brought in many new designs in receiving apparatus. By means of the adapter shown here, the short wave signals are heterodyned to a longer wave-length and received on a standard broadcast receiver.



WGY at Schenectady and KFKN at Hastings, Nebraska, and many experimental European stations as they put their programs on the air for trans-Atlantic tests.

List of Required Parts for the Construction of the Short Wave Adapter

- 2—Low loss straight line wave-length low minimum capacity condensers with frame insulated from plates.
- 1—Pound No. 18 D.C.C. magnet wire.
- 1—6N25 low loss fixed condenser.
- 1—One-half to 10-megohm variable resistance of the compression pile type.
- 1—LV-199 vacuum tube with "A" and "B" batteries.
- 1—Vacuum socket, panel mounting, with shock absorbing base.
- 1—Two-foot length of telephone receiver cord.
- 1—Sixty turn spider-web coil.
- Panel 7 by 12 inches, screws, nuts.

FOR the past two years much has been said and written concerning the experiments with short waves, those waves which lie below the broadcast and amateur bands. However, most of the stories concerning the great distances and ease of communication made available by the use of this new field told of much special apparatus and great technical questions involved. After reading a few such reports, the ordinary fan relegated the subject to the scientist and went again to more pertinent problems dealing with questions nearer his heart concerning the efficiency and the distortion in his loud speaker.

Many of the largest broadcast stations in the country such as WGY, KDKA and KFKN are now using short waves with regularity and it is only remains for the fan to construct a set or an attachment for his present set which will enable him to receive these wave bands in order to get into the forefront of radio experimentation.

With the simple device shown in these columns attached to any receiving set one may listen nightly and with less trouble to the programs of KDKA at Pittsburgh,

Above: Front view of the completed short wave adapter. The parts refer to the following parts: 1, tuning condenser; 2, oscillator condenser; 4, switch; and 5, variable grid leak.

Right: Circuit diagram showing connections of the short wave adapter. The Trogodyne principle is used for heterodyning the incoming signals.

Below: The method of coupling the short wave adapter to a standard broadcasting receiver. The illustration shows the adapter coupled to the Neutrodyne, which combination works very well. Note that this arrangement forms a Super-Heterodyne circuit.

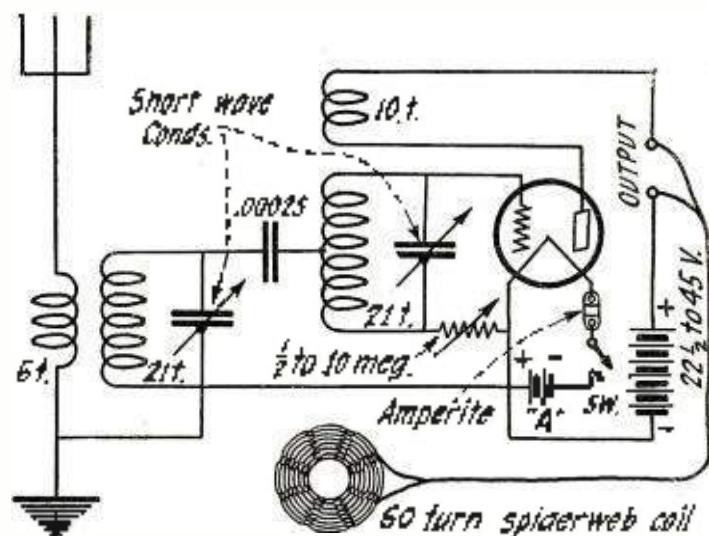


Fig. 3

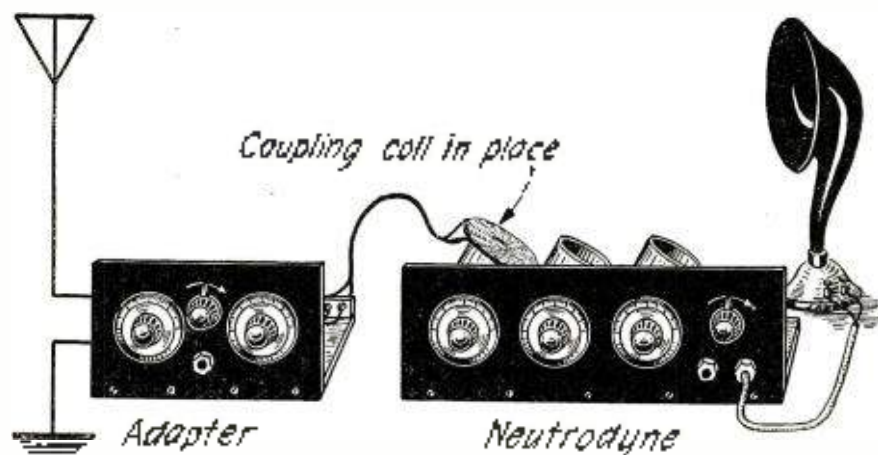


Fig. 6

Advantage is taken of the Super-Heterodyne principle. Essentially, the apparatus is a short wave tuner with an oscillator. The incoming signal, which for example may be of a 60-meter wave-length, is picked up by the tuner, passed on to the oscillator and heterodyned to a higher wave-length of about 350 meters which may be easily picked up by the ordinary tuner. Thus every set can be easily made into a Super-Heterodyne receiver.

And the addition of the short wave oscillator tube increases the range of the set since it acts as an amplifier. Also, the receiving set proper may be worked at its most efficient point.


Still another betterment is gained through the adoption of the Trogodyne principle in the short wave tuning unit. By using the standard Super-Heterodyne circuit the short wave adapter would require two tubes. In this case only one tube is required.

The heart of the apparatus is embodied

in the variable condensers. Several tests were made with the adapter before the present design was evolved, but due to the design usually employed in the manufacture of commercial condensers the scheme was found to be impracticable. It was necessary with their use to cut out a number of plates in order to tune down to the short waves. And in this particular case, since neither side of the oscillator circuit may be grounded, the body capacity of the operator was so great that it was practically impossible to tune in a station.

A low loss condenser, having a straight line wave-length, can be and separately grounded frame to eliminate body capacity.

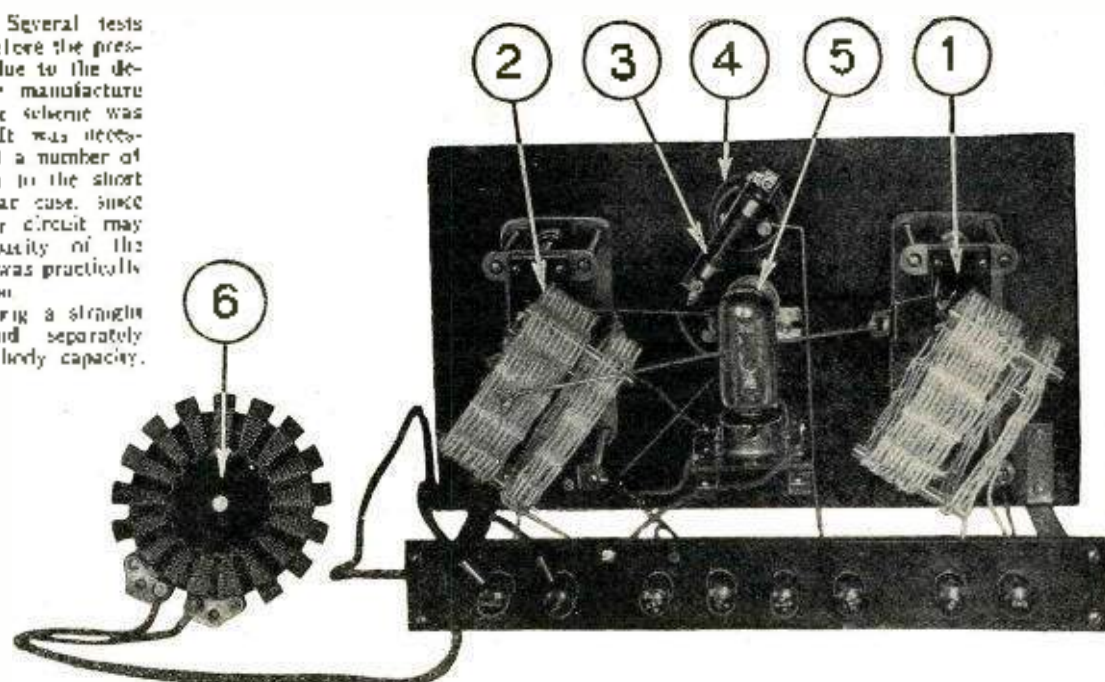Rear view of the short wave adapter. Note the spider-web coupling coil and the low loss stagger wound tuner and oscillator coils.



was used. With this type of condenser, the adapter works admirably.

Of course, the ordinary type may be used for the tuner circuit if its capacity is reduced. Usually four plates have to be taken from the ordinary 4MM25 condenser to make it serve for short wave work. The condenser selected must have low losses, or the efficiency of the adapter will be dropped to a low point.

Figs. 1 and 2 are photographs of the completed unit and Fig. 3 is the wiring diagram. In constructing the adapter, the first point is to wind the low loss coils. Fig. 4 is a template for the winding form and may be cut from the page and used as a marker

for the base. A bit of one inch soft wood may be used for the form base. Over this the template is pasted and nails or pins driven in as indicated. If nails are used, the heads will have to be sawed off before being driven into the wood so the completed coil will slip off the form. The coils will have a mean diameter of three inches.

No. 18 D.C.C. wire is used throughout in making the coils. Four are necessary. The first consists of six turns. Begin at any pin on the form and wind the wire in front of one pin and behind the next. On account of the odd number of pins, each turn will be staggered over the next. Besides the six-turn coil, one of 10 turns and two of 21


turns will be necessary. In the center turn of one of the 21-turn coils at the opposite side from the beginning of the coil a tap is taken. This is exactly at $10\frac{1}{2}$ turns. The windings are securely banded with twine before being taken from the form.

The six turn coil and the 21-turn coil are fastened together with three glass tubes two inches long, as shown in Fig. 3, and form the primary and secondary of the tuning circuit. Very little insulating substance should be used in supporting the coils as insulating substances increase losses. The primary and secondary are spaced one-quarter inch apart. The 21-turn coil, with the tap in the center, and the 10-turn coil are mounted together with three more bits of glass tubing and serve as the oscillator circuit.

The apparatus is mounted on a standard 7 by 12 inch panel. Instead of the usual sub-base, brass strips were used as seen in the photographs of the set. The extra bracing strips shown will be found necessary for the stability of the set, as the least vibration will detune it. An insulating strip of hard rubber $1\frac{1}{2}$ by 11 inches to carry the eight binding posts is mounted at the back of the two bottom strips.

(Continued on page 1099)


13 Pins equally spaced

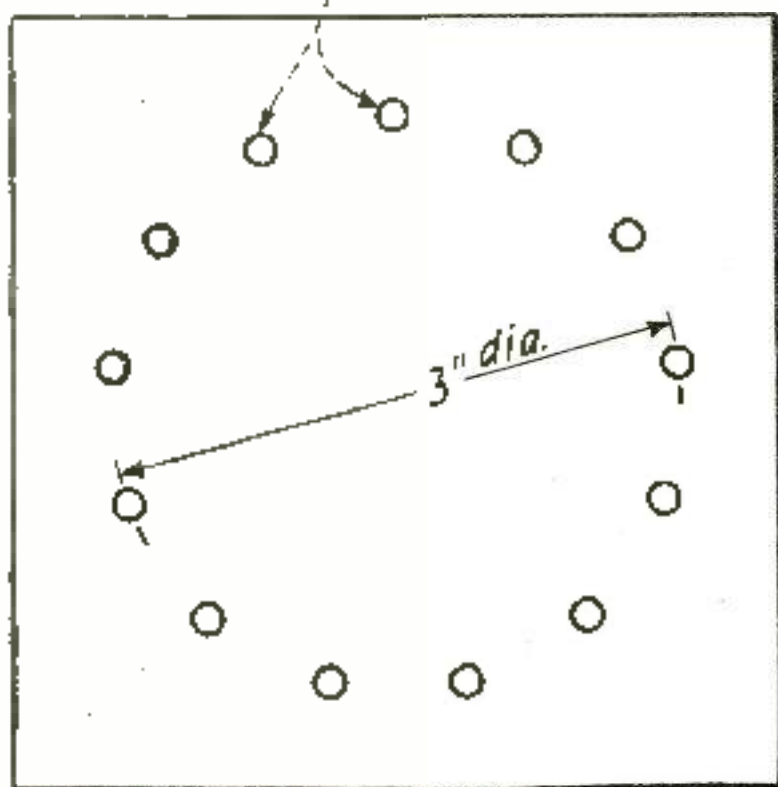

Basketwound Coils

Fig. 4: Full size template for making a form for winding the low loss coils. This should be cut out, pasted to a board and nails driven through the centers of the small circles. The heads of the nails must be removed in order to remove the coil.

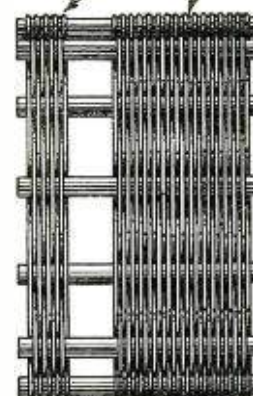Right: The finished stagger wound coil. Note that the wire passes under any glass rod and over the next.



Glass tubes 2" long

Fig. 5

The Heterodyne Wavemeter

By JAMES WOOD, JR., 2ALG

Part 2

This article deals exclusively with condenser calibration and inductance measurement by use of the Heterodyne Wavemeter described by Mr. Wood in the November issue of Radio News.

THE wavemeter described in the first part of this article can be put to a great many uses. Some of these will be described below. The wave-length range of the wavemeter is from 60 to 235 meters, which is ample for ordinary requirements in the experimenter's laboratory.

In the formulae given below, capacity is expressed in microfarads, inductance in microhenries and wave-lengths in meters. The symbol C_1 will be used to denote all the capacity in the circuit which is not due to

again to resonance with the receiver. Call this wave-length λ_2 .

The capacity of the unknown condenser at the particular setting chosen, corrected for the capacity we denote by C_1 (see above) is given by the expression:

$$C_x = \frac{C(\lambda_1^2 - \lambda_2^2)}{(\lambda_1^2 - \lambda_2^2)} \quad \text{eq. (1)}$$

The value of C_1 may be obtained from the expression:

$$C_1 = \frac{\lambda_1^2 C}{\lambda_1^2 - \lambda_2^2} \quad \text{eq. (2)}$$

It becomes apparent that if it should so happen that the wave-length of the circuit, when both standard and unknown capacities have been disconnected, is lower than the minimum wave-length of the wavemeter, the method falls down. This can be easily remedied. Tune the wavemeter until its second harmonic is in resonance with the receiver. Note the wave-length, divide by two and call it λ_2 . The above formula (1) then gives the capacity of the unknown condenser. Care should be taken to see that the adjustment of the receiver is not changed except as directed.

The above method is very satisfactory for all ordinary capacities used by the radio experimenter (.00001-.0005 mfd.). For example, assuming the accuracy of the wavemeter calibration to be .1 of 1 per cent, which is the value given for WAVV's standard signals, the wavemeter when calibrated

capacity and other capacity which is not due to the tuning condenser. Most of the formulae given are corrected for these capacities, not because it is necessary but to show how it can be done.

For capacities larger than .0005 mfd. the method is very much the same. Perform parts (a) and (c) as above. In place of part (b) proceed as follows:

Connect the known and unknown capacities in series. Bring the wavemeter to resonance with the receiver. Call the wave-length λ_2 . The capacity of the unknown condenser at the particular setting chosen is then given by:

$$C_x = \frac{C(\lambda_1^2 - \lambda_2^2)}{(\lambda_1^2 - \lambda_2^2)} \quad \text{eq. (3)}$$

The above methods of capacity measurement are accurate and in addition allow the use of the capacity standard for other purposes. The writer wishes to again emphasize the importance of careful adjustments and the necessity of leaving the receiving set in one adjustment whenever the directions call for this. The experimenter should make a practice, in all calibration work, of taking several readings for each particular point. Individual readings are bound to vary somewhat and it is only by taking several readings and averaging them that the most accurate results are realized.

Once we have a calibrated variable condenser, the problem of other types of measurement is greatly simplified.

INDUCTANCE MEASUREMENT CAPACITY CURVE OF WAVEMETER CONDENSER KNOWN

Bring the receiver and wavemeter to resonance. Use a known wave-length (λ) of at least 150 meters, since the accuracy of the final result will be greater and the adjustments will be more easily made. Call the wavemeter condenser reading C . Shunt the unknown inductance across the wavemeter condenser (See Fig. 6) and re-adjust the latter to bring the wavemeter again to resonance with the receiver. The capacity of the condenser will always have to be increased in this case, because when two inductances are connected in parallel, the effective inductance of the whole system is reduced. The receiver should not be touched throughout the experiment. Call the second capacity of the wavemeter condenser C_1 . The unknown inductance uncorrected for distributed capacity is then given by:

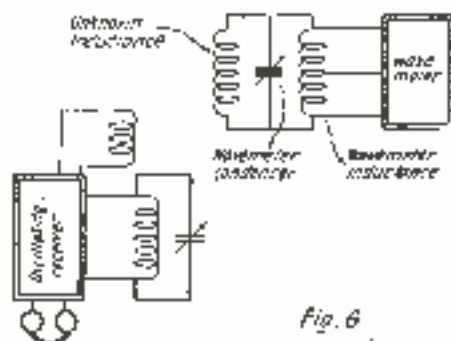


Fig. 6
Circuit and arrangement used in determining the inductance of a coil: capacity curve of wavemeter condenser known.

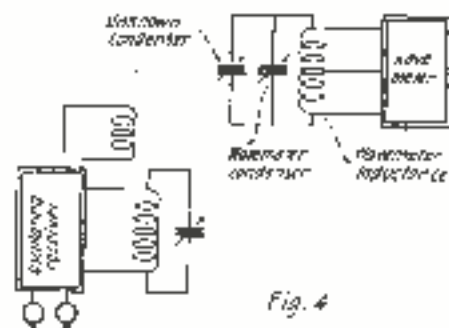


Fig. 4
Circuit and arrangement and method employed for the calibration of a condenser of unknown capacity: capacity curve of wavemeter condenser known.

the receiving condenser or to the condenser being calibrated. This will include then, capacity due to leads, the vacuum tube, and the distributed capacity of the inductances, except where otherwise noted.

CONDENSER CALIBRATION WAVEMETER CONDENSER CAPACITY CURVE KNOWN

Set the wavemeter at any convenient value above 150 meters, and adjust the receiver to resonance (zero beat). Note the wavemeter condenser reading. Then shunt the wavemeter condenser with the unknown condenser (See Fig. 4) and re-tune the wavemeter to resonance with the receiver. The unknown capacity is then equal to the difference in the capacities of the wavemeter condenser in the two positions. This is of course relatively simple. As is often the case, however, the wavemeter condenser capacity curve is unknown and it then becomes necessary to use a slightly different method.

WAVEMETER CONDENSER CAPACITY CURVE UNKNOWN

For this method we also require a standard capacity, but it need not be variable. It should be known accurately to three significant figures, for example .000357 mfd. The method is as follows:

(a) Allow the receiver to oscillate and connect the standard capacity, which we will call C_1 , across the receiving inductance. Bring the wavemeter to resonance with the receiver. Note the wave-length and denote it by λ_1 .

(b) Disconnect the standard capacity and connect in its place the unknown variable capacity. (See Fig. 5). Set the latter at any desired value. Now bring the wavemeter to resonance with the receiver. Call this wave-length λ_2 .

(c) Now disconnect the unknown capacity and allow the receiver to oscillate without either condenser. Bring the wavemeter

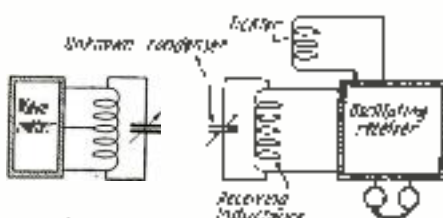


Fig. 5
Method utilized for determining capacity of a condenser when the wavemeter condenser capacity curve is unknown.

from this source would very likely read anywhere from 1994 to 2006 when actually the wave was 200 meters. Working it out mathematically shows that this inaccuracy in the wave-length will cause the condenser, which was just calibrated by the above method, to vary from 1 per cent, below to 1 per cent above its actual value. In other words, the capacity of the unknown condenser might come out anywhere from say .000311 to .000316, when the actual capacity is .000313. Toward the upper end of the wavemeter scale we may expect an accuracy of 1 per cent, provided the measurements are carefully made. This is about the greatest accuracy possible with the type of wavemeter described. It is, however, quite sufficient for most purposes. This degree of accuracy will not be obtained on small capacities. It is not very satisfactory, for example, to measure capacities of less than .00001 mfd., since even on this capacity the value obtained may vary 30 per cent, either way. On this account it is often useless to correct for distributed ca-

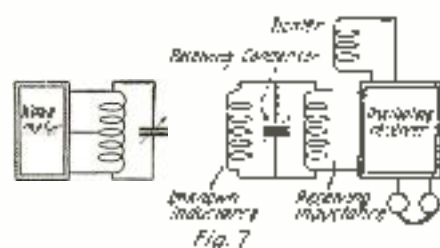


Fig. 7

Circuit and arrangement used in determining the inductance of a coil: capacity curve of wavemeter condenser unknown.

$$L_x = \frac{\lambda^2}{(1885)^2 (C_1 - C_2)} \quad \text{eq. (4)}$$

To correct for the distributed capacity of the inductance proceed as follows:

Adjust the receiver and wavemeter to resonance and read the wavemeter condenser. Call it C_1 . Call the wave-length λ . Short the wavemeter condenser with the unknown inductance and again bring the wavemeter to resonance with the receiver, leaving the latter in its original adjustment. Denote this second reading of the condenser by C_2 . Now reduce the wavemeter condenser capacity until the wavemeter is in resonance with the second harmonic of the receiver. Read the condenser again and this time call it $4C_2$. The inductance of the coil corrected for distributed capacity is:

$$L_x = \frac{3\lambda^2}{(1885)^2 (4C_2 - 3C_1 - C_2)} \quad \text{eq. (5)}$$

The distributed capacity may be found from the expression:

$$Cd = \frac{C_1 - 4C_2}{3} \quad \text{eq. (6)}$$

CAPACITY CURVE OF WAVEMETER CONDENSER UNKNOWN

When the capacity of the wavemeter condenser is unknown we proceed in much the same manner as in the corresponding case for capacity. Here, however, we must use a calibrated variable condenser to tune the receiving set.

Bring the receiver and wavemeter to resonance. Denote the receiving condenser capacity by C and the wave-length used by λ . Now short the unknown inductance across the receiving condenser (See Fig. 7) and re-adjust the latter until the receiver is again in resonance with the wavemeter. The wavemeter is of course left as it was first adjusted. Call the second reading of the condenser C_1 . The inductance of the coil will then be given by equation (4) above. The value obtained is not corrected for the C_1 capacity nor the distributed capacity of the unknown inductance itself. To get the pure inductance requires more measurements. Get the following as described above: C, C_1, C_2 (eq. 2) and λ . We also must take one more reading with the wavemeter. After C and C_1 have been determined as above, leave the unknown inductance connected to the receiver, but reduce the capacity of the condenser until the receiver is in resonance with the second harmonic of the wavemeter. Call the capacity of the receiving condenser in this adjustment $4C_2$. The pure inductance of the coil is then given by:

$$L_x = \frac{3\lambda^2}{(1885)^2 (4C_2 - 3C_1 - C)} \quad \text{eq. (7)}$$

The distributed capacity of the coil can be found by substituting the value obtained for L_x in equation (7), in the following expression:

$$Cd = \frac{\lambda^2 - L_x (1885)^2 (C_1 - C)}{L_x (1885)^2} \quad \text{eq. (8)}$$

This completes the measurement of capacity and inductance.

WAVELENGTH OF TRANSMITTERS

The wave-length of a transmitting station is found by the same method that was used for calibrating the wavemeter from the standard signals of WWV.

MUTUAL INDUCTANCE

When two coils are connected in series and electromagnetically coupled, the mutual inductance is given by:

$$M = \frac{L_1 - L_2}{4} \quad \text{eq. (9)}$$

In the above L_1 is the effective inductance when the fields of the two coils assist each other, and L_2 is the effective inductance when the fields oppose each other. The degree of coupling must remain the same when the fields are changed from assisting to opposing (See Fig. 8.) To measure M by means of the wavemeter, all that is necessary is to measure L_1 and L_2 by one of the means already suggested, and substitute the values in the above equation.

Sometimes we also wish to determine the degree of coupling between the two coils. This is also easily done.

COEFFICIENT OF COUPLING

The coefficient of coupling tells us how closely two circuits are coupled. For the two coils considered above, the coefficient of coupling is given by:

$$K = \sqrt{\frac{M}{L_1 L_2}} \quad \text{eq. (10)}$$

To find K it is simply necessary to mea-

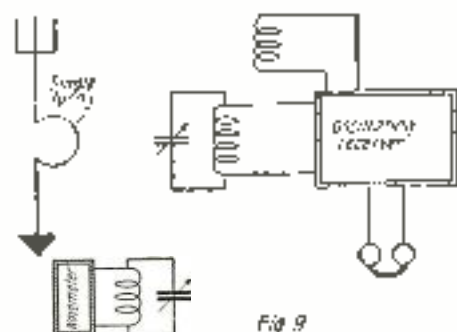


Fig. 9

Arrangement for measuring the fundamental wave-length of an antenna system.

ure individually the inductance of each coil and substitute the two values, together with the value of the mutual inductance found above, in the formula.

ANTENNA MEASUREMENTS

With the aid of the Heterodyne wavemeter we may measure the fundamental, the capacity and the inductance of the antenna system. We cannot, however, measure the resistance of the antenna. This is due to the fact that the energy delivered by such a low powered oscillator as the one described, would not be sufficient to actuate any but a very sensitive meter, which few experimenters possess.

FUNDAMENTAL WAVELENGTH

Connect the antenna directly to the ground, make a single turn loop of the lead and couple this closely to the receiver (See Fig. 9). Allow the latter to oscillate and gradually adjust the receiving condenser. A point will be reached where the oscillations will cease and the familiar click will be heard in the phones. If the condenser is turned further, the circuit will again oscillate and the click will again be heard. It will usually be found that these two points are quite a few degrees apart on the condenser scale. Reduce the coupling between the single turn loop and the receiver until only one click is heard when the resonance point is passed. Now reduce the coupling a little more until

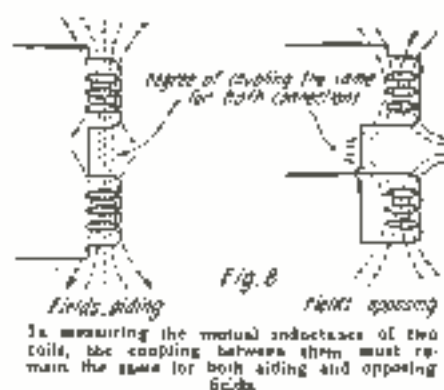


Fig. 8

the receiver just oscillates at the resonance point. Tune the wavemeter to resonance with the receiver. Read the wave-length. This is the antenna fundamental.

ANTENNA CAPACITY

The capacity of the antenna system can be measured quite accurately in spite of the fact that as yet we do not know its inductance. By taking three separate measurements we can get an expression for the capacity of the antenna system that does not involve its inductance.

First find the antenna fundamental by the method already described. Call it λ . Now connect an inductance, which has been calibrated by one of the methods already described, in series with the antenna. (See Fig. 10.) Call the inductance L_1 . Find the wave-length of the antenna system with this coil in series. Denote it by λ_1 . Now disconnect L_1 and connect in its place another standard inductance which will denote by L_2 . Again measure the wave-length of the antenna system. Call it λ_2 . The capacity of the antenna is given by:

$$Ca = \frac{K(\lambda_1^2 - \lambda_2^2)}{(1885)^2 (\lambda_1^2 L_1 - \lambda_2^2 L_2)} \quad \text{eq. (11)}$$

The above formula may look a bit formidable to those unaccustomed to algebra, but it is only necessary to substitute the numerical values for the symbols and then do a little simple arithmetic. The formula given does not take into account the distributed capacity of the inductances used, but on well-made inductances of the size used in the average experimenter's laboratory, the distributed capacity is so small that it can be disregarded. It is a wise plan, when inductances are made up for use as standards, to keep the distributed capacity as low as possible. This can be done by using spaced windings and as little insulating material as is consistent with rigidity.

ANTENNA INDUCTANCE

Once the fundamental and the capacity of the antenna have been measured, it is a simple matter to determine the inductance by means of the formula:

$$L_a = \frac{\lambda^2}{C_a (1885)^2} \quad \text{eq. (12)}$$

(Continued on page 1038)

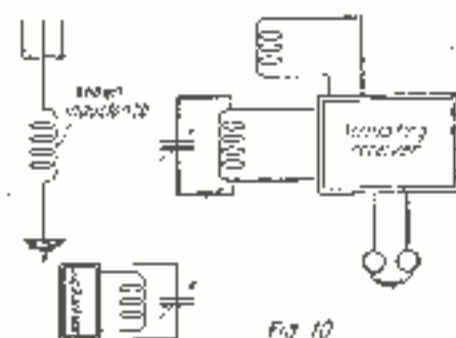


Fig. 10

Arrangement for measuring the capacity of an antenna system.


Multi-Stage Radio Frequency Amplification

By JOHN SCOTT-TAGGART, F. Inst. P., A.M.I.E.E.

Part II



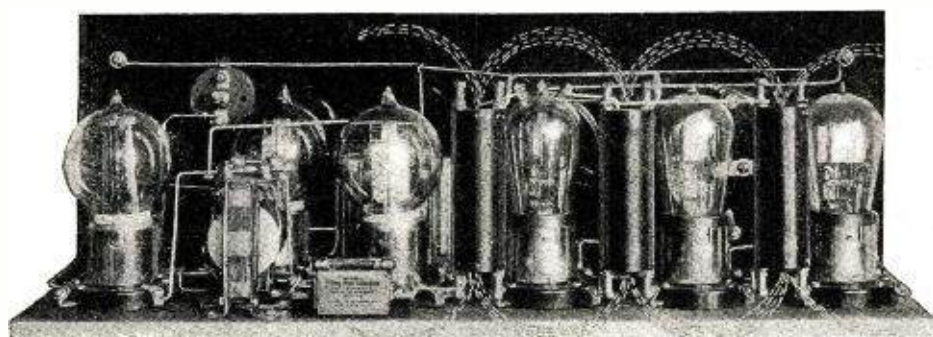This, the second article of a series, deals principally with the stabilization of multi-stage radio frequency amplifiers and is probably the most important consideration relative to circuits of this nature.



The dotted lines representing the magnetic fields of the radio frequency transformers show how one transformer is coupled to another. This is one of the most common couplings in radio frequency amplifiers.

A VERY common and successful method of reducing the tendency of oscillation in a tube is to place a resistance in the grid circuit. Sometimes it consists of an actual resistance of the ordinary kind, and in other cases the grid to filament path itself is used as the resistance. In the latter case what we do is to take advantage of the fact that when the grid becomes positive with respect to the negative end of the filament, electrons are at-

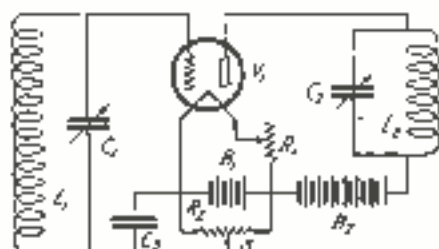


Fig. 15. The usual method of setting up a steady grid current: the employment of a potentiometer connected across the "A" battery.

tracted to the grid from the filament; these electrons are attracted to the grid from the filament; these electrons travel around the grid circuit, through the grid inductance, back to the filament. This setting up of a grid current introduces damping into the grid circuit. In other words, some of the energy in the grid circuit is consumed and losses are incurred by making the oscillations in the grid circuit produce a grid current. This loss may be made sufficiently great to stabilize the circuit in which it is used and prevent the tube from oscillating. To set up a steady grid current is a simple matter, and the usual method is that illustrated in Fig. 15, where the slider S moves along a potentiometer of about 400 ohms resistance connected across the filament battery B_1 . A fixed condenser C_1 of .002 mfd. may be connected in the position shown to avoid making the radio frequency currents travel through the potentiometer resistance itself. This condenser C_1 may frequently be omitted. When the slider S is at the extreme left position, the grid is at zero volts; as the slider is moved further to the right the grid will be given an increasing potential, which will become 5 volts positive if the slider S is moved in the right side of R_1 , assuming the battery B_1 gives 6 volts. Any

degree of damping, within limits, may therefore be introduced into the grid circuit, and the slider S will usually be adjusted to such a point that the tube is just off the oscillation point.

It is rather important to note in this method that the position of the rheostat R_1 is of importance. If it is connected in the negative lead it will not be possible to give the grid the full 6 volts because when F is at the left side of R_1 the grid will be at a negative potential depending upon the drop in potential across the rheostat. As F is moved to the right a point will be reached where the grid has a potential of zero volts and a further movement of F to the right will begin to give the grid a positive potential. If the drop in potential across the rheostat is normally two volts, it will only be possible to give the grid a maximum potential of four volts positive which, however, in most cases, would be all that is necessary. Where it is desired to be able to give the grid any positive voltage from zero to positive 6, it is desirable to connect the rheostat in the positive lead.

Fig. 16 shows the connection of an actual resistance element R_1 in the grid oscillatory circuit. This resistance may have a value between 20 and 50 ohms, according to various factors, such as the amplification factor of the tube and the constants of the oscillating circuits and the natural coupling between grid and plate circuits. Its correct value is best found by experiment. If it is variable, so much the better.

Fig. 17 shows the resistance R_1 included in the plate oscillatory circuit. This is an alternative arrangement and self-oscillation may be prevented, either by introducing

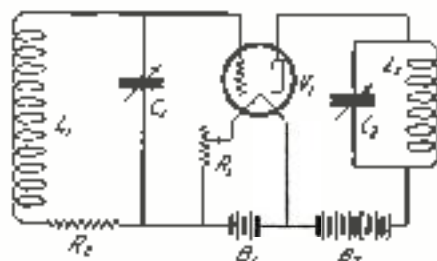


Fig. 16. The grid circuit of this hook-up is damped by the insertion of a resistance directly in the grid circuit.

damping into the grid or the plate oscillatory circuits. In some cases the damping is introduced into both circuits by any of the methods specified.

Fig. 18 shows the use of a resistance R_1 in parallel with the oscillatory circuit $L_1 C_1$. This method has been advocated by the author on several occasions, because it does not involve the production of direct currents in the grid circuit which are liable to cause distortion. The resistance R_1 now has a value of the order of 100,000 ohms, and a variable resistance having this maximum value will be found very convenient.

Fig. 19 is the same arrangement as Fig. 18, except that the resistance R_1 has been connected across the plate oscillatory circuit.

Fig. 20 shows the use of a resistance R_1 in the grid circuit of the tube, but in rather a different position to that shown in Fig. 16. The effect, however, is very similar, and the value of R_1 is usually of the same order as the resistance R_1 described in connection with Fig. 16.

It is desirable to make all the resistances used in these various cases devoid of capacity.

OBTAINING STABILITY BY REDUCING AMPLIFICATION

A rather obvious method of increasing the stability of a radio frequency amplifying circuit is to reduce the amount of amplification given by the tube. We can do this,

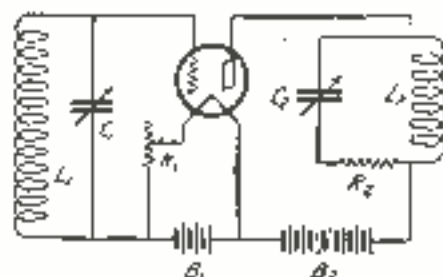


Fig. 17. The utilization of a resistance in series with the plate oscillatory circuit is another effective method of preventing self-oscillation.

either by a tube having a poorer amplification factor or by reducing the amplification given by the tube in use. This may be done by reducing the filament current, a very common expedient, and by reducing the "B" battery voltage. Drilling the filaments is usually a very effective method of stabilizing a radio frequency amplifier, but at the same time, any beginner will appreciate that reducing the efficiency of the apparatus in this way is wrong, and that the necessity for doing this is merely due to lack of proper design elsewhere.

PLATE IMPEDANCE METHOD

An interesting and useful method of stabilizing a radio frequency amplifier is that illustrated in Fig. 21. We have an impedance Z shunted by a variable condenser C_1 . The impedance Z , which may be a choke coil with or without an iron-core inductance, has in parallel with it the small variable condenser C_2 and the choking effect on the radio frequency oscillations in the

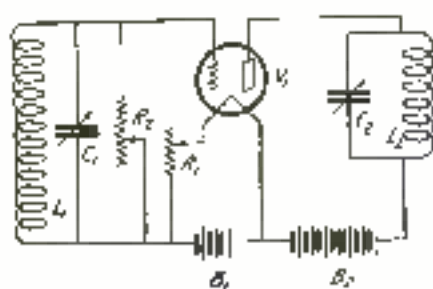


Fig. 18. A variable resistance connected in parallel with the grid oscillatory circuit provides a means for controlling self-oscillation.

plate circuit may be controlled by means of a condenser C_p . The smaller the value of C_p , the less tendency will the tube have to generate oscillations and vice versa.

USE OF REVERSED FEED-BACK

Reversed feed-back, which consists in feeding back energy into the grid circuit in a direction opposite to that which produces the signal effect, may be employed for stabilizing a radio frequency amplifier.

Fig. 22 shows how the inductance L_2 is connected in a reverse direction to produce an inverted feed-back effect which will tend to oppose the natural reception effect due to capacity coupling, etc.

In the Fig. 22 arrangement the reverse feed-back effect may be obtained when the coils L_1 and L_2 are fairly loosely coupled in a reverse direction. If L_2 is brought too close up to L_1 , the reverse inductive effect is swamped by the increased capacity coupling between L_2 and L_1 , and this produces a greater tendency to self-oscillation. A coupling of two tuned circuits to feed-back effect is, therefore, not a very practicable arrangement, although when the plate circuit is not tuned, reversed feed-back may be quite useful in stabilizing a receiver.

Fig. 23 shows a modified arrangement in which the feed-back coil L_2 is not a part of the main tuned plate circuit but is connected in series with it. This circuit will, in general, be found better than Fig. 22, although the coil L_2 should be kept small.

ELIMINATING THE CAUSES OF OSCILLATION

The method we have described above may be regarded as general means of counteracting the ill-effects of faulty design. The design of the receiving apparatus should be such that palliatives should not be necessary, but while it is a simple matter to make theoretical comments on the problem of radio frequency amplification, the fact remains that there is today no really satisfactory method of radio frequency amplification. If all experimenters who at present are working in directions where great success has already been achieved were to turn their attention to the problem of long distance reception and multi-stage amplification, probably some solution could be found.

It is the purpose of this article to explain the difficulties and to indicate what has already been done to overcome the troubles experienced in multi-stage radio frequency

amplification. A method of the author's own is also given.

The elimination of the causes of oscillation is a practical impossibility, but much can be done to balance them out with a minimum of energy loss.

In the first place, since the grid-to-plate capacity of the tube is one of the chief troubles, an improvement is made by decreasing it. Sometimes the capacity is between the electrodes themselves, but more often in the leads to the electrodes. The B_1 tube, for example, which is an audio frequency amplifier of great utility, has the advantage that the grid-to-plate capacity is large. The Myers tube and the V_p are, however, admirable for radio frequency work, because the capacities between the electrodes, and the leads going to the electrodes, is small.

Much can be done, however, with the ordinary type of tube, provided a suitable

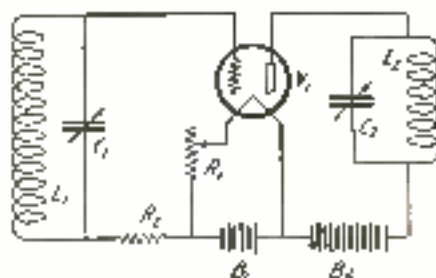


Fig. 20. An arrangement similar to Fig. 18, but with the resistance in a slightly different position.

tube holder is used. One apart from the other merits the widely-spaced contacts on certain types of special tube holders are particularly suitable for radio frequency work. The ordinary arrangement where the socket pins are very close together, the nuts and washers being frequently only a matter of 1/16th inch apart, are entirely unsuitable.

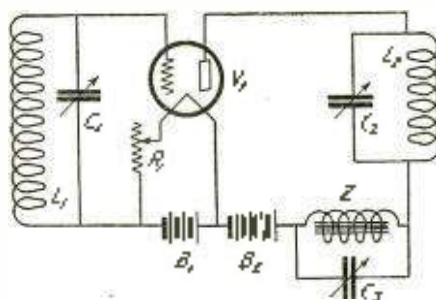


Fig. 21. A circuit employing a variable impedance in the plate circuit as a means for stabilizing the radio frequency amplifier.

for radio frequency, or, in fact, for any other work.

All leads, of course, should be kept as short as possible, and as far apart as can be arranged. Both bus bar wire connections are probably the best for wiring a set with several stages of radio frequency amplification.

OVERCOMING INDUCTIVE COUPLING

The overcoming of inductive coupling has received very little attention, probably because capacity coupling is much more insidious and dangerous.

Inductive coupling may be made very small by arranging that the fields of coils in the grid and plate circuits do not interact. The coils should be kept well apart, so as not to influence each other, and they may conveniently be arranged at right angles. To keep the inductive fields as small as possible the coils may be wound on small diameter tubes with fine wire, but this may lead to a certain amount of inefficiency. It is, however, a direction in which experiments may

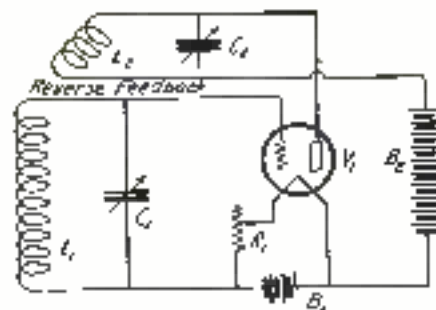


Fig. 22. A circuit employing reverse feed back for preventing self-oscillation. This is similar to the system employed by the Superdync.

be made. The smaller the coil the less will be the inductive effect of it on another coil.

A method of reducing the magnetic effect of one coil on another is illustrated in Fig. 24, which shows both coils L_1 and L_2 enclosed in metal boxes, having only small openings to allow the connecting wires to pass through. The metal ratings E_1 and E_2 should be of fairly substantial size, and the coils arranged clear of the sides. Sometimes it may be desirable to earth the fields.

Fig. 25 shows the inductances L_1 and L_2 wound on tubes which are staggered in relation to each other. This arrangement has been used by Prof. Hazeltine in his Neurodyne receiver, which involves the use of radio frequency transformers. The same arrangement, however, could be used for tuned plate circuits. The fields of the two coils are shown in dotted lines, and it will be seen that by arranging the coils in a suitable manner it is possible to avoid any appreciable inductive coupling between the inductances.

An interesting arrangement which has been tried by Mr. C. P. Kendall and the author is that illustrated in Fig. 26. Here the inductance coils L_1 and L_2 are in the form of toroids. The inductances are shaped like a curtain ring. If we obtained a wooden curtain ring and completely wound it with insulated wire, the ends, however, being separated by a fraction of an inch and leads taken from the ends, we would have a toroidal coil. The same effect would be obtained by taking a long cylindrical coil and bending it round so that the ends met. In the case of such a coil the magnetic field is entirely enclosed, and while the coil possesses all the properties of an inductance, there is no external field which could influence another coil. In Fig. 26 both grid and plate coils are shown of toroidal shape. A practical coil may be made by taking, say, a 3-inch length of insulating tubing 3 or 4 inches in diameter and cutting a slit in the tube. A toroidal coil can then be wound on the tube.

Fig. 27 shows a circuit using two tuned plate circuits employing toroidal coils. In this arrangement there will be no inductive effect between the coils, but this does not mean that there will be no capacity coupling, which is the most trouble in multi-stage radio frequency amplifiers. The fact that

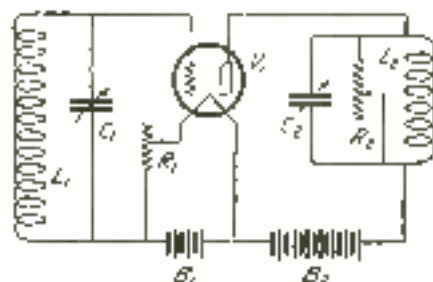


Fig. 19. Practically the same arrangement as that of Fig. 18, except the resistance is in parallel with the plate oscillatory circuit.

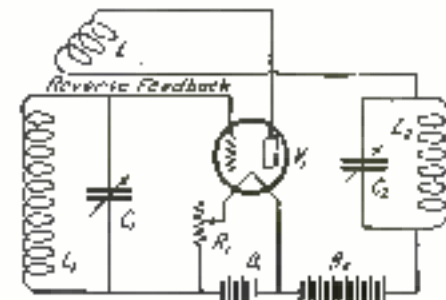


Fig. 23. Another reverse feed-back system wherein the tickler coil L_2 is a part of the tuned plate circuit.

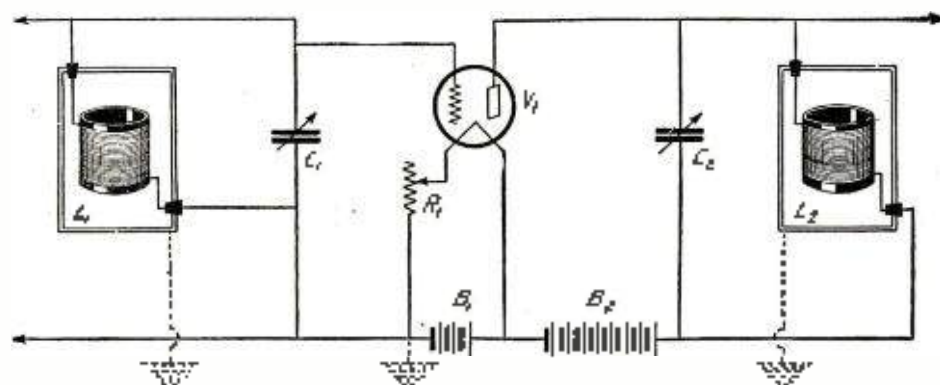


Fig. 24. Enclosing coils having extensive magnetic fields, in metal boxes, reduces or eliminates magnetic interference between one and another.

toroidal coils are used does not mean that the coils can be put close together because we then get a substantial capacity coupling between the coils, even though there is no inductive coupling, and the capacity coupling is generally the most troublesome. The Fig. 27 arrangement must therefore not be taken as a solution of the problem of multi-

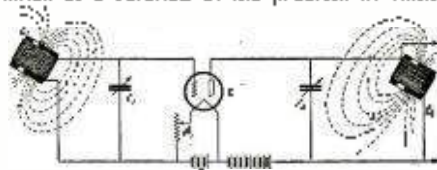


Fig. 25. The usual system employed in a Neutrodyne. The coils are placed in conventional angles so that the magnetic field of one cannot enter the magnetic field of another.

stage radio frequency amplification; it is, however, a very interesting suggestion for overcoming one of the coupling effects likely to cause instability.

THE "ASTATIC" PLATE COIL

An interesting suggestion for the plate circuit of a tube in the grid circuit is that illustrated in Fig. 28. We here have two plate coils L_2 and L_3 wound in opposite directions. The idea is that the inductive effect of L_2 on L_1 would be neutralized by the opposite inductive effect of the coil L_3 on L_1 . The coupling between L_2 and L_3 should not be sufficiently great as to add materially to reduce the total inductance of

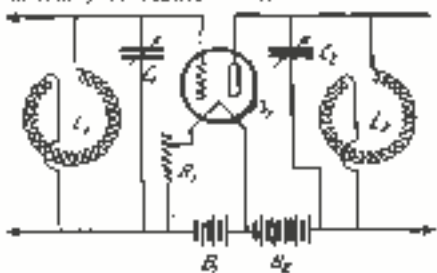


Fig. 26. A circuit employing toroidal coils. In these coils the magnetic fields are enclosed by the coils, then the fields are confined to the center.

the two coils in series. It would seem that the positioning of the combined coil L_2 should be symmetrical with respect to the coil L_1 in any set built using such a coil.

BALANCING OUT THE CAPACITY EFFECT IN A TUBE

Since the coupling inside the tube is effected by means of a capacity, it is only natural that we should turn to a capacity for the purpose of neutralizing this coupling. The effect of the coupling inside the tube is for potentials to be communicated from the plate circuit to the grid circuit in such a direction as to increase the tendency to oscillate. To counteract this capacity effect, we therefore require to introduce in the grid potentials of opposite, but similar magnitude. If the ca-

capacity of the tube is more than balanced, a reverse feed-back effect will be obtained which will weaken signals. It is therefore desirable, that the balance should be an exact one. It is, of course, no use connecting a condenser from the plate to the grid because this condenser would merely assist the existing capacity. It is necessary to obtain a reversal of phase and this reversal may be obtained by tapping either the grid or plate inductance or by the use of transformer coupling. These methods will now be described.

Fig. 29 shows a simple tube amplifier in which, however, the direct current plate circuit contains only a portion of the oscillatory circuit. In this figure it will be seen that a tapping S is taken away from about half-way along the inductance L_2 and, therefore, the direct plate current only flows

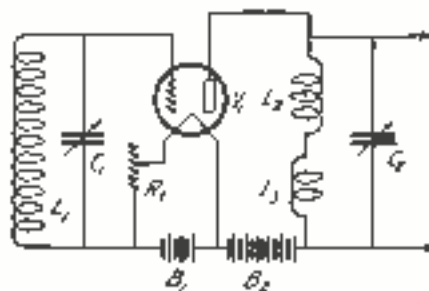


Fig. 27. Coils L_2 and L_3 are wound in opposite directions, consequently the inductive effect of L_2 on L_1 is neutralized by the opposite inductive effect of the coil L_3 on L_1 .

from the top of the inductance L_2 to the middle tapping. It is, of course, sufficient to pass a varying plate current through a part of the oscillatory circuit to set up oscillations in that circuit, but it will be found in practice that usually the maximum amplification is obtained when the whole of the inductance in the plate circuit is included in the direct current plate circuit. In Fig. 29, when the end E_1 is negative the end E_2 will be positive with respect to the tapping S , and therefore with respect to the filament of the tube, the end E_1

being connected to the grid of the tube through the grid to plate capacity shown in dotted lines by the condenser C_2 and these potentials will be opposite at any given moment to those of the end E_1 . We now connect the end E_2 through a very small condenser C_1 to the grid of the tube, and it will be seen that, whereas the capacity in the tube producing certain potentials on the grid, exactly opposite potentials are being communicated to the grid through the condenser C_1 from the end E_2 of the inductance L_2 . By making C_1 of the correct size, the feed-back impulses communicated through C_1 will be exactly neutralized by the reverse feed-back through C_2 . The result is that the capacity of the tube has been neutralized, and the circuit will consequently not oscillate.

The condenser C_1 may also be used to balance out the capacity coupling between the coils L_1 and L_2 . In order to enable a more correct balance to be obtained I have

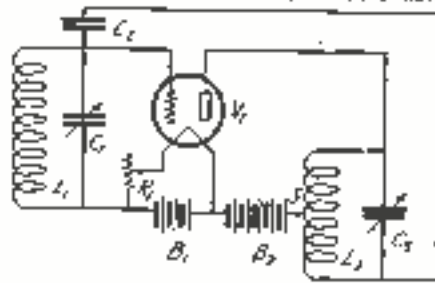


Fig. 28. A simple vacuum tube amplifier in which the direct current plate circuit contains only a portion of the oscillatory circuit and the direct plate current flows thence only.

suggested connecting an actual condenser in the position shown in C_1 in Fig. 29. This condenser will actually increase the tendency to oscillate, but by making C_1 larger it is possible to balance C_2 and C_1 accurately, whereas when we are relying upon capacity between grid and plate of the tube, we are dealing with a very small capacity and one which is liable to fluctuate; a change of tube might easily upset the balance.

Having got the amplified oscillations in the circuit L_2 C_2 we have to find some method of using them and we can couple an inductance to L_2 , this inductance being connected in the grid circuit of another tube. Another arrangement would be to connect the point E_1 through a grid condenser to a second tube, but in this case we would only be obtaining about half the potentials developed across the inductance L_2 . We can, however, overcome this difficulty by seeing that the tapping S is not in the middle but nearer to the end E_2 . In order to obtain a balance we then have to make the condenser C_1 very much larger, and if the distance S and E_2 is, say, one-tenth of the distance between E_1 and E_2 , then the capacity C_1 will have to be ten times the capacity between the grid and plate of the tube (and, of course, the other undesirable coupling capacities).

(Continued on page 1306)

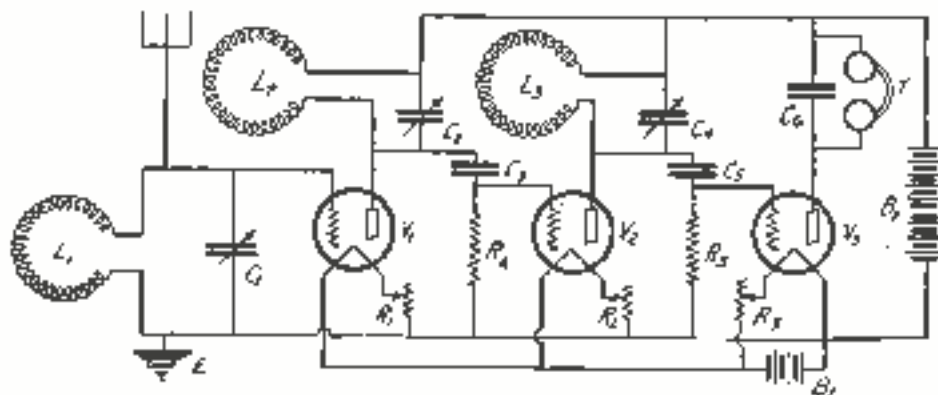


Fig. 29. A circuit employing two tuned plate circuits, with toroidal coils. There is no inductive effect between these coils.

What's What About Radio Horns


By CARTER FISKE

A description of some interesting tests made to determine the behavior of sound waves in loud speaker horns.

ALTHOUGH the radio horn is apparently one of the least technical things about a radio set, it is at the same time the least understood. The physical appearance of a thing is not always an indication of the way in which it functions. A piece of newspaper wound into a cone makes a horn, but the way the sound waves leaving the diaphragm of our loud speaker unit act when they burst forth from this horn is quite another matter. The most peculiar thing about the simple megaphone is that physicists themselves are not familiar with its operation and they are constantly contradicting each other. One says,

If there is anything that will chew up and destroy the symmetry and harmony of a good reproducing element it is a poorly constructed horn. Since no two reproducing elements of different design have the same acoustic properties, it is evident that the horn which will serve one efficiently will not serve the other. All the logic of the physics of sound point to the necessity of designing a special horn to fit each reproducing unit.

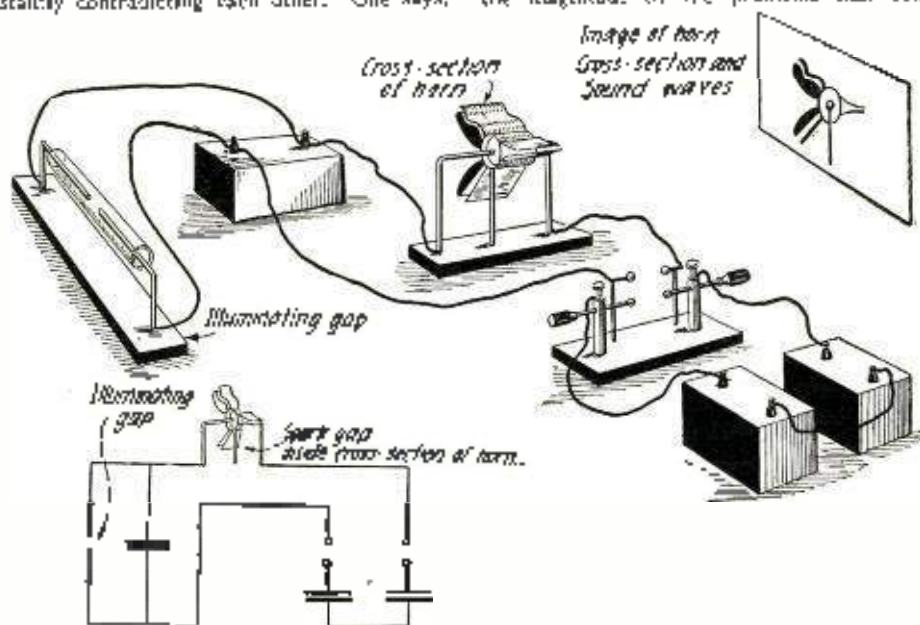We have some especially good horns today, and in every case they are produced by manufacturers who thoroughly appreciate the magnitude of the problems that con-



The apparatus used in the experiments described in this article.


"It is this way," and another says, "No, it is this way."

Now a radio horn is a mighty important part of a radio outfit—far more important than the average radio fan realizes. In this regard, it is interesting to know that the phonograph manufacturers had many worries over the horn for their reproducing unit. They spent barrels of money in experimentation and they found that the various horns they used made a world of difference in the quality of the music. Whether the horn was large or small, of tin or wood, long or short, round or square, made a great difference.

It is evident that a radio horn performs the same function as the phonograph horn. We have the diaphragm of the reproducing element. At the small end of the radio horn we have exactly the same thing. The problem is the same, yet what manufacturer of radio horns has spent the money that the phonograph people spent on the same problem? Not one, indeed. The art is too young, and it goes without saying that 95 per cent. of our horn manufacturers completely overlooked the technicalities of the problem and supply went out and bought a stock horn to fit their reproducing element. This procedure is fundamentally wrong to say nothing of being unscientific. Consequently we have numerous loud speakers on the market not worth the powder to blow them up with.

about them. They have spent money experimenting, and as a result they put forth a product which was as well as could be expected considering the youth of the art. With due respect to the efforts of these conscientious manufacturers—and bless the few of them—the author still holds that there is a great deal of room for improvement. The market is still thirsty for a horn that will give absolutely faithful reproduction for all the varied frequencies that come forth from the loud speaker.

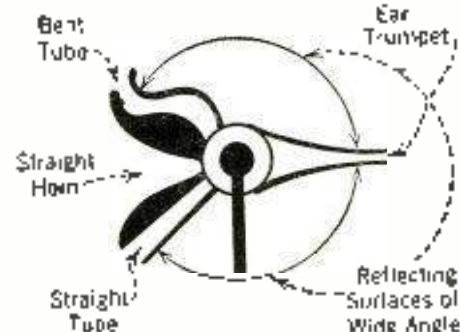If the author were purchasing a radio (Continued on page 932)



The sound produced in the center of this instrument was amplified through the various horns attached to it and photographed taken in rapid succession. These pictures are shown on the left.

These pictures show the propagation and reflection of sound waves through various shapes of horns.



PROFESSOR BARON HEINRICH RAUSCH
VON TRAUBENBERG

LIFE OF THE AUTHOR

The author of this article, Professor Dr. Baron Heinrich Rausch von Traubenberg, was born in Estland, which was then a part of Russia. He got his scientific training in Germany and after the completion of his physical studies in Würzburg under Professor Wien in 1905, he took occasion to devote himself for several years to wireless telegraphy, taking part in its rapid development. Ever today it is remembered with pleasure, how he, along with his friend, the then director of the Sigmund Company, H. Hahnemann, was in active touch with Duke Arco in the national development of the spark machine of those days. The system of producing undamped waves of Waldeyer-Poulson made such a sensation in its application that our author resolved to make a connection with the newly founded Amalgamated Radio Telegraph Company.

Interesting experiments with the new system in England, Russia and Germany, in which the author took an active part, led to great activity in this branch. In the following years he devoted himself again to pure science; he worked first in the Interior Academy of Science in St. Petersburg with Prince B. Golitsin and then went to the University of Göttingen. At the end of the war he took up again the work of the wireless company to solve a technical problem, which was the determination of the absolute radiant energy of a modern great station. He succeeded in carrying out the incomplete work of the former superintendent, Professor F. Braun, of measuring accurately the radiations of far distant transmitters. Further experiments in which Professor Max Abraham, who died all too early, one of the most renowned students of the Maxwell theories, took active part by theoretical co-operation, touched upon the resistance of the surface of the earth and upon the grounding of antennas. Various publications of the author, in co-operation partly with Professors Abraham and Pusch embodied the results obtained.

After peace was declared the author returned again to Göttingen and was called therefrom to serve as Professor of Experimental Physics and Director of the Physical Institute of the German University in Prague, where for a while he busied himself with his second important range of studies, that of the atom.

The Significance of Rays In Physics

By Prof. BARON HEINRICH VON TRAUBENBERG



The first of a series of articles dealing with that part of Physics closely related to radio.



RADIO NEWS is a distinctive paper. It will hardly be possible to find another in which the field of pure science, technique and practical application of science is so thoroughly covered and in which not even humor is omitted. It is easily understandable then, that the circle of readers belonging to such a publication should be interested in a wide field and should have great interest in the constant advances of science.

The object of these articles is to show as clearly as possible how this constantly

mathematical, physical and technical developments, the gargantuan scope of this subject. It is easy to imagine a wave receiving apparatus constantly being acted upon by molecules, receiving rays of all sorts. Suppose this receiving apparatus to be a dozen times more complicated or more sensitive than the most intricate radio receiver. Such an apparatus is the human mind. The reader need not be frightened because of the enlarging on the peculiarity and intricacies of our mental process, but may at least say this much in outline:

The happenings of the outside world are conveyed to us through our senses and every improvement and refinement brought about in the method of physical observation is made solely to establish a greater range or give greater perfection to these senses of ours. Although the civilization man has brought about has actually diminished the sensitivity of many of our senses—shown clearly by the supremacy of many beasts to man in this particular realm—modern physical methods and apparatus of such fineness and exactitude have been perfected to assist our regular senses that man is able to "hear and see" the most subtle sounds and moves in nature. Through the use of such apparatus, our scope of reception is widened. Every day our world becomes richer and more beautiful. Today we know with equal

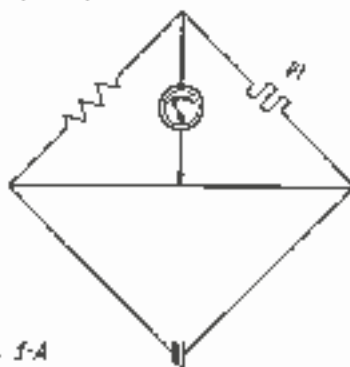


Fig. 1-A

Diagram of the Langley Bolometer. The radiator heats the platinum foil P, whose change of resistance in a Wheatstone Bridge connection gives the desired reading.

broadening range of science going hand in hand with a similar advance in technique, is enabling us to go deeper and deeper into the secrets of Nature. Most particularly we will deal with the adoption and use of rays in physical investigation. As the name of the magazine indicates, its readers are not only interested in radio communication but also in new things or developments made in connection with rays.

While man is unacquainted completely with the laws of nature, he cannot of course appreciate entirely certain phenomena which seem apparently arbitrary. The development of more than a century was necessary before physicists investigating such phenomena were able to distinguish between accidental and subjective nature. By the discovery of objective power, however, we have been able to change ourselves from the slaves to the masters of Nature.

Since the greater part of nature's powers are electro-magnetic, I will not attempt to show without going into the intricacies of

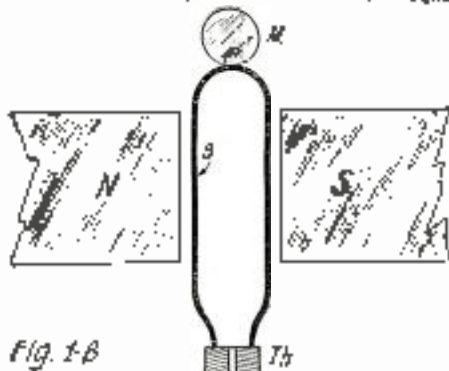



Fig. 1-B

Diagram of the Radio-micrometer; the radiations heat the thermo-element Th; the current thereby produced in the coil B, which lies in the electro-magnetic field NS rotates the mirror M.

exactly the chemical composition of a star 100,000 light years distant and the size and construction of a hydrogen atom. We can give with absolute accuracy the line con-

(Continued on page 934)

Fig. 2a. Photograph of a typical form of Photoelectric Cell employed principally for the measure of weak light rays.

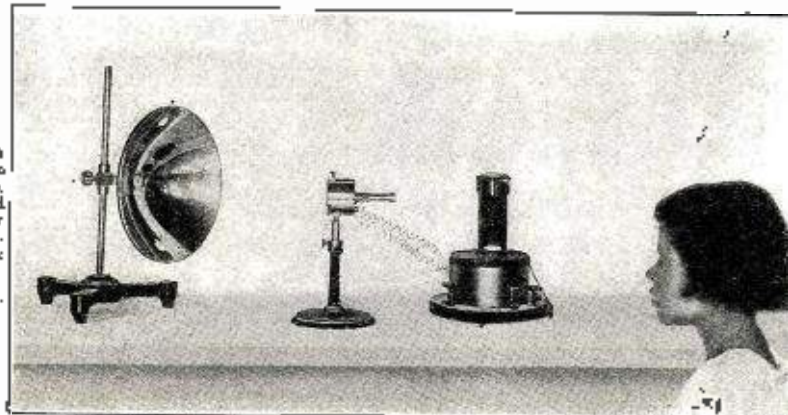

The Barometer and Radio Reception

M. J. CAUENEY, CAN. 3GG

An exceedingly interesting article dealing with the effects of the rise and decline of barometer readings on radio reception. Mr. Cauey's tests covered a period of two years, in which time he collected enough data to form definite and, let us say, authentic conclusions on the subject.

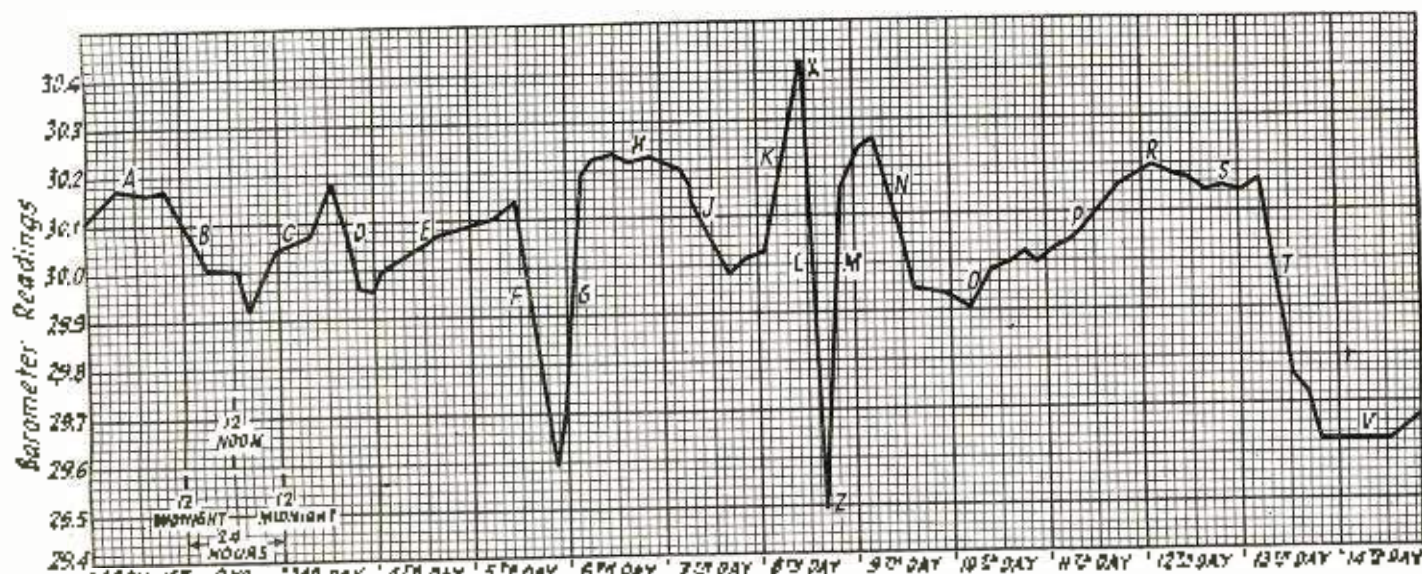


Fig. 1

Typical graph of barometer readings, those for the first 14 days of April, 1923. Note that a sudden decline of pressure is invariably followed by an immediate rise and that the average normal is usually reached again. As a rule radio reception is bettered by a rise of the barometer and hindered by a decline.

DOES the weather affect radio reception? If so how? Why do we get "good air" on one night and "poor air" the next night when both are clear, moon light nights?

If the weather does affect our indoor pastime, then what kind of weather will give us clear nights when the air is like clear, sparkling wine—when the "tip" old receiver does her stuff, and you can pull the dials any place at all, and pull in DX stations from way over the other side of the radio map?

On the other hand, if the weather man is the real "nigger in the woodpile," then just what particular brand of weather does he use to spout away those distant and infrequent visitors to our dials, and also seriously reduce the volume of those nearer stations which we always call upon for music when skeptical friends or boasting radio rivals call on us?

In an endeavor to answer some of these questions I began, two years ago, to keep a record of the weather in conjunction with daily curves of the atmospheric pressure as shown by the barometer.

The quality of the radio reception was also recorded each night on the barometer chart, with special notes of any exceptionally good or poor reception.

To eliminate as much as possible the chances of error or variation here at the receiving station, the design of the receiver and antenna were left constant, not a wire in a vacuum tube being changed during the whole period of two years. The makers of the tubes may be pleased to know that they were Radiatrons 200 and 201. They have been burning over 4,000 hours now, and are still going strong.

Storage batteries were installed for both the filament and plate supply, and kept fully charged each day. Meters were used in the filament and plate circuits and when once the correct setting was found, it was never changed from year to year.

In addition, and in order to test the transmitting qualities of certain weather conditions here in this locality (Lat. 48, Long. 81, Northern Ontario, Canada) a low powered radiophone was installed using 10 watts with 500 volts of storage battery for the plate supply, and 10 volts of storage battery current for the filament.

The transmitting tests were recorded each night to run concurrent with the reception records and weather chart, and it might be well to mention that this station is 500 miles

from the nearest broadcast station and in an irregular manner, as shown in Fig. 1.

A cursory glance will show that the "glass" or, to be more exact, the atmospheric pressure, rises and falls also at various speeds. Sometimes it rises or falls slowly, sometimes not at all. Take the curve at the fourth day at the point E. Here we find our glass climbing slowly at an angle of about 25 degrees. If we now move along the curve to the right, on the eighth day we reach the portion of the curve M. You will notice that the angle of climb now is about 88 degrees, the ascent being almost vertical in fact. A study of the curve at points marked R, S and V will show how the barometer at times moves steadily in an almost straight line at a comparatively high or low position or the pressure chart.

It should be clearly understood at the start that the barometer does not tell the present weather so much as the future weather, which may arrive within the next 24 or 48 hours. Almost without exception when the glass falls, making a steep curve, as shown at Fig. 1 at E, L or T, it will bring stormy weather, and short dips in the curve like those of B, D, J, etc., will usually foretell a change in the weather prevailing at the time of the barometer decline. When the barometer rises rapidly, making a curve like that shown at G and M, it usually ushers in an improvement on the bad weather caused by the previous swift drops on the curve and invariably is accompanied by fresh, brisk or high winds, now and again amounting to a gale but eventually clearing up for much better weather.

The portions of the barometer curve most favored by mariners, farmers and all those persons whose lives are spent mostly outdoors, are the sections shown at A, R, S and V. Here we find the glass either steadily rising at an easy slope or traveling leisurely in a somewhat straight line from one day to the next; an almost infallible

(Continued on page 982)

YOUR CAR!

Are you interested in motoring, touring or camping? If you are, do not fail to read the December issue of

MOTOR CAMPER AND TOURIST

Here is a magazine that tells you things in connection with your car—things that you never even suspected.

Are you just running around the country or are you getting the full benefit of your car? **MOTOR CAMPER & TOURIST** shows you the way. On all newsmagazines

CONTENTS FOR DECEMBER ISSUE
Down to Winter Haven.

William Gilbert Irwin
The Rascal of the Snow Diggers
George Parks
Invading Alligator Land
Gene Thomas
The Tam Saucer Trail
Edgar White
The Mississippi Scenic Highway.

Truman Nelson
Continous Auto Parks
Pete L. Koch
Do Strange Cities Puzzle You.
Frederick R. Rutledge

from the nearest broadcast station and 250 miles from any radio transmitting station either amateur or commercial.


If the readings of any ordinary barometer are taken every few hours and the readings plotted on squared paper, with a line running from one reading to the next, it will be seen that the atmospheric pressure is con-

A Three Electrode Tube in 1899?

By D. C. WILKERSON



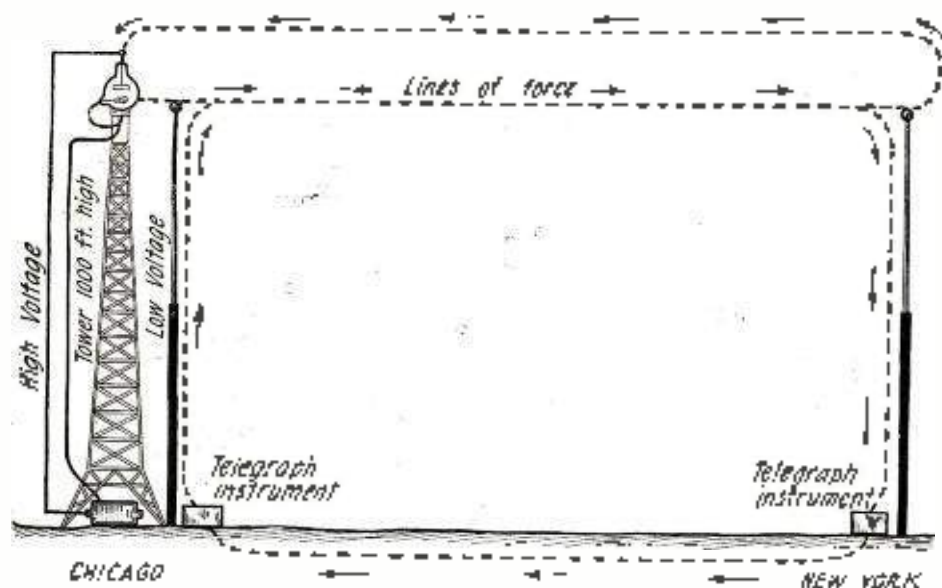Another page of radio history which is exceedingly interesting if only for the reason that the system suggested is parallel in principle of operation to the vacuum tube of today.



A copy of the original sketch of Dr. Pratt's system of signaling without wires. The upper atmosphere was to act as the conducting medium for the X-Rays, the return circuit to be through the earth. This system could be completed to a huge vacuum tube; the principle of operation is similar.

WITH the courts of the United States jammed with legal proceedings of all sorts, injunctions, damage suits, patent litigation and suits for recovery, the radio business is suffering from a somewhat uncertain patent basis. Many manufacturers are disinclined to hazard the manufacture of any radio accessories whatsoever on account of it, and the producers of complete sets are in a similar predicament.

The question of the three electrode tube now being discussed throughout the radio trade, and also in the United States and other courts is one of the most involved subjects in the radio field.

DeForest was supposed to be the originator of the device when he added the grid to the old two electrode tube brought out by Dr. Fleming. Armstrong claimed the origin of the discovery of regeneration and Meissner and Langmuir also filed patent claims on the same idea.

The history of the radio art in the United States is a colorful one, and in its early length, from the days of the early 1860 experiments of the Washington, D. C. dentist Louiss, up to the present day, there have been constant arguments as to the men entitled to the proper credit for the inventions related to the development of the radio art.

There is a matter of public record of a three electrode radio tube transmission system which was proposed to send signals from Chicago to New York, in 1899. This device was supposed to be directional in its transmission, and it had the advantage that it actually did function at short distances.

The device referred to, is the one brought out by the eminent Dr. H. P. Pratt, noted Chicago scientist, who has been interested and engaged in the problems of signal transmission for over 40 years.

It consisted of a tube constructed in the manner of the X-ray tube of the early non-Fleming type, and its secondary circuit was intended to take a potential of from 2,000,000 to 5,000,000 volts. At the time there

were no accurate means of determining such high voltages, and even today, the measuring of such high electrical pressures is only approximate, so the calculation of the Pratt secondary voltage was of a guess-work character.

This tube developed a cathode stream, from a source of emission, which was to be modulated by a magnetic device operated from a low voltage source. This means of modulation, please note, is included in the first DeForest patent, where he desired to modulate the current of electrons from the source of emission to the collector electrode by exactly the same means.

Another interesting feature of the Pratt transmission system was the means for collecting the energy at the receiving end. He desired to use a tall mast with a large metal ball affixed to the top, properly connected to the ground through recording instruments.

This X-ray method of transmission can be appreciated when we consider the interference set up by the average X-ray tube of today in the reception of radio programs. Especially is this annoying in metropolitan districts where dental and surgical laboratories are in continuous operation each day. Surely, a source of such heavy interference could certainly operate as a radio transmitter.

These experiments were carried on at South Bend, and in Chicago, in conjunction with tests parallel to the work with the Marconi System. It is noteworthy, also, that the scientists of that day realized the universal dispersion accompanying the transmission of radio signals, and turned their endeavors towards accumulating the transmission of energy in a directional manner to avoid waste and to attain a degree of secrecy.

That this Pratt system was designed to transmit telephone as well as telegraph signals is noteworthy and this development shows itself to be one of the eddy currents set up by the ambitious Bell, in scientific waters, when he actually performed the feat

of telephoning down a beam of light, so many years ago. Bell modulated a beam of light with the current flowing in a microphone circuit, and Pratt proposed to do the same with the X-ray discharge.

In this system, however, the third electrode was placed outside of the tube containing the emitter of electrons, and the collector plate was placed 1,000 miles away, connected by a common ground the earth itself.


Regarding this Pratt device in the light of the present day vacuum tube containing three electrodes, one would have to consider the whole area located between Chicago and New York as the electrostatic field between the grid and plate electrodes. In other words, Pratt was trying to set up a vacuum tube source of electronic emission in Chicago, modulate the stream from outside the tube, and put his plate 1,000 miles away in New York. The fallacy of that, in the light of present day knowledge, is that the ionization collision caused by the many gaseous molecules in the atmosphere would rob the electron stream of so much energy, that its effect would be lost within a few feet, or fractions of a mile from the transmitting station.

At that, Dr. Pratt recognized that he had to get into rarer atmosphere approaching a vacuum condition, and he thought rightly enough that the higher he went into the air, the rarer it would be, and, therefore, the greater the range of his signals.

The system which was designed to transmit signals from Chicago to New York was never installed on the scale projected but the fact remains that in this experimental work a vacuum vessel, having a source of electron emission, a collector plate and a means for modulating this electron stream, was devised.

The world owes a debt of gratitude to these hardy, early experimenters who supplied the groundwork for the marvelous development of the radio art of today, and

(Continued on page 1074)

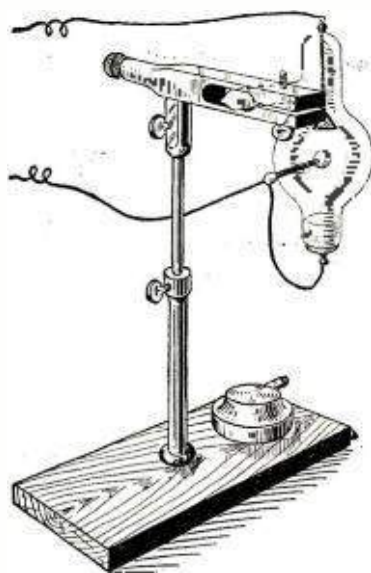

A copy of Dr. Pratt's original sketch of his X-ray tube and mounting, originally printed in the "Chicago Daily News" in the year 1899.

The Cold Tube of the Future

By J. H. T. Roberts, D.Sc.

It is evident that future tube developments must tend towards the production of an appliance which does not make such exorbitant demands upon its supply batteries as the present type. Dr. Roberts indicates in a most interesting manner the lines upon which the desired ideal may be approached.



THE recharging of the storage battery which is employed for heating the tube filaments constitutes perhaps the principal item of expenditure in the maintenance of a receiving set. It is natural, therefore, that many attempts should be made to produce a tube which should be altogether independent of heating batteries—in other words, a "cold tube."


This desirable appliance has been approached, but has not, up to the present, been reached. Tubes have recently been introduced with special filaments, which require only about one-tenth of the heating current consumed by those with the ordinary metallic filament. Such tubes are known as "dull emitters," because they give the necessary electronic emission when their filaments are raised merely to a dull red heat. They have proved very successful in operation, and mark an important step forward in the simplification of radio apparatus.

The ideal cold tube, however, still remains a dream of the future, and as its development constitutes one of the fascinating problems of radio, the reader may be interested in a short description of the workings of the present-day tube filaments, followed by a simple account of the phenomena of radioactivity, which will enable him to indulge in speculation as to the form which the cold tube of the future may possibly take.

EMISSION OF ELECTRONS FROM HEATED SUBSTANCES

It is well known that the electric current which passes in the plate circuit is carried through the tube by a stream of electrons which are emitted from the heated filament. Let us consider for a moment why it is necessary to have a heated filament to provide these electronic carriers in the tube.

The theory of the conduction of electricity through a metal conductor supposes that the atoms of the metal readily part with electrons which, under the influence of the electromotive force, pass from one atom to the next, and so on; there is thus an average "drift" of electrons in one direction, and it is this electronic drift which constitutes the current. But in so drifting an electron is never very much out of the sphere of attraction of one atom before it is within the sphere of attraction of another, and so the electromotive force required to maintain the drift is comparatively

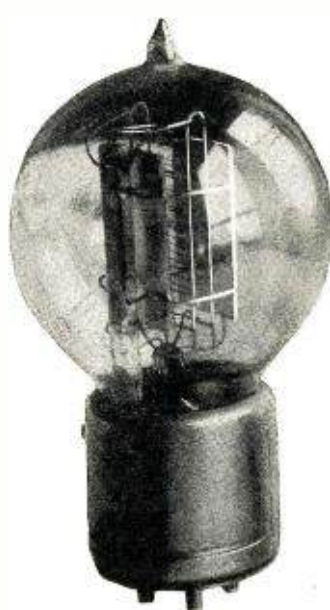

Examples of present types of "dull-emitter" tubes.

small. If an electron wished to leave the metal altogether and escape entirely from the attraction of the atoms, it would need a large force to enable it to do so. Under ordinary circumstances, therefore, the electrons are unable to leave the metal, and they can only be enabled to do so by special influences. If, for example, the metal is sufficiently heated, the vibrations of the atoms may become so great that some of their electrons are thrown out far enough to escape from the ordinary atomic attraction. This is what happens in the heated filament of the tube.

It must not be supposed that a substance must be electrically heated to make it emit electrons. The tube filament is electrically heated merely for convenience, and it is true that the heating in this case is supposed to be caused by the agitation of the molecules of the metal by the rapid drift of the "free" electrons. But a substance heated in any other way (e.g. a metal ball heated in a flame) will similarly emit electrons.

WASTE OF ENERGY

The heating of a filament is a wasteful method of causing it to emit electrons, for only a very small portion of the energy employed in heating the filament is used in detaching the emitted electrons—most of the energy is conducted and radiated away as heat. We are obliged to put up with this waste, however, as we do not at present know of any other convenient way of producing our tube-electrons. In the ideal "cold tube" the electrons will be emitted spontaneously, or the energy absorbed by the tube will be only that which is necessary for the emission.

COLD LIGHT

There are many other cases of this incidental waste. In order to obtain light from an incandescent gas mantle we have to raise the mantle to a high temperature and only a very small percentage of the total energy reappears in the required form of light, by far the greatest part being lost

as heat. All practical lighting devices are extremely inefficient in this sense.

The cold emission of light has, however, been more nearly approached (in a practical way) than has the cold emission of electrons. The phenomenon of phosphorescence apparently represents the production of light with only a small incidental loss of energy in the form of heat. It is thought by some that the glow-worm and certain fishes and insects hold the secret of cold light—light without heat.

Much experimental work has been done on the discharge of electricity through glass tubes containing certain gases at fairly low pressures, and cases are known where the incidental waste of energy in the production of light energy has, in this way, been very considerably reduced. This problem is a very important one and about as difficult as the production of cold electronic emission.

EVAPORATION OF ELECTRONS

The emission of electrons from a heated filament has been usefully compared with (Continued on page 936)

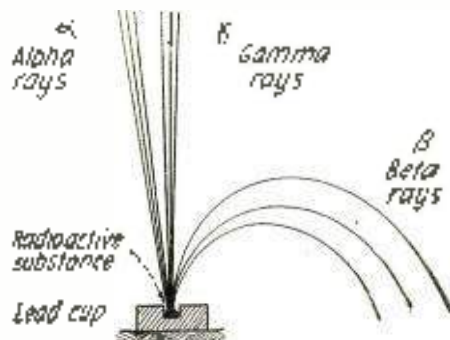


Fig. 3. A magnetic field at right angles to plane of paper deflects alpha and beta rays in opposite directions and to different extents, but does not affect the gamma rays, since these are not electrical particles, but waves.


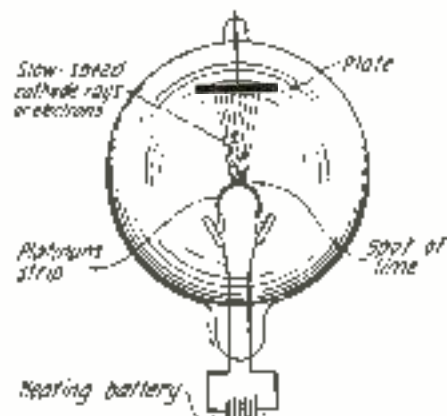


Fig. 2. A large number of electrons are emitted from the tube at a dull red heat, when the emission from the evaporated part of the strip is practically nil.

The Radiation Eliminator Contest

A few of the radiation eliminating devices submitted.

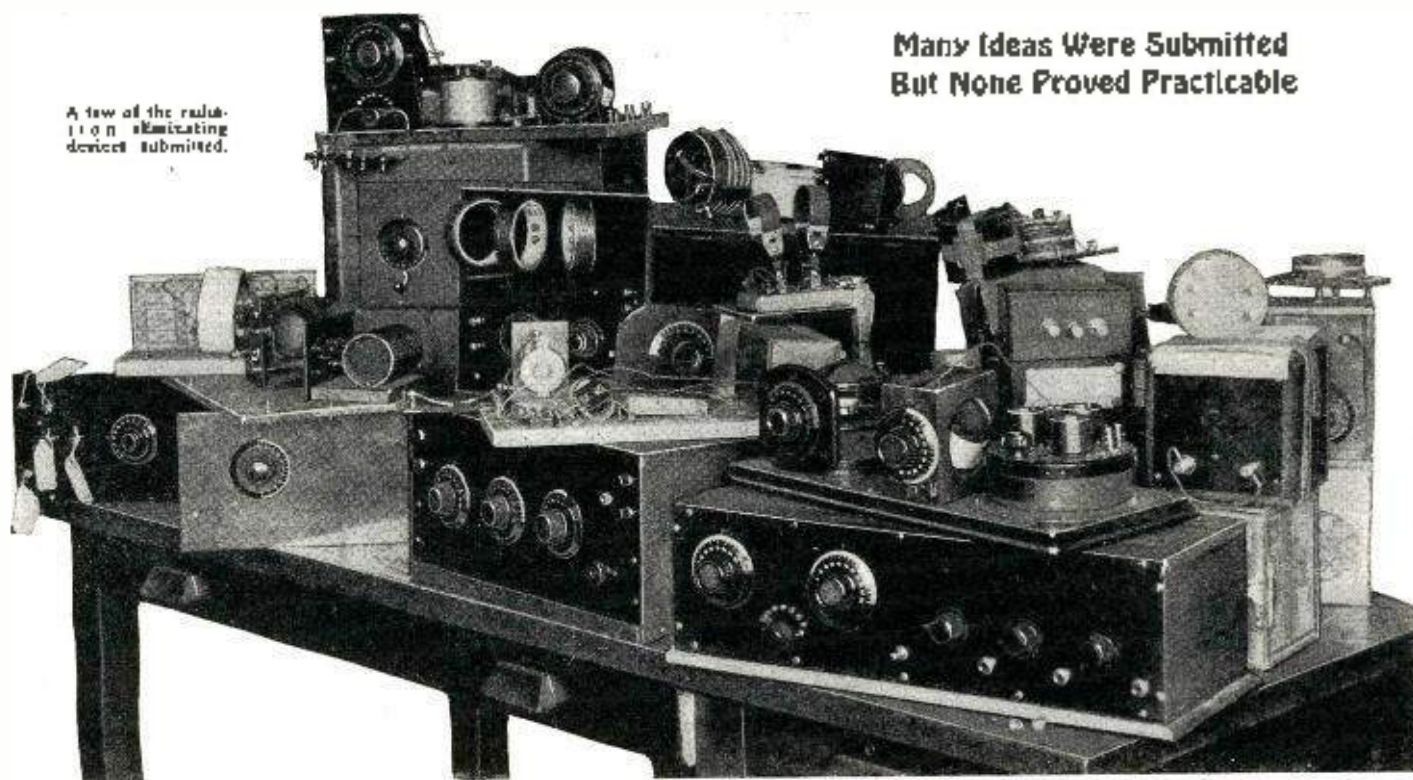Many Ideas Were Submitted
But None Proved Practicable



THE Radiation Eliminator Contest run by RADIO NEWS in an attempt to find a practical device which would prevent radiation from regenerative receiving sets in a state of oscillation was greeted with a huge response. Every conceivable form of device was submitted, ranging from special condensers and spaced coils to complete receivers embodying complicated circuits. This proves that a great many radio enthusiasts were interested in the problem and that many had attempted to prevent their sets from interfering with the reception of programs on neighboring receivers. For this, at least, they should receive credit, although their devices DID NOT prevent radiation. All the sets and instruments submitted were thoroughly tested in the RADIO NEWS LABORATORIES, but not one was found to be practicable.

Much to our surprise, the majority of the devices submitted failed to comply with the rules of the contest, yet the rules were specifically stated.

Nevertheless, we tested these devices, which, like the rest, proved of no value.

Some of the devices submitted managed to reduce radiation slightly, but they also reduced the volume of received signals and in proportion to the reduction of radiation. Such devices are of no value.

The contest has disclosed one fact, namely, so-called radiation eliminators had been devised before our contest was announced and were being used, but to no avail. It is assumed that propaganda against radiating receiving sets has at least managed to stimulate interest and that numerous experimenters have striven to devise a fool-proof attachment. We regret that none of the entries in our contest succeeded in doing so.

Of course, we can award no prizes. We offered prizes for devices, easily attached to any receiving set, which would ELIMINATE RADIATION. As stated, none of the devices submitted did any such thing.

Why Radio News Favors Esperanto

VARIOUS International Language Associations have been striving to stimulate an interest in the United States in their pet tongue. Up to the present time so little publicity has been given the International Language Movement on this side of the water that very few people are aware of its existence. However, the times show that in the United States even as in Europe there will be a use for one of the many tongues advocated. The extent of the usefulness of a Universal Language in the United States is a matter of speculation and whether or not it would benefit more than a choice is at present a question. Nevertheless, the ever increasing adaptability of radio to commerce, entertainment and its usefulness as a medium for the advancement of education and complete understanding between the Nations of the earth warrants the use of an international language.

It is fully realized by Radio News that some day a Universal Language is to play an important part in world affairs. It is realized equally well that at the present time the employment of an international language in the United States would prove of little value.

The American amateurs, however, who communicate nightly with amateurs in for-

ign countries are in dire need of a simple universal language. Communication is greatly hampered for the want of such a

Over 18 Pages of Advertising Omitted From This Issue of Radio News

owing to the tremendous increase in the circulation of Radio News to 400,000 copies and the record breaking growth of advertising to over 63,000 lines per issue, it became necessary to adhere rigidly to our schedule for closing this and all subsequent issues.

Consequently we were unable to handle any orders for advertising on which the copy was not received by our published advertising closing date—however for advertising terms for Radio News close on the first of the second month preceding the date of issue.

Although we were forced to leave out 8127 lines of advertising from this issue, because it reached us after the closing date, the December number has again broken all preceding records for advertising space with the stupendous total of 63,957 lines of paid display space.

medium of speech. Still, with a thought to the American amateur and a thought to the future, we see no harm and possibly

some good in promoting one of the many so-called international languages now in existence. But at the same time we strongly believe that the greatest care should be taken in selecting the particular language which will be the most serviceable from all standpoints. In selecting an automobile it is usually very pleasing to purchase one that is different, in some respect at least, from that of your neighbor. It is a human whim to be exclusive, but when it comes to the selection of a language that is to be universal, it is quite important that all whims be set aside and that each lamh follow the next, not of course to the exclusion of the best, but we argue from the point that the people are intelligent enough, with the help of authentic information to select the most desirable tongue.

The International Language movement has been run to extremes; there is no doubt of this, for at the present writing there are some 20 odd languages, all being pushed to the limit, and there are only two which have even a slight chance of being recognized, Esperanto and Elo! The followers of the less prominent manufactured tongues might realize that all their pains are in

(Continued on page 1052)



The Beginner's Tube Set

By A. P. PECK



The fifth of a series of articles by Mr. Peck written especially for the layman. Instructions are given for the construction of a simple vacuum tube receiving set and each part is lucidly described.



THE winter season is now coming on and, to the dismay of the radio fan, that means good reception weather. Then static, that growling and grumbling heard all summer, will be at a minimum and DX or distance reception

oxidizes rapidly in open air and soon burns up. Also, molecules of air would impede the progress of electrons from the filament to the plate, but this will be explained later.

The plate, 5, encloses the other elements. It usually consists of a nickel or a nickel plated metal sheet pressed to the required shape. The grid, 6, is placed between the plate and the filament and is usually a length of nickel or copper wire wound in a spiral form. The filament is a fine wire that becomes red hot when a current passes through it. In the latest types of tubes, this wire is coated with a chemical which increases its activity with a relative decrease in the brilliancy to which the filament must be lighted and a consequent increase in efficiency and saving of current from the battery which heats it.

All of the elements of the tube are supported on wires. The glass rod into which the supporting and connecting wires are sealed is shown at 9 in Fig. 1.

When you go into a radio store, the salesman may try to sell you what is known as

statics, and when the set is eventually made into a multi-tube one, the battery on hand will operate it at the least possible expense.

However, many either cannot invest in a storage battery, as it is expensive, or the facilities for charging it may not be available. In such cases the so-called dry cell tubes are practical. These tubes are so designed that the filament may be heated by one or more dry cells, which are obtainable almost everywhere. When they are used up, they can be replaced very cheaply. There are two prominent types of tubes operating on dry cells. One uses one cell and the other, three. The former consumes 25 amperes and the latter .06 ampere. Roughly speaking, the latter is somewhat cheaper to operate.

THE BATTERIES

In every practical receiving set yet in general use, two and sometimes three separate and distinct batteries are necessary. This statement does not include the Solodyne circuit that is, as yet, in the experimental stage and which only uses one battery. In detector circuits such as we are concerned with at the present time, only two batteries are used, so we will confine ourselves to a discussion of them. These two are known as the "A" or filament battery and the "B" or plate battery. The former is of the lowest voltage and it is essential that in connecting a set, the "A" and "B" battery wires do not become mixed.

Every battery has what is known as polarity, and has at least two poles or terminals to which connections may be made. These are known as the negative and the positive terminals and are usually plainly marked. At "A" in Fig. 2, we show a standard dry cell with the terminals marked with their

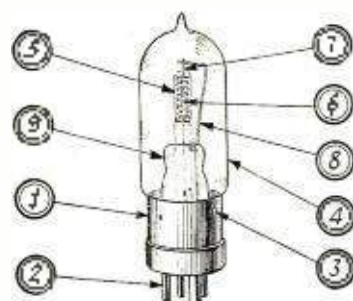


Fig. 1

Details of a vacuum tube. The prominent parts are designated by numbers and described in the text.

will be at its best. With a vacuum tube detector added to the set described in this department scores of stations will be heard that could not be picked up with the crystal outfit. So we are sure you will agree that now is the time to start work on a tube set and later a study may be made of its action after you are familiar with the working of the diode.

THE TUBE

The most important requisite for the new set is, without a doubt, the vacuum tube, or as it is variously called, the tube, both audio or light. The last name is one to avoid as it smacks of ignorance and its use leads to misunderstanding.

Let us see what the essential parts of a vacuum tube are. Refer to Fig. 1. Here we show a view of a standard dry cell type of tube in phantom. That is, the interior parts that are not ordinarily seen are indicated in dotted lines. The numbers on the drawing indicate the following parts. No. 1 is the base or shell. It is usually made of brass. No. 2 indicates the pins. To the ends of these, enclosed in the base, are fastened wires connected to the elements. In other words, the pins connect the elements with the other instruments of the set through the socket. No. 3 indicates the pins. It is placed on the base so that the tube will fit into the socket in the correct position. The glass bulb is indicated by 4. The interior of this bulb has been exhausted of almost all traces of air so that the filament can be lighted without its burning out as would be the case if it were in the open air. The glass here plays the same purpose as the glass in an ordinary electric light bulb. Heated wire

The parts necessary for converting the Beginner's Crystal Set to one employing a vacuum tube and capable of greater distance reception and louder reproduction of music and voice are:

- One vacuum tube.
- One vacuum tube socket.
- One grid leak.
- One grid condenser.
- One rheostat.
- "A" battery.
- "B" battery.
- One variometer.

a "bottle" tube. Many of these "bottle" or "independent" tubes are very good and will give perfect satisfaction, but unless the dealer will absolutely guarantee them, the purchase of one is a big gamble since it may be unsatisfactory. At best, the purchase of any tube, genuine or otherwise is somewhat of a gamble. Genuine tubes are stamped and the guarantee and license numbers are stamped on the carton.

There are many types of tubes for sale and each operates on a different "A" battery voltage. The "A" battery heats or lights the filament. Therefore the type of tube you buy will depend on facilities available for using it.

If you have electricity in your home to charge a storage battery or have facilities near at hand for so doing and you can afford the initial cost of a storage battery, by all means get one of the 6 volt, 5/4 ampere or 11 volt, 1 ampere tubes. They give best re-

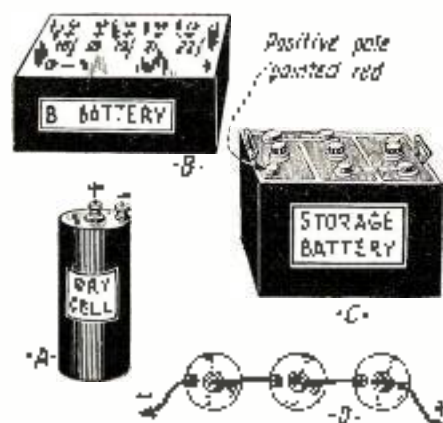



Fig. 2.

Forms of batteries employed in conjunction with a vacuum tube receiving set.

wax or paraffin over the binding post screw heads. Take a permanent magnet to the nearest machine shop and with it gather up the fine iron filings around the emery wheel. Pack these filings tightly around and in the center of the coil, which is in the tin cylinder. Then fit a tin circle to the bottom of the cylinder and solder in place. Be sure the coil is entirely surrounded by the filings. The coil should also be tested for an open circuit before putting in the tin cylinder. The condenser which is included with the Ford spark coil should also be taken out and used in series with the plate of the tube and the loud speaker as shown in the diagram. When using this circuit high voltages may be used on the plate of the tube without fear of damaging the magnets or burning up the windings of the loud speaker.

ROTOR SHAFT BEARINGS FOR CARDBOARD TUBES

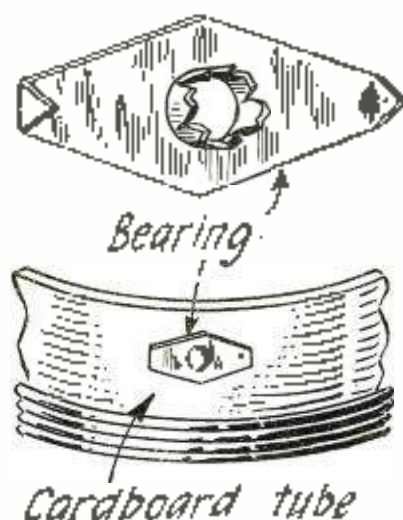Since paper tubes are both common and admittedly good from the electrical standpoint, it is desirable to have suitable bearings in them for the rotor shaft. The paper



A cone shell bearing, made from a piece of sheet brass. The hole for the shaft is made with a reamer punch.


tube is not sufficiently rugged in itself to have a hole through it remain a permanently good bearing and though the tube can be reinforced with leather-board or other material, and the whole treated with shellac, it is better to provide metal bearings. My first were made with pairs of sheet brass strips, one piece each side of the tube wall—a laborious and unsatisfactory method, but later good bearings were quickly and easily made by cutting diamond-shaped pieces of sheet brass or aluminum, say 1½ inches long, with enough of each end bent to a right angle to reach through the paper tube and clinch, making a good and substantial bearing.

The hole for the shaft should be made with a small punch and then spun out to the required size by revolving a smooth tapering spindle in it; this is better than a drilled hole, as it leaves the bearing with considerable wearing surface and the burr tends to hold the shaft snugly and without play. —Contributed by Frank A. Biele.

A QUICKLY MADE EXPERI-
MENTAL JACK

To the experimenter who delights in making up new circuits in breadboard fashion, the jack described here will prove very handy. It is constructed of two ordinary spring clip binding posts, as shown in the illustration. Two holes are drilled in the

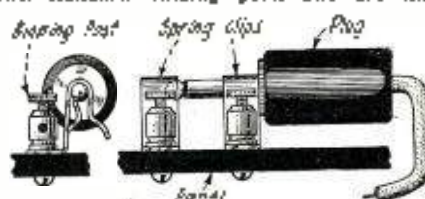board for mounting the clips and should be about 1½ inches apart. The spring clip binding posts are fastened to the board by two standard binding posts and are then



A simple jack made from two Ealinstock clips attached directly to the clamp bonding posts.

bent upward as shown. The plug can easily be forced under the spring clips so that the tip and the main shaft are securely held by the spring binding clips. If it is not desired to use the plug, the phones may be fastened directly to the spring clips in the usual manner. With this emergency jack in use, it will not be necessary to disconnect the phones from the plug when changing from the regular set to the experimental one.

—Contributed by J. E. Dixon

A SIMPLE "B" BATTERY ELIMINATOR

The radio fan desiring to build a rectifier which will take the place of "B" batteries is often puzzled as to how to secure a transformer to step up the A.C. voltage before rectification. Fig. 1 shows how a bell ringing transformer can be used for this purpose. This half wave rectifier will supply both detector and amplifier plate cur-

The Resistoflex!

Something new in the form of reflex amplifiers. Devised by John Scott-Taggart, F. Inst. P., A.M.I.E.E., who is an authority on Dual Amplification. Full details of this new circuit will appear in the January issue of *RADIO NEWS*.

rent and give excellent results on sets using up to four lugs.

Transformer No. 1 steps the 110-volt A.C. down to 6 volts to light the filament of the tube also 12 volts to transformer No. 2, which is used as a step up transformer. By using 12 volts from No. 1 to the 6-0-12 winding of No. 2, 220 volts A.C. is obtained from No. 2, which is supplied to the grid and plate of the tube. The secondary of an audio transformer can

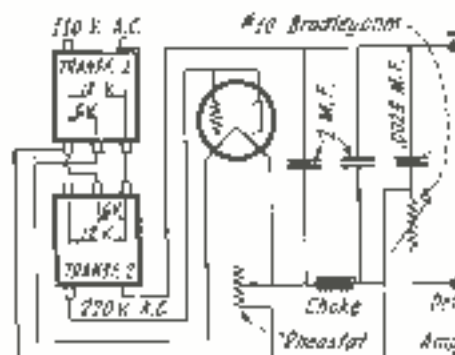



Diagram of connections of the "B" battery eliminator. With this arrangement the 110 volt A.C. can be used in place of the "B" batteries.

be used for a choke coil, but it is better to rewind it with 5,000 turns of either No. 12 or No. 34 B. & S., S.S.C. wire, which will give sufficient chocking effect with a minimum of D.C. resistance so that the drop in voltage is small. The Bradkevohm is used to cut down the voltage to 22½ volts for use in the detector. In checking voltages obtained from the rectifier, only a high resistance voltmeter should be used, otherwise, the reading will be incorrect. The small warch case type should not be used, as it is too low in resistance.

—Contributed by J. R. Deane

A CHEAP AND EFFICIENT INSULATOR

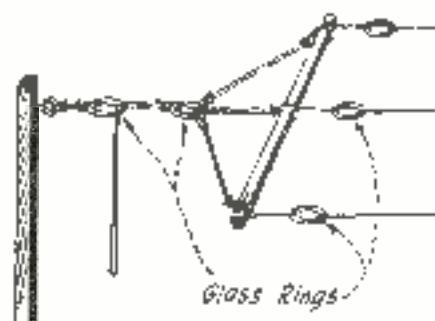Here is a cheap but very efficient antenna pulley or insulator, which I have been using for quite some time with excellent results. It consists of glass rings such as are used on awnings and which can be obtained at



Glass sewing rings make excellent antenna insulators. They are tough and will stand considerable strain.

any hardware store for five cents each. These rings will withstand several hundred pounds direct pull and can be safely used whenever a good insulator is required. The rings make excellent pulleys, as they will not rust or bind and they work very smoothly. Where only a receiving antenna is erected, they will prove extremely satisfactory and if two or three are employed in series they may be used for a low power transmitting antenna.

— *Contributed by Dr. J. L. Parker.*

AN AID TO PANEL MARKING

One of the most important things to be done in building a radio set, as far as looks are concerned, is laying out the panel. A great many schemes have been proposed, such as laying out on paper the proper place for each instrument, pasting this on the panel and then drilling. However, the writer has found by experience that drawing the locations directly upon the panel itself is much easier and more accurate. Here is the trick. Purchase a black waxed crayon such as is used for marking packages, leather, glass, etc.; smear the crayon upon the panel where it is desired to draw a line. Measure exactly where the line is to be drawn and with a ruler and tooth-pick draw the line through the wax. Should it be in the wrong location, it is a simple matter to smear the crayon over it and try again. When drilling is completed, a soft rag will remove the crayon, leaving the panel in perfect condition.

Contributed by Edw. B. Johnson.

THE SIMPLEST SWITCH STOP

In building a receiver in which switches and jacks are used, this little device will be found of value to the constructor. It will not be necessary to drill extra holes.

(Continued on page 1078)

How to Build A Battery Control Panel

By RUDOLPH G. LAWRENCE




A front view of the completed battery charging panel. All the controls and measuring instruments are mounted on the front of the panel.

WITH the larger type radio sets, the wiring problem becomes an important one. When three or four separate sets of batteries are used to supply the power and the various charging agents for the batteries are installed, the usual result is a mess of haphazard wiring making an otherwise efficient layout resemble the junk shop of an experimenter. About the only practical way to bring order into this chaos is the use of a charging panel, such as the one delineated in this article. With its use the necessary for thousands of those wires, voltmeters, ammeters and other measuring instruments lying about the radio table, is obviated.


One of the most distinct advantages to be gained through the construction of such a control device lies in the fact that when the operator has before him, easily accessible, means for measuring the battery charge, the chances are much greater in his giving these power units proper attention than when he must dip down through a pile of his radio instruments in order to obtain the necessary voltmeter. Another distinct advantage of

the same style is that the operator has a constant check on the plate voltage supplied to his set. Immediately it drops below normal, resulting in howls and noises in the set, the voltmeter across the plate makes known the seat of the trouble, and the operator will not have to look through the entire set for the difficulty.

The layout and construction of the panel is very simple, as will be seen from the wiring diagram shown in Fig. 1. The "A" battery circuit is entirely controlled by a D.P.D.T. switch. In the upper position the "A" battery is on charge. In the lower position it is connected to the filaments of the set. The leads from the battery are connected to the center terminals of the switch, the positive one passing through the ammeter. The lower points of the switch

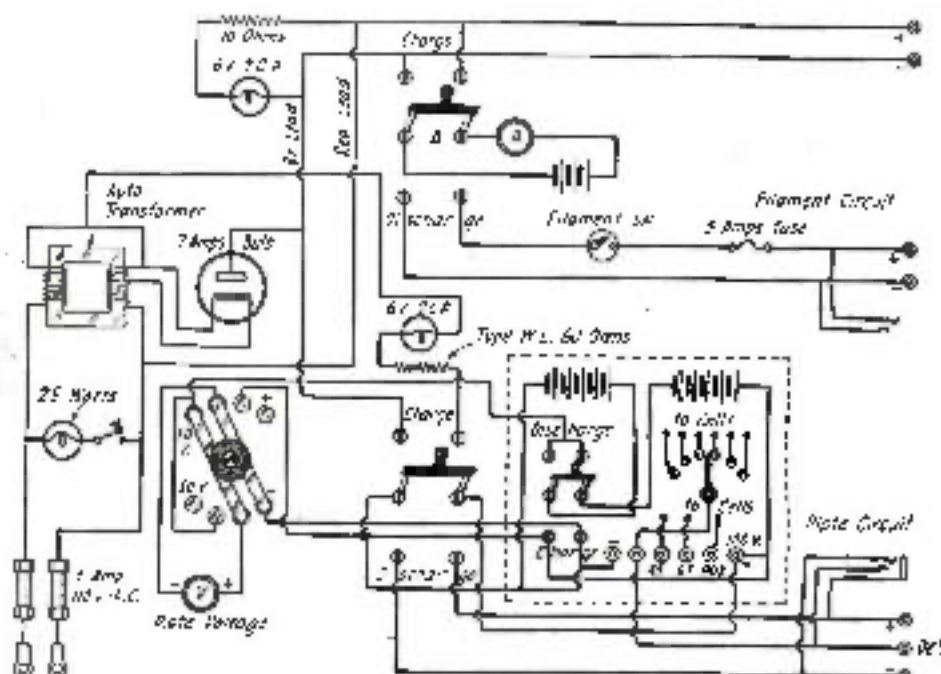

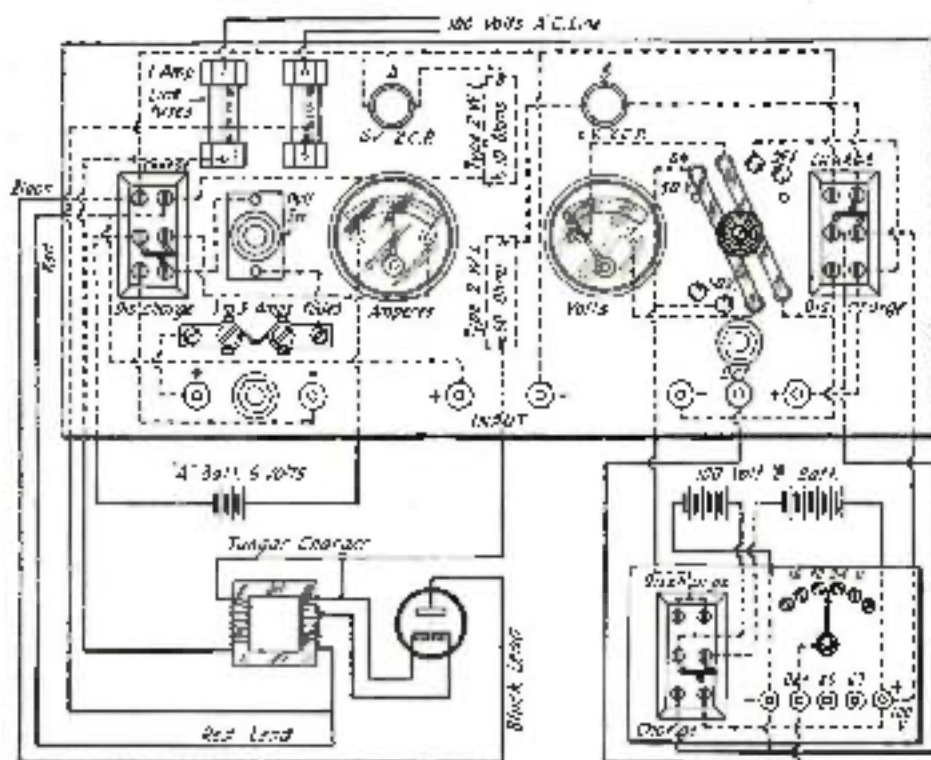Above is the schematic circuit diagram of the battery control unit and below is the working diagram showing all the connections in their proper positions.



connect to a pair of binding posts which, in turn, lead to a filament set. The positive lead to the passes is later united by a filament pull switch. A five ampere fuse is also provided in these output leads for protection of the battery as well as the filaments.

A Tungar charger is used to supply power to the battery from the 110 volt A.C. line. The red and black leads from the charger go directly to the upper terminals of the D.P.D.T. switch, the red lead going to the positive side. Across the charger is placed a 5.5 volt twin C.P. lamp which is used as a monitor serving to indicate when the battery is on charge. It is mounted on a bracket behind the panel and is seen through a hole.

A 10-ohm resistance is put in series with the lamp to decrease the current consumed by it. Two other binding posts are provided for the purpose of charging auxiliary batteries.

The "A" battery Tungar charger is also used to charge the "B" battery, provided the proper connections be made and the correct resistance used. It is understood that the "B" battery used in this device is the storage or re-chargeable type. The battery used is 100 volts, alkaline type, built with Edison

(Continued on page 1082)

Single Control Receivers

One of the latest developments in radio sets is here pictured. Instead of using two separate dials for the two tuning condensers, the condensers are geared by means of fine mesh fibre gears. There is, therefore, only a single control directly attached to the center gear. The system works out surprisingly well in practice and will probably be the forerunner of such simplified sets.

SINGLE control for receiving sets has become a guiding principle with the radio designers during the past year. From time to time new sets having complete control vested in one adjusting dial have made their appearance. The matter was comparatively simple when dealing with the single circuit receiver. But even with the addition of regeneration the problem was complicated. And it has been only quite recently that serious thought has been given to ways and means of incorporating the single control idea in the multistage amplifier set.

With the use of tuned radio frequency amplification constantly increasing, it was obvious that, if the set was to become a popular one with the fans, the controls would have to be simplified. One of the greatest difficulties with tuned radio frequency receivers is the multiplicity of controls.

The latest development along this line is the use of gears for connecting the tuning condensers on the radio frequency amplification stages with the detector circuit condenser and working all of them from a common control.

It is often difficult with such an arrangement to obtain sharp tuning in all the circuits on account of the small differences which are practically unavoidable in the variable condensers and the radio frequency transformers. The system of tuning several stages of radio frequency amplification with a single control is more practical when only one stage of radio frequency amplification is employed in the receiver.

In the set used in the illustration, the arrangement is plainly seen. Advantage is taken of a small vernier condenser to make the final adjustment of the tuning if necessary.

In the assembly of the set the condensers and coils are matched as carefully as possible so that the adjustment of the vernier will be reduced to a minimum.


Still another simplification has been used in the adoption of a somewhat new principle of damping in the radio frequency stage. Until the advent of this new principle, it was necessary to rely upon the neutralization of the internal capacity of the tube by the use of the Neutrodyne principle or

through the addition of another control in the form of a potentiometer. Otherwise, the tendency of the tube used in this position to oscillate could not be controlled. It was, of course, necessary to give the grid a negative bias in order to get the greatest efficiency from it, and in doing so, it was brought near the point of oscillation necessitating some sort of oscillation control.

In the present set, the filament resistance of the tube is incorporated in the grid circuit. The addition of this resistance allows the tube to be operated at the proper point for greatest efficiency and at the same time introduces just enough damping to prevent the unwanted oscillations.

Experiment has shown that a set can be so built as to obviate the use of a separate adjustable rheostat for each tube. The addition of the automatic filament resistances, amperes, cares for the necessary adjustment without being hand operated. The set used for the illustrations employs such device for each tube. The set consists of one stage of tuned radio frequency amplification, detector and two stages of audio frequency amplification. On the front panel a large dial in the center does the bulk of the tuning. After the station has been brought in, final tuning for clarity and volume is made with a small vernier knob under the larger one. The only other instrument on the panel is the filament switch.

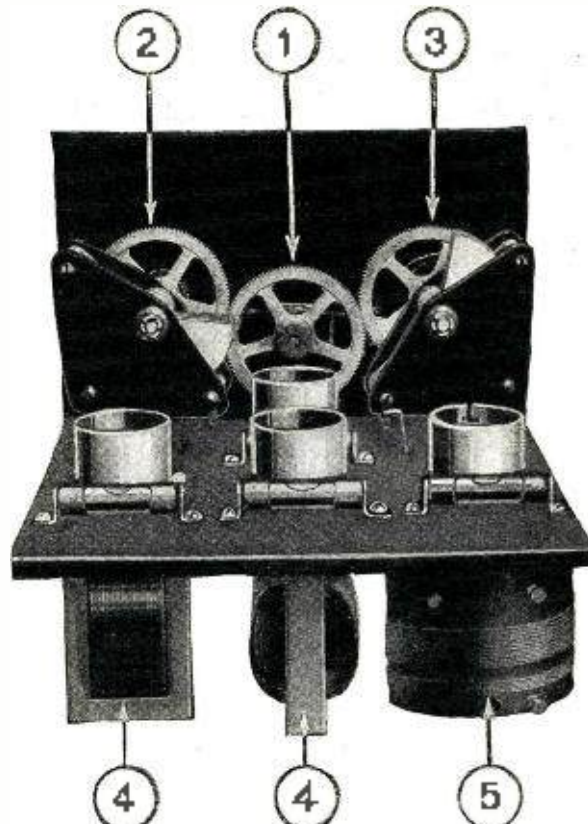A word might be said regarding the complete set. It is self contained. The actual tuning instruments, tubes, etc., are contained in the center portion of the cabinet behind the panel. At the left is the mouth of the loud speaker, also contained in the cabinet. The left side of the cabinet is reserved for



Inside view of a single control radio frequency receiver. The main gear, No. 1, turns the two variable condensers No. 2 and No. 3 simultaneously. Below the sub-panel the radio frequency transformers No. 4 and tuning coil No. 5 may be seen. Photo by courtesy of National Aircraft Corp.


batteries. There is ample space for a 50-ampere hour storage battery and two 45-volt "B" battery units.

Altogether, a design of this type is the forerunner of the chief developments to be made in the commercial broadcast receivers to be brought out during the coming year. Simplicity is the pass-word.

NATIONAL BROADCASTING NETS

Very soon now the radio public, even the crystal listeners, in New York, Washington, Cincinnati and possibly also in Pittsburgh, Hastings and Oakland, may get more long-distance radio programs. The Radio Corporation has a wire line connecting its New York broadcasters, WJZ and WJY with WGY in Schenectady, and a line strung between New York and WRC at Washington ready for use. The Corporation is planning to extend its inter-connections by both wires and radio retransmission to include several radio stations, which will of course compete with the big circuit of the American Telephone & Telegraph Co.

In confirmation of Secretary Hoover's prophecy that interconnection through the interconnection of high-power broadcasters was the greatest development in broadcasting, the Bell System and the Radio Corporation are extending their broadcasting nets. On Defense Day, 19 stations were connected by telephone, the greatest number ever hooked up, and, as radio fans from coast to coast know, it worked excellently.

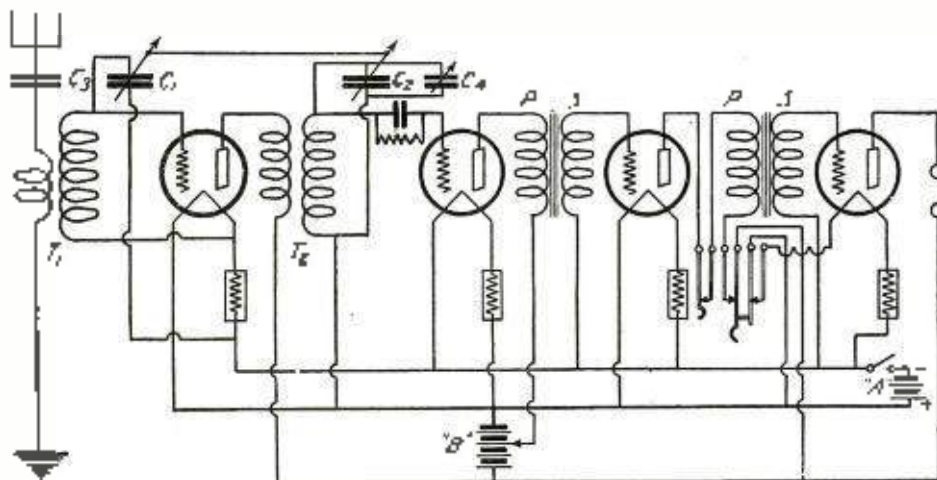

Circuit of the single control receiver. Note that the two variable condensers C1 and C2 are moved simultaneously. C4 is a small vernier condenser.

Radiotics

HARNESS YOURSELF TO A RADIO WAVE



The July 26, 1924, issue of the *Radio Digest* carried an advertisement of "HARNESS REFLEX KITS." We know the average reflex set required some sort of harnessing, but never knew how to go about it. Supposedly one need not worry about this any more. Contributed by H. Ward Camp.

A PYRADIONMANIAC!

The *Washington Herald* informs us in a news item that a "six tube radio set operated at No. 1621 K St. N. W., IGNITED BED CLOTHING LAST NIGHT." Must have picked up some hot stuff from a nearby broadcast station. But these big sets will hear watching. Never can tell what they will do next.

Contributed by Solomon Fishman.

A WILD ONE, THIS



The *North Carolina State College Alumni News* relates the story of a "210 Pliotron couple in cascade by resistance and CAPTIVITY." Guess they put it behind bars to keep it from oscillating all over the place, and possibly to keep it from igniting bed clothing! It had 2000 volts on the plate. That's a bad symptom. Contributed by Robert S. Morris.

NO MORE "B" BATTERIES

The See Jay Battery Company blare forth in the August 10, 1924, edition of the *New York Herald-Tribune* with an advertisement of "100 VOLT MAHOGANY CABINETS." Now that's a right fine idea. Helps to make a set portable but a rubber insulating covering would be necessary if you are to carry it. This is the original "Kabinet with a Kick." Contributed by Martin Frankel.



ALL SET FOR THE WINTER



The *Detroit Argus* of Sept. 12, 1924, carries the advertisement of the Calfan Radio Company in which they announce something new under the sun, namely an "A-cme FUR-TURE Reflex Kit!" No winter blast will be able to give your vacuum tubes the oscillating shivers when donned with these "Cats Overcoats." Contributed by Edward Abard.

WHAT DO YOU GET?



The Solomon Brothers in the *Los Angeles Examiner* carried the following advertisement: Crosley 3-tube sets WITHOUT PARTS \$30. This, no doubt, is the new Crosley Model 400 set with etherial instruments and everything. It would seem that this set would present a serious problem in tuning to the average radio fan. Contributed by D. J. Jves.

HOLD 'EM BACK!

In the June issue of *QST* there is a Ham ad. reading: "For Sale—One ten watt C.W. transmitter complete with power transformer and everything except tubes. 50c!" I bet the rush for that set would put a silk stocking sale on a Saturday afternoon in the shade. Must have been some straw hats broken in the stampede.

Contributed by Harry Wauderfish.



If you happen to see any humorous misprints in the press, we will be glad to have you clip them and send to us. No **RADIO TIC** will be accepted unless the printed original giving the name of the newspaper or magazine is submitted. We will pay \$1.00 for each **RADIO TIC** accepted and printed here. A few humorous lines from each correspondent should accompany each **RADIO TIC**. The most humorous ones will be printed. Address all **RADIO TIC**s to:

Editor **RADIO TIC** DEPARTMENT,
c/o *Radio News*

A CHUNK OF THE WESTERN UNION THROWN IN

The following ad appeared in the *Boston Globe*, August 10, 1924: "A Radio Tube Set for \$12: this includes the tube in a circuit of 1,500 miles!" Now, there wasn't anything wireless about that set, it must have included a chunk of the Western Union Lines. What will they give away next?

Contributed by John F. Condon.



A NEW RADIO INSTRUMENT



In the *Boston Post* of August 29, 1924, is advertised: "U. S. Tool V E R N I E R BENCHES." Just the thing for the set showing symptoms of body capacity. Tune in the desired station and make the final adjustment for volume and clarity on the bench. More power to the U. S. Tool Company! Contributed by Remond H. Hays.

MOTHERS, JUST THE THING!



The *Radio Specialty Company* carried a classified advertisement in the August issue of *Radio News* reading as follows: "Boys! Don't overlook this. The **RADIO BABY DETECTOR**." I think we all feel that this is just the thing for Mother who has stopped long enough for little brother to get out of sight. Kidnappers had better be careful after this. The **Baby Detector** is infallible. Contributed by John D. Duffin.

A SHANGHAI CREATION

The *Oakland Tribune* of August 17, 1924, carried the advertisement of the Offenbach Electric Company in which we find listed "Variometer, WITH PIGTAIL, \$1.95." Is it that Mah Jongg is having such an effect on the design of radio apparatus that they have to put a pigtail on a variometer? An Oriental atmosphere is quite the thing, but why stretch the fad to include radio?

Contributed by Nathan H. Szwed.



THE GOLEM



One John R. Meagher in his article "Make Your Own Power Unit" in the *Radio Section* of the *New York Sun*, July 26, 1924, speaks of "A battery charger as 'usually of FORGOTTABLE proportions.'" Now possibly they are, to the terrified who, for the first time, connects me up to his storage battery and hopes it will "charge" or something, but we are more inclined to believe that someone has been having nightmares.

Contributed by Paul F. Hirt.

FOR THE PORTABLE SUPER-HETERODYNE

Sears, Roebuck & Co. in their advertisement of WD-12 and C-12 vacuum tubes state that they have "standard 4-POUND BASE." Sure, and this is a weighty argument in favor of the tube. The advantage is, if you drop one, it won't land buttered-side down.

Contributed by Paul K. Whitaker.



LET US IN ON THE SECRET

In the advertisement of the National Radio Institute in the August, 1924, issue of *Radio News*, is a letter in which is stated: "I had a first-class outfit WITH A WAVE-LENGTH CAPABLE OF 'PICKING UP' THE PROGRAMS FROM INSTANT STATIONS." He must have trained that wave-length to go out and bring back the goods. Not knowing how much programs weigh we do not know whether this is a feat of strength or not, but anyway, it's a good stunt.

Contributed by E. A. Morrison.



STANDARD HOOK-UPS


EVERY month we present here standard hook-ups which the Editors have tried out and which are known to give excellent results. This leaf has perforation marks on the left-hand margin and can be cut from the magazine and kept for further reference. These sheets can also be produced from us at the cost of 5c to pay for mailing charges.

RADIO NEWS has also prepared a handsome heavy cardboard binder into which these sheets may be fastened. This binder will be sent to any address, prepaid on receipt of 20c. In time there will be enough sheets to make a good-sized volume containing all important hook-ups. Every year an alphabetical index will be published summarizing and classifying the various hook-ups.

Handy Reference Data for the Experimenter

Circuit No. 63. In this diagram we have a circuit of a two stage audio frequency amplifier which may be added to any standard one tube receiver. Audio frequency transformers are used and a ratio of one higher than five to one is advised. One single circuit and two double circuit jacks are employed, thus allowing either detector, first or second stage of audio frequency to be used. The output of the detector tube is connected directly to the two input binding posts on the amplifier. A fixed condenser C is shown shunted across the primary of the first transformer. This condenser is of low capacity, approximately 0.0025 mfd., and is employed to compensate for the loss of capacity of the phone coils when the phones are removed from the detector circuit. If this condenser is of the right size, there will be no need of retuning when the change is made from the detector to the first stage. The same "A" and "B" batteries are employed for both detector and amplifier.

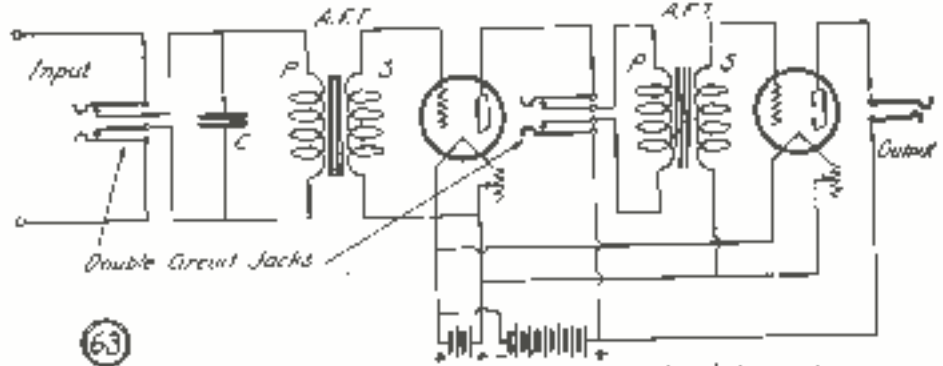All that is necessary is to connect the positive and the negative filament binding posts of the detector to the respective terminals of the "A" battery and take a tap off at 22½ or 45 volts on the "B" battery and connect it to the plus "B" battery post




Circuit diagram of a two stage audio frequency amplifier with telephone jacks

and the circuit shown will be free from this trouble. As a resistance coupled amplifier does not give as much volume as one using transformers, three stages will be required instead of two. The resistances R should be approximately 50,000 to 70,000 ohms. Grid condensers C are employed in the grid circuits and should be of fairly high capacity, approximately ½ mfd. These condensers must be employed so that the plate volt-

age is not applied to the grid of the tubes. The resistances shown as R_1 are ordinary grid leaks of approximately ½ megohm resistance. Best results will be obtained with a rather high "B" battery voltage and 120 to 150 volts are recommended.

It is necessary, no matter the type of tube employed, that a high "B" voltage be employed, as there is a considerable drop of potential across the resistances, thus making the effective plate voltage a good deal lower than the actual voltage of the "B" battery. This circuit is shown to be used in conjunction with any standard receiving circuit and is arranged so that the "A" and "B" batteries are common to both. The return circuit to the filament of the first resistance R is completed through the receiver in use.

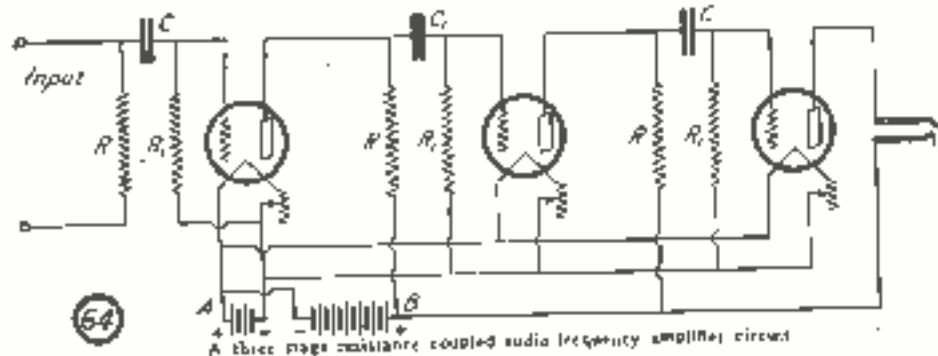

A three stage resistance coupled audio frequency amplifier circuit

of the detector on the receiver. No wire need be connected to the minus "B" battery binding post on the receiver as the negative circuit of the "B" battery is completed to the "A" battery in the audio frequency amplifier.

The type of tube to be employed in this audio frequency amplifier circuit is a matter of preference. If WD-11, WD-12 or 1V-199 tubes are used, employ a 1½ volt "A" battery for the first two types and a 4½ volt "A" battery and 25 to 30 ohm rheostats for the last mentioned type. "B" voltages from 45 to 60 can be safely utilized. If 1V-201A or Western Electric 8 tubes are used, a six volt "A" battery will be required, and 25 ohm rheostats if one of the first two mentioned types of tubes are employed. "B" voltages from 45 to 100 may be used.


Circuit No. 64. Where an audio frequency amplifier is desired, which will give very little distortion, three stages of resistance coupled amplification are recommended. Distortion is always present when audio frequency transformers are employed.

age is not applied to the grid of the tubes. The resistances shown as R_1 are ordinary grid leaks of approximately ½ megohm resistance. Best results will be obtained with a rather high "B" battery voltage and 120 to 150 volts are recommended.


It is necessary, no matter the type of tube employed, that a high "B" voltage be employed, as there is a considerable drop of potential across the resistances, thus making the effective plate voltage a good deal lower than the actual voltage of the "B" battery.

Circuit No. 65. Here is a three stage audio frequency amplifier combining an audio frequency transformer and resistance coupled amplification. The audio frequency transformer is employed in the first stage and a double circuit jack is also used after the first amplifying tube so that the phones may be plugged in at this position. The grid condensers in the grid circuits of the last two tubes are of ½ mfd. capacity and the resistances R are approximately 50,000 ohms. The grid leaks shown as R_1 are of ½ megohm resistance and are connected directly to the negative of the "A" battery. One rheostat of 10 ohms shown as R_2 is employed to light the filaments of the last two tubes. The same "B" battery voltage may be employed for all three stages, but it is recommended that the last two tubes have a much higher voltage than the first. The amplifier may be employed with any standard one tube circuit and will give exceptionally good results.

The combination is exceedingly good.

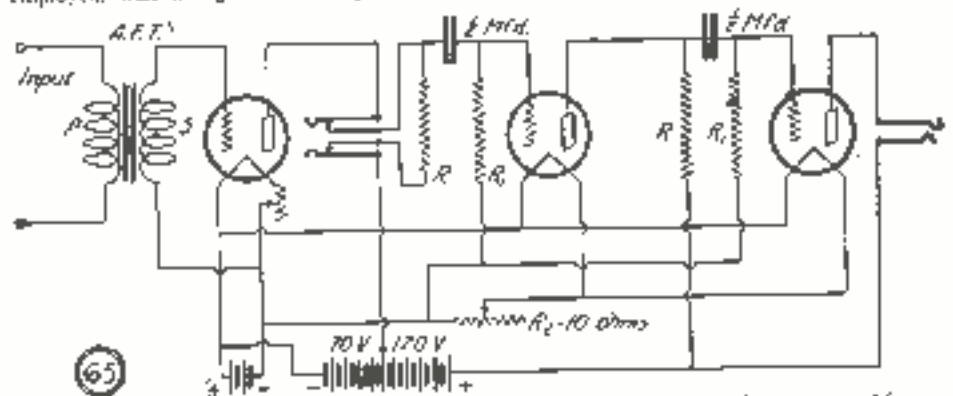


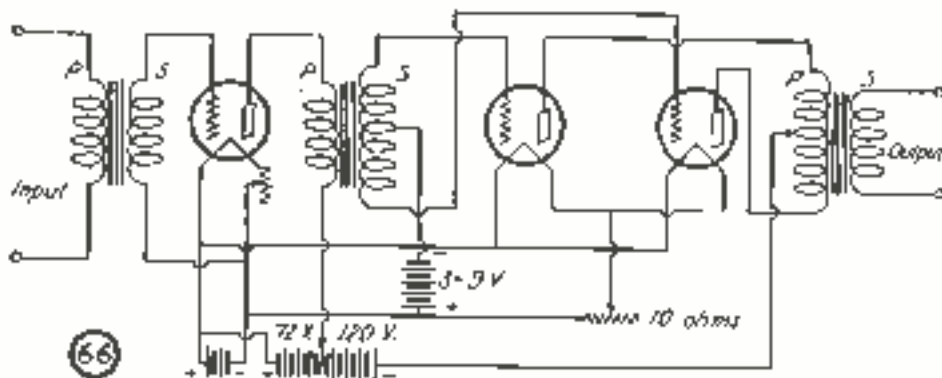A single stage transformer coupled and two stage resistance coupled audio frequency amplifier circuit.



A two stage audio frequency amplifier circuit the first stage being a push-pull amplifier.


Circuit No. 66. Here we have a two stage audio frequency amplifier using the push-pull method of amplification. In a circuit of this kind three tubes are employed for two stages of amplification. It will be seen that special transformers are employed for the last two tubes. The secondary of the first transformer has its two opposite terminals connected to the grids of the tubes and the primary of the last transformer has its two end terminals connected to the plates of the tubes. These two windings have center taps which are connected to the negative filament and positive "B" battery respectively. It will be readily seen that while one end of the winding is negative, the other end will be positive and a continuous action will thereby be had which will eliminate to a great degree the distortion which is prevalent in the standard amplifier. This type of amplifier will also give greater volume on most stations received. Push-pull transformers are obtainable on the market, they being manufactured by a number of companies and sold in sets of two.

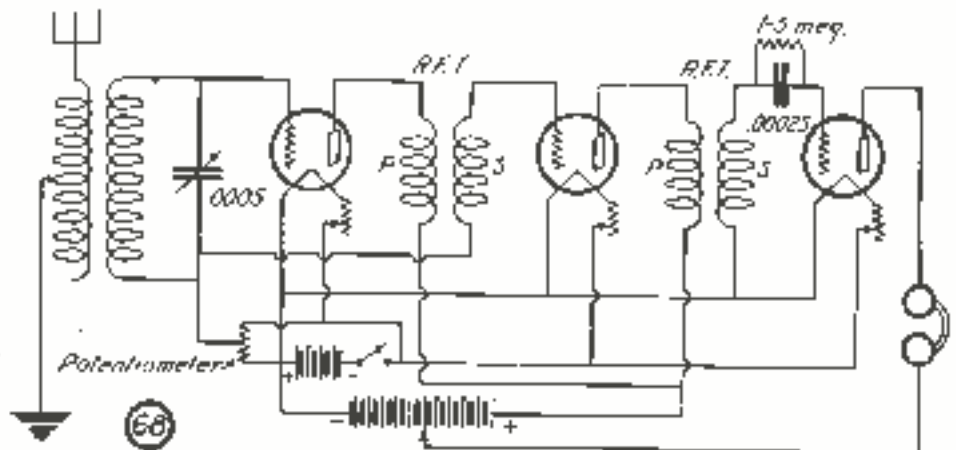

Receiving circuit employing two stages of untuned transformer radio frequency amplification.


When a high voltage is used on the plates, as it cuts down the current consumption and helps toward the elimination of distortion.

Circuit No. 69. Here we have a circuit combining one stage of radio frequency with regeneration in the detector circuit. As one stage of audio frequency is also used, a loud speaker may be employed on practically all stations received. The antenna tuner consists of an untuned primary coupler without the rotor. The radio frequency transformer is an ordinary untuned primary coupler, like that described in circuit No. 29 of the August issue. The primary of this coupler must be wound with large wire, of not more than 10 turns. The secondaries of both couplers are shunted by variable condensers of .0005 mfd. capacity for tuning. Both condensers must be varied at the same time, as both secondary circuits must be in resonance before any station can be picked up. No potentiometer is necessary in this receiver, the grid return of the first tube being connected directly to the negative of the "A" battery. Properly handled, a circuit of this kind will be equivalent to one having two stages of radio frequency amplification and long distance stations will be easily picked up.

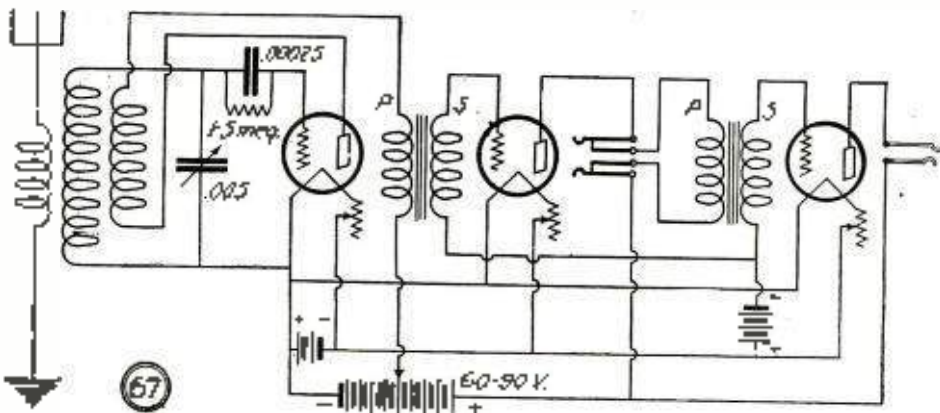

A regenerative receiving circuit and two stage audio frequency amplifier.

Circuit No. 67. Here is shown a regenerative receiver in conjunction with two stages of audio frequency amplification. The tuner in this receiver is an untuned primary coupler and was described in circuit No. 29 in the August issue. Audio frequency transformers are used in the amplifier and should not have a ratio higher than 5:1. A double circuit jack is inserted after the first stage so that the phones may be plugged in at this point. When the loud speaker is used, it is plugged into the single circuit jack after the last stage. If a good antenna is used with this receiver, fair volume will be obtained on the loud speaker on the first stage when local stations are received. The grid returns of the two amplifying tubes are connected together and run to the negative terminal of a "C" battery which will have a voltage of from three to nine volts, depending upon the voltage of the "B" battery. This "C" battery has its positive terminal connected to the negative of the "A" battery. A "C" battery is necessary

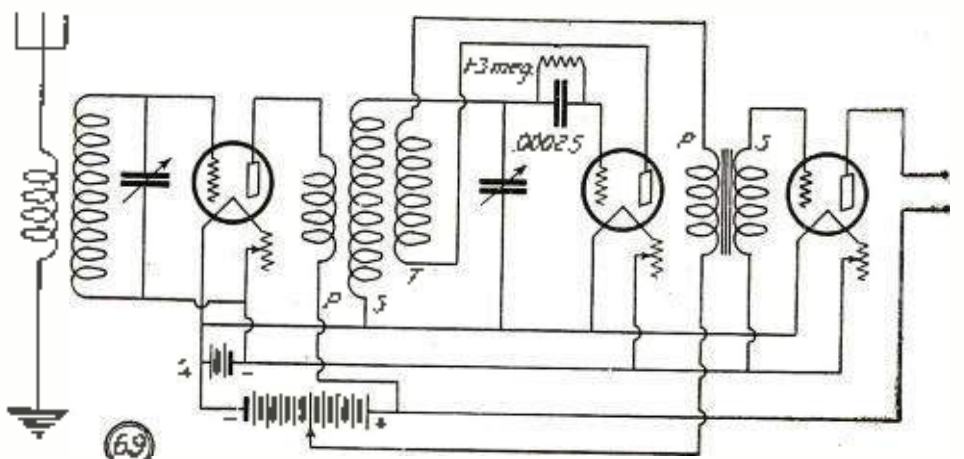

One stage of R. F., one stage of A. P. and regeneration in the detector circuit.

Correspondence from Readers

THE MARS RADIO CHECKUP

Editor, RADIO NEWS:

Your readers may be interested in knowing that important discoveries may result from the assistance given by the use of radio in the "Mars Checkup" conducted by a committee headed by Professor David Todd, the noted astronomer-physicist, under the auspices of the Aerial League of America.

Those of your readers who have records of the radio audibility covering one or more days between July 24 and September 24, 1924, can aid the Committee in ascertaining whether or not Mars' magnetism, or other factors, were responsible for the electromagnetic phenomena registered when Mars was close to the earth.

This Mars Radio Checkup may give the world more knowledge about the "ruddy" planet than has been obtained by astronomic study since Aristotle made his first observation of Mars 356 years before our era, or 2280 years ago.

All that Professor Todd needs from radio fans is a record of the radio strength at the time they listened to whatever happened to be on the air, with the approximate time when it was strong or faint. Reports covering a day or longer will be most helpful, but those covering an hour in a day will have value.

These reports should be addressed to Professor David Todd, Chairman of the Mars Checkup, Aerial League of America, 280 Madison Avenue, New York City.

This information will be tabulated and compared with similar tabulations of the magnetic variations registered for the same period of time, and data from astronomic observations of Mars and other data, and it is expected that the results will make it possible to ascertain whether Mars and other planets affect the earth's conductive media and aid or interfere with our radio communication.

The Aerial League of America had asked Professor Todd to ascertain, if possible, by a world-wide checkup, using radio astronomical and magnetic instruments:

(1) Whether the mysterious flashes on the surface of Mars heretofore registered by astronomers are likely to be huge curtains of auroral light, from 300 to 500 miles deep, similar to the auroral displays that are registered in the Arctic and Antarctic regions of the earth, and caused by electro-magnetic discharges from the sun striking the planet's most intensive magnetic fields in the magnetic polar regions.

(2) Whether any electromagnetic disturbances took place on the earth within three minutes of the auroral flashes appearing on Mars, and whether these disturbances correspond in time sufficiently to justify a belief that there is an interplanetary electromagnetic effect playing upon the two planets at the speed of light, above 186,000 miles per second.

(3) Whether it is justifiable to hold that Mars has north and south magnetic poles and a magnetic equator the same as the earth, and whether they are sufficiently powerful as magnets for the earth to be affected as they present to each other intermittently their positive and negative poles in their daily rotation, as well as in their motion along their celestial orbits, and other motions.

(4) Whether the earth is as sensitive to the nearness of other magnetic bodies as all magnetic bodies are, and as compasses are sensitive to the changes of direction of terrestrial magnetism and whether radio reception is affected by the variations in the direction of the earth's magnetism, and whether it is affected by the disturbances created by auroral displays.

(5) Whether through the above or other phenomena the earth's conductive media for radio communication is aided or interfered with by the nearness or position of other planets, or other phenomena yet undefined, acting upon the earth's radio conductive media as auroral displays have been shown to do by the data already secured in the 12-month Aurora Checkup started by the League a few months ago.

Scientists are placing great reliance on the results to be obtained by the radio checkup.

HENRY WOODHOUSE, President,
The Aerial League of America.

ABOUT THE "SIX TUBE RECEIVER OF ADVANCED DESIGN"

Editor, RADIO NEWS:

I wrote you September 3 in regard to first night's DX on your "Six Tube Receiver of Advanced Design" described in the September issue, and requested a little information

40 Non-Technical Radio Articles

every month for the beginner, the layman and those who like radio from the non-technical side.

SCIENCE & INVENTION, which can be bought at any newsstand, contains the largest and most interesting section of radio articles of any non-radio magazine in existence.

Many of "How To Make It" radio articles and plenty of straightened hook-ups for the layman and experimenter. The radio section of SCIENCE & INVENTION is so good that many RADIO NEWS readers buy it solely for this feature.

List of Radio Articles Appearing in the December Issue of "Science and Invention"

Night Versus Day Radio Transmission
Over 1,000 Miles.
Latest Radio News in Pictures.
Radio Lighthouse—New British Invention.
Broadcasting Station Cuts Up to Date.
Newest Solenoid Circuits.
Neutralizing Methods, Part 2, by L. Adelman.
Radio Oracle—Questions and Answers.

regarding best aerial to use. Tried it out on an aerial using "Radio in the House" formula but it did not balance. So I am still using it with a small variable condenser in the aerial circuit.

Would say that the set has brought in California stations 11 different nights, including KPO, KFI, KFJ and KGO; this was practically every time KGO had operated. Several nights with WSAI on the air. KGO was brought in perfectly, and I shifted from KGO to WSAI with the vernier of the second condenser throughout the evening. On September 1, WSAI seemed to have moved over to KGO's wave and I was unable to tune either clearly; however, with the setting on WSAI I immediately picked up KGO when WSAI shut down, and shortly after got that station on the speaker, when I heard a talk by the Superintendent of Schools of Oakland, followed by Joseph Henry Jackson literary editor, with an eulogy on Wallace Lwin. During this broadcast I used a UV-199 tube in the R.F. circuit with about 31 volts on the plate of the R.F. tube, and with careful tuning seemed to advance the tickler to a higher point without spilling, actually bringing KGO in with the clearness of an eastern station. WFAA, Dallas, Texas and Fort Worth were nearly as good earlier in the

evening. Seventy stations were logged in one night's test recently. However, picking up the Pacific Coast 11 times in 12 tries, between September 2 and September 15 inclusive, proves the set is exceptionally good on DX, the one failure being caused by heavy static. I will experiment further on this with English stations as soon as the evenings become longer.

B. H. TAYLOR,
Haverhill, Mass.

NOT A BAD IDEA

Editor, RADIO NEWS:

I suggest the following plan to get more applause cards:

(1) Radio Listener has on his table a pencil and a few dozen pieces of paper about two inches square. He listens to a program, likes it, and then writes on one of the slips something as follows:

To WNAC.

Ukulele concert great.

John Doe.

Bank Street.

Boston, Mass.

(2) Once or twice a week he collects the slips, puts them all in one envelope with a two-cent stamp and sends them to the local broadcast station.

(3) Local station assigns slips from the various senders, in piles, each one containing slip sent to a specific station.

(4) One to seven times a week, depending on number, local station sends slips for a specific station to them, putting them in one envelope with needed postage.

Thus the individual BCL sends large number of applause cards at lowest possible expense, and the broadcasters, by mutual co-operation, will get lots of "applause."

H. FLAGMAN,
37 Schuyler Street,
Boston, Mass.

NEUTRODYNE VS REGENERATIVE SET

Editor, RADIO NEWS:

Upon reading an article in RADIO NEWS, written by A. L. Groves, in regard to the Neutrodyne receiver, I discovered what appeared to me to be an inaccurate statement of the results usually obtained from such a receiver as compared to a good regenerative set, and wish to give my experience as well as observation of the two receivers. The statement I refer to is contained in paragraph five of the article where Mr. Groves in substance says that the Neutrodyne is the equal of a regenerator only on strong signals and that the regenerative set will pick up weak signals that will not be audible on a Neutrodyne. To a person who has used both receivers the statement needs no correction, but for those unfamiliar with the results of the Neutrodyne it does.

Facts upon which I base the statement that the Neutrodyne gives louder results on the same signal than a good regenerator follow: I travel over the State of Texas, a place far removed from the principal broadcast stations and where you must have a good receiver to get loud speaker results. For the past two years I have taken particular notice of radio receivers that were used throughout the state, in such places as drug stores, electric shops and radio stores. At most of those places during the early part of last winter a set put out by the Radio Corporation and known as the "RC" was used, a single circuit receiver, a regenerative and a set that gave good results. Always in connection with this three tube receiver you would find some type of power amplifier, either one or two stages. I also found in use other types of receivers such as Ken-

(Continued on page 1008)



RADIO NEWS LABORATORIES



RADIO manufacturers are invited to send to RADIO NEWS LABORATORIES, samples of their products for test. It does not matter whether or not they advertise in RADIO NEWS, the RADIO NEWS LABORATORIES being an independent organization, with the improvement of radio apparatus as its aim. If, after being tested, the instruments submitted prove to be built according to modern radio engineering practice, they will each be awarded a certificate of merit, and a "write-up" such as those given below will appear in this department of RADIO NEWS. If the apparatus does not pass the Laboratories tests, it will be returned to the manufacturers with suggestions for improvements. No "write-ups" sent by manufacturers are published on these pages, and only apparatus which has been tested by the Laboratories and found to be of good mechanical and electrical construction is described. Inasmuch as the service of the RADIO NEWS LABORATORIES is free to all manufacturers whether they are advertisers or not, it is necessary that all goods to be tested be forwarded prepaid, otherwise they cannot be accepted by the Laboratories. Address all communications and all parcels to RADIO NEWS LABORATORIES, 31 Park Place, New York City.

Apparatus Awarded Certificates

GEN-WIN LOW LOSS TUNER

Selectivity in a receiving set is obtained only by the use of low loss instruments in the radio frequency circuits. This is especially true of variable condensers and tuning coils. Insulating material causes losses, and as high insulating material as possible should be used in the construction of the instrument. The Gen-Win tuner employs a stagger sound secondary,



spider-web vibrator and a bare wire when paired primary outside of the secondary. Three small clamps of insulating material are used for supporting the instrument as the illustration shows. It covers a range of 150 to 150 meters when used with a .0005 mfd. variable condenser. Manufactured by the General Radio Winding Co., 214 Fulton Street, New York City.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 543

FALL MALL VARIOCOUPLES

The Evans Manufacturing Co., 117 Mulberry Street, Newark, N. J., submitted a sample of their improved Fall Mall 330-degree variocoupler. This coupler employs two windings, primary and secondary. The primary winding is provided with eight taps. On the last tap



it covers a range of 320 to 1,000 meters when used with a .0005 mfd. variable condenser. The instrument is small in size and may be conveniently mounted in a set. Either single or double circuit may be used.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

DERESNADYNE RECEIVER

This is a five tube receiver of excellent electrical and mechanical construction. It consists of two stages of tuned radio frequency amplification, detector, and two stages of audio amplification. Low loss variable condensers and spider-web variocouplers are used in the radio frequency amplifier. It is a non-neutralized receiver, but a variable

resistance of about 200,000 ohms maximum is connected in the plate circuit of the radio frequency tubes for stabilizing the circuit. This



gives a very fine degree of control and the frequency of the receiver is thereby increased considerably. A switch is provided for changing to the first stage, second stage or off positions. Manufactured by the Andrews Radio Co., 327 South La Salle Street, Chicago, Ill.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 576

HARMONEX TRANSFORMER

The Harmonex All-Wave Radio Frequency Transformer manufactured by the

Katzen Electric Co., 4140 North Rockwell Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

BRUNO TUNER

The Bruno Tuner, manufactured by the Bruno Radio Corporation, 1111 North Dearborn Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Bruno Tuner, manufactured by the Bruno Radio Corporation, 1111 North Dearborn Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Bruno Tuner, manufactured by the Bruno Radio Corporation, 1111 North Dearborn Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Bruno Tuner, manufactured by the Bruno Radio Corporation, 1111 North Dearborn Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Bruno Tuner, manufactured by the Bruno Radio Corporation, 1111 North Dearborn Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

data were noted on a separate sheet. The instrument is very neat in appearance and of rugged mechanical construction. When used with a .0005 mfd. variable condenser it covers a wavelength range of 175 to 560 meters. Excellent results were obtained with this tuner when used in a three tube receiver. It is manufactured by the Bruno Radio Corporation, 102 West Scrabble, New York City.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 561



AIR CORE TRANSFORMERS

When submitted by a .0005 mfd. variable condenser, this transformer covers a wavelength range of 120 to 625 meters. This transformer is of brass construction and the primary is wound on a cardboard core over a secondary. The transformer is equipped with an angle bracket for mounting. Three of these transformers will make an excellent two stage tuned radio frequency receiver. Manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Air Core Transformer, manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Air Core Transformer, manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Air Core Transformer, manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Air Core Transformer, manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Air Core Transformer, manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 569

The Air Core Transformer, manufactured by the General Manufacturing Co., 7614 South State Street, Chicago, Ill., is of brass construction and operates with minimum efficiency over practically the entire audio frequency range. The voltage transformation ratio is exceptionally high and extends far into the lower frequencies. As a voltage amplification of from four to ten and current of from one to two is obtained. The instrument is constructed very like a transformer and the quality of the reproduction is exceptional. The transformer is entirely protected and shielded by a metal casing.

ally designed for use in multi-tube receiving sets where there is



a load drawn from the "B" battery. The normal rating of this battery is from 15 to 20 milliamperes. Those who have multi-tube receivers will find a rugged battery of this type less expensive in the long run than smaller batteries. As shown in the illustration this battery is provided with a 210 volt tap. Manufactured by the National Carbon Co., Inc., Thompson Ave. and Oregon St., Long Island City.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 575

SHEPCO COUPLER

The illustration shows the Shepco All-Wave Junior DX coupler. This instrument comprises a loop and link wound B-4400 and a rotary



secondary. The primary is wound with a number of taps so as to cover a wide wavelength range. The construction of the coupler is very simple and it responds with efficiency throughout the entire range. Manufactured by the Shepco and Foster Co., Inc., Plainfield, N. J.

Awarded in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 566

GOODRICH RADIO PANEL

The Goodrich radio panels are made in high quality black and mahogany hard rubber. These panels are very attractive and are easily maintained. A minimum amount of sulphur is used in the material so that it does not turn green with age. Some cheaper grades of hard rubber usually do. The material was tested for losses at a frequency of 1,000 cycles and a phase difference angle of 2 degrees. 11 minutes was obtained. This small phase difference angle indicates that the material is one of the best available for radio use. Manufactured by the Goodrich Rubber Co., Akron, Ohio.



BRUNO TUNER

This tuner comprises primary, secondary and output windings of



EVEREADY "B" BATTERY

The Eveready No. 270 heavy duty 15 volt "B" battery is espe-

lured by the D. F. Goodrich Rubber Co., Akron, Ohio.
Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 373.

GOODRICH HARD RUBBER TUBES

As hard rubber is one of the best insulating materials for use in the construction of audio instruments, it is of course advisable to use hard rubber tubing for supporting radio coils. The D. F. Goodrich Rubber Co., Akron, Ohio, recently placed on the market suitable hard rubber tubes for this purpose. Although the tubes have only a 1/16-inch wall, they are strong enough for the usual windings.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 374.

DAVENPORT LOW LOSS TUNER

The Davenport low loss tuner comprises three stagger wound coils, consisting of primary, secondary and tickler. This tuner is manufactured by the Davenport Radio Laboratories, 44 Cedar Street, Davenport Iowa. As shown in the illustration, very little insulating material is used for supporting the windings. The coupling be-



tween the primary and secondary, and between tickler and secondary is variable. This allows a maximum selectivity. This instrument covers a wavelength range of 135 to 600 meters when used with a 5000 volt. variable condenser.

Arrived in fine packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 358.

RADIO FREQUENCY TRANSFORMER

A wavelength range of 210 to 575 meters is easily covered with this fixed radio frequency transformer, provided a good low loss tuner is used in the grid circuit of the first tube. When so used, the circuit oscillates freely throughout the above range and the oscillations




are easily controlled by a suitable potentiometer. The transformer is small in size and easily mounted. It is manufactured by the Uttergrill Electric and Manufacturing Co., 1108 National Bank Building, Pittsburgh, Pa.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 557.

SHEPCO SINGLE TUBE RECEIVER

This receiver is furnished all assembled with leads brought to a row of binding posts in the top of the panel and separate tube connections supplied, so that the experimenter may connect it up and use any circuit he desires. The directions furnished with the receiver show several circuits that may be used. The receiver consists of a Shepcos amplifier, variable condenser, vacuum tube socket and the necessary accessories. A tap switch is provided for changing the wave-

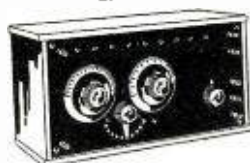length range which may be covered. On the last tap a range of 500 to 1,000 meters is obtained. Manufactured by the Shepcos Radio Co., Inc., Macleburg, N. Y.



Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 561.

LEGO FIXED DETECTOR

The Lego fixed crystal detector is enclosed in a glass tube fitted with metal end caps and binding posts. The detector is small in size and can easily be connected in any part



of the receiver. This detector is very good for reflex receivers and works well in the ordinary crystal set. The large samples submitted by the Lego Corporation, 607 West 42nd Street, New York City, were all very sensitive and uniform. As regards speed of use, the resistance of this detector is about four times as great with the current passing through one direction as the other. **AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 354.**

RADIO CRYSTAL DETECTOR

This is a very neat crystal detector that may be panel or base mounted and is constructed of two parts so that the crystal holder can be easily exchanged. The novel features of this detector are the variable or micro-meter adjustment provided and the use of an inner metal screen in front of the crystal. The purpose of this screen is to hold the whisker in a fixed position so that its pressure on the crystal can be regulated without



having it slip off the sensitive spot. This detector is manufactured by the Electric City Novelty and Manufacturing Co., 126 Odell Street, Schenectady, N. Y.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 364.

TWIN DRY CELLS

The Twin Dry Cell Battery Co., 11401 Madison Ave., Cleveland, Ohio, submitted samples of their general duty No. 4 1 1/2-volt Du-Al dry cells, No. 2 1 1/2-volt Twin Radio dry cell, and No. 61 1 1/2-volt Twin Radio Special cell battery. These dry cells are of somewhat different construction than the usual type. The number six cell is of the standard size and construction. The number 211 is somewhat larger in



size and has a greater output. The 12-cell battery is larger than the other two and is specially designed for radio work where long life is required. The illustration shows the number six type. All of these cells gave excellent service for a considerable length of time.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 5108. 521 552 and 571.

REMLER VARIABLE CONDENSER

The Remler variable condenser is of a radically different construction than the lamellar type. Instead of the usual rotary and stationary plates, this condenser has two sets of plates mounted so that both swing and mesh into each other. Each set of plates is mounted on a shaft geared to the dial shaft and one complete turn of the dial varies the condenser from maximum to minimum. On account of this special design the condenser has the



extremely low maximum capacity of 5.41 mmf. The maximum capacity is 58.88 mmf. The dielectric absorption losses at 1,000 cycles with the condenser set at maximum capacity are equivalent to a series resistance of 160 ohms. The plates are shaped so as to give practically a straight line wavelength curve on the 180 degrees of the dial and a straight line capacity curve for the remainder. This instrument is manufactured by the Remler Radio Manufacturing Co., 192 Saratoga Street, San Francisco, Calif.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 355.

THE KANT-BLO SIGNAL POST

This is merely a binding post for the negative "B" battery connection fitted with a series resistance and a signal lamp. In case of a short circuit inside of the set that



would ordinarily burn out the vacuum tubes or ruin the "B" battery, this safety device limits the "B" battery current, saves the tubes and gives the signal to the operator by lighting the lamp. It is merely a protective device and is recommended for use on all receiving sets. Manufactured by the Kant-Blo Manufacturing Corp., 120 Broadway, New York City.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 365.

THE KANT-BLO SIGNAL SWITCH

The Kant-Blo signal switch controls both "A" battery switch and vacuum tube protective devices. Only one hole is required for mounting and it is easily installed in the



set. It is fitted with a separate terminal for the negative "B" battery lead. In case of a short circuit inside of the set that would cause the "B" battery current to flow through the filament, the Kant-Blo device is fitted with a signal lamp and a resistance that limits the "B" battery current and saves the tubes. As the lamp lights up in case of a short circuit, the operator instantly knows where to look for trouble. Manufactured by the Kant-Blo Manufacturing Corp., 120 Broadway, New York City.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 567.

CALIBRATED TRANSFORMER

The Calibrated audio frequency amplifying transformer is manufactured by the National Airplane Corp., 16 Hudson Street, New York City, embodies all the latest im-

provements in audio frequency transformer design. It operates with high efficiency over the entire audio frequency range, and the voltage amplification curve is exceptionally flat and extends far into the lower frequencies. An average




amplification of 5 to 50 volts is obtained throughout the entire range. The core is clamped with a metal casing and no holes are drilled through the iron. The core is protected with bakelite shield so that electrostatic coupling between the plate and grid circuits is reduced.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 371.

PRECISE PUSH-PULL TRANSFORMERS

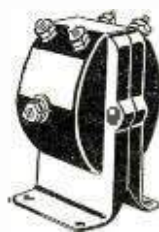Although small in size the Precise push-pull transformers give excellent results throughout practically the entire audio frequency range.



The voltage amplification curves of the input transformer, No. 390, measured between the center terminal and each outside terminal of the secondary, are practically identical. The curves extend well into the lower audio notes—in the neighborhood of 200 cycles—and consequently cause very little distortion. A voltage amplification in the neighborhood of two and one-half to three is obtained throughout the entire range. The output transformer, No. 361, is of the same general construction and approaches 25 db. output type. Manufactured by the Precise Manufacturing Corporation, 214 Mills Street, Rochester, N. Y.

Arrived in excellent packing.
AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 563.

KEYSTONE TUBE

The Keystone Electric and Radio Co., New York City, submitted three of their type 20-A tubes. Although no life tests were made on these tubes, all three gave very good results. The amplifiers gave a range from seven and one-half to eight and one-half. The tubes consume non-quarter ampere at five volts. The tubes are



very well as oscillators, detectors and amplifiers and will stand 90 to 120 volts on the plate.

AWARDED THE RADIO NEWS LABORATORIES CERTIFICATE OF MERIT NO. 564.




By JOHN B. BRADY*

RADIO RECEIVING CIRCUIT

(Patent No. 1,499,341, B. C. Dwyer. Filed Dec. 31, 1922, issued July 1, 1924. Assigned to Westinghouse Electric & Mfg. Co. of Pa.)

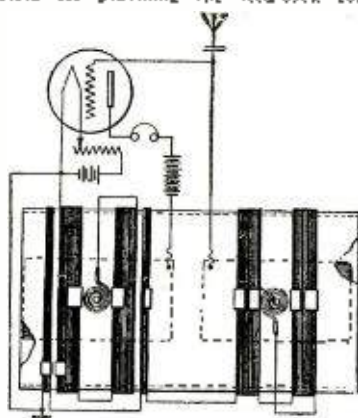Radio receiving circuit employing the feedback principle where the input and output circuits of an electron tube each are provided with variable inductors for providing the feedback coupling




there between. Additional inductance is provided in each of the circuits for establishing such additional feedback coupling than the degree of regeneration is substantially independent of adjustment of the inductor in the input circuit of the tube. The circuit arrangement provides a compact radio receiving set.

METHOD AND APPARATUS FOR ELECTRICALLY TRANSFERRING ELECTRICAL OSCILLATORY ENERGY

(Patent No. 1,456,828, M. W. Horst. Filed March 29, 1920, issued Dec. 13, 1923.)

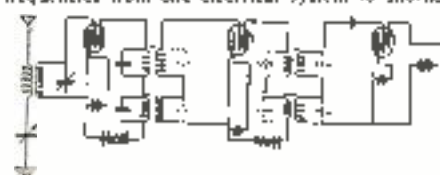Method and apparatus for selectively transferring electrical oscillatory energy of any frequency or frequencies lying within a continuous band of frequencies from one electrical system to another.



This patent shows an electron tube amplifier in which the input and output circuits of the several tubes are coupled by means of a series of parallel circuits tuned to different frequencies. Each circuit is resonant to a different frequency so that the circuit has a highly efficient selective effect over a range of frequencies which includes the band of frequencies.

ELECTRICAL SIGNALING

(Patent No. 1,504,470, J. O. Sienkiewicz et al. Filed July 25, 1922, issued Aug. 12, 1924.)

Electrical signaling wherein radio signals may be received substantially free of interference by a combination loop antenna and wave coil receiving



circuit. The loop antenna is closed through a variable condenser and connected at one point to ground and to the terminal of a wave coil. The receiving apparatus is coupled by means of a movable ring to the wave coil which is moved along the wave coil to a position for best reception.

ELECTROSTATIC CONDENSER


(Patent No. 1,506,002, E. Thomson. Filed Nov. 13, 1920, issued Aug. 5, 1924. Assigned to General Electric Co. of New York.)

Electrostatic condenser for high power operation where the condenser is constructed in a stack

of thin layers of alternate conducting material and insulating material. The feature of the invention is the insertion of heat conducting sheets between the several condenser sections for carrying away heat developed in the condenser.

VARIABLE CONDENSER

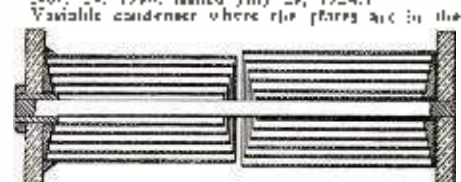(Patent No. 1,502,860, D. S. McCrum. Filed Nov. 24, 1922, issued July 29, 1924.)




form of cylinders arranged to wipe over one within the other forming extended cylindrical contact areas.

TONE PRODUCING RADIO RECEIVER

(Patent No. 1,502,875, M. I. Pappe et al. Filed Feb. 14, 1920, issued July 29, 1924. Assigned to Westinghouse Electric & Mfg. Co.)

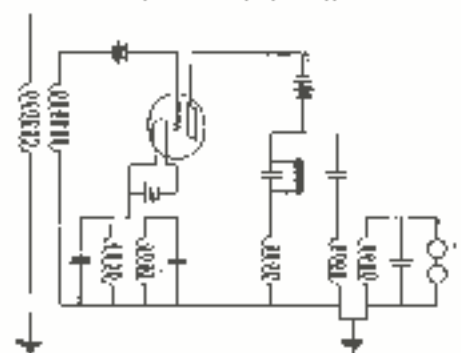Tone producing radio receiver, wherein the receiving amplifier is arranged to repeat the incoming waves of an amplitude which varies periodically at an audible frequency so that the resultant electric waves produce a physical tone in the ear.



receiving system. An electron tube circuit is provided at the receiver with a filter coupling the input and output circuits thereof. The filter including a plurality of like units, each unit comprising two reactances of opposite sign such as the reactance of one sign connected in series and all those of the other sign connected in parallel whereby electrical currents are repeated at a periodically varying amplitude.

SYSTEM FOR TRANSMITTING ENERGY WITHOUT WIRES


(Patent No. 1,504,974, C. Remo. Filed March 8, 1920, issued Aug. 12, 1924.)

System for transmitting energy without wires in a confined path in any direction. A spirally revolving magnetic field is produced in a pair of symmetrically segmented conductors. A parabolic reflecting surface is arranged for focusing the magnetic field in a desired direction.

METHOD OF AND APPARATUS FOR ELECTRICALLY TRANSMITTING INTELLIGENCE

(Patent No. 1,561,598, C. D. Thier. Filed Oct. 21, 1920, issued July 29, 1924.)

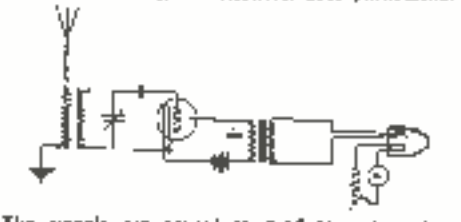Method of and apparatus for electrically transmitting intelligence in the form of sustained waves without the use of the electrical heat phenomena.



The signals are caused to produce a tone frequency and at a point adjacent the production of such tone frequency a magnetically produced

sound wave is generated. The sound wave produced by the incoming signal combines with the mechanically produced sound wave to produce a wave beat of audible frequency for observing the incoming signals.

MEANS FOR PROTECTING RADIO OUT-FITS FROM STATIC DISTURBANCES

(Patent No. 1,504,600, O. A. Brackett. Filed Jan. 16, 1918, issued Aug. 12, 1924. Assigned to Westinghouse Electric & Mfg. Co.)


Means for protecting radio outfits from static disturbances wherein the major portion of the energy of static disturbances is shunted around the receiving apparatus so as to be substantially ineffective in disturbing the receipt of signaling impulses. A pair of rectifying devices are connected in shunt with each other and placed directly across the receiving circuit.

SECRET SYSTEM FOR RADIO-TELEGRAPHY

(Patent No. 1,505,055, A. R. Nollins. Filed May 19, 1922, issued Aug. 12, 1924.)


Secret system for radiotelegraphy wherein a

Fig. 1.

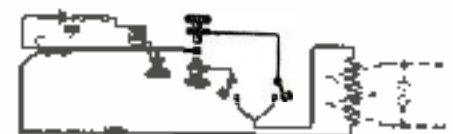

tuning lock is provided at both the transmitting and receiving stations and arranged to vibrate in synchronism to close sets of contacts connected in different circuits whereby one series of signals

Fig. 1a.

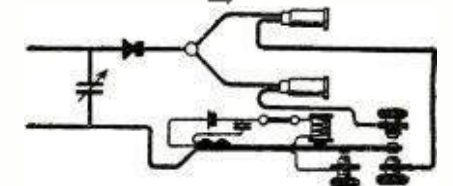


may be radiated through the spaces of another series of signals. The messages are therefore transmitted in mixed relation and separated by a synchronized device at the distant receiving station.

VARIABLE PLATE ELECTRIC CONDENSER

(Patent No. 1,500,528, F. R. Rathbun. Filed July 2, 1922, issued July 8, 1924.)

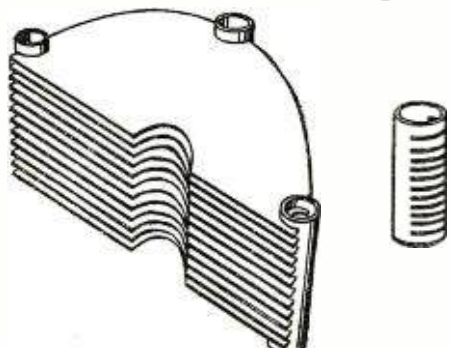Variable plate electric condenser having stationary



stationary and movable plates for facilitating the protection of the instrument. The stationary plates are supported at three points about the periphery thereof by cast metal poured into slots in the support members. The movable plates are similarly supported by a slotted tubular member in which molten metal is poured over the plates.

TUNING SYSTEM OF ANTENNAE

(Patent No. 1,502,848, P. Conrad. Filed July 7, 1920, issued July 29, 1924. Assigned to Westinghouse Electric & Mfg. Co.)

(Continued on page 1028)

*Patent Lawyer, Ocean Building, Washington, D. C.



This "Service Farce"

By HOWARD S. PYLE

"A BCD de MINOP Hr Svc Sa Om. Any chance to come aboard and look a over when we reach port?" Service? How do they get that way? And yet, 15 minutes casual listening on 600 meters will bring in several similar "Services." The practice is on the increase; particularly on the Great Lakes is it extremely obnoxious. The prefix, "Svc" is used as a thin veneer to disguise unnecessary and prohibited conversation between commercial radio stations. The practice is despicable from many standpoints and its early elimination should be one of the objects of commercial radio operators. There is now a tremendous amount of necessary interference from the standpoint of communications handled—without adding to it, such unofficial and unlawful transmissions.


A more mild form of service message, but one which is also inherently wrong in structure, is that relating to the radio equipment or service between stations. It seems that the meaning of a service message is generally misunderstood, but reference to the London Convention or to a Western Union tariff book will reveal the fact that a service message is one referring strictly to tariff handled. It is as short and concise as possible to still convey the necessary information. An inquiry relative to the shipment of certain spare parts for a ship's transmitter, sent by that vessel to a shore station is distinctly not a service message. Neither is a request to the shore station to have the office mail additional stationery to the next port, a message of this class. These are actually messages and should be handled and abstracted as such and carry a full address and the signature of the senior operator. Whether or not they are charged for or are "franked" messages depends entirely upon whether they reach their destination entirely through the stations of the radio company or whether "other line charges" enter into it.

Proper structure of a service message is also something not generally known among the present day marine operators. Again reference to a Western Union or Postal Telegraph tariff book will show the proper procedure. A service message, by reason of the fact that it ordinarily carries no charges, and is in reference to another message, and as such is handled only by operators, can be abbreviated considerably, and should be. The more common abbreviations in general use are as follows:

GBA—Give better address.
GSA—Give some address.
NSN—No such number.
SVS—See your service.
SOS—(Should not be used in marine work.) See our service.
UNLOCATP—Unable to locate.
UNDELVD—Undelivered.

Others will occur as the occasion arises. An example of the proper use of a service message where a message has been undelivered by a shore station, would be addressed to the office of origin and read somewhat as follows:

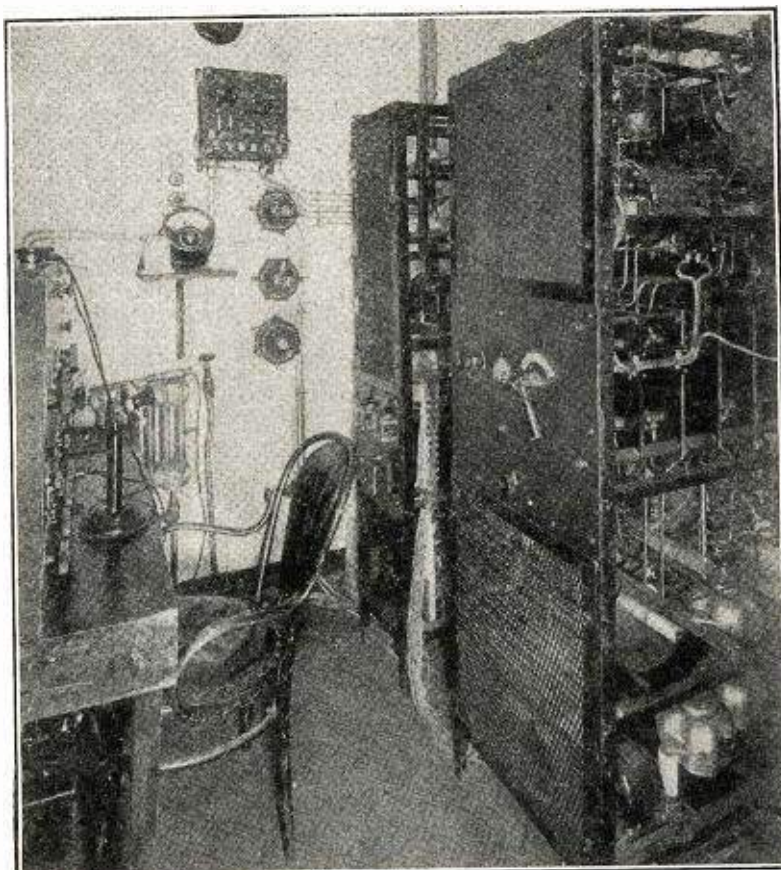The Duplex Radio Telephone Equipment aboard the S.S. Antrim, the first set of its type to make two way communication by radiophone a possibility. The receiving equipment consists of long and short wave receivers each with a separate heterodyne for the reception of C.W. and a Super-Heterodyne receiver. All of the equipment is of General Electric Manufacture.



"S. S. Greater Detroit
Yr Nr 4 date Simpkins signed Thompson
Undelvd NSN. GBA.
CX Boston Mass. 15th"

Interpreted the above would be:
"S. S. Greater Detroit:
Your message number four of this date to Simpkins signed Thompson undelivered. No such number. Give better address.
CX Office Boston, Mass. 15th."

It is readily apparent that the above service applies directly to message traffic and is, therefore, greatly shortened by using the abbreviations that have become standard.

Let us endeavor to eliminate the unnecessary conversation and confine ourselves to actual business. It gains a better name for the operator, both professionally and with the company, and it is only a selfish operator who will clutter the air with such useless stuff as quoted at the beginning of this article, and thus deprive others of the legitimate use of the air.

A MARINE RADIO OPERATORS' ASSOCIATION


FOR well over a year almost every article or letter published as written by a Marine Radio Operator contains a few lines, or in way of conclusion has something to say regarding a Union or an Association for the Marine Operator and these articles or letters

invariably end with the words, "Why Not?" A few of these appear in some of the back issues of RADIO NEWS and now that the "With the Sea-going Op's" department has started again, more and more, no doubt, will be written by operators regarding an association, and the profession, as it may be called.

The whole thing is that the operators really want an association "by, for and with" the Marine Operator. Many of the older group of operators generally favor an association; but all of the operators, both the old timers now at sea and the newcomers into the game will come to the conclusion that they will not desire to support any kind of a "money making scheme" while they are doing their duty at sea and have someone at the head of their organization at a desk ashore holding down a so-called "soft job."

A great number are truly contented with their lot. One of the good reasons for this attitude is that most of the men doing their very best and being conscientious in their work are quite aware of the fact that the radio service companies are very fair and do justice to their desirable operators. On the whole they are "by, for and with" those who do what is right. Operators employed aboard the Shipping Board vessels who have had occasion to find out know that the Board Radio Supervisors back up their men.

(Continued on page 1043)

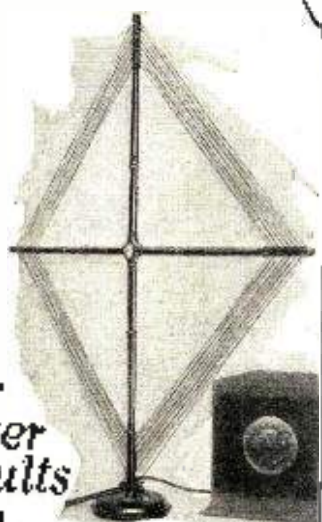

For
Better
Results
from
All Loop Circuits.

BODINE BASKET-WEAVE LOOP AERIAL

The Finest Loop That You Can Buy!

A better loop—has more effective in design and greatly improved in appearance. A really beautiful folding loop, finished to match the most expensive sets and using a new approved winding that picks up the most distant stations and delivers the signals to your set with full strength.

Use this loop to increase the range and volume of your present loop set or to ensure greatest satisfaction from the set that you are building.

The high-weave basket-weave wire used in the BODINE Loop has lower distributed capacity, less high-frequency resistance and greater efficiency in collecting weak signals.

The new design, with thorough lagging and heavy stranding, still carries the same increased volume from distant stations.



Collapsible and Portable

The BODINE LOOP is two feet square when erected. It folds in an instant to fit into a compact box. It is handsomely finished in English Mahogany and is fitted with a satin-silver graduated dial and 24 adjusting handles for your convenience in tuning in and logging distant stations.

A TYPE FOR EVERY CIRCUIT

Standard, Super-Hit Special and High Inductance \$ 8.50
Metal-Tapped Loop 10.00

Ask your dealer to show you this remarkable superior loop today. An inspection of the many exclusive features will convince you that no better loop can be built. From today on, request.


BODINE ELECTRIC COMPANY
7235 W. Ohio St. Chicago, Ill.
Quality electrical products for eighteen years

List of Broadcast Stations

(Continued from page 954)

Call Letters	Name	Location	Power & Wave Length
KFQE	Dickmann-Henry Radio Laboratory, Colorado Springs, Colo.		5—224
KFQF	Donald A. Runkle, 2544 Mesquite Ave., Minneapolis, Minn.		10—224
KFQG	Southern California Radio Association, Los Angeles, Calif., Army, Exposition Park		800—228
KFQH	Albert Sherman, Hollsbrough, Box 51, Burlingame, Calif.		50—231
KFQI	Tacoma H. Luce Corp., Calver City, Calif.		100—234
KFQJ	Harbour-Longmore Co., Okla. human, Okla.		50—236
KFQK	Democrat Leader, Fayette, Mo.		30—236
KFQL	Oklahoma Free State Fair Association, Muskogee, Okla.		20—252
KFQM	Texas Highway Bulletin, Austin, Texas		300—258
KFQN	Third Baptist Church, Portland, Oregon		5—255
KFQO	Power Radio Shop, Russell, Kansas		10—261
KFQI	George S. Carsten, Jr., 906 E. College St., Iowa City, Iowa		10—264
KFOR	Walter L. Ellis, 625 East 8th St., Oklahoma, Okla.		10—250
KFUS	Dickson-Henry Radio Lab., Manitou, Colo.		10—246
KFOT	Texas National Guard, Thirty-sixth Signal Co., Denison, Texas		10—252
KFOU	W. Baker, Holy City, Calif.		150—234
KFOV	Omaha Grain Exchange, Omaha, Neb.		100—231
KFQW	C. F. Knierim (Radio Band & Electric Shop, North Bend, Wash.		50—245
KFOX	Alfred M. Hubbard, 314 Green Ridge, Seattle, Wash.		350—277
KFYJ	Farmers State Bank, Belden, Neb.		10—271
KFQZ	Taft Radio Co., 400 N. Long Ave., Hollywood, Calif.		250—240
KPRC	Radiant Studio, San Francisco, Calif.		5—280
KPRP	W. B. Brown, Alexandria, La.		10—242
KPRC	Cleveland High School, St. Louis, Mo.		20—236
KFRH	The Radio Shop, Graham, N. D.		30—263
KPSG	Echo Park Evangelistic Association, Los Angeles, Calif.		300—278
KFSY	Van Blarstone Co., 26 So. Main St., Helena, Mont.		10—261
KGR	Taroma Daily Ledger, Tacoma, Wash.		50—252
KGG	Hillock & Watson Radio Service, Portland, Ore.		50—260
KGM	Gowat Electric Co., Oakland, Calif.		300—312
KGU	Marian A. Mulrany, Honolulu, Hawaii		500—360
KGW	Portland Morning Oregonian, Portland, Ore.		500—452
KGY	St. Martins College, Lacey, Wash.		5—258
KHI	Times Mirror Co., Los Angeles, Calif.		500—365
KHO	Louis Wassner, Seattle, Wash.		100—360
KIJ	C. O. Gould, Stockton, Calif.		5—271
KJW	Northwest Radio Service, Seattle, Wash.		30—255
KJS	Rabe Institute of Los Angeles, Los Angeles, Calif.		750—360
KLS	Wagner Bros Radio Supplies Co., Oakland, Calif.		350—360
KLN	Tribune Publishing Co., Oakland, Calif.		500—505
KLY	Reynolds Radio Co., Denver, Colo.		500—283
KMJ	San Joaquin L. & Power Corp., Fresno, Calif.		50—248
KMO	Live Electric Co., Tacoma, Wash.		10—350
KNT	Walter Heinrich, Kotik Bay, Alaska		100—263
KNX	"Hollywood" — Los Angeles Evening Express		—
KOR	New Mexico College of Agriculture and Mechanic Arts, State College, N. M.		500—360
KOP	DeLeon Police Dept., Detroit, Mich.		500—286
KPO	Hale Bros., San Francisco, Cal.		500—423
KOP	Angelo City Radio Club, Hood River, Ore.		10—360
KOV	Doubleday Hill Electric Co., Pittsburgh, Pa.		530—270
KQW	Chas. D. Herold, 467 First St., San Jose, Calif.		30—360
KRE	Herkley Daily Gazette, Berkeley, Calif.		50—275
KSD	Peop Dispatch (Minister Pub. Co.), St. Louis, Mo.		500—346
KTW	First Presbyterian Church, Seattle, Wash.		750—369

QUICK POSITIVE CONNECTIONS!

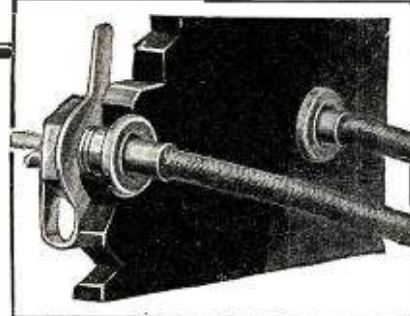

Union Radio Tip Jacks (Patent Pending) 25c a pair

Just what you want when building your own set or experimenting with new hook-ups. Not only give positive electrical contact, they improve the appearance of your set.

Two sizes for all mountings. STANDARD TYPE A for panels up to 1/4 inch thickness. SPECIAL TYPE B for panels, cabinet walls and partitions from 5/16 to 1/2 inch thickness. Will firmly grip all wires from No. 12 to 24 B & S gauge, and can be turned in pass and build antenna wire, battery leads, loading coils and vacuum tube lugs.

No parts to lose, chip or deteriorate. All parts heavily nicked. Price 25c a pair.

OTHER GUARANTEED UNION RADIO PARTS

DIAL ADJUSTERS for minute variations in capacities of variable condensers. Price 60c.


TUBE SOCKETS of moulded condenser highly polished Phosphor Bronze contact springs. Reinforced bayonet slot prevents breakage. Accommodates all standard tubes. Price 70c.

Should your favorite Radio Store not carry Union Radio Tip Jacks and Guaranteed Parts send your order direct to us, also write for your copy of "The Union Radio Catalogue 'A'".

RETAILERS AND WHOLESALE

Samples of our guaranteed, reasonably priced "Quality Products" sent on request. Our terms and trade discounts are liberal. Write for our proposition, and a copy of our illustrated Pamphlet H.

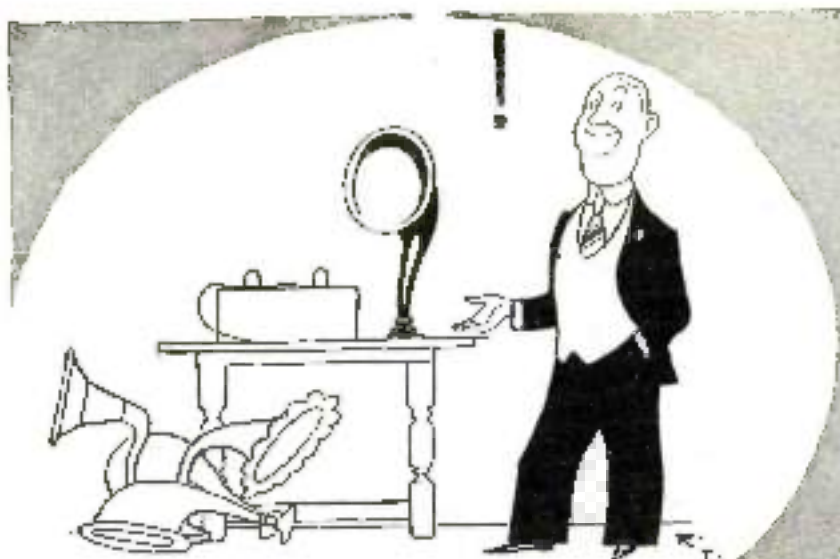UNION-RADIO-CORPORATION
200 MT. PLEASANT AVENUE, NEWARK, N.J.
NEW YORK OFFICE: 110 WEST 32ND STREET



Hear the difference!

A loudspeaker is a critical thing. Any vibration in the horn adds sounds that nature never gave to the speaker's voice. And limited range thins down the tone to flat, unreal quality. Some people think that a near-real voice is the best that radio can give . . . but not after they have heard a Radiola Loudspeaker!

The difference is the result of elaborate experiment and extended scientific study. The Radiola Loudspeaker has an extraordinary range—gets the full richness of tone. And it adds no sound of its own. To know how clear—how mellow—how *real* your music can be—ask to hear a Radiola Loudspeaker.

Radiola

U. S. PAT. OFF.

LOUDSPEAKER



Radiola Loudspeaker
Type UZ-1325
Now \$25.00

This symbol
of quality




is your
guarantee

**RADIO CORPORATION
OF AMERICA**

Sole Offices:

213 Broadway, New York
10 So. La Salle St., Chicago, Ill.
28 Geary St., San Francisco, Cal.

Duo-Spiral Folding Loop

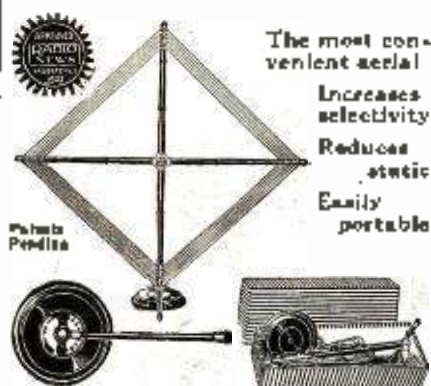

The most convenient aerial
Increases selectivity
Reduces static
Easily portable

The DUO-SPIRAL FOLDING LOOP is a favorite because of its great convenience, handsome appearance and superior performance. It brings in the far distant stations. It is a superior loop for permanent installations or portable sets.

The DUO-SPIRAL winding—an exclusive feature—makes possible an aerial wire of unusual length, giving greater signal strength without sacrificing neatness or compactness. The wire is stranded copper with heavy silk insulation. Tension is always just right for maximum efficiency. Connection is made direct from antenna wire to receiver. The base has a silvered dial graduated for calibration. The handle permits adjustment without body capacity effects.

DUO-SPIRAL is handsomely finished in silver and mahogany and harmonizes with the finest home furnishings. It can be used indoors or wherever you go when you want to take your receiving set with you.

Price complete, \$8.50

Tiny-Turn Vernier Control

Every owner of a radio set knows how difficult it is at times to tune in distant stations. All adjustments must be exact. Only one position on each dial gives maximum signal strength. The greater the selectivity of the set the greater the need for close adjustment.

TINY-TURN makes it easy to adjust the dials to exactly the right position. It has a gear ratio of 30 to 1. Signal strength is increased through perfect tuning. Rotates in same direction as dials. Can be disengaged leaving dials free. Easily attached to any standard panel. Increases range and volume and improves tone quality. Handsome nickel and ebony black finish.

If your dealer cannot supply DUO-SPIRAL or TINY-TURN write us direct.

Radio Units Inc.
Maywood, Illinois

1300 First Avenue
Capitol Broadcasting
Parkway Electric Co., Montreal



Price 75 cents

Call Letters	Name	Location	Power & Wave Length
KTLJ	Francisco Printing Co.	San Francisco, Calif.	150-160
KCV	Coast Radio Co.	El Monte, Calif.	50-256
KWG	Eustatic Wireless Telephone Co.	Stockton, Calif.	50-260
KWH	Los Angeles Examiner	Los Angeles, Calif.	250-360
KYG	Electric Shop	Hood River, Oregon	100-270
KLV	Westinghouse Electric & Mfg. Co.	Chicago, Ill.	1000-316
KXM	Frederic D. Allen, Ltd. & Frank	San Jose, Oakland, Calif.	100-360
WAAB	Valdemaar Jensen	137 S. St. Patrick St., New Orleans, La.	100-260
WAAC	Tulane University	New Orleans, La.	400-360
WAAD	Ohio Mechanics Institute	Cincinnati, Ohio	25-360
WAAP	Chicago Daily Worker's Journal	Chicago, Ill.	200-286
WAAS	J. R. Nelson Co.	Newark, N. J.	250-261
WAAT	University of Missouri	Columbia, Mo.	50-254
WAAY	Chicago Grain Exchange	Chicago, Ill.	500-286
WADB	Harrisburg Sporting Goods Co.	Harrisburg, Pa.	10-266
WABD	Parter High School	Mayano, Ohio	5-281
WABE	Young Men's Christian Association	Washington, D. C.	100-281
WABH	Lake Shore Tint Co.	San Jose, Calif.	10-240
WABI	Banger Radio & Electric Co.	Bangor, Maine	100-240
WADL	Connecticut Agricultural College	Storrs, Conn.	100-283
WABM	F. K. Doherty Associates & Radio Equipment Co.	Saginaw, Mich.	100-254
WABN	See Radio, Inc.	1027 Shaw St. Lafayette, Wis.	100-244
WABO	Lake Ave. Baptist Church	Brooklyn, N. Y.	10-281
WADP	Robert E. Weisig	522 Woodier Ave., Dorset, Ohio	200-266
WABQ	Haverford College Radio Club	Haverford, Pa.	50-261
WABR	Scott High School	Toledo, Ohio	50-270
WABU	Veter Talking Machine Co.	London, N. J.	10-276
WABW	College of Wooster	Wooster, Ohio	10-254
WABX	Henry B. Day Women's Club	Richmond, Mich.	500-270
WABY	John Magaldi, Jr.	211 Keshoff St., Philadelphia, Pa.	10-241
WABZ	Coliseum Place Baptist Church	New Orleans, La.	50-243
WBAA	Purdue University	West La. Fayette, Ind.	250-284
WBAN	Wireless Phone Corporation	Pasadena, N. J.	100-211
WBAO	James McKim University	Deerfield, Ill.	50-275
WBAP	Western-Vernier Publishing Co.	(Star-Telegram), Fort Worth, Texas	750-476
WBAY	Kaiser & Hopkins Co.	Columbus, Ohio	500-421
WBAX	John H. Seeger, Jr.	66 Gilchrist St., Wilkesboro, Pa.	20-360
WBAY	The Western Electric Co.	New York, N. Y.	500-442
WBBD	Batter Battery Service	Richmond, Pa.	50-254
WBBO	Young Verity's	Madisonville, Mo.	500-245
WBHF	J. Luther Bell	1511 Gordon St., Port Huron, Mich.	50-246
WBHL	Grace Episcopal Church	Richmond, Va.	5-251
WBHP	Pequot High School	Pequot, Mich.	100-246
WBHN	Pequot High School Association	Pequot, Mich.	500-275
WBHT	Lloyd Brothers	Philadelphia, Pa.	5-274
WBHU	Wicks Motor Sales Co.	Monmouth, Ill.	10-276
WBHV	Johnson Radio Co.	Indianapolis, Ind.	5-248
WBHW	Hillier Junior High School	Norfolk, Va.	50-272
WBHY	Washington Light Infantry	Charleston, S. C.	10-269
WBHZ	Noble H. Watson	251 Iowa St., Indianapolis, Ind.	50-227
WBIC	T. & H. Radio Co.	Anthony, Kansas	100-254
WBIS	D. W. Star	Newark, N. J.	50-160
WBIT	Southern Radio Corp.	Charlotte, N. C.	250-160
WBIZ	Westinghouse Electric & Mfg. Co.	Springfield, Mass.	1000-315
WBAD	St. Lawrence University	Canton, N. Y.	250-180
WBCE	Kaufman & Bate Co.	Philadelphia, Pa.	500-462
WBAG	Clyde R. Randall	2811 Calhoun St., New Orleans, La.	50-268
WBCH	Embeck Electric Co.	Columbus, Ohio	100-256
WBCT	Schuyler Wesleyan University	University Place, N. Y.	100-245

HEATH

Permanently FLAT Plates

The well known HEATH process of stamping rotor plates to lasting flatness, makes the new Heath a permanently satisfactory instrument.



Heath Radiant—NON-DIELECTRIC CONDENSERS

A new type of end plate which banishes leakage and capacity effects, added to the popular Heath features of permanently FLAT Plates and the most perfect type of vernier. These advantages of Heath condensers are the best guarantee of lasting satisfaction.

PRICES FOR VERNIER CONDENSERS

No.	24V 12 Plate	With Flat .50 mm	Without Flat
No. 24V 24 Plate	5.50	6.85	
No. 44V 44 Plate	6.50	8.45	

Thin type in all sizes




Heath Sockets with the Exclusive Shock Absorber Feature

Baskets host into which reinforced phosphor bronze, self-cleaning contacts are securely embedded. Binding posts are slotted hexagon nuts. HEATH Standards of material and workmanship. Price 75c

Heath Dials in Three Sizes

HEATH RADIO & ELECTRIC MFG. COMPANY

206 First Street Newark, N. J.
Exclusive Canadian Distributors
Maple & White Telephone Co., Ltd., Montreal, Canada

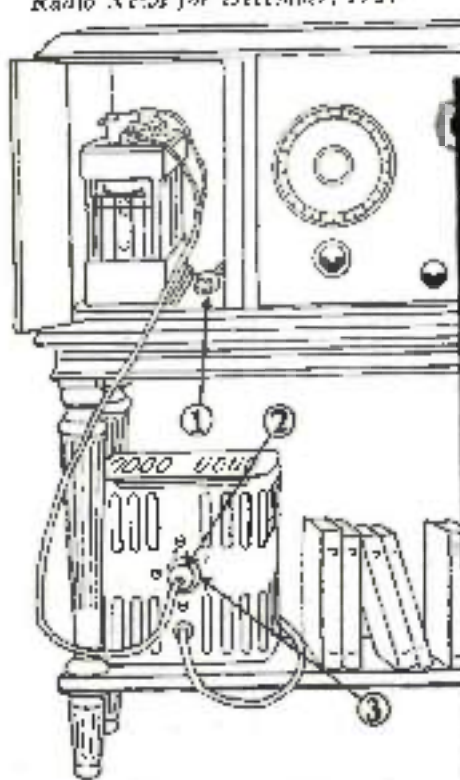**Philco Battery can Charge**

To connect the battery to your receiving set, call on plug (2) from rear panel of the Philco NOISELESS Charger and push into receptacle (1). You now operate as before. Radio Receivers in the same movement feature Philco Charger for 6-volt "A" batteries and all "B" batteries. Philco Charger for 12-volt tube "A" batteries and all "B" batteries. Prices: 12-volt 12.25; 6-volt 12.25. Prices include post and receptacle (1, 2 and 3).

"B" Charging Panel \$2.75



Philco Type UIM4 - Price \$8

**Philco "B" Battery**

Storage "B" batteries are ideal for direct and indirect reception. Philco "B" battery is size 100 and 120.

With 40 tube machines which take a 120 volt battery (120 volt) \$12.50

With 12-volt machines which take a 120 volt battery (120 volt) \$12.50

**Philco "A" Battery**

For standard 6-volt tubes. Anti-light glass case. Philco Charge Indicator. Price \$12.50

**Philco "A" Battery**

Manufactured from top for standard 6-volt tubes. Price \$12.50. Charge Indicator. Anti-light glass case. Philco Charge Indicator. Price \$12.50.

A Philco Rechargeable "Dry-Cell Replacement" Battery

A Philco "dry-cell replacement" storage battery gives better reception at much less expense than dry cells, even on dry cell tubes. There is no appreciable dropping in reception from the start to finish of a discharge.

Dry-cell voltage falls continuously from the very day the cell is manufactured, whether it is used or not.

Storage battery voltage stays within 12% of maximum at all times and can be restored to maximum at any time by recharging.

Recharging with a Philco NOISELESS Charger means merely pulling a plug from the radio socket and pushing it into the charger socket. No wires to change. No worry about getting positive and negative mixed.

This Philco "dry-cell replacement" battery has other big advantages. It has a built-in Charge Indicator that tells you at a glance

how far the battery is charged or discharged. Exclusive anti-light sealing makes it practical for use inside radio cabinets.

It delivers strong, non-rippling current without hum, roar or buzz — an absolute essential for clear radio reception.

Like all Philco Rechargeable Radio Batteries, it is Drymatic (shipped by the factory dry but charged). Its life doesn't start until you or your dealer plugs in the electrolyte. You are sure to get a new, fresh battery.

This Philco Type UD44 operates either UV116 or WD11 type tubes. It occupies only the same space as three dry cells but easily replaces six dry cells as used on multi-tube receivers.

Philco also makes batteries of similar convenience and economy for storage battery tubulars for your automobile. See your nearest Philco Service Station, Radio or Music Dealer.

The Philadelphia Storage Battery Company, Philadelphia

PHILCO

DRYDYNAMIC RADIO BATTERIES

RADIO DEALERS—Let us send you our new Radio Manual. It tells you all you want to know about radio batteries. Just sign this coupon and mail to us.

Name
Address
City State

RADIO MANUAL FREE
Name
Address
City State
Philco Radio Dealer or
Write for details.



**CHARMITONE
LOUD SINGER**

A New Sensational Improvement for Your Radio!

THIS is more than a standard loud speaker. It is a charmingly mellow and clear musical instrument of exceptional performance; and in addition has exclusive mechanical features which make its perfect operation merely a matter of moving a lever.

Dual Action

Tuning and Amplifying off the same Master Phone located in the base of the instrument. No Head Phones Needed!

Supersensitive Stethoscope Attachment

Both as Physicians use, increases the pleasure and satisfaction from your Radio Set.

After tuning in with Stethoscope in ears, one turn of the lever in the base cuts off Stethoscope and operates horn. No plugging in and out of the set; no chance of losing volume when changing from headset to horn, or disturbing the dial adjustments and tuning station. Same lever also controls the volume, from soft to loud, in both Stethoscope and horn. Any number of Stethoscope Attachments may be used without putting extra tax on the batteries.

The CHARMITONE LOUD SINGER is a Real Musical Instrument for the Radio; a beautiful ornament for use with the most elaborate cabinet, and as practical as it is beautiful. One-piece horn, silver-plated metal parts; best workmanship throughout, and handsome, dark gray, crystalline finish.

Made in two styles, see illustration above. Extra Stethoscope Attachments, complete, \$1.50.

Ask your favorite dealer to show you the CHARMITONE LOUD SINGER; or write us for more detailed descriptive literature.

Dual Loud Speaker Co.
210 West 54th St., New York

Call Letters	Name	Location	Power & Wave Length
WCAK	Miriel P. Danet, 2504 Bucky St.	Houston, Texas	10-161
WCEM	St. Orl College	Norwalk, Conn.	50-162
WCAO	The Sanders and Graydon Co.	Baltimore, Md.	50-160
WCAP	Chesapeake & Potomac Telephone Co.	Washington, D. C.	500-460
WCAR	Southern Radio Corp. of Texas	San Antonio, Texas	100-160
WCAS	Wm. H. Bond, Chesapeake Radio Corp.	Eastport, Maryland	100-280
WCAT	South Dakota State School of James	Rapid City, S. D.	50-240
WCAU	Dechert & Co.	Philadelphia, Pa.	250-236
WCAV	J. C. Dice Electric Co.	Little Rock, Ark.	10-350
WCAN	University of Vermont	Burlington, Vt.	50-160
WCAY	Milwaukee Civic Broadcasting Station	Hotel Ancker, Milwaukee, W.	250-161
WCBA	Charles W. H. Hatch, 3015 Allen St.	Albuquerque, N. M.	10-280
WCBH	University of Michigan	Ann Arbor, Mich.	200-280
WCBD	Walton G. Venable, 2001 N. W.	Washington, D. C.	500-145
WCBK	Chate Radio Co.	New Orleans, La.	5-243
WCBC	Howard S. Williams, Passenger	St. Louis, Mo.	10-268
WCBF	University of Mississippi	Oxford, Miss. (near)	10-242
WCBT	Norfolk, Danvers & Rock, Boston, Tenn.		50-190
WCBY	J. C. Stone, Jennings, La.		10-244
WCBK	E. Richard Hall, 2001 Central Ave.	St. Petersburg, Fla.	540-266
WCBL	Northern Radio Mfg. Co.	Houlton, Me.	50-280
WCBM	Charles Schwarz, Charles and North Ave.	Baltimore, Md.	50-120
WCBP	Radio Shop, Inc.	Memphis, Tenn.	20-190
WCBQ	First Baptist Church	Nashville, Tenn.	100-250
WCBR	Charles H. Meador, Providence B. I. Hospital		5-246
WCBT	Clark University	Worcester, Mass.	250-161
WCBU	Arnold Wireless Supply Co.	Arnold, Pa.	10-254
WCBV	Tulahoma Radio Club	Tallahassee, Fla.	10-252
WCBW	George P. Rankin, Jr., and Mainland Salomon, Macon, Ga.		10-226
WCBX	Radio Shop of Newark, Newark, N. J.		100-213
WCBY	Fork Electrical Shop	Bird Hill, Pa.	10-268
WCBZ	Coppelli Brothers Music House	Chicago Heights, Ill.	50-248
WCC	St. B. & Fuller Dry Goods Co.	St. Louis, Mo.	100-163
WCA	The Journal Free Press	Deerfield, Mich.	500-517
WCAE	Tampa Daily Times	Tampa, Fla.	250-360
WCAP	Reynolds City Star	Kansas City, Mo.	500-441
WCAG	J. Lawrence Martin	Austin, Texas	100-263
WCAN	Trinity Methodist Church	El Paso, Texas	50-266
WCAR	145 Broad	Philadelphia, Pa.	500-193
WCAS	Sara White's Radio Shop	Worcester, Mass.	10-360
WCAU	Shuman & Kilburn	New Bedford, Mass.	100-360
WCAY	Radio Equipment Corp.	Fargo, N. D.	50-744
WCBV	A. H. Watts & Co.	Taunton, Mass.	10-220
WCBH	Kirk Johnson & Co.	Lawrence, Pa.	50-218
WCBT	Herman F. Burns	Marshallburg, W. Va.	5-268
WCBF	Robert G. Phillips	Youngstown, Ohio	50-246
WCBG	C. T. Sherris Co.	Worcester, Mass.	100-264
WCBH	Radio Specialty Co.	St. Petersburg, Fla.	20-270
WCBJ	Richardson-Walsh Electrical Corp.	Kennett, Va.	50-220
WCBK	M. F. Bros. Furniture	Dayton, Ohio	100-248
WCBN	Main Electric Light & Power Co.	Bangor, Me.	5-270
WCBP	Rollins College	Winter Park, Fla.	50-240
WCBQ	Sumner State Normal School	Sumner, Wis.	50-261
WCBR	Jefferson Radio Supply Co.	Salmon, N. J.	10-254
WCBT	First Baptist Church	Boston, Mass.	100-236
WCBU	S. M. & Radio Corp.	Dayton, Ohio	5-281

For Every Radio Requirement—



—there is a proper FAHNESTOCK Clip

FAHNESTOCK solderless connectors are made in 47 styles and sizes designed to cover a multitude of requirements and are in every case undoubtedly the best for the particular need.

The display case illustrated contains 24 varieties, which have been proven by past sales the most popular with the radio buying public. Wide awake dealers everywhere are enjoying increased business by installing these display cases, which show the prospective purchaser instantly the type of connector best suited to his needs.



Improved Ground Clamp
Equipped with Fahnestock Patent Wire Connectors Easily Attached.
No Soldering—For Radio Use Only

ASK Your Dealer to tell you about the FAHNESTOCK Antenna Connector, which assures a Perfect Connection.

None genuine without our stamp

**FAHNESTOCK
ELECTRIC CO.**
LONG ISLAND CITY, N. Y.

VACUUM TUBES REPAIRED

WU-11, WU-12, \$2.00
UV-201A, UV-199,
And others for

Quick service. All tubes repaired by us guaranteed to work as good as new. Send your dead tubes. All you pay is \$2.00 plus Postage or Postman.

THOMAS BROWN CO.
511-519 Orange St., Newark, N. J.

Coto
"Built First to Last"

**GUARANTEED
RADIO PRODUCTS**
Coto-Coil Co.
Providence, R. I.



THIS BATTERY WILL
MATERIALLY REDUCE
YOUR OPERATING
COSTS ON HEAVY
CURRENT SETS

NEW!

Eveready Heavy Duty "B" Battery, 45 volts, Three Fast-acting Cells. Length, 9 3/16 inches, Width, 4 1/16 inches; height, 7 1/16 inches; weight, 13 1/2 pounds.

Price \$4.75

Stands up to heavy duty

THE new Eveready 45-volt heavy duty "B" Battery (No. 770) is made to stand up and deliver the large plate current required by multi-tube receiving sets. Extra large powerful cells, packed with the famous Eveready vim and vigor, give longer life on severe service. For "B" Battery economy use the Eveready 45-volt "B" Battery No. 770 on receiving sets using four or more tubes and operating at 90 volts or more, and all power amplifiers. There is an Eveready Radio Battery for every radio use. Buy them from your dealer.

Manufactured and guaranteed by
NATIONAL CARBON COMPANY, Inc.
Headquarters for Radio Battery Information
New York San Francisco
Canadian National Carbon Co., Limited, Toronto, Ont.

EVEREADY

Radio Batteries

—they last longer



No. 772
Vertical 45-volt, large
size "B" Battery
Price \$3.75



No. 764
Vertical 21 1/2 volt
"B" Battery
Price \$1.75

No. 711
Eveready Radio
"A" Dry Cell
Specially
manufactured for
use with dry cell
sets
Price 40 cents



No. 766
Eveready "A" 21 1/2 volt, six
Tabernock spring
clip connections
Price \$2.00



Science Finds Perfect Loud Speaker in This Beautiful Table Lamp

Nothing like this marvelous *Radiolamp* has ever before been devised. It combines perfect radio tone production with an artistic home fixture of unusual beauty and charm. A demonstration at your dealer's will delight you. Or we'll gladly send complete descriptive literature. Simply mail the Coupon.

YOU may have the finest radio set money can buy. You may have tried about every kind of loud speaker—box, cabinet, and the old horn types. But a delightful surprise awaits you if you have not seen and heard that marvelous new invention—the *Radiolamp*.

This amazing twin-arrangement, which has created a sensation among radio-lovers in New York and elsewhere, offers two astonishingly big values in one. It combines the perfect loud speaker—the last word in radio tone reproduction—with a library lamp of artistic beauty and charm. And the price is no more than if you bought either a loud speaker or a library table lamp separately.

Manufactured under
U. S. Patent Nos.
1,145,501 1,373,343.
Other Patents Pending.

New Scientific Features

The *Radiolamp* is an incomparably better speaker because it is constructed according to the most recently discovered scientific principles. From the perfected loud speaking unit concealed in the base of the lamp, the tone is amplified through the tapered tone chamber in the stem to the "sound mirror" in the top of the shade. Here the sound passes through the warm, dry air of the light

globes and is deflected by the



Attach In An Instant

Simply attach the Radiolamp to any lamp and enjoy an light. The result is a soft, musical, mellowness. These attach Radiolamps to your machine set. No new wiring needed. No adjustments to make.

User Praises Radiolamp

"We have had a few nice days in the last ten weeks or enough to demonstrate that you have not exaggerated any when saying your lamp speaker was the best in the world. I would not take a hundred dollars for mine, if I could not get another. Every one who has seen and heard it has been in their praise of it."

W. R. CONNER
Bishop, Ark.
P. O. Box 72
Exeter, Pa.

And this is but one of the many enthusiastic letters received.

specially constructed parchment shade. The result is an evenness, a purity, a clear, human tone found in no other type of loud speaker. You can keep your receiving set in a separate room if you wish to—connecting it by a long wire with your table lamp.

But to fully appreciate how wonderfully successful this unique combination is—both as a loud speaker and as a permanent, artistic, useful fixture in your home—you should see the *Radiolamp* for yourself. Step in at your dealer's today, and ask for a demonstration. Or if he hasn't it, mail the coupon for free descriptive literature. This will place you under no obligation. So act at once—right away.

Radiolamp Company

Dept. 112
134 Fifth Avenue, New York

RADIOLAMP CO., Dept. 112,
134 Fifth Ave., New York.

Please send me at once complete information about the *Radiolamp* loud speaker.

Name
Address
City State

On Sale At Leading Radio Dealers

RADIOLAMP

TRADE MARK
LOUD SPEAKER



The Midget
Loud Speaker
With the
Giant Voice
\$8.00

Unusual Volume
Secured by
Scientific Sound
Reflection.

Actual appearance

-and only 5 inches high

AS excellent acoustics carry a man's normal speaking voice to the far corners of a vast cathedral through voice-reflection on a sounding board—

Just so, sound is skillfully reflected from one tonal chamber to another in the small Reflectone whose unique construction also eliminates distortion and amplifies the sound—big.

Made from a beautiful, highly polished material simulating tortoise shell, Reflectone has engaging charm, besides the smallness preferable for home ornamentation.

At your dealers, otherwise send purchase price and you will be supplied postpaid.

Write for descriptive circular.

RICE & HOCHSTER
134 Washington Place New York City

Reflectone

THE MIDGET LOUD SPEAKER WITH THE GIANT VOICE

SEND FOR YOUR FREE COPY

TESTED HOOK-UPS

SUBMITTED BY USERS OF OUR



Price \$1.00
POSTPAID
with instructions

**WONDERFUL
TRANSMITTER**

**BUTTON FOR LOUD
SPEAKERS**

**AMPLIFICATION
AND EXPERIMENTS**

K. ELECTRIC CO.

35 PARK ROW

NEW YORK

24 Pages OUR NEW CATALOGUE 2400 Items

CATALOGUE

JUST OFF THE PRESS

In this terrific complete list of Radio Sets and Parts you will find the latest and greatest patterns on material for building all the best circuits ever made.

Super-Heterodyne - Televisor

Clintondyne - Cockeddy Superdyne

Neurodyne

Electricity Reflex

Electric Reflex

and many others

It also contains, printed on paper and in gold, special paper

with the name of the

Radio News, March, 1925, page

100, 101, 102, 999, 1000




SIMPLEX RADIO SALES CO.
1804 Lafayette Ave. St. Louis, Mo.

Call Letters	Name	Location	Power & Wave Length
WJAM	Seaside Hotel, Atlantic City, N. J.	Atlantic City, N. J.	100-275
WJAS	Courier-Journal and Louisville Times	Louisville, Ky.	500-400
WJAV	Williamson Electrical Specialty Co., Inc.	Washington, D. C.	100-260
WJAZ	Xenonair Polytechnic Inst.	Truy, N. Y.	500-180
WJIB	Steeley School Co.	Kansas City, Mo.	500-411
WJIC	Madison Co.	Cleveland, Ohio	100-275
WJIN	George Schubel, Lute's Store	Tierras Bls., New York, N. Y.	500-260
WJIO	Bar-ers Life Co.	Des Moines, Iowa	500-520
WJIB	Art A. Johnson's Garage	Kochford, Ill.	50-25
WJAC	Galveston Tribune	Galveston, Texas	100-460
WJAB	Howard R. Miller	818 N. Park Ave., Philadelphia, Pa.	810-75
WJAX	Journal Stockman Co.	Omaha, Neb.	750-275
WJX	R & L Electric Co.	McKeesport, Pa.	100-210
WJY	Gimbel Bros.	Philadelphia, Pa.	500-500
WJAB	American Electric Co.	Lincoln, Neb.	800-220
WJAD	Jackson's Radio Engineering Lab.	Waco, Texas	150-100
WJAG	The Norfolk Daily News	Norfolk, Neb.	250-280
WJAR	Clifford L. White	Greenville, Ind.	30-250
WJAM	D. M. Verhagen	311 Third Ave. W., Cedar Rapids, Iowa	20-260
WJAN	Joanna Star	Peoria, Ill.	150-280
WJAR	The Hotel Co.	Providence, R. I.	500-510
WJAS	Pittsburgh Radio Supply Co.	Pittsburgh, Pa.	500-280
WJAX	Union Trust Co.	Cleveland, Ohio	500-370
WJAZ	Chicago Radio Laboratory	Chicago, Ill.	20-260
WJD	Denison University	Granville, Ohio	10-220
WJD	Meuchner, Meuchner	Ill.	500-275
WJY	R. C. A.	New York, N. Y.	750-405
WJZ	R. C. A.	New York, N. Y.	500-450
WRAA	El J. Star	144 Second Ave. E., Cedar Rapids, Iowa	50-275
WRAD	Charles Leoff	Crescent Park, East Providence, R. I.	20-240
WRAP	W. S. Radio Supply Co.	Wichita Falls, Texas	800-360
WRAN	United Battery Service Co.	Montgomery, Ala.	85-220
WRAP	Dexter W. Flint	Cranston, R. I.	50-360
WNAQ	Radio Corp. of Porto Rico	San Juan, Porto Rico	100-260
WKAX	Michigan Agricultural College	East Lansing, Mich.	500-280
WKAY	Lagoon Radio Club	Laconia, N. H.	50-250
WXPY	Dexter W. Flint	Cranston, R. I.	500-230
WEV	W. K. Y. Radio Shop	Okla. City, Okla.	100-360
WLAD	Samuel Woodworth	267 Brown St., Syracuse, N. Y.	100-430
WLAL	Naylor Electrical Co.	Tulsa, Okla.	100-360
WLAP	W. F. Jordan	305 W. H. Jackson St., Louisville, Ky.	50-280
WLAX	Greenleaf Community Broadcasting Sta.	Greencastle, Ind.	10-270
WLRL	Wisconsin Department of Marine	Marine, Wis.	500-270
WLS	Sears, Roebuck & Co.	Chicago, Ill.	500-345
WLW	Cresley Radio Corp.	Cincinnati, Ohio	500-420
WMAC	Chas. H. Meredith	Cleveland, N. Y.	100-260
WMAF	Round Hill Radio Corp.	Danvers, Mass.	100-500
WMAH	General Supply Co.	Lincoln, Neb.	100-250
WMAK	Lockport Board of Commerce	Lockport, N. Y.	500-370
WMAN	First Baptist Church	Columbus, Ohio	10-280
WMAD	Chicago Daily News	Chicago, Ill.	500-445
WMAY	Alabama Polytechnic Inst.	Auburn, Ala.	500-530
WMAY	Kingsbury	Freeburg, Ill.	100-280
WMAR	Merced University	Merced, Cal.	100-260
WMG	Commercial Appeal	Memphis, Tenn.	500-500
WMH	Amannorth-Gates Radio Co.	Cincinnati, Ohio	750-100
WME	Dougherty Hill Electric Co.	Washington, D. C.	100-260
WMAC	Shepard Stores	Boston, Mass.	100-270
WMAD	University of Oklahoma	Norman, Okla.	50-360
WMAL	Omaha Central High School	Omaha, Neb.	20-250
WMAP	Wabens College	Springfield, Ohio	100-275
WMAR	First Christian Church	Butler, Mo.	20-220
WMAT	Leung Bros. Co.	Philadelphia, Pa.	100-360

ZENITH RADIO

—it tunes through everything

Super-Zenith VII

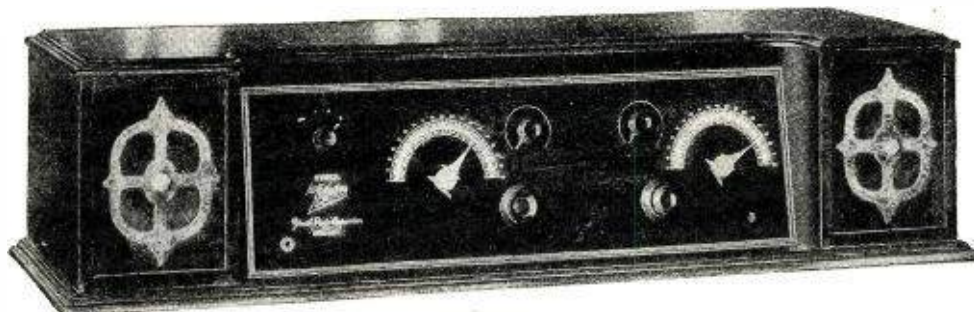

The New SUPER-ZENITH

for people who take pride in their homes

ONE glance at the new Super-Zenith and you are instantly impressed with the sheer artistry of its design, the excellence of its craftsmanship, the superb beauty of its finish—you know that within its case is a receiving set capable of the most extraordinary performance—a receiving set entitled to the place of distinction in the finest home.

Radio enthusiasts: Note that the new Super-Zenith is NOT regenerative. It is a six-tube set in four different models ranging from \$230 to \$550, with a new, unique and really different patented circuit controlled exclusively by the Zenith Radio Corporation. Amplification is always at a maximum in each stage for any wave-length. *The Super-Zenith line is not affected by moisture.* For the first time, you have here a set that—

- 1—tunes through everything and selects the station you really want.
- 2—requires only two hands—not three—to operate.
- 3—brings in each station at only one point on the dial.
- 4—affords such mathematical precision and simplicity that you can run over the entire dial in 1½ minutes and pick up more stations with greater clarity and volume than any other set on the market. Direct comparisons invited.

Write for the name of the nearest dealer from whom you can obtain a demonstration of this outstanding marvel of the radio world.

Dealers and Jobbers: Write or wire for our exclusive territorial franchises.

Zenith Radio Corporation

Engineer Office, 126th Broadway, New York Executive Office, 332 South Michigan Ave., CHICAGO

ZENITH—the exclusive radio of MacMillan for his North Pole Expedition
—Holder of the Paramount Record

Super-Zenith VII (Not regenerative)—6 tubes—2 stages tuned frequency amplification—detector and 3 stages audio frequency amplification. Installed in a beautifully finished cabinet of solid mahogany—44½ inches long, 16½ inches wide, 11½ inches high. Door panels inlaid. Mounting panel of sheet brass, mahogany finish, with scale and indicators in multiple relief. Gold plated pointers, to prevent tarnish. Compartments at either end for six batteries. Can be operated on either wet or dry batteries. Either inside or outside antenna. Price (exclusive of tubes and batteries).....\$230

Super-Zenith VIII Same as VII except—built with mahogany legs of well-proportioned appropriate design, converting model into console type. Price (exclusive of tubes and batteries).....\$250

Super-Zenith IX Same as VII except—built with legs and additional compartments containing built-in Zenith loud speaker on the one side and generous storage battery compartment on the other. Price (exclusive of tubes and batteries).....\$350

Super-Zenith X Contains two new features superseding all previous. 1st—Built-in, patented, Super-Zenith Duo-Loud Speakers, (harmonically synchronized tone speakers and horns) designed to reproduce both high and low pitch tones otherwise impossible with single unit speakers. 2nd—Zenith Battery Eliminator, distinctly a Zenith achievement. Requires no A or B batteries or charger. Price (exclusive of tubes).....\$550

Zenith Radio Corporation

Dept. 128
332 South Michigan Avenue, Chicago, Illinois
Comment: Please send me illustrated literature giving full details of the Super-Zenith.

Name

Address



Adopted by Leading Manufacturers

THE unqualified endorsement of these leading radio manufacturers is in itself the greatest recommendation of Spaulding Bakelite-Duresto quality.



These men know bakelite. They know quality depends solely upon manufacture. They know by actual experience that Spaulding Bakelite-Duresto panels possess high dielectric properties and great strength; that it drills, saws, engraves without chipping; that it will not warp; that it retains an everlasting lustre.

For efficiency and lasting beauty, you should use Bakelite-Duresto. Your dealer can furnish standard sizes, individually packed in Spaulding envelopes, special sizes to order. Look for Bakelite-Duresto panels on the sets you buy.

Write nearest office for descriptive circular.

SPaulding FIBRE COMPANY, INC., TUNAWANDA, N. Y.

Spaulding
BAKELITE-DURESTO
Panels - Sheets - Tube - Rods

Factory: Tunawanda, N. Y.
Sales Office: Washington

401 Broadway Bldg., N. Y. C.
649 W. Lake St., Chicago
111 N. Pennsylvania St., Phila.
15 E. 14th St., New York
210 N. 1st St., St. Paul
111 Second Street, San Francisco
500 First National Bank Bldg., Milwaukee

RADIO DEALERS

Complete catalogue just out.
Right up to the minute.
Nationally advertised and
most wanted sets and parts.

Write for copy and receive
liberal dealer discounts.

Van-Ashe Radio Co.

210 North 10th St. ST. LOUIS, MO.

DEALERS

Sharp Discounts On Standard Quality Parts

Every dealer and builder of sets for remote barbers should have his big business making special handling of standard radio parts, tubes and much more. Write for free catalogue and see your list of orders.


FREE CATALOG

WESTERN RADIO
MFG. CO.
158 W. LAKE ST. CHICAGO

SUPERHERIAL See notes regarding installation on Standard new's designed antenna. Follows dealer, from dealer, distance and low the wonderful advance and the price. When are delivered and installed. All diagrams and material information for sale \$3.00.
I. E. HAMILTON, 7 Weber Street, Boston, Mass.

Call Letters	Name	Location	Power & Wave Length
WNAW	Henry Kunzmann, Box 167, Fort Monroe, Va.		5-150
WNAX	Dakota Radio Apparatus Co., Yankton, S. D.		100-244
WNYC	City of New York, New York, N. Y.		1000-526
WOAC	Page Organ Co., Lima, Ohio		50-266
WOAE	Midland College, Fremont, Neb.		15-280
WOAF	Tyler Commercial College, Tyler, Texas		10-260
WNAI	Southern Equipment Co., San Antonio, Texas		500-185
WOAJ	Evins Electrical Co., Panama, Kan.		15-258
WOAN	Vaughn Conservatory of Music, Lawrenceburg, Tenn.		200-350
WOAR	Henry P. Lusk, Kansas, Wis.		50-225
WQAV	2nd Battalion, 112th Inf., U. S. E., Pa.		50-242
WNAW	Woodmen of the World, Omaha, Neb.		500-526
WUAX	Franklin J. Webb, 600 12th St., San Francisco, N. J.		500-240
WQC	The Palmer School of Chiropractic, Davenport, Iowa		500-464
WQE	Iowa State College, Ames, Iowa		500-350
WQO	John W. Wampler, Phila., Pa.		500-164
WQO	Western Radio Co., Kansas City, Mo.		500-160
WOR	L. R. Harberger & Co., Newark, N. J.		500-405
WOS	Missouri State Marketing Bureau, Jefferson City, Mo.		500-445
WPAB	Pennsylvania State College, State College, Pa.		500-281
WPAC	Donaldson Radio Co., Okla.		800-760
WPAT	Doolittle Radio Corp., New Haven, Conn.		100-268
WPAR	North Dakota Agricultural College, Agricultural College, N. D.		50-263
WPAM	Amerbach & Gustel, Topeka, Kan.		100-275
WPAR	Ward Battery & Radio Co., St. Louis, Mo.		10-276
WPAU	Concordia College, Moorhead, Minn.		30-286
WPAZ	Dr. John E. Koch, Charleston, W. Va.		30-273
WQAA	Harold A. Drake, Jr., Parker, Pa.		500-350
WQAC	Gray Radio Service, Amarillo, Texas		800-234
WQAE	Moore Radio News Station, Springfield, Va.		50-275
WQAP	Sandusky Register, Sandusky, Ohio		5-240
WQAM	Electrical Equipment Co., Miami, Fla.		100-181
WQAN	Scranton Times, Scranton, Pa.		100-281
WQAO	Calvary Baptist Church, New York, N. Y.		100-360
WQAO	West Texas Radio Co., Abilene Daily Reporter, Abilene, Tex.		300-160
WUAS	Prince-Walker Co., Lowell, Mass.		300-266
WQAX	Rick Equipment Co., Joliet, Ill.		300-248
WQJ	Calmer Radio Broadcasting Co., Chicago, Ill.		500-465
WRAP	The Radio Club, Laporte, Ind.		10-214
WRAL	Northwestern Power Co., St. Croix Falls, Wis.		300-226
WRAM	Lombard College, Galesburg, Ill.		300-244
WRAN	Black Hawk Electrical Co., Waterloo, Iowa		10-256
WRAD	St. Louis Radio Service Co., St. Louis, Mo.		10-362
WRAV	American College, Yellow Springs, Ohio		100-242
WRAW	Avenue Radio Shop, Reading, Pa.		10-238
WRAX	Florence Garage, Gloucester City, N. J.		100-268
WRBC	Immanuel Lutheran Church, Valparaiso, Ind.		500-278
WRE	Radio Corp. of America, Washington, D. C.		500-462
WRE	Dorcas Bros. Elec. Co., Hamilton, Ohio		200-160
WRL	Culpeper College, Schenectady, N. Y.		500-362
WRM	University of Illinois, Urbana, Ill.		500-530
WRR	City of Dallas Police and Fire Signal Dept., Dallas, Texas		30-350
WRW	Tarrytown Radio Research Laboratory, Tarrytown, N. Y.		500-273
WSAH	South East Missouri State Teachers College, Cape Girardeau, Mo.		100-362
WSAC	Clemson Agricultural College, Clemson College, S. C.		500-350
WSAD	J. A. Foster Co., Providence, R. I.		100-281
WSAI	United States Playing Cards Co., Cincinnati, Ohio		500-309
WSAJ	Grove City College, Grove City, Pa.		250-740
WSAF	Seventh Day Adventist Church, New York, N. Y.		250-283
WSAR	Dougherty & Welch Elec. Co., Fall River, Mass.		100-254
WSAU	Camp Meridenfield, Chesham, N. H.		10-220

WORKRITE RADIO SELLS WORKRITE

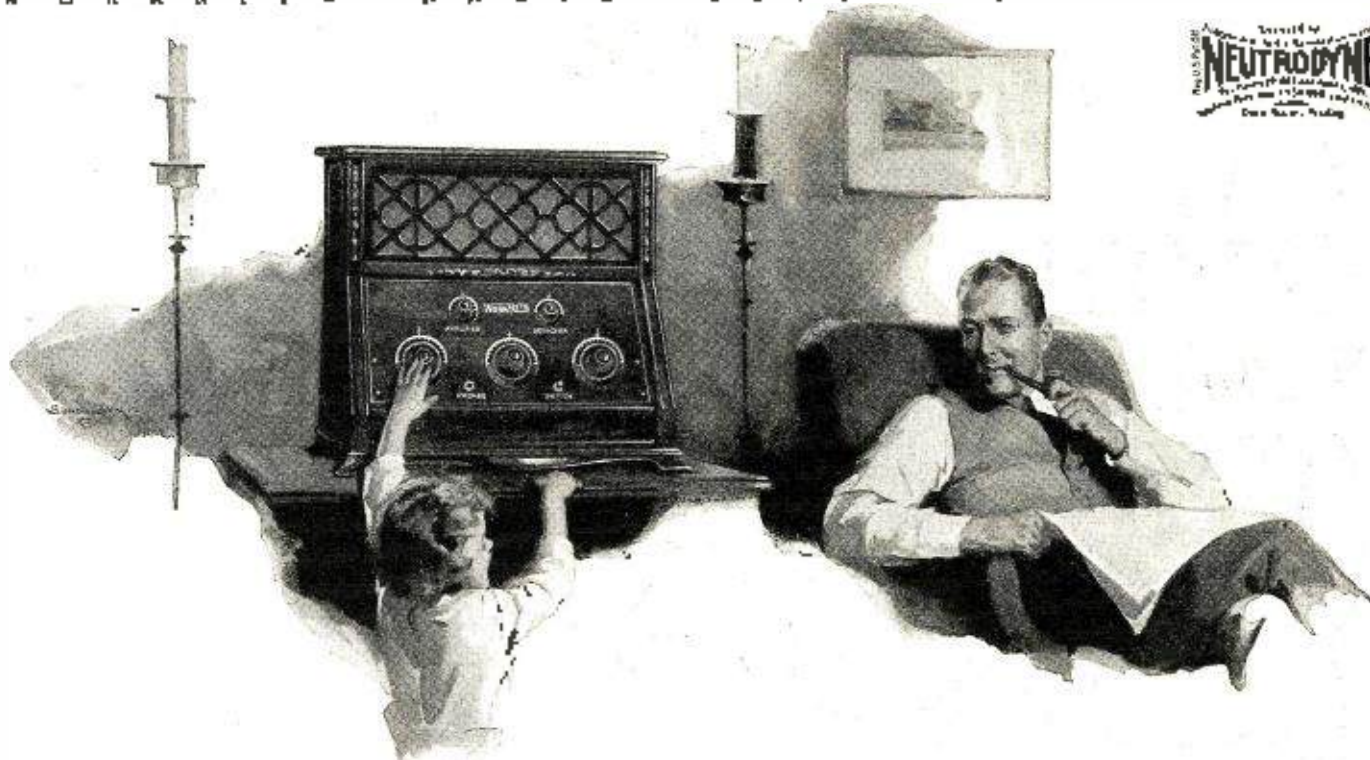

"Look Daddy! I can make music, too!"

Anybody can "make music" with Workrite Super Neutrodyne Receivers. Workrite is so simple to operate and yet so unerring in results that it is a continuous source of delight and fascination for everyone in the family.

Really, if you've never used a Workrite set you'll be astonished to learn how easy it is to get—and hold—any station you want. You'll find no provoking interruptions, no irritating discords. And once you have tuned in a station you can get it instantly at any time, simply by using your previous dial settings.

Workrite positively assures an unusually vigorous reception with all the original depth and clarity of tone—unmarred by howls, whistles and other disturbing noises.

Another Workrite superiority that's a revelation even to experienced radio fans, is the astounding selectivity of these superb sets. Just a slight turn of the dials tunes out the most powerful local stations—and keeps them out. If you live in a city you know what an advantage that is.

Then there's Workrite's exceptional range! Under favorable

conditions it will easily span the continent for you. Even distant stations come in regularly and distinctly on the loud speaker.

There are other Workrite advantages, of course. The ingenious super neutrodyne "hook-up"—the fine materials that we use—the painstaking care given to building each individual Workrite set—all these combine to make receivers that establish a brand new peak in radio performance.

Don't be disappointed if the dealer you visit can't demonstrate Workrite for you. Workrite has won such tremendous popularity both among novices and experienced operators that most stores find themselves pressed to meet the demand.

So, if the one you visit hasn't Workrite in stock, write us and we will send you the name of a store that has. Also, if you want a beautifully illustrated rotogravure folder, giving full information on all Workrite models, fill in the coupon below and send it to us. You'll get the booklet by return mail.

But above all, know what Workrite will do before you invest another dollar in radio.

WORKRITE ARISTOCRAT

A 3-tube Neutrodyne Set
In this beautiful mahogany console, the loud speaker is placed on one side and controls for A and B receivers on other side. All controls non-adjustable with cable and plug. A set unsurpassed in any price range. Price, without accessories \$350



Send Coupon for FREE
Rotogravure Booklet

The Workrite Manufacturing Co.
1825 East 25th Street, Cleveland, Ohio

Please send me FREE a copy of the
rotogravure booklet which describes Workrite

Name
Address
City State



WORKRITE AIR MASTER

A 3-tube Neutrodyne Set
Encased in genuine brown mahogany cabinet with graceful sloping panel. Almost identical with Workrite Radio King, shown in main illustration, except the latter has a loud speaker built into cabinet.

Prices:
Air Master, in above appearance, \$160
Radio King, without accessories, \$220

WORKRITE CHUM

A 3-tube Neutrodyne Receptor Set
Similar to Air Master in appearance. Equal in tube sets in performance. Cabinet provides space for both A and B receivers.

Price, without accessories \$175

THE WORKRITE MANUFACTURING COMPANY
1406 EAST 25TH STREET CLEVELAND, OHIO

Districts: Chicago, 316 Lake Shore Drive; Los Angeles, 238 South Los Angeles Street

WORKRITE

SUPER NEUTRODYNE RADIO SETS

The people's choice

De Roy

Phusiformer

Manufactured under license

The public have long been waiting for a **UNIFORM, PROGRESSIVE SYSTEMATIC** method of set building. The De Roy Phusiformer embodies this advancement.

You can start with one De Roy Phusiformer, building a crystal or 1 tube set and add additional units until the ultra 5 or 6 tube receiver is completed—**STEP BY STEP**. Eliminates tremendous cost at outset. You pay as you build—you waste nothing. Fifty or more circuits can be constructed.

Simplicity of construction and exceptional performance, are the distinguishing features. Built on entirely new principles which overcome **ALL** the drawbacks of present-day receivers.

Write for literature.

DE ROY RADIO CORPORATION

284 Plane Street Newark, New Jersey, U. S. A.

Call Letters	Name	Location	Power & Wave Length
WBAV	Clifford W. Vick Radio Construction Co.	Houston, Texas	100-167
WBAZ	Chase Electric Shop	Pomeroys, Ohio	50-258
WSE	Atlanta Journal	Atlanta, Ga.	500-420
WEL	J. & M. Electric Co.	Ulica, N. Y.	10-273
WSE	School of Engineering of Milwaukee	Milwaukee, Wis.	100-244
WSY	Alabama Power Co.	Birmingham, Ala.	500-500
WTAB	Fall River Daily Herald Pub. Co.	Fall River, Mass.	100-250
WTAC	Penn Traffic Co.	Johannstown, Pa.	150-215
WTAF	Louis J. Gallo	2222 Lafayette St., New Orleans, La.	10-268
WTAF	The Radio Shop	Portland, Me.	10-250
WTAL	Toledo Radio & Elec. Co.	Toledo, Ohio	10-252
WTAM	Willard Storage Battery Co.	Cleveland, Ohio	1000-100
WTAP	Cambridge Radio & Elec. Co.	Cambridge, Ill.	50-242
WTAQ	S. H. Van Gordon & Son	Duane, Wis.	100-154
WTAR	Reliance Elec. Co.	Norfolk, Va.	100-280
WTAS	Charles E. Eubank, R. Y. D.	6, Box 75, Elgin, Ill. (near)	500-236
WTAT	Edison Electric Illuminating Co.	Boston, Mass. (prophetic)	100-244
WTAU	Ruggs Battery and Electric Co.	Tecumseh, Mich.	10-242
WTAW	Agricultural & Mechanical College	College Station, Texas	250-280
WTAX	Williams Hardware Co.	Sarasota, Fla.	50-233
WTAY	Oak Leaves Broadcasting Station	Oak Park, Ill.	500-283
WTAZ	Thomas J. McGuire	Tambrville, N. Y.	15-253
WTG	Holland State Agricultural College	Manhattan, Kan.	50-273
WTH	H. G. Sael Co.	Chicago, Ill.	10-263
WWAD	Wright & Wright, Inc.	Philadelphia, Pa.	100-360
WWI	Ford Motor Co.	Dearborn, Mich.	250-273
WWJ	Detroit News	Detroit, Mich.	500-517
WWL	Loyola University	New Orleans, La.	5-280

BROADCAST STATIONS OF AUSTRALIA

- 1 VA Auckland Radio Service, Ltd., Auckland—500 watts; 260 meters.
- 2 VK Dominion Radio Company, Ltd., Wellington—300 watts; 273 meters.
- 4 VO Radio Supply Company (Norman Arundell), Dunedin—500 watts; 270 meters.
- 6 VA British Electrical and Engineering Co. (J. J. O'Brien), Dunedin—500 watts; 270 meters.
- 2 VBI Gisterna Radio Company, Gisborne—500 watts; 265 meters.
- 1 VB Pearson, Charles Henry (on behalf of Newcombe, Ltd.), Auckland—500 watts; 260 meters.
- 2 VD Wellington Broadcasters, Ltd., Wellington—500 watts; 275 meters.

EXPERIMENTAL STATIONS

- 4 XD Professor Robert Jack Alur University of Otago, Dunedin—50 watts; 305 meters.
- 2 XB Victoria University College, Wellington—50 watts; 305 meters.
- 1 AH Harila Gray & Co.

BROADCAST STATIONS IN FOREIGN COUNTRIES

Austria—Vienna (Radio-Hekaphon), 600 meters.

Belgium—Brussels, BAV, 1,100 meters, at 2 and 6.50 p. m., meteorological forecast. Brussels (Radio Electrique), 265 meters, daily at 5 to 6 p. m., concert at 8 to 8:15 p. m., general talk at 8:15 to 10 p. m., concert.

China—Macao (Portuguese colony), no particulars available except that an excellent station of high power is located there.

Czechoslovakia—Prague, PRG, 1,800 meters, 8 to 12 a. m. and 4 p. m., meteorological bulletin and news; 4,500 meters, 10 a. m., 3 and 10 p. m., concert. Khejly (near Prague), 1,150 meters, weekdays 7:15 and 10 p. m., Sundays 11 to 12 a. m., concert and news. Brunn, 1,800 meters, 10 to 11 a. m., concert, 2:30 p. m. news.

Denmark—Lyngby, OXE, 2,400 meters,

The Standard of the World

The 688-7238

Freshman Variable Grid Leak

is the standard for those who build their own sets. It is the most compact and having superior action it always remains unaffected by any climatic conditions.

Complete with silver 49428 or .0005 Freshman Condenser—\$1.00 without condenser..... 75

Any dealer, advertiser and postpaid price and you will be supplied postpaid

Chas. Freshman Company, Inc.
300, 302 Ave., New York

AMERICAN BRAND CONDENSERS

with the

~100 to 1~

Worm Drive Vernier

Finest Condenser Made

and the

Greatest Radio Value

Offered the Public

23 PLATE only \$5.00 In Canada \$7.00

AMERICAN BRAND CORPORATION
NEWARK, N. J.



AN Ultradyne receiver operating in New York City easily tunes out the powerful broadcasting of WOR, Newark, N. J.—495 meters and brings in WDAF, Philadelphia—395 meters; PWX Havana, Cuba—400 meters; WDAF Kansas City—411 meters.

Regardless of close similarity in wave-length, the Ultradyne selects any station within range—brings in broadcasting clearly, distinctly, faithfully.

In addition to this Ultra-selectivity, the Ultradyne is the most sensitive receiver known. It employs the "Modulation System" of radio reception, the achievement of Mr. R. E. Lacault, F.E., A.M.I.R.E., Consulting Engineer of this company and formerly Radio Research Engineer with the French Signal Corps Research Laboratories.

The "Modulation System" responds to weaker signals than the conventional method of detection—because it provides greater rectification. Weakest signals are made to operate the loud speaker.

Ultravision performance is the crux of the radio industry.

Write for descriptive circular

PHENIX RADIO CORPORATION

3.7 Beekman Street

New York

ULTRADYNE

MODEL L-2



Modulation Plus Regeneration In the New Ultracyn®

To the "stimulation system" of radio reception, R. V. Lavut has successfully applied the use of regeneration in the new Model L-2 DL. GRADYNE.

The result is ultra-sensitivity never before thought possible. The use of regeneration produces tremendous amplification, such a more noticeable when receiving weak signals.

The Radio Section of the U. S. Bureau of Standards has proven by actual measurement that the generation becomes more effective as the received signal diminishes in strength.

Regeneration applied to the "Modulation System" allows the ULTRADYNAMIC to respond to an extremely small amount of energy. This energy is further amplified thousands of times by the intermediate frequency amplifier before it is detected and made audible. This amplifier is designed for maximum efficiency without distorting the tone or quality of music and speech.

The reception of distant stations is only limited by atmospheric conditions and ranges beyond the control of Model 1.3 ULTRA-ORANGE.

Loud Speaker Reception Using Loop Aerial

Efficient loud speaker reception using a loop aerial is possible with the Model 1-2 ULTRADYNE. Ordinarily loop reception is considerably less efficient than an outside aerial. However, the application of regeneration to the "Modulation System" reduces the resistance of the loop circuit, thereby allowing the loop to pick up fainter signals.

The use of a loop also increases selectivity and decreases static and other interference.

How to Build the New Model

This 32-page illustrated book gives latest authentic information on drilling, wiring, assembling and tuning the new Model L-2 Ultracyc. This book explains the "Magna-



lution System" in detail and also deals with the application of regeneration to this new system of radio reception.

It is edited by R. T. Lescage, inventor of the Ultradyne Receiver. Price 50c.

**Model L-2 ULTRADYNE
Kit Is Ready**

This is the new Model 1-2 Ultradyne Kit which contains one low loss tuning coil and one low loss Oscillator Coil, one special low loss Coupler, one true "A" Transformer, three




The Ultratronics are new improved

\$30.00

\$30.00 Each long wave radio frequency transformer, especially designed by R. E. Luciak.

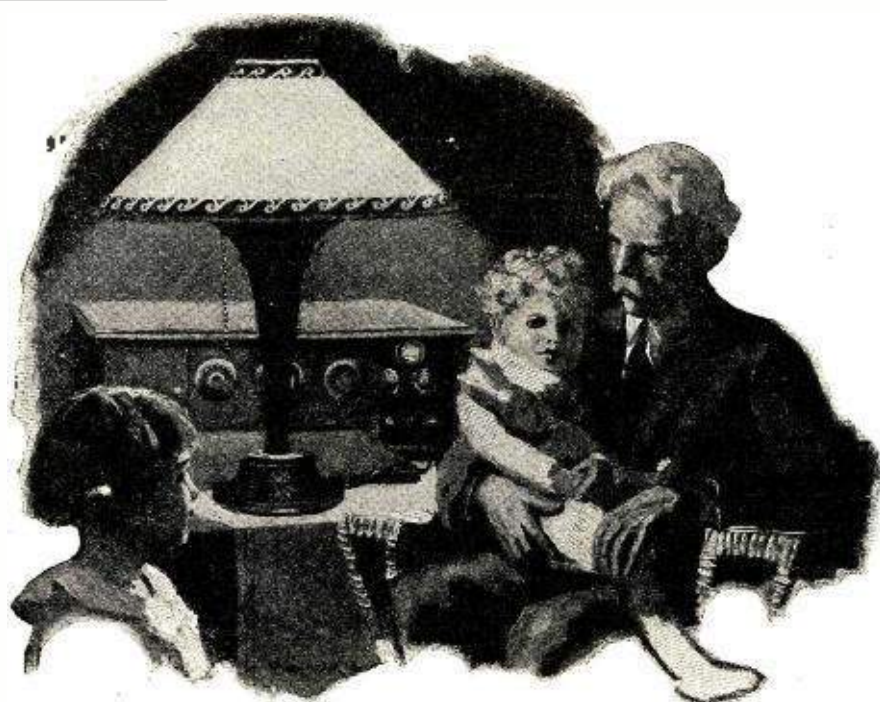Inventor of the Ultraform. As a precaution against substitution, R. E. Luciak's personal monogram seal (R.E.L.) is placed on all genuine Ultraforms. All Ultraforms are guaranteed to last as this seal remains undisturbed—forever.



—let this companionable Radio Gift brighten your home Christmas!

In keeping with the age-old beauty of the Christmas sentiment itself, Thor Speaker Lamp, by its radiant beauty, expresses the spirit of the holiday season.

Fulfilling the demand for grace and utility in a radio loud speaker, Thor Speaker Lamp is truly a decorative factor in home furnishing. Its beautiful shade of parchment, or silk (any color), and its well-proportioned base of antique styled polyethylene gold veritably breathe the atmosphere of Yuletide companionship.

In appearance, Thor Speaker Lamp gives no suggestion that within its housing is hidden a marvelous speaker unit that reproduces vocal and instrumental tones, as clear, as absolutely true, as though the individual or instrumental, stood in the room.

Thor Speaker Lamp is bi-directional. Feet from the gurgler, throaty sounds protest

to all horn-type loud speakers, it distributes its mellow tones to all parts of the room with equal volume and clarity. You do not have to sit at foot of a horn to hear distinctly.

Abundant with Christmas cheer and happiness, Thor Speaker Lamp, by the evocation of its tapestry and wafts friendly light, is sure to bring forth the admiring comment of young and old, as a gift. Indeed, it is a radio gift that brightens the home.

Your dealer has Thor Speaker Lamp in both floor and table lamp models. Table Lamp, \$33.00. If your dealer cannot supply you send us your name and address and we will ship one by prepaid express. Return at cost expense, if not satisfied.

Franchises in certain territories still open. Jobbers and dealers are invited to write for literature and full details.

THOR Radio Division of the Golden Gate Brass Mfg. Co.
1239-1243 Sutter Street, San Francisco, California

THOR SPEAKER LAMP

1111

NO SOLDERING NECESSARY

WHEN
YOU USE THE



BAKELITE
JACK

Look for the
Green Cico Box



An improved new principle. Moulded completely from bakelite. No metal in frame construction. Shock springs of special phosphor bronze which is non-corrosive. Sterling silver contact points assure perfect contacts. Scientifically perfect in every detail. Something well worth all the pride you will take in it.

CONSOLIDATED INSTRUMENT CO. OF AMERICA, INC.
41 East 42nd Street, New York, N. Y.

ALL CICO RADIO PARTS ARE
UNQUALIFIEDLY GUARANTEED

CICO Bakelite Rheostat, Plain, \$1.35; Variable, \$1.50
CICO 2-Way Plug, 40c CICO Automatic Plug, 75c

No. 30 Single circuit open ... \$2.00
No. 31 Single circuit closed85
No. 32 Double circuit90
No. 33 "A" Battery Switch40

8:30 to 9:45 p. m. weekdays, 8 to 9 Sunday concert.

France.—Paris (Eiffel Tower), FL, 2,600 meters, 7:40 a. m. weather forecasts, 11 a. m. Sunday; 10:45 a. m. cotton prices, 12 noon market report; 12:35 to 12:50 weekdays, time signal and weather forecast; 3:40 p. m. financial reports; 5:30 p. m. Bourse closing prices; 6:15 p. m. concert; 8 p. m. weather report; 9 p. m. Wednesday and Sunday concert; 10:10 p. m. weather forecast. Paris (Radio Paris), SPB, 1,780 meters; 12:30 p. m. cotton prices and news; 12:45 p. m. concert; 1:30 p. m. Exchange prices; 4:30 p. m. financial report; 5 p. m. concert; 8:30 p. m. news and concert. Paris (Ecole Supérieure des Postes et Télégraphes), 450 meters, 3:45 p. m. Wednesday talk on history; 8 p. m. Tuesday English lesson; 8:30 p. m. concert; 9 p. m. relayed concert or play. Paris (Station du Petit Parisien), 340 meters, 8:30 p. m. tests.

Germany.—Berlin (Königsplatzhaus), LP, 2,370 meters, Sunday 10:40 to 11:45 a. m. concert, 4,000 meters, 7 to 8 a. m. music and speech; 12:30 to 1:30 p. m. music and speech; 5 to 5:30 p. m. news. Eberswalde, 2,930 meters, daily 1 to 2 p. m. address and concert; 6 to 7:30 p. m. address and concert; Thursday and Saturday 7:20 p. m. concert. Berlin (Vox Haus), 430 meters, 11 a. m. stock exchange, 1:55 p. m. time signals; 5:40 to 7 p. m. concert; 7 to 8 p. m. Sunday, concert. Breslau, 415 meters. Frankfurt am Main, 467 meters, 7:30 to 10 p. m. tests, graphophone records. Hamburg, 392 meters. Königsberg, 460 meters. Leipzig (Mitteldeutsche Rundfunk A. G.), 452 meters. München (Die Deutsche Stunde in Bayern), 485 meters. Stuttgart, 437 meters.

Great Britain.—Aberdeen, 2B1, 405 meters. Birmingham, 31T, 475 meters. Bournemouth, 6B3L, 385 meters. Cardiff, 5WA, 351 meters. Chelmsford, 5XX, 1,600 meters, weekdays, 11:30 a. m. to 12:30 p. m., 4:30 to 5:30 and 7:30 to 8:30 p. m. tests. Edinburgh, 2FH (relay), 325 meters. Glasgow, SC, 420 meters. Leeds-Bradford, 2LS (relay), 346 and 310 meters. Tuesdays, Thursdays and Fridays, 1 to 2 p. m. (2LO only), regular daily programs, 3 to 7:30 p. m., 8 to 11:30 p. m., Sundays, 3 to 5 and 6:30 to 10:30 p. m. Liverpool, 6LV (relay), 318 meters. Manchester, 2ZY, 375 meters. Newcastle, 5ND, 400 meters. London, 2LO, 365 meters. Plymouth, 3PY (relay), 335 meters. Sheffield, 6FL (relay), 303 meters.

Holland.—Amsterdam, PA5, 1,050 meters (irregular). 8:40 to 10:10 p. m. concert. Amsterdam (Vas Diaz), PCFF, 2,000 meters, 9 a. m. to 5 p. m., share market report, exchange rates and news. Hilversum, 1,050 meters, 9:10 to 11:10, Sunday, concert and news. IJmuiden (Middelwaard), PCMM, 1,050 meters, Saturday, 9:10 to 10:40 p. m., concert. The Hague, PCGG, 1,070 meters, 4-6 p. m., Sunday 9:40 to 11:40 p. m. Monday and Thursday, concerts. The Hague (Velthuisen), PCKK, 1,050 meters, 9:40 to 10:40 p. m., Friday, concert. The Hague (Heussen laboratory), PCUL, 1,050 meters, 10:40 to 11:40 a. m., Sunday, concert; 9:40 to 10:40 p. m., concert; 8:45 to 9 p. m., Thursday, concert.

Italy.—Rome, 1CF, 3,200 meters, weekdays, 12 a. m., 1,800 meters, 4 and 8:30 p. m. tests and graphophone records.

Portugal.—Lisbon (Aero Lisboa), 370 to 400 meters, Wednesdays and Fridays, 9:30 to 12 p. m. irregular tests.

Spain.—Carragena, FBX, 1,200 meters, 12 to 12:30 and 5 to 5:30 p. m. lectures and concerts. Madrid, PTT, 400 to 700 meters, 6:08 p. m. tests. Madrid (Radio

ATWATER KENT LOUD SPEAKERS

Bring Out the Best from Any Set

TO the never ceasing thrill of your radio;
Add a final touch—the ATWATER KENT
Loud Speaker.

Radio Reception is for all your family to hear—free them from the bondage of ear-phones. Let the music pour forth into your home from some far distant orchestra.


Your ATWATER KENT Loud Speaker will faithfully recreate the notes of every instrument, from the sweet piping of the piccolo to the deep, booming chords of the bass viol.

It is this natural reproduction of sound that is the basis of ATWATER KENT Loud Speaker success.


In the little niceties of design, and in the use of correct material for every part, lie the secrets of this new joy in radio. It is living music, clear and generous in volume, made possible by fine materials and master workmanship.

You'll always remember the day you took home an ATWATER KENT Loud Speaker. Your dealer has three models for your selection.

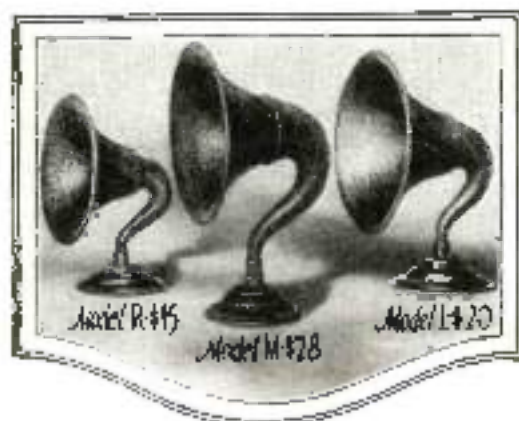ATWATER KENT MANUFACTURING COMPANY
4223 Wisconsin Ave., Philadelphia, Pa.



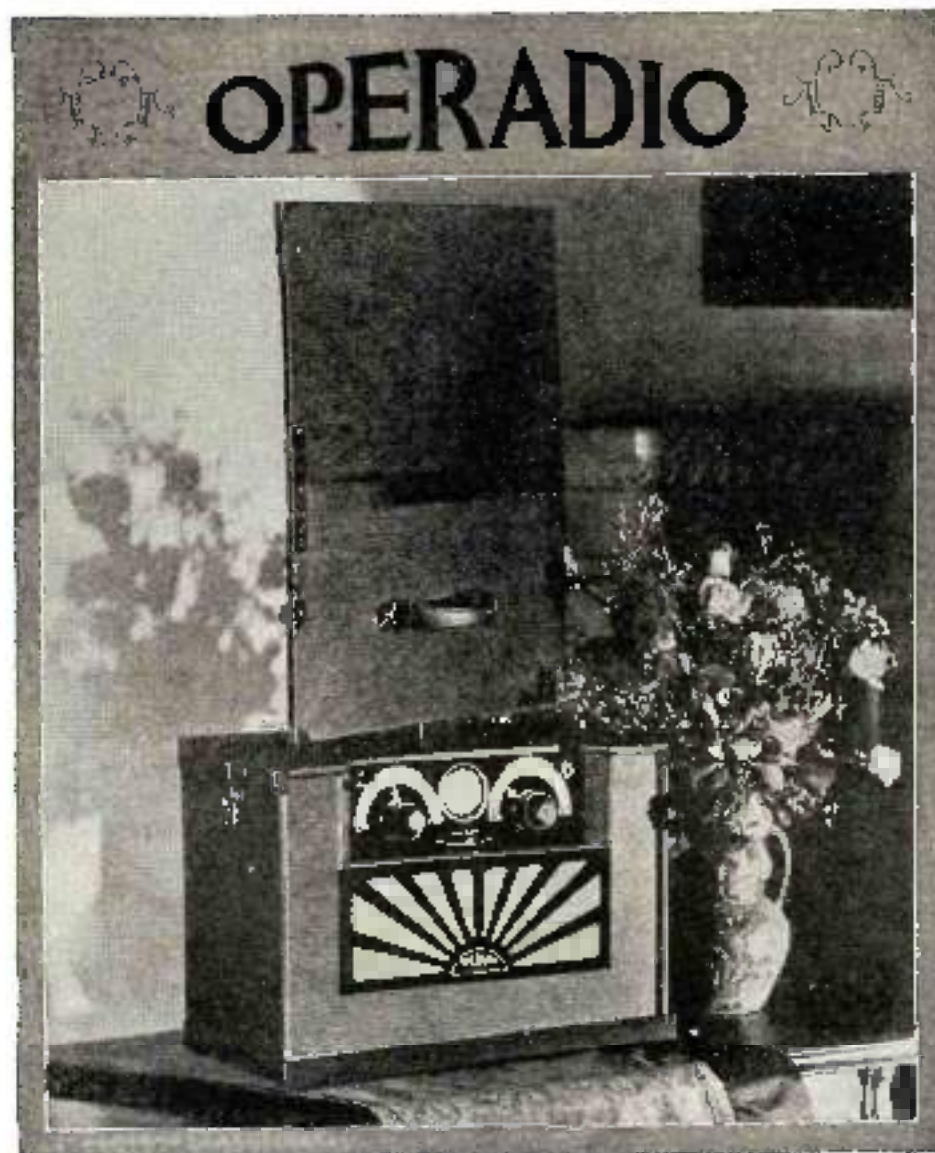Atwater Kent Loud Speaker made by the makers of Atwater Kent Recording Sets.



Everything You Want in a Radio Set

PERFORMANCE—BEAUTY—AVAILABILITY—the three things you really want in a radio set, are offered to a new degree in the 1925 Operadio.

The efficiency of this compact receiver has called forth the highest praise—clear, natural tone, range, volume and selectivity, simplicity of operation and reliability under severe conditions.

In its attractive new case, the Operadio conforms to the most discriminating standards of good taste—harmonizing with the most beautiful surroundings.

DEALERS: The Operadio Sales Franchise is granted, worldwide, including A.R. for details.

THE OPERADIO CORPORATION :: 6 South Dearborn Street, Chicago

And, in addition, the Operadio has been specially designed that it may be readily connected to any part of the house, or easily taken along when travelling or visiting.

This set contains a self-contained No. 1 aerial, ground or outside connections of any kind required. A patented wave-bridge in the cover replaces the "loop" used on some sets. Loud speaker, six tubes, exceptionally large supply of dry cell batteries and all parts are fitted into the cabinet.

Write for an illustrated folder giving complete particulars.

Iberica), 392 meters, daily, except Thursdays and Sundays, 7 to 9 p. m. Thursdays and Sundays, 10 to 12 p. m., concert. Madrid, 1,800 meters, irregular.

Sweden.—Döla, 2,800 meters, Tuesdays and Fridays, 5:30 to 7:30 p. m., Sundays, 5:30 to 6:30 p. m., concert and news. Gothenburg (Nya Varvet), 700 meters, Wednesday 7 to 8 p. m. Stockholm (Radiolagret), 470 meters, Tuesdays and Thursdays, 8 to 9:30 p. m., concert and news. Stockholm (Telegrafverket), 440 meters, daily 12:45 to 1 p. m., weather report and Nava's time signal; Monday, Wednesday and Saturday, 8 to 9 p. m., concert and news; Sunday 11 a. m. to 12:30 p. m., divine service from St. James Church.

Switzerland.—Geneva, 1,100 meters, weekdays, 11:15 and 8 p. m., concert or lecture. Lausanne, HD2, 850 meters, daily, 9:15 p. m., concert and address.

—Abstracts Radio Service Bulletin.

(All schedules given in time of locality)

What's What About Radio Horns

(Continued from page 941)

horn he would shop for days until he found one that would stir his sense of musical values. Many fans assemble their collections with great care, choosing their transmitters, sockets and vacuum tubes with finer pains, and yet buy the first radio horn they see. The chances are about 95 to 1 that they buy the wrong horn and then wonder why the quality of the reproduction is so poor, never once thinking that their troubles might be located in such a simple thing as the horn. To many people a horn is simply a horn, but these people do not fully appreciate the peculiar properties of sound waves and their associated phenomena.

Experimentation has caused the sound physicist to vote the metal horn out of order. Regardless of its design it is responsible for a tinny tone and is altogether too resonant to be suitable. A horn should be made out of a non-resonant material such as wood, fibre or paper mache.

There are a lot of other fallacies about loud speakers. They are called amplifiers by those who do not understand their operation. Just how they amplify is quite a mystery as we are to still maintain our respect for the law of the conservation of energy. If a horn can be made to amplify, why use vacuum tubes? The truth of the matter is that they do not amplify. They concentrate and condense. When we take the horn from our loud speaker unit, the sound waves it produces spread out in all directions, just like an electric light without a shade. When we put an electric light in front of a reflector the light is concentrated and shoots off in one direction. Such a light can be seen a greater distance than a light that is shooting its rays off at all points of the compass. As proof of this, look at the railway signals. A radio horn acts in much the same manner. When it is put over the loud speaking unit the sound waves are concentrated and they come forth in much the same way that they leave the mouth of a person.

As the author has said, many of the great sound physicists are in thorough disagreement regarding the phenomena associated with horns, or megaphones as they are called. One peculiar thing about them is that the sharp things appear to amplify at both ends. When the sound is put into the small end it comes forth from the large end apparently increased in volume, and when a deaf person puts the small end to his ear and the sound goes in the large

MAILED ABSOLUTELY GUARANTEED



Double Dutch D-123, 10-12, 15-12, 18-12, 21-12, 3540-12, 3543-1



The New Goodrich V. T. Socket

A Spring Lock—No Turning or Twisting the Tube

The socket in which the tube can be either inserted and fastened or unfastened and removed without turning or twisting.

A spring lock—an exclusive Goodrich feature—accounts for this tremendous socket improvement.

Tube locks automatically when inserted—touch the spring lock . . . it is released.

"Wiping" type contacts automatically cleaned when tube is inserted—can be further cleaned without unlocking tube with slight turn back and forth.

Completely eliminates danger of tube breakage due to forgetting which way to turn tube to unlock it—a vast improvement over bayonet lock style.

Socket construction of specially treated hard rubber—so dielectric losses are much lower than in sockets made of other materials. Furnished complete with all fittings. Get the new and improved Goodrich V. T. Socket today.

THE B. F. GOODRICH RUBBER COMPANY
Akron, Ohio

ESTABLISHED 1870

Goodrich V.T.Socket

A CHRISTMAS PRESENT

*that any fan
would like
to give
himself*



WHAT present could you give yourself that would please you more than a dependable battery charger? No more spilling acid on the carpets from dragging batteries through the house. No more battery-going-dead on the very evening when you particularly want your set working. No more relying on outside help for the entertainment energy in your battery—help you can't get when you most need it.

The Radio Unitron—made just as suggested and efficient as the big Unitron Industrial Battery Chargers—supplies the answer to this important Radio problem. It assures the lover of Radio, entertainment unbroken by a battery going dead without warning.

The Unitron Radio Battery Chargers are made in two sizes—a smaller one for small sets, and a large one for multi-tube sets. Both are efficient—each is simple, safe and economical. Economy is important in a Radio charger. It must do its re-charging without wasting current, and it must be so built that it never needs repairing or adjusting.

The Unitrons are low-loss chargers. They waste no current—and that means quicker re-charging at lower cost. They have no moving parts to be adjusted, repaired or replaced—no mechanism to get out of order—and this means there never are repair bills.

An ideal Christmas present. Either size. And one that will last as long as Radio.

Fool-proof, requiring no attention whatever, self-regulating and guaranteed fireproof by the National Board of Fire Underwriters, a Unitron is a delightful Holiday gift whether you give it or get it.

Fig. 1

Send for the Story:

"A Little Less Noise.... Please"

Model No. \$18

Charges any type of A battery



Model No. \$34
Charges A and B batteries and automobile batteries

FOREST ELECTRIC COMPANY

Pioneer Manufacturers of Industrial Current Rectifiers

New and Wilsey Streets

Newark, New Jersey

Authorized by Patent Office, U. S. P. O.

Greater Distance. Less Noise

TURN-IT

ADJUSTABLE
GRID LEAK



Only \$1.00 at Your Dealers, or Direct From Us.

TURN-IT RADIO SALES, Inc.
71 Mulberry St., N. Y. C.

BROWNIE

CRYSTAL

Guaranteed the Best



\$1.00

"REFLEX SPECIAL"
QUICK CONTACT
RECTIFIER

Withstands Heavy Plate Voltage
The Arco Associates Co. has "proved" detection and tuning by using a BROWNIE CRYSTAL IN REFLEX SETS.

Order From Your Dealer or Direct

ROLAND BROWNIE & CO.
22 Broadway Street

Weymouth, Mass.


end it would also appear that amplification is effected.

Let us hear what Lord Raleigh has to say in his famous book, "The Theory of Sound." "The case of progressive sound waves moving in a tube of variable section is also interesting. In its general form the problem would be one of great difficulty, but where the change of section is so gradual and no considerable alterations occur within a great many wave-lengths, the principle of energy will guide us to an approximate solution. It is not difficult to see that in the case supposed, there will be no sensible reflection of the wave at any part of its course, and that the energy of the motion must remain unchanged. From which it follows, that, as the waves advance, the amplitude of vibration varies inversely as the square root of the section of the tube. In all other respects the type of vibration remains absolutely unchanged. From these results we may get a general idea of the action of an ear trumpet. It appears that according to the ordinary approximate equations there is no limit to the concentration of sound which may be produced in a tube of gradually diminishing section."

Needless to say, there are lots of physicists who do not agree with Lord Raleigh. In this connection it is interesting to briefly review the work of a man who has recently actually photographed sound waves as they originate and leave various shaped horns. This man is Arthur L. Foley. Mr. Foley holds that seeing is believing. He became tired of reading the contradictions of sound physicists, so he rigged up an electrical apparatus which will allow him to photograph sound waves. The device is extremely simple and we see it pictured in the sketch. In place of using the regular conical shaped horn, Mr. Foley employed what would amount to a cross-section of a horn. This cross section he made up of brass plates. In the sketch AA are spark gaps and BB condensers. C is another spark gap employed for illumination purposes. D is another condenser, and E is a photographic plate. In the center of the dummy horn there is another spark gap which is used primarily to set up the sound waves. The whole device is operated from a small spark coil. When a spark passes across the gaps a shadow of the horn is thrown upon the photographic plate by the light-giving gap C. This throws not only a shadow of the horn, but of the sound waves as well. Since we know that sound effects the density of air it is evident that the light will also leave an impression of the waves. In some of the photographs attached, Figs. 2 to 7, Mr. Foley shows the successive stages of an expanding wave, the average time interval between each of the six wave processes being about a 300,000th of a second. The pictures show that there was energy reflected in every wave, except when the wave front was at right angles to the surface of the air parallel to the surface of the tube. During these experiments Mr. Foley brought forth the fact that the condensing power of a horn is not the quotient of the area of the two ends, that it is not even of the order of magnitude in the size of horns of considerable angle.

Mr. Foley's general conclusions follow:

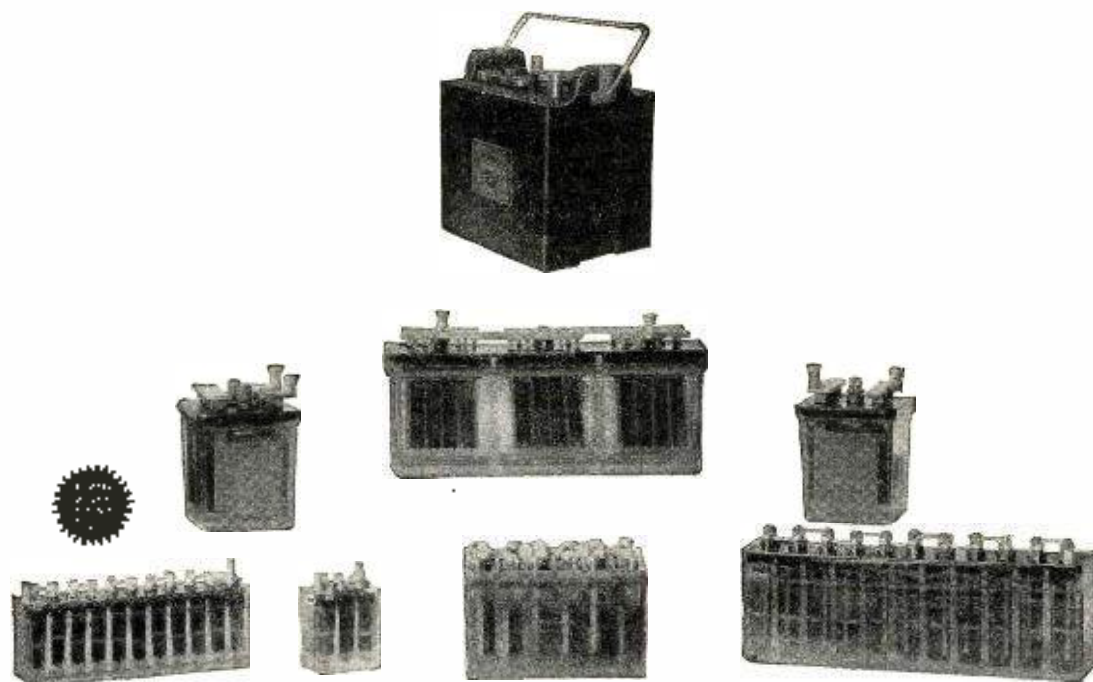1. The amplifications of sound at the small end of a conical receiving horn is due to peak resonance and condensation.
2. The amount of sound energy "condensed" at the small end of a conical horn receiver is but a small fraction of that demanded by the "condenser" theory. This theory is not tenable.
3. Sound pulses do not "glide around bends" in tubes and "slip" along starting walls "without appreciable reflection." There is reflection at a surface wherever the molecules of air next the surface vibrate in any direction not parallel to that surface.



A BATTERY FOR EVERY RADIO NEED

It makes no difference what set you are using, whether one or nine tubes, whether two or six volts, single or multiple circuit, regenerative or reflex, or one of the numerous "dynes," there is a Westinghouse Rechargeable "A," "B" or "C" Battery to fit it.

Furthermore: If you are not already a user of Westinghouse Radio Batteries, you have no idea of the increased economy, reliability and all-around satisfaction to be had by using storage batteries, particularly Westinghouse Batteries, for all receiving sets.

WESTINGHOUSE UNION BATTERY COMPANY
SWISSVALE, PA.

Distributor for South America, Mexico and Cuba
THE WESTINGHOUSE ELECTRIC INTERNATIONAL COMPANY
Mexico City, Buenos Aires and Havana

Distributor for Canada
CANADIAN WESTINGHOUSE CO., LTD.
Offices in all principal Canadian Cities

WESTINGHOUSE

RADIO

"A," "B" and "C"

BATTERIES



ADLER-ROYAL 199 Operates on dry cells. Price \$165.00.

A 5-tube Neutrodyne that operates on dry cells

YOU may have your choice of two different styles of Adler-Royal Neutrodyne. Set 201A operates with the usual storage battery. Set 199 operates on dry cells. This is an achievement that has baffled radio engineers since the introduction of Neutrodyne.

Adler-Royal Neutrodyne also has separated the control for radio frequency and audio frequency. In simple language this means that with Adler-Royal, when

a station is amplified, the desired tone quality and volume is controlled without detuning or distortion.

Not only their beauty of cabinet design but the workmanship and simplicity of the sets themselves are outstanding features of Adler-Royal.

Adler-Royal is on exhibit only at the higher class stores whose reputation is an additional guarantee of the quality of the Royal line.

ADLER MANUFACTURING COMPANY, INC.
General Sales Office: 881 Broadway, New York City
Factories: Louisville, Ky.



One of the three cabinet sizes of Adler-Royal Combination Radio and Phonograph Cabinet Model 10. Price \$300.00.



The Adler-Royal Neutrodyne is licensed under the Hazeltine Neutrodyne patents and manufactured for us by King-Hinners Radio Co.




ADLER-ROYAL Elisabethian Floor Type Neutrodyne No. 1 in figured walnut or mahogany finish; storage battery or dry cell equipment. Price \$350.00.

Adler-Royal

NEUTRODYNE

FRESHMAN MASTERPIECE

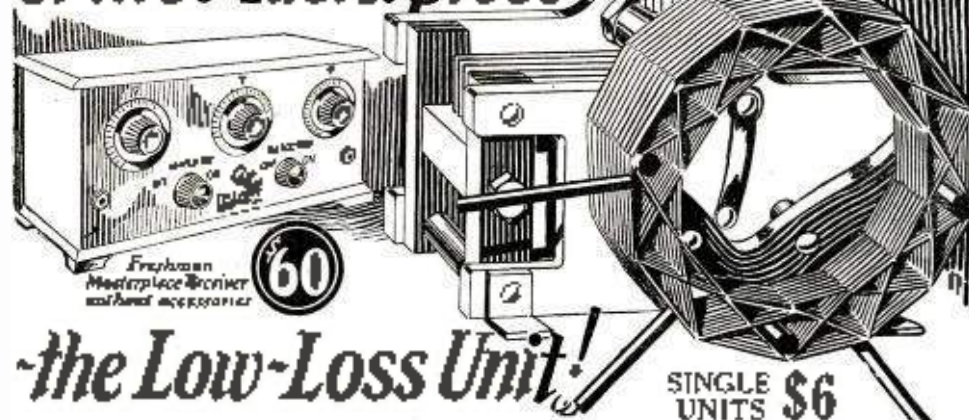The Secret of the Success of the Masterpiece



the Low-Loss Unit!

It's Easy to Build

A Five Tube Radio Frequency
Receiver when you use the

FRESHMAN MASTERPIECE KIT

No Neutralizing or Balancing
Condensers Required

when you build with the Masterpiece Kit which produces a tuned Radio Frequency Receiver, that will bring in even the most distant stations with the volume and clarity of locals. So selective that stations can be brought in day after day at the same dial settings. A set that is the equal, if not the superior, to any 5 tube receiver on the market, and what's more, it's the easiest set in the world to operate.

Each and every Freshman Masterpiece Coil bears a serial number and trademark—our guarantee of electrical and mechanical perfection. Every genuine Freshman Coil is made of specially insulated wire to prevent short-circuiting, so often caused by inferior coils. For your protection demand only the genuine.


**SINGLE
UNITS \$6**

For Reflex and other circuits

**MASTERPIECE TUNED
RADIO FREQUENCY
KIT COMPLETE**

with 5 MASTERPIECE UNITS carefully matched and balanced. Complete with wiring diagrams and instructions for building any 5 tube Tuned Radio Frequency Receiver and drilling template for proper mounting.

\$17.50

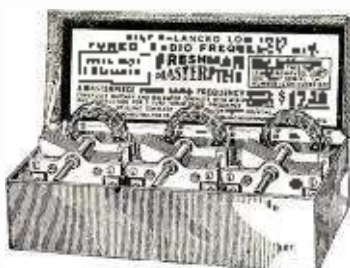

At your dealer's, otherwise send purchase price and you will be supplied without further charge.

Chas. Freshman Co. Inc.
Radio & Condenser Products
106 Seventh Ave. New York, U.S.A.

FREE Catalog!



**Dealers
send name
TODAY**

For DEALERS Only

Send name TODAY for our big new 1925 catalog. FREE to dealers only. Not illustrated, with descriptions and special prices on high grade standard sets and supplies.

Unusually attractive discounts to dependable dealers. Orders filled same day received. Write NOW for copy, free catalog.

FEDERAL RADIO COMPANY

Distributors of High Grade Radio Sets and Supplies

332 So. 29th St. OMAHA, NEBRASKA



FREE
A COMPLETE instruction booklet telling how to build the TRI-COIL Reflex Set is yours for the asking. The TRI-COIL Reflex, by the way, is one of the most powerful and reliable reflex sets ever designed—direct for distance and volume. TRI-COIL Transformers \$2 at all good dealers. If your dealer cannot supply you, send money order direct.

SEWING METAL STAMPING Co.
714 Atlantic and Broadway, N.Y.

shows a vernier type, wire wound, rheostat. A vernier is simply an attachment by means of which the resistance of the instrument may be varied in smaller steps than with the plain type illustrated at 1. The vernier type is extremely useful in connection with a tube requiring critical adjustment of the filament current. This is particularly true of the 6-volt, 1-ampere type, known as the UV-200, which, by the way, makes an excellent detector tube for use with a storage battery.

There is still another important type of rheostat to consider that combines the plain type and the vernier type into one adjustment. It is illustrated at 3 in Fig. 4.

This does not make use of resistance wire, but consists of a series of carbon disks or a quantity of carbon grains so arranged that they can be compressed or released at will. The resistance of the carbon decreases as it is compressed and increases when released. By using a fine pitch screw thread on the rod compressing the carbon, very fine control can be obtained, fully equal to a wire wound rheostat with a vernier. This type is also very good for use with a tube requiring a critical adjustment of the filament current.

Regardless of the type of rheostat selected it should be mounted on a small unit panel so that it will match up with the other instruments. The method of mounting will depend upon the type bought. The unit panel will be the same as that used for the coupler or the variable condenser, but, of course, smaller. The mounted rheostat is indicated in Fig. 6.

THE GRID LEAK AND CONDENSER

The grid condenser is very similar in construction to the phone condenser described in this department in the July issue. However, it must be more accurate in construction and it is advisable to buy one rather than attempt to make it. In purchasing this instrument get one made with mica insulation and equipped with two clips for holding the grid leak. Since the leak is to be connected in parallel with, or across, the condenser, you will save space and wiring by getting one of the type described. A condenser and leak of this type are shown in Fig. 5.



The grid leak is nothing more than a high resistance. It should be so made that it cannot be affected by the weather, because if it is, the resistance will be lowered when the weather is damp and increased when dry and poor reception will be the result. All good leaks are usually sealed air-tight in glass tubes. The leak may be of a fixed resistance and should be rated at about 2 megohms (two million ohms).

If, however, you wish to have your set as flexible as possible, equip it with a variable leak. There are many of these on the market but most of them have the fault of being open to the air and therefore not reliable. Others have a sliding or scraping contact on a carbon or graphite surface that soon changes the resistance of that surface at any particular setting by wearing or scraping the resistance material away. Thus it is soon rendered unreliable. The best leak is the one illustrated at Fig. 5A. This is a small glass cylinder with metal ends. Within is a small quantity of a liquid that has a fairly high resistance. Two peculiar shaped electrodes are arranged in the tube, one fastened to each metal cap. They are so arranged that by rotating the cylinder as it is held in a standard leak holder, they will dip further into the liquid and so lower the resistance of the unit. Turning back or past the minimum mark on one of the ends increases the resistance. This type of variable leak is efficient and regular in action.

THE VARIOMETER

The variometer is very similar to a coupler in that it consists of two coils of wire placed one within the other. There is a differ-

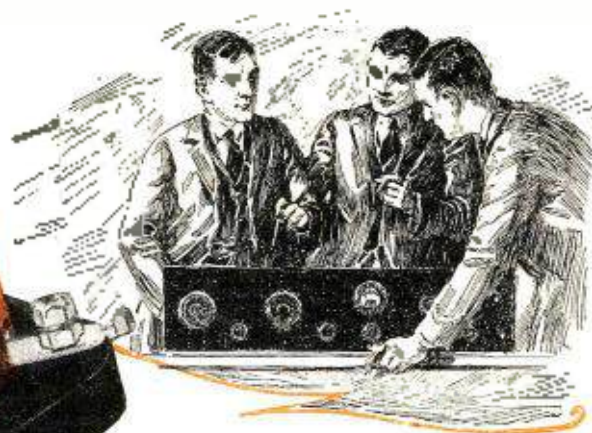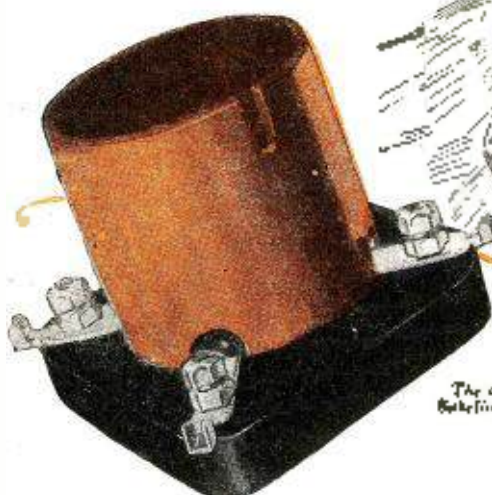Get a Handy Binder for your RADIO NEWS. Holds and preserves six issues, each of which can be inserted or removed at will. Price 60c. Experimenter Pub. Co., Inc., Book Dept., 53 Park Place, N. Y.



The shell is ORANGE
Bakelite—the base genuine
Thermoplas

The More You Know About Radio the Better You Will Like This Socket

If ever a device were designed to increase the efficiency of all receiving sets, it was this new socket by the Master Builder. Radio engineers praise it — new set builders marvel at its ease of installation and the clear, loud reception obtained that bespeaks the absence of losses — many old-timers have even rewired their sets to establish new distance records and enjoy clearer reception with this better socket.

You'll like its construction, embodying a minimum of both insulation and metal — capacity absolutely minimized *without sacrifice of mechanical strength*. And its base of ebony Thermoplas in beautiful color contrast with the thin shell of orange Bakelite adds as greatly to the appearance of any set as the construction does to its efficiency.

You'll like its contacts (the source of losses and noise in most sockets); they are radically new in design, formed of phosphor bronze and *silver plated* — because the contact resistance of silver does not increase as it stands exposed to air. Then, too, electrical losses are minimized by providing maximum spacing between terminals, both in the insulation and in the air.

You will like the way the tube is inserted and removed without turning — which prevents twisting the bulb from its base. You will like its appearance — its small size — its neatness. You will like its silvered posts with slotted nuts that are fastened *well* with either screw driver or wrench. You will like the way these terminals are arranged for soldering — extra long so that they may be bent down where under-wiring is desired — and provided with ears to hold the wire in place for soldering. And best of all you will like the price, 90¢. *This socket that meets the specifications of the most exacting radio engineer costs no more than most of those on the market today!* If your dealer has not yet been stocked, you can be supplied direct from factory at regular price plus 10¢ for packing and postage.


THE CUTLER-HAMMER MFG. CO.

Member Radio Section, Associated Manufacturers of Electrical Supplies
Works: MILWAUKEE and NEW YORK

"Built By The Master Builder"

CH

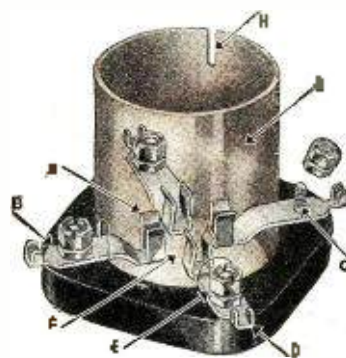These Exclusive Features Assure Better Reception



A Perfect contact. Both ideal tube prong cleaned when inserted — no contact on worn unwelded end.

B All metal parts *silver plated* — perfect contact for the life of the set. Silver may tarnish but its contact resistance does not change.

C One piece contact construction. The binding post is *NO* 1 a part of the circuit — the wire to the socket always touches the contact strip which carries the current direct to the tube prong — no joints to cause losses.

D Convertible terminals for soldering — full length to allow bending down for under-wiring. Ears hold wire in place for soldering.

E Extra heavy binding posts — tight connections with either wrench or screw driver. Lock washers hold terminals rigid.

F Wide spacing of current carrying parts both in air and insulation — true low-loss construction.

G A minimum of both metal and insulation for low capacity. Shell of thin Bakelite — the base of genuine Thermoplas.

H The tube is held in place by merely a vertical motion — no twisting to separate bulb from base.

The attractive orange shell helps identify this better socket, but the famous C.H. trade mark deep on the socket and on the orange and blue box is your genuine protection.



RADIO SOCKET



Dear Jim:

Last night I heard them sing, "Give a Man a Horse He Can Ride", from old WTAM.


I'm going to write a new title for that song. "Give a Man a Radio Battery He Can Charge," I say.

Willard Rechargeable Radio Batteries remind me of a fine big clock. A good clock keeps time, all the time, because you wind it occasionally.

That's the way with Willards. They keep the power in the radio set and you don't have to wind them often. Just a little freshening charge once in a while and they're good as new again. Seems like you can't wear 'em out. I know lads who have had them for several years and their Willards are just as good now, as the day they bought them.

Get the kind that last, I say,

Sam.

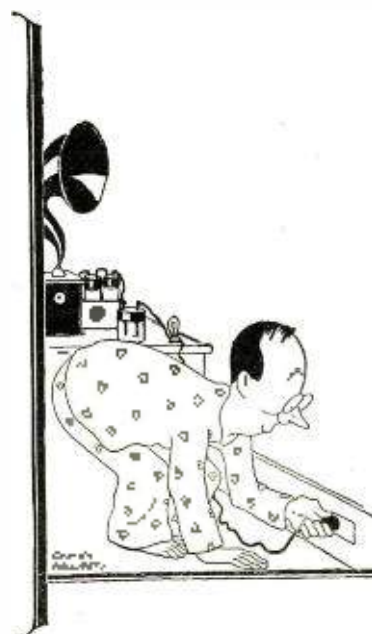

WILLARD RADIO BATTERIES

FOR SALE AT WILLARD SERVICE STATIONS AND RADIO DEALERS

Write for WTAM's new booklet,
"The Proper Use and Care of Radio
Storage Batteries." Mailed to you
with our compliments.

Write to **WTAM** for this booklet—

(The Voice of the Storage Battery)

WTAM is the Radio Research Laboratory and Broadcasting Station of the Willard Storage Battery Company, Cleveland, Ohio.

Its function consists of research which is being done to improve the quality of radio reception and the broadcasting of radio programs for your entertainment.

Tear me off the page and mail me to WTAM. I'll bring you "The Proper Use and Care of Radio Storage Batteries."


.....
Name

.....
City and State

.....
Street Address

.....
R.F.D.



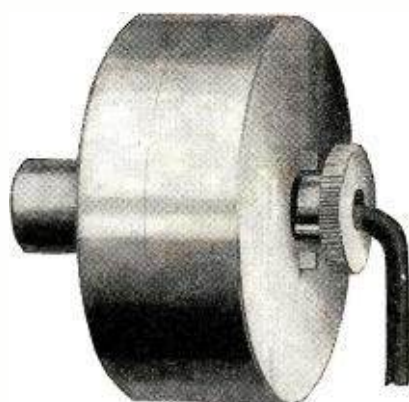

Giant Phonodapter

This unit doubles the value of your phonograph. An easy adjustment provides instant control of tone and volume. Large size diaphragm assures maximum signal strength and a bell-like clearness of tone. Light weight construction permits use of unit without supporting stand. It is designed to fit all standard makes of talking machines. The Giant Phonodapter is recommended for use with high-powered multi-stage sets and is guaranteed to give perfect satisfaction.

Trimm Products Proved Best

TRIMM Quality Reproducers

Headsets

Professional - \$7.50
Dependable - \$5.00

Speakers

Concert Model \$25.00
Home Speaker \$10.00

Phonodapters

GIANT Unit \$10.00
Little Wonder \$4.50

Trimm reproducers were the choice of the MacMillan Polar Expedition and the Wm. Hale Thompson 'Round the World Cruise. Trimm Headsets are the unanimous choice of those to whom radio is life's vocation. Their superiority is apparent when comparative tests are made. If you want the most sensitive headset made, purchase a "Professional." We'll guarantee you perfect satisfaction.



Member Radio Manufacturers' Association

DEALER'S SERVICE

An established service to dealers is offered on all standard lines allowing the regular discount. Write for quotations on the things you need.

Everything in Radio
**FRIEDLANDER-
KOPPLE RADIO
SERVICE**
140 Church Street
New York City



Niles Battery Chargers Stay Sold

A solid, durable, efficient charger for Niles A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R, S, T, U, V, W, X, Y, Z, and all other Niles batteries.

Delivers 15 percent of power in 100 hours. Two full days of charging here. Best in operation. Efficient. Economical. Guaranteed. Write for a catalog and details.

SALE BY DEALERS
Model A \$14.00
Model B \$21.00
Model C \$21.00
Write for details today

NILES MANUFACTURING COMPANY
Dept. 10, Yonkers, N.Y.

Insure your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.

has been extended to include what are termed free stock exchange reports rendered daily. Now it is planned to further extend the service so as to cover agricultural information, but, about \$42 annually is to be added to the regular charges. Few American fans would swear it NAA or KDKA began charging for this sort of information. Owners of receiving sets in Germany are called "amateurs"—certainly then, the broadcasters are "professionals."

The Barometer and Radio Reception

(Continued from page 933)

harbinger of fine settled weather when the day sky is a clear blue, and beautiful white clouds sail stately overhead, and the dark purple dome of night shows the moon like a silver queen silently gliding in parade before the admiring gaze of a billion brilliant stars.

So the task in hand was to discover if there were any portion of the atmospheric pressure curve, or combination of curves which would be more favorable to radio reception than other sections. While an exhaustive study of the data accumulated within the last two years has failed to bring to light any formula, which by using the barometer curve as the major factor, would enable one to accurately forecast the quality of radio reception for two or three nights in advance, yet there seems to be quite a mass of evidence in favor of the theory that a slowly rising barometer, or better still, a barometer whose curve is virtually steady, or flat in any position, is the most favorable for radio reception. On the other hand, there is ample evidence on record which points to the rapidly falling glass as the most persistent enemy of good radio reception.

There are exceptions, of course, strikingly so in some cases, but as I am writing more for the sake of presenting the facts rather than trying to prove anything, it might be interesting for those who have kept a log of their radio reception for the last year or so, to check up on any dates I may mention as I go along. To begin with, 100 good nights were selected from the records which stated that these nights were ideal for reception, many in fact being what might be termed "super" nights with "DX" rampant from sundown to far into the following breaking day.

RESULTS

On 48 of these nights the barometer was found to be rising—on 40 more it was steady and showing curves similar to A, B, C, D, E, F, G, H, I, J, K, L, M, N, O, P, Q, R, S, T, U, V, W, X, Y, Z, and on the remaining 12 nights the glass was falling, thus showing that out of 100 excellent nights for radio reception 88 per cent. of the total found the barometer either rising or set steady. Again, selecting 100 instances when excellent runs of good reception or average reception were broken up, we find that in 72 per cent. of these cases a rapidly falling barometer preceded them, in 12 per cent. of them the glass was halted in a "valley" similar to that shown under D and E in Fig. 1, preparatory to a "climb." The remaining 16 per cent. of the time, when our reception went bad, the glass was found to be climbing at various angles from 60 degrees to 85 degrees.

For the benefit of those who desire to check their reception logs, I will quote a few instances, specifying the dates. In the following, the symbol R will mean that the glass was rising, and the symbol D will show that the barometer was dropping. The numbers accompanying the symbols R or D are used to show the rapidity of rise or fall; for instance, R30 would mean that the glass was rising at an angle of 30 degrees, and a D48 would be used to show where the glass



Enjoy the best radio in your neighborhood

The Shamrock-Harkness Two Tube Reflex!



Licensed under U. S. Patent Office Serial No. 719,264 for Radio Receiving Stations.

PRICE
\$35

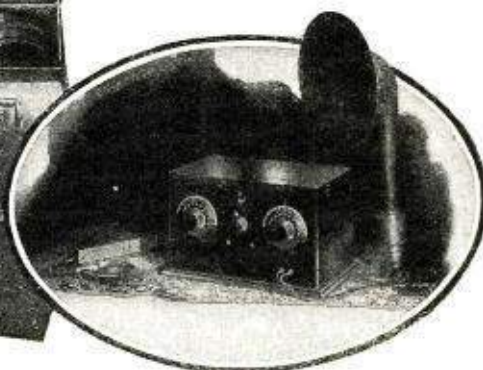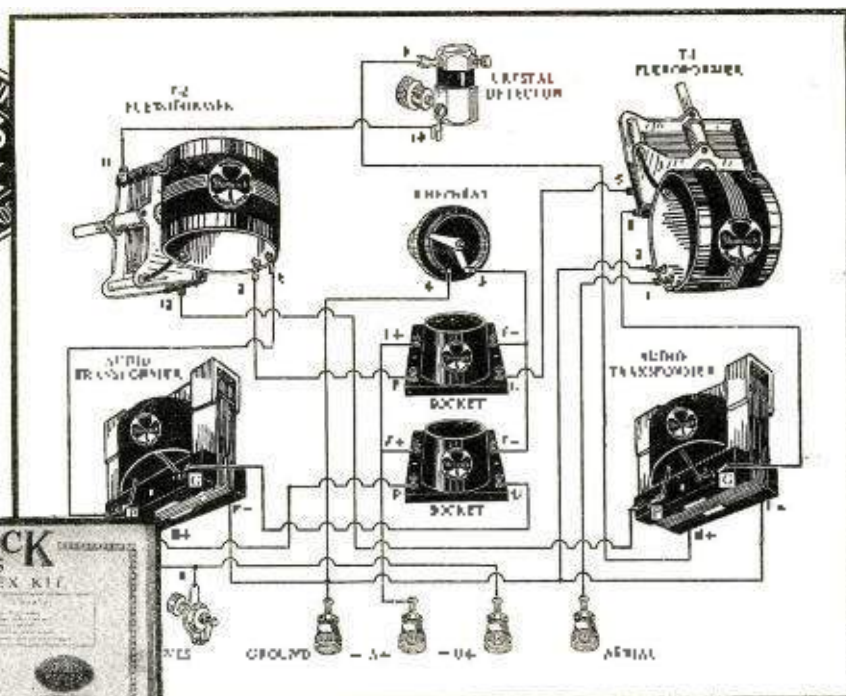

The set for the masses as well as the classes. Combines best features of leading circuits.

NEUTRODYNE DISTANCE
+
REFLEX CLARITY
+
REGENERATIVE VOLUME

THAT'S the Shamrock-Harkness Two Tube Reflex which has created such a sensation among experimenters and amateurs by its amazing performances. It combines the best features of the leading circuits in use today.

DISTANCE AND SELECTIVITY FROM THE NEUTRODYNE: Radio frequency controlled by variable condensers mounted on air core transformers gives the Neutrodyne its remarkable distance and selectivity.

CLARITY FROM THE REFLEX: Just one unit is responsible for the reflex's well-known tone clarity. This is the crystal detector.

VOLUME FROM THE REGENERATIVE: The two audio transformers found in the regenerative are responsible for its powerful loud speaker volume.

THE SHAMROCK KIT CONTAINS all parts necessary to build this marvelous set. Enjoy the best radio in your neighborhood this winter. Buy this Shamrock Kit and make your own set at half the cost.

BUY ONLY SHAMROCK-HARKNESS LICENSED PARTS: True Harkness reception can only be achieved by using genuine licensed parts. Avoid imitations. Accept only the genuine.

BEFORE BUILDING YOUR SET mail coupon for "Shamrock Radio Builders' Guide Book."

FEATURES

- Operates a loud speaker.
- Two tubes do the work of five.
- Cuts battery costs 60%.
- Does not squeal, howl or radiate.
- Stations can be logged.
- Amazing clarity and volume.

SHAMROCK MANUFACTURING CO.
Dept. 66, Market St., Newark, N. J.

SHAMROCK

FOR SELECTIVE TUNING

SHAMROCK MANUFACTURING CO.
Dept. 66, Market St., Newark, N. J.

I enclose 10 cents (10¢, stamps or coin) for copy of "Shamrock Radio Builders' Guide Book" containing diagrams and complete instructions for building 14 sets at prices ranging from \$15 to \$50.

Name

Address

Dealer's Name

The DAYRADIA



The New DAY-FAN OEM Model

*A complete unit ready to attach to
light sockets, astragal, and ground.*

This beautiful instrument embodies all the remarkable qualities of tone, simplicity of operation, and volume which distinguish the other DAY-FAN models.

In addition to this, it is complete with built-in loud speaker and battery equipment. The batteries automatically remain fully charged.

Price complete with everything but tubes . . . \$225.00

THE DAYTON FAN & MOTOR CO., Dayton, Ohio

SEND US YOUR BROKEN OR BURNED OUT RADIO TUBES

ALL TUBES REPAIRED AND
REBUILT LIKE NEW

We Save Half Your Tube Cost
A Working Radio with New Tubes
NEW TUBES ALL TYPES—A-50

Doyle—Write for Price
RADIO TUBE MANUFACTURING CO.

151 E. Madison Street New York City
Selling Order Radio Repair Agencies—We Ship C.O.D.

\$2.00

WHEN YOU TUNE IN ON WRS YOU TUNE IN ON SERVICE

WORKSMAN RADIO SERVICE

"Always at your service"

If it's anything in Radio—we have it

Our BUREAU of Sales lists thousands of items

WILL SAVE YOU MONEY

WORKSMAN RADIO SERVICE

14-16 Vesey Street New York, N. Y.

EARN MONEY AT HOME

YOU can earn \$1 to \$2 an hour in your spare time writing short radio scripts. No experience necessary. We instruct you by our new simple Dictograph System, supply you with work and pay you each week. Write today for full particulars and free booklet.

WEST-ANGLO SHOW CARD SERVICE LIMITED
Authorized Capital \$1,250,000.00
134 Colborne Building, Toronto, Can.

ADJUSTABLE CIRCLE CUTTER

A great help in the work of the machinist. It cuts circles of any size from 1/8" to 12" in diameter. Adjustable from 1/8" to 12" in diameter. Price \$1.75. Write for full particulars and free booklet. Sent by Cash or Money Order. Johnson & Distributors, 1000 Broadway, New York City. Patent Pending. Write for full particulars and free booklet.

was dropping or falling at an angle of 48 degrees.

Beginning on July 25, 1922, a series of good nights terminated with the barometer showing D29. After a week of bad static the glass climbed on an R38 on August 4. Remarkable DX was accomplished until August 6, when the good air was spoiled by a D42 and restored on August 7 by an R35. Another favorable run of reception ended with a D42 on August 17, 1922, but the following day an R38 repaired the damage, and the glass settled steady, giving us two splendid nights on August 19 and 20, only to desert us again when a D60 appeared on August 21 disturbing things temporarily for a night until an R51 came along and landed us a brace of radio nights worth saving home for. On August 24 we find a D55 and poor reception, and on August 25 good work being done on the receiver with an R70; also, the barometer took a vacation and rested on a practically "flat" curve similar to H in Fig. 1 for a period of five days, during which time the air was first-class all through, yet it is certainly interesting to find a D43 again putting a stop to such ideal conditions on Sept. 1, giving only indifferent reception for the next two days. As usual, an R75 cleared things up again for us, but a D42 next day ruined the good work, the latter eventually giving way to an R51 again on September 5, which pacified us until September 7, when a D38 served up such a very poor quality of reception for four nights straight that we were extremely thankful for the surprisingly slow climb of the glass on an R14 to perch on our battered air again on September 11, 1922.

While I am around this date, let me tell of an unusual occurrence on September 13. This particular night was really a wonderful one for radio and the glass was passing through a relatively high position, climbing at the rate of 0.6 degrees, the pressure registering 30.25 inches, but the barometer suddenly felt youthful and vigorous that night for I went on climbing to an abnormally high position seldom attained here, namely 30.5 inches. For a period of four days after that "Super" night of September 13 when the glass climbed out of sight, the air was simply "dead" and it took three more days before the barometer got over its foolish notions and slid down to a rational level when our reception materially improved on September 20.

This phenomenon was duplicated more recently on April 26 this year, when the barometer curve almost ran over the top of the pressure chart, spiking to an altitude of 30.65 inches at 12 noon that day. The reception that night was exasperating, to say the least, yet at midnight the glass selected and was seen to be tumbling, reaching the following day, passing through a normal zone of 30.12 on April 27, the night of which was exhilaratingly examined with listening jars. To quote each instance in detail would take up too much space, but in very many instances we find the barometer curve rising and falling in direct sympathy with the barometer curve. The first two ideal weeks of January, 1923, culminated finally in a severe attack of the barometer which, after being passive for those two weeks, ran amok. On January 26 it dove violently, and rose again, then plunged again like a broom early on January 28. That was enough. Our long spell of lovely reception while the glass was steadily suffered terribly under such treatment, withering almost visibly from that time on, and was at a critically low ebb on January 29, when a low looked for R45 just arrived in time with an altitude for our disgust of radio in general and for January 29 we were back on full face, during royally on plump DX reception again.

I am simply repeating the story with a change of dates when I refer to February 24, 1923. Here again, a high-pressure-like DX scattered a splendid succession of good

"MONODYNE," the Universal Receiver

SPECIAL MONODYNE FEATURES

1. The single tube on the Monodyne acts as amplifier and detector equaling a volume of two tubes.
2. Uses but one dry cell tube, preferably WD-12 or C-12.
3. Only one tuning control—simple and easy to operate.
4. Selectivity — sharp-tuning always on all wave lengths.
5. No storage batteries. Operates on single dry cells.
6. Easy to install—permits all kinds of "hook-ups."
7. Can be used with head phones or loud speaker.
8. Costs only \$10 post-paid (without tube).



Within everyone's purse. Operated by anyone using only one Tuning Knob and one Tube.

PRICE including two inductance coils, but without tube, batteries or phones

\$10⁰⁰

Only one knob for tuning. No longer do you spend half the night in needless fussing, turning this and twisting that, missing all the pleasure of the entertainment.

"Like talking over the back fence" is the way one customer describes a political speech he heard broadcast over a thousand miles away.

The **MONODYNE** circuit is one of the most radical advances in Radio engineering. Parts heretofore considered essential are omitted with no loss of efficiency. One simple tuning control gives selectivity equal, if not superior, to sets costing hundreds of dollars.

Size $4\frac{1}{4} \times 6\frac{1}{2}$ weighs less than 3 lbs.

ALL WAVE LENGTHS—NO STORAGE BATTERIES

Calibrated Audio Transformer

Here is a transformer that not only positively eliminates all the draw-backs of other makes, but in addition stands head and shoulders above any other audio frequency transformer on the market today. To prove this amazingly flowery language, note the following:

From recent tests conducted in the RADIO NEWS LABORATORIES this transformer was found to have the following characteristics: The voltage amplification curve, obtained by applying a constant peak voltage across the primary in series with a 10,000 ohm resistance and measuring the secondary peak voltage at various audio frequencies without absorbing any energy from the secondary, was found to be exceptionally flat throughout the entire band of audio frequencies. Tests were made at frequencies ranging from 150 to 6000 cycles, and the curve extended well into the lower frequencies where other transformers fail. In fact the amplification at 200 cycles was almost equal to the amplification at 1200 cycles, a condition not found in any other high grade transformer. The curve is flat from 1200 to 6000 cycles, giving a direct voltage amplification of from $\frac{1}{2}$ to 2 times throughout the entire range. Thus



\$5⁰⁰

there is virtually no distortion caused by the transformer.

Tests made on the transformer in actual operation corroborated our electrical tests. Broadcast music was not only amplified and reproduced with life like fidelity, but the volume was greater than that obtained from other transformers. The transformers had no tendency to oscillate at audio frequency, or squeal, as many do, and consequently require no artificial feed condensers or resistances. Of particular note was the volume and quality of the base notes of the saxophone, piano, etc. These notes, although missing in most receivers, came through with astounding volume.

A Calibrated Transformer

A print showing the calibrated curve is included in the user can tell how to get best results.

The "Calibrated" Audio Transformer is specially designed for Radio Broadcast reception reproducing voice and music faithfully and with freedom from distortion. High amplification at all frequencies. A high grade transformer giving results heretofore unobtainable. Superior in design and beautiful in appearance. Improved terminal mounting giving maximum separation of grid and plate and admitting connections being made with equal facility in any direction, thus insuring short leads.

Manufactured in 2 styles: 1 1/2 to 1 (Medium drive ratio) and 4 1/2 to 1 (all stage ratio). Price each style..... **\$5.00**

If your dealer cannot supply you, use coupon

SEND NO MONEY

NATIONAL AIRPHONE CORPORATION
18 Hudson Street, New York City.

Gentlemen:—

Please send prepaid ☐ Monodyne Receiver ☐ Calibrated Transformer for which I will pay the balance, upon delivery, the advertised price.


Name

Address

City State

**NATIONAL
AIRPHONE
CORPORATION**
18 HUDSON STREET
NEW YORK

R.N.-12

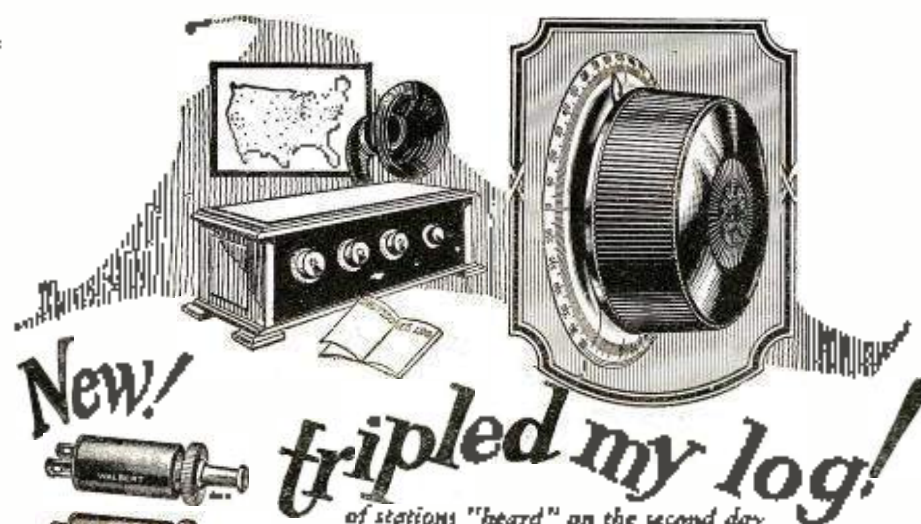

Don't worry any more about someone meddling with your radio set while you are away. Simply remove the three Walbert Filament Lock Switches and take it with you. Just as you'll take the ignition key from an auto. Sturdy, compact, efficient. Shift and key handles insulated from circuit.



The Walbert Safety-Run-Sorter is guaranteed not to break at the slot. Special heavy bakelite design decreases inductance capacity thereby utilizing all available grid voltage for producing signals. (Note: tubes have built-in lights for same reason.) Soldering lug and double-sealing cap on integral. The most efficient design on the market.



Members of
R. M. A. and
N. R. T. A.

WALBERT UNIVERNIER Micro-Selective Tuning Control

That is what the UNIVERNIER did for A. H. Klingbeil of Ashtabula, O. Tripled his entire log in a single night! "Last night," writes Bishop Francis of Chicago, "I put a UNIVERNIER on my Neutrodyne and got 30 stations I never heard before!" You can do the same. Tune in those hard-to-get distant stations quickly, easily, clear and loud. Don't have to alter your set. Simply replace each of your dials with a UNIVERNIER, the original 11-to-1 ratio micro-selective tuning dial.

WHY A 11-to-1 RATIO IS BEST

Careful tests prove that a 11-to-1 ratio is sufficient, a higher ratio requires more adjustment. With higher-ratio dials the actual "searching" for stations is done with the coarse adjustment. The operator finds the correct adjustment too slow and uses it only for "clearing-up" a

station after it has been detected with the coarse adjustment. Many stations are overlooked with the coarse adjustment. With the Univernier both "searching" and "clearing-up" are done easily and efficiently with the same adjustment. And a large knob helps do it!

COSTS NO MORE THAN A GOOD DIAL—

And does away entirely with the need for variable condensers. Very successful with new "dial-off" dial. Micro-dialism with built-in tuning. Positive continuous service—No slippage! For use

with any set. A slight necessary amount of play in the knob prevents involuntary disturbance of tuning adjustment when the hand is removed.

Matheony Knob and Gold-plated dial \$1.50

Black Knob and Silver-plated dial \$1.25

At your dealer or write for price on request of purchase price. (Place in order dealer's name.)

Jobbers and Dealers: Write for Discounts

THE WALBERT MANUFACTURING COMPANY
343 Weymouth Avenue Chicago, Illinois

WALBERT

Parts with a Purpose

FREE!
Send to know for
FREE copy of
UNIVERNIER
LOG BOOK.

ALL WALBERT PARTS PROTECTED BY PATS. OR PATS. PEND. U. S. AND FOREIGN

RADIO

FOR AMBITIOUS MEN

A new booklet just off the press. If you are interested in entering the Radio field, send for this booklet which explains our Radio Operating and Radio Mechanics Courses.

Y. M. C. A. RADIO INSTITUTE
158 East 86th Street
New York, N. Y.

RADIO TUBES REPAIRED

Like \$2.00 and
new 50c guaranteed.
ALL TYPES

Mail in last receipt or broken tubes. Radio-licious guarantee. Prompt service or full refund.
OHIO RADIO SALES, Dept. R
723 ROSS BUILD. CLEVELAND, OHIO

MU-RAD
LABORATORIES, INC.
Asbury Park, New Jersey

KESTER Radio SOLDER

(Rosin-Core)

If your dealer cannot supply you
send us 25c in postage

CHICAGO SOLDER COMPANY
CHICAGO, U. S. A.

nights and practically left us desolate for five or six days. Coming further and picking at random we find September 14, 15, 16 and 17, 1923, delivering superb radio, but a 1928 put an end to it all until the 20th of the month, when an R65 was exceedingly welcome.

Rippling over the months for the benefit of our newcomers who only got into the game this year with their logs, let us go to Jan. 25 of this year (1924) and see how poor the stations were and failing very bad. Well, a nasty D7n set in on the day before and the glass had fallen remarkably low on the 25th with a frightful blizzard here. On Jan. 26 an R70 arrived, continuing through the 27th, on the night of which your log will undoubtedly prove unique for startling DX records.

EFFECTS OF RAPID DECLINE

Since recently still, let us pause at the first week in July, 1924, so as to select a difference in seasons.

Here we watched the barometer ambling along for several days on a comparatively "flat" curve, nice and steady in a fair weather zone. Radio reception was very good during the whole of this period, but on July 7 the break came. The glass fell away rapidly and was in a "bad way" next day, reaching its worst on the night of July 9.

Thousands of logs of radio amateurs will show that the Canadian Polar ship Arctic (call YD31) whose signals had been roaring in for several days, then fell away to a weak volume on July 11. Turning back now to July 10 on their log books, these amateurs will find that their transmitters put over some nice DX (if they were working) for the time of the year, but on the night of July 11 that strange magic which flung their signals into distant states had vanished and on the whole reception was jotted down as very poor.

Once again the charts show that the DX night was the night of the rising glass and the poor night the one of the falling glass.

The Arctic was wonderful in volume when the glass was steady or rising, wheezy and swinging when the glass was falling, and back to her usual trumpet note on the 14th when the glass rose again, although the ship was considerably further away.

The evidence up to now tries to show the rising or steady barometer as our best friend, and the falling or erratic barometer our worst enemy, but there are exceptions, of course; in fact there are instances which will cause one to ponder before coming to a conclusion on anything. A log of transmissions from this station shows that while the bulk of my DX was accomplished during the periods of the rising or steady glass, yet I was only able to reach the West Coast (2,500 miles distant) and to England once in a period of four months with 20 watts of C.W.


Then one morning I worked the West Coast three times inside the hour on 15 watts C.W., while the barometer was falling rapidly.

We will carry confusion further by relating that my average range on the phone (10 watts) was 800 miles, easily conversing for hours at a range of 600 miles, and many reports from ranges of 1,000 to 1,200 miles of good reception, yet on both occasions when I have been notified that my voice has been heard plainly 1,300 miles South, the barometer was falling here.

CLOUDS

Many lovers of radio prefer clear bright nights and others favor a dark cloudy night. Let me tell them that the records show that first class reception has been tabulated on innumerable occasions with both clear and cloudy nights, with the balance in favor of a night with low lying rain or snow clouds after a generally cloudy day which seems

NO MORE ~~BATTERIES~~

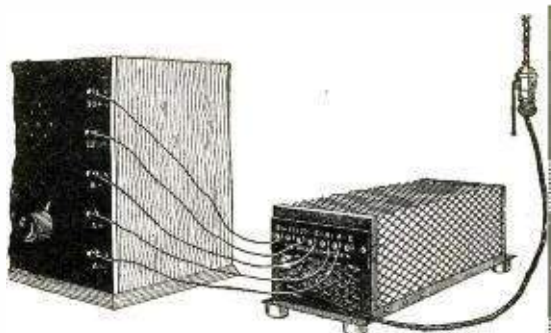

A-B POWER UNIT

The New Radio Unit
That attaches to any
Radio Set replacing
both A and B Batteries.

Read These Facts

- 1—Absolutely eliminates all batteries.
- 2—NOISELESS at all times.
- 3—Will operate any set—no change whatsoever necessary in your set.
- 4—Steady current at full voltage always—a feature not found in batteries.
- 5—Will not overheat.
- 6—All connections identical to battery posts.
- 7—Will operate efficiently up to 10 tubes (½ Amp. each).
- 8—Eliminates danger of burning out tubes.
- 9—Attaches to any Light Socket 110 Volt D. C.

PRICE
\$25.00

Sent Express Collect

Better order to-day. In two weeks' time we will be so swamped with orders that they will have to wait their turn. Orders sent now can be filled immediately.

THE RADIOGEM CORP.


66-R—West Broadway, New York City.

(Gentlemen.—) enclose \$25.00. Kindly ship me express collect one A-B Power Unit (for 110 volt direct current only).

Name

Address

City and State

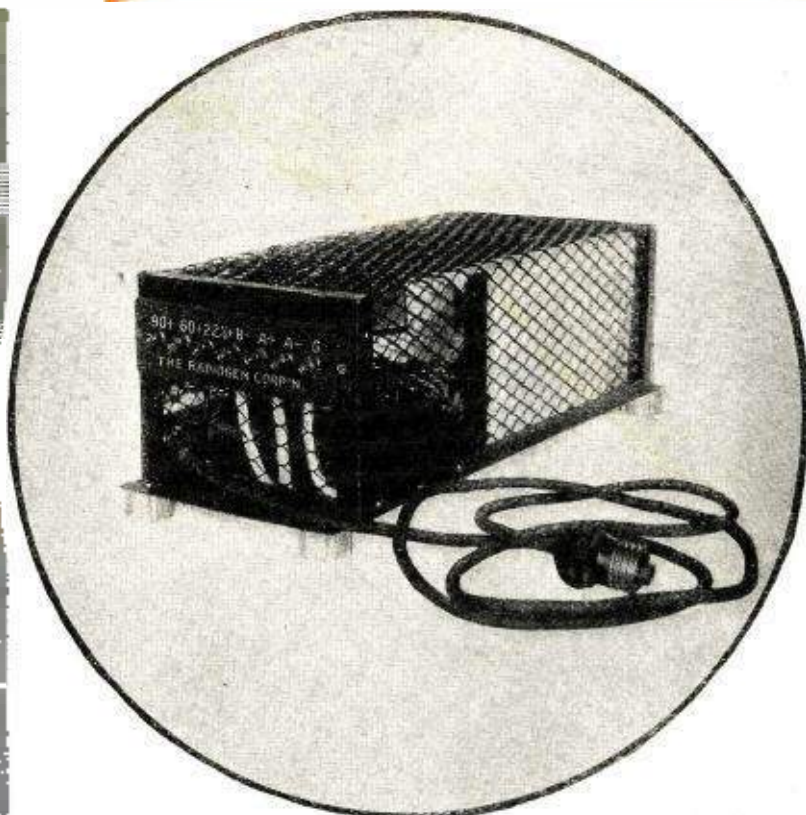

Patent

Pending

AT LAST

The Logical Unit for Operating
the Radio Set—Cleaner, Steadier,
More Compact and More Eco-
nomical than Batteries

You can dispose of your batteries. Both A and B types. You can use the large space they occupied for other and more valuable material. You can rid your radio set of the unsightliness of the A and B batteries.

We have just perfected this logical ideal unit for the operation of the modern radio receiving outfit, a unit that takes the place of your batteries and operates direct from 110 Volt D. C. house current from the nearest socket.

The unit is small, neat, compact, not messy. It is silent in operation, does not overheat and IT DELIVERS A STEADY CURRENT AT ALL TIMES FOR BOTH FILAMENT AND PLATE, THEREBY INCREASING THE SIMPLICITY OF OPERATION OF THE MULTI-TUBE SET.

It is easier to hook up than batteries, absolutely no change necessary in your set. All connections are identical to battery posts, and are so marked. Has taps for the following voltages: 6, 22, 60, 90.

Entire unit is only 14 inches long by 6 inches wide by 3 inches high. Construction is of the finest materials for dependable long life. The unit is beautifully finished and will not detract from the appearance of the most ornate receiving set.

This Unit for Direct Current Only
AC Unit Under Construction

Use the Coupon on the Left

The Radiogem Corporation

66-R—West Broadway

New York City

"What a whale of a difference just a few cents make!"

—all the difference between just an ordinary cigarette and—FATIMA, the most skillful blend in cigarette history.

3 Brings you a Genuine UNDERWOOD TYPEWRITER

10 DAYS FREE TRIAL Test it. Underwood is extended at 25¢ per day. If you are not satisfied, return it for a full refund. No obligation.

GREAT PRICE SAVING Underwood is the most popular typewriter in the world. It is the most reliable and the most durable.

EASY MONTHLY PAYMENTS You can buy an Underwood typewriter on easy monthly payments. No cash outlay. No interest.

FREE BOOK OF FACTS Send for a free book of facts about Underwood typewriters. It contains all the information you need to know.

Act Today! Mail Coupon

5 Year Guarantee

Shipman-Ward Mfg. Company
250 Shipman-Ward Building
Newark, N. J.

Name _____
St. and No. _____
City _____ State _____

DeJUR ONE HOLE RHEOSTAT

Radio Editors Agree that the De Jur one hole genuine bakelite rheostat is the standard of comparison. De Jur Rheostat: sturdy, precise, exclusive features—non-corrosive and heat resisting, interchangeable resistance elements held securely in place by special metal brackets. Sliding and supporting the slide arm has long brass bearing, allowing absolute contact.

Guaranteed—dry, not replaced any more.

AT DEALERS EVERYWHERE
Jubbers and Dealers
Write for literature

DeJur Products Co.
Lafayette 280 Avenue of the Americas, New York.

to prevent the light sun from sending the tide out of the air.

RAIN

No evidence is at hand that rain helps or hinders radio transmission. Rain is generally prevalent after a barometer decline, and very often also when the glass is recovering after a bad "low." However, we find that DX can be brought in during a deluge, whereas again, very poor work on the receiver will be recorded under like conditions.

SNOW

Usually the majority of snowy nights are good, but so is the season during which snow is encountered.

Blizzards have a bad habit of tying up reception, on first thought, until we note that it is the falling barometer that foretells the blizzard, so why blame the blizzard?

WIND

Severe flogging has been imposed on many nights during a high wind, and on quoting figures we find that fading appeared on 51 nights out of 100 nights that signals were known to be swinging.

I am prone to blame quite a deal of this upon antenna systems both at the transmitting and receiving ends. A high diving or fast climbing barometer invariably brings winds ranging from a brisk breeze to a young tornado and a characteristic symptom of unsettled weather is the slow "fade out" of our music, which appears to leave us and go somewhere to recruit its strength and after periods ranging from 15 and very seldom at more than 90 seconds, return to us with apparently renewed vigor. It might be interesting to note here that very often when a station fades from the East coast receivers it is reported strong to the West of the transmitter, and vice versa.

NORTHERN LIGHTS

While the Northern Lights may have a lot to answer for in the way of interfering with telegraph and cable communication, the records reveal nothing substantial in the way of evidence to show that they are very detrimental to radio reception.

Both excellent and poor reception have been met when the lights have been playing. I will quote the best of some exceptionally unique displays.

Oct. 14, 1922, 1:05 p.m.—North Lights magnificent tonight, showing low in broad curtains of varied colors, changing from the N. W. horizon to the S. E. Some curtains sweep so low a hissing crackle is plainly heard overhead. Reception is splendid tonight.

March 26, 1923, 11:40 p.m.—North Lights making wonderful picture tonight. Dogs are frolic with static, sparks flying from ears, nose and tail when fur is rubbed. Radio is simply rotten.

PHASES OF THE MOON

It may not be generally known that the first quarter of the moon surely earned a bad reputation in 1923 as a breaker up of good radio weather. Look at these records.

Jan. 24, 1923 Reception has fallen off considerably tonight.—First quarter of the moon.

Feb. 23, 1923 First quarter of the moon.—No radio concerts heard at all for three nights after that date.

March 26, 1923 First quarter of the moon. Hardly a radio station in the world for the next six nights!

It looked very bad for that particular phase of the moon, but before or since I have been utterly unable to fasten a lasting clasp on to that, or in fact any phase of the moon. There is nothing consistent about it. Even as I write (September 6, 1924) it is the first quarter of the moon and my wife is filling the sitting room with radio music from almost anywhere on the American continent. As the Irishman said, "There's good an' bad everywhere."

A VIOLIN *could crash it!*



THOROLINE is not a luxury to the tremors of the greatest of skyscrapers. Amplify sufficiently you—and rock whole buildings to the ground.

Unmistakable? Hardly more so than the proportionally greater amplification which is Radio itself.

Out of the air your antennae sifts infinitely rare impulses. Your receiver courses them along, amplifies them stage by stage, and translates them into sound waves—waves which can be made audible a city block distant by Thorola Loud Speakers.

The extreme volume which only Thorola makes possible, allows you to tune down for local stations, and it does bring in weak, distant signals with

strength never known before. Double the power of your set and hear new stations for the first time ever. Thorola.

Thorola power alone varies a radio epoch. Even greater is the exquisite reproduction. Famous songs and words of greatest composers; entertainers' personalities all come to you with unprecedented fidelity. Such marked excitement results only from the many Thorola secretisms new to radio, its fundamental is a great musical instrument.

The Thorola reproduces, in size and design, radio's perfect true precision construction. Thorola Controlled Music Diaphragms bring radio the highest development in sound re-



See Thorola Radio Models for the full line of Thorola.

production. The exclusive Thorola Separo eliminates blurring and preserves every station. The Thorola horn compound, Thorola, ends compromise with acoustic laws. And, finally, the exclusive Thorola Synthesizer harmonizes your Thorola with your receiver.

Wherever you are, if radio runs, go hear Thorola. New character of government, new stations now heard. Look for The Thorola 10-Day Refund Warranty is a guarantee to assert that Thorola fulfills every claim.

REICHMANN COMPANY
1234-15 West 34th Street, CHICAGO
RADIOSET REPRODUCED THOROLINE

Thorola

THE SPEAKING LIKENESS



THOROLA 4, \$15	THOROLA 5, \$20
THOROLA 6, \$25	THOROLA 7, \$30
THOROLA 8, \$35	THOROLA 9, \$40
THOROLA 10, \$45	THOROLA 11, \$50

Thorola does not sell radio sets. It sells the power to hear. The Thorola 10-Day Refund Warranty is a guarantee to assert that Thorola fulfills every claim.

Everyone interested in radio should have this

68-page book of approved
parts and sets—it's free!

Ward's New Radio Catalogue

ONE copy of Ward's New Complete
Radio Catalogue is yours Free—you
need merely to write for your copy.

It shows you everything new in Radio,
everything that has been tested and ap-
proved by the Radio Laboratories. Simple
instructions are furnished with every Ward
receiving set enabling you to put up and
operate it without outside help.

And the prices on everything in this
book are surprisingly low!

A Price and Quality Guide

Study this Catalogue every time you need any-
thing in Radio, whether parts or a complete set.
See what at the lowest price for standard quality
goods.

Everything shown in this Catalogue has been
selected by an expert. Everything is standard.
Remember at Ward's we never sacrifice quality
to make a low price. Yet our prices are always
low because we sell direct to you by mail—and
without the usual "Radio Profit."



Write for
Your Free Copy

Bring the Joy of Radio Into Your Home

You can get the most enjoyment out of Radio
only by using standard, high grade equipment.
You know what you are getting when you buy at
Ward's. You are sure of high quality as well as
a big saving when you order from this book, for
our Radio equipment is sold under the same liberal
guarantee we have made for 52 years on every
article sold by Ward's—"Satisfaction Guaranteed
or Your Money Back."

Write for your free copy of the new Radio
Catalogue—Write to our home department and
address Dept. 2-R.

ESTABLISHED 1872
Montgomery Ward & Co.

The Oldest Mail Order House is Today the Most Progressive

Chicago Kansas City St. Paul Portland, Ore. Oakland, Calif. Ft. Worth


STATIC PRACTICALLY ELIMINATED BY THE NEW STATIC-CHOKE

REG. U. S. PAT. OFFICE

Radio's most objectionable features reduced to a mini-
mum and tone quality improved to a remarkable degree
by this thoroughly tested and dependable device.

PROGRAMS COME THROUGH AS NEVER BEFORE

INCREASES
AUDIBILITY

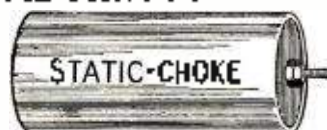

One-Half Actual Size

DECREASES
NOISE

www.americanradiohistory.com

Hadn't I followed that radio writer's in-
struction? I pulled up the easy chair, settled
myself, and with great care and dignity
adjusted the head phones. Apprehensive, ex-
pectant, I turned on the rheostat. The tube
lighted up brilliantly and then suddenly went
out. "Great Caesar!" I groaned, "She can't
be busted!" I turned and turned again, but
the tube very politely and apologetically refused to
respond to my frantic attentions.

In perfect agony, I heard a car drive up
and I knew that in it was my wife, who,
evidently, had been brought home by a friend.
First I thought I'd hide the whole "darned"
mess quickly. That would be better than
being joined with it and displaying it to
Herb's gang when they came in later. But
that was impossible. I just had to try it
once more. And so, once more I wrenched
the rheostat, but to no avail. In utter dis-
gust, I tore off the phones. And the most
surprising thing. The tube lighted at its
own accord!!

Quickly I returned the phones to my head.
I turned the dials until they fairly whirled,
but all I heard was a bedlam of whistles,
scratches, and howls,—enough to wake the
dead. I turned and adjusted, redoubling
my efforts desperately when I heard the
front door open and slam, and a sweet, clear
voice call "Where are you dear?" I gave
the condenser one last, mad wrench and the
set settled into the quiet silence of the tomb
of an Egyptian mummy!

A rather creepy sensation was coming
over me. Somebody was watching me. I
just knew Alice was in the room; I could
feel her eyes upon me; I could imagine how
her little mouth was just twitching to find
the appropriate word with which to begin
as she looked first at me and then at that
clanking mass of boards, and zinc, and
tangled wire. I turned ever so little with
lowered eyes, with the trepidation of a child
caught in a forbidden act. And there, sure
enough, she stood, arms akimbo, eyes a
picture of amazement, mouth quivering, face
flushed with angry blushes. Her eyes
traveled down to my ankles and centered
there so long that I was constrained to look
there myself. What I saw was a pair of
perfectly healthy ankles, undamaged by any
bruise. Evidently I had lost the bandage in
the "shuffle." A groan escaped me. That
must have been the signal for action. She
stepped forward so heavily that the floor
actually shook and began in a high-pitched
voice the harangue to which I had resigned
myself.

"Full Gaskins? Are you a fool? Do you
mean—"


She never got a syllable further. I came
near peeping out of the window. Perhaps
I should have, but I, now, was paralyzed
with astonishment and thrilled into a state
of rapture. I simply could not believe my
ears. Without one whistle, or one scratch,
or one howl, came clearly and distinctly a
voice announcing,—

"This is KDKA, the station of the West-
inghouse Manufacturing Company, East
Pittsburgh, Pennsylvania. . . ."

Unmuffled, I could only gasp, "Pitts-
burgh Pennsylvania! And me in Marshall,
Texas!"

Until two o'clock in the morning I had to
stay up for my wife, for she became so
fascinated that she wouldn't let me have
the head phones for more than a minute at a
time. Cuba, Schenectady, Detroit, Denver,
Los Angeles, Atlanta, Dayton, Min-
neapolis, . . . and the New York Times

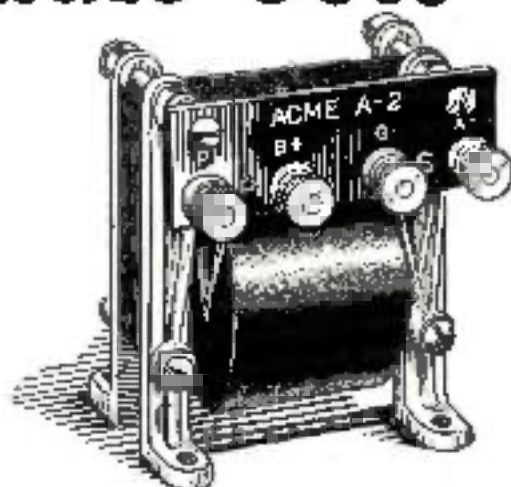This Transformer Has Improved Thousands of Radio Sets - - -



ACME A-2
—for volume.

"... Your letter answering mine of December 10th came just as I got home with an ACME A-2 in my pocket. I installed it in my reflex set in place of the — and believe me you cannot exaggerate its good qualities..." From Winnetka, Illinois.

"... Am using your four-tube Acme circuit, using three audio and three radio transformers, and can pick up any 50 watt station in the U. S. A...." From Fitzsimmons, Colorado.

These are just typical samples of testimonials picked out at random from our files. If we tried to show

them all to you, we'd have to publish a book. You couldn't read them through in a day.

But right here and now today you can, if you will, get the benefit of ACME Transformers. Use them in the set you build. Insist on them in the set you buy. Then your loud-speaker will have a chance to reproduce loud and clear without distortion.

Send 10 cents for 36-page book, "Amplification without Distortion," containing many practical wiring diagrams and many hints for getting the best out of your set.

ACME APPARATUS COMPANY
Transformer and Radio Engineers and Manufacturers
Dept. 71, Cambridge, Mass.

ACME

~ for amplification

ACME APPARATUS COMPANY,
Dept. 71, Cambridge, Mass.

Gentlemen: Enclosed find 10 cents for copy of "Amplification without Distortion."

Name

Street

City..... State.....

Telmaco Acme Receiver

The Ideal Receiver for all Seasons



The Telmaco Acme Receiver is truly portable. May be instantly removed from handsome carrying case and inserted into beautiful two-tone mahogany case. No outside loop, no aerial, no ground required.

Size of Case 8" x 10" x 14". Weighs only 22 pounds complete. Easily Carried.



Acme 4-Tube Reflex Circuit Used

securing selectivity, distance and volume with minimum battery consumption.

Complete in itself. Easily carried from room to room in your home or to office, neighbors, etc. Take it along and have music, entertainment, speeches, news, market reports wherever you happen to be.

Instantly ready for use as it is. You can use external antenna and ground, loop and loud speaker if desired. 4 tubes (fully protected by shock absorber sockets) = equal to 7 tubes, due to reflexing and use of crystal detector.

Reasonably Priced Write for free illustrated circular fully describing Telmaco Acme Receiver.

Complete Telmaco 6" over cabinet containing 20 circuits in blue and describing the best in radio sets compiled for you.

Dealers! Catalog and Price List furnished to all bona fide dealers making request on their business stationery.

Radio Division

Quality Radio
Exclusively
Established 1918

TELEPHONE MAINTENANCE CO.

29 South Wells Street

Dept. B

Chicago, Illinois

It is only a matter of time to descend the ladder from one task to another until the performance of mental work in connection with operating will be a regular thing. Obviously the only solution when matters reach this point is for all operators to refuse to accept employment under such conditions.

I wish to take exception to the use of the word "humble" in Mr. Pyle's article. I do not believe he intends it the way it will generally be interpreted. It seems to me that a policy of some operators in using "too humble" is the direct cause of the subject of Mr. Pyle's complaint. When we succeeded in having our status recognized as that of an officer, it does not follow that we should be more humble than any other officer, but an attitude of fellow-officer, the same as there exists toward each other, is in my opinion the only one to be taken. Modesty and respect for others, as well as for yourself, however, are commendable qualities in all, be he of high or low estate, and when coupled with a thorough knowledge of one's job cannot fail to command respect in return.

Every ship presents its own particular problem, and as circumstances alter cases and every individual is different, a superabundance of plain common sense and good judgment is a prime requisite of every operator. If he has these, it won't take long to adjust himself aboard any ship and uphold his end with credit and to the betterment of the profession.

In the matter of extra tasks, these are usually beyond us sailors and in a spirit of accommodation, but people are prone to take advantage of good nature. This is especially true of sea-captains, so it is always best to let it be known early that there is a limit to this accommodation, or it won't be long before accommodation turns to obligation in the eyes of the Captain.

Another thing mentioned by Mr. Martin, to which I can bear witness (although I didn't know cases of this kind were happening in the past two or three years, as I thought our status as officers was established well enough to preclude this form of abuse) is the habit of some Captains ordering the operator to take his meals with the petty officers. I signed on a ship in 1919, after two years operating in the Navy, during which time I had considerable experience aboard merchant vessels, so I wasn't green. I found, however, I was to eat in the petty officers' mess. When I protested to the Captain, he informed me that his word was law aboard his vessel (note, *Sra Wolf type*) and that if I didn't like it, I would soon find myself in the fore-castle. Later, however, I had the satisfaction of having him come to me with an invitation to eat in the Saloon, which I refused with the implication I found the petty officers preferable as table mates. After a six months' voyage, needless to say, I refused to ship on that vessel again.

I agree with Mr. Pyle in that the dignity of the profession can be recalled and upheld only by the conduct of the men in it. It seems strange, however, considering the growing use and importance of radio in navigation that it should be necessary to be continually fighting in some quarters to maintain our position. It can be readily seen what a handicap a young operator just out of school is laboring under should he find his first assignment aboard a ship where such antagonistic ideas are prevalent. Incidentally, the profession in itself is a handicap, in that it is one into which a great amount of new blood is always being infused. New blood in itself is well enough and is essential in all lines of endeavor, but where this fact alone is a cause of contention with some Captains and Steamship Companies it requires a particularly high type of man to overcome this disadvantage.

The schools, as Mr. Martin says, can help to remedy the situation to a great extent in



Don't—

—Let your batteries get run down. If you do you are bound to have a lot of grief.

With a Jewell No. 55 on your receiving set panel you can check your batteries daily recharging them when needed.



Double and Triple Reading Instrument for Receiving Set Panel.

Order from Dealer

Ask your dealer or write for our 15-A Catalog.

Jewell Electrical Instrument Co.

1650 Walnut St., Chicago
"25 Years Making Good Instruments"

The Brandola

The Ultimate Radio Receiver

One dial—six tubes

List Price \$125.00

The J. F. Brandola Corporation
336 Oxford Street
Newark, N. J.

MAKE MONEY SELL MADISON SHIRTS
Direct from our factory to you. No middlemen. No capital investment required. Large steady income. Many shirts sold weekly. Write for free samples. Madison Mills, 555 Broadway, New York.

The RED SEAL VARIABLE CONDENSER



At Last—an ideal vernier to control a low-loss condenser

You have probably often wished for such a combination. Now for the first time the vernier of the Red Seal enables you to easily take full advantage of high condenser efficiency without tuning right through the sharp peak of the wave.

No more slipping, lost motion, or tight bearings. No more tuning with one knob and adjusting with another. All the adjusting may be done with the vernier knob alone.

The above does not give you an adequate picture of the Red Seal Condenser. Go to your dealer and ask to see it. As you operate the vernier for yourself, note these six important features which make it the ideal control for this efficient, low-loss instrument.

1. The action of the vernier is positive, giving delicate, smooth adjustment.

2. There is no lost motion or play at any point.

3. All tuning may be done with the vernier alone.

4. Only one dial setting—stations easily logged.

5. There is no fibre, rubber, or gears. Nothing to wear or get out of order.

6. Plates turn freely. Balanced vernier eliminates need for friction at bearings.

The Red Seal has four other points of note:

1. Plates are of brass and are soldered.

2. Spring "pig-tail" connection employed.

3. End plates are grounded, eliminating the effect of hand capacity. For supercritical work, insist on the Red Seal Variable Condenser.

4. To facilitate tuning the movable plates are given a special shape, making the Red Seal of the "straight-line" type.

Manhattan Electrical Supply Co.

Incorporated

New York

Chicago

St. Louis

San Francisco

Manhattan

RADIO PRODUCTS

MADE BY THE MAKERS OF THE FAMOUS RED SEAL DRY BATTERIES



Manhattan Junior Loud Speaker

A real musical instrument containing a specially designed reproducer unit for loud speaker work. Not just a headset in a base. Has "Concert Modulator" adjustment giving best results under all conditions—\$10.00.



Red Seal Headset

Designed for "DX" work. Tone quality excellent. Workmanship the best. No distortion or chattering. Bakelite case, soft rubber sanitary headband—\$6.00.



Red Seal Phonograph Attachment

Makes a loud speaker of your phonograph. A high grade reproducer reproducing the work of the broadcasting artists with fidelity—\$5.00.



Red Seal Batteries

The dependable dry battery for "A" circuits. Long operating life and great recuperative power make Red Seals ideal for radio work. Sold by all classes of dealers. Remember, fresh Red Seal brings in fresh stations.

Folks! meet a friendly condenser

Dear Fred:

I didn't know what a real job my Radio was until I equipped it with the Rathbun Superior Condenser. The single-hole mounting feature certainly saves a lot of time and trouble. Thanks for the tip.

I'm driving to the city Sunday and hope I'll find you home.

Your friend,
Bill



You fellows who don't claim to know all about condensers, may learn something worth while about a friendly condenser. You, too, may not know what a real job your Radio set is until you equip it with a Rathbun single-hole-mounting Superior Condenser.

Compare 'em at your dealers or write (mention Radio News) for complete details. Prices: "3 to 45 Plates"—\$1.00 to \$6.00. Rathbun Manufacturing Company, Inc., Jamestown, N. Y.



RATHBUN

SINGLE-HOLE MOUNTING
SUPERIOR CONDENSERS

Molded on every original single-hole-mounting top-top unconditionally guaranteed Condenser.

Real reason
for the success
of the Rathbun
Condenser is
its simplicity.

Real reason
for the success
of the Rathbun
Condenser is
its simplicity.

Real reason
for the success
of the Rathbun
Condenser is
its simplicity.

The Commissioners of Lower Merion Township
Montgomery County, Pennsylvania
Township Building

W. L. Rathbun
Jamestown, N. Y.
Rathbun Manufacturing
Company, Inc.
Jamestown, N. Y.

W. L. Rathbun
Jamestown, N. Y.
Rathbun Manufacturing
Company, Inc.
Jamestown, N. Y.

Indinor, Pa. Gladys, Pa.
Sept. 19, 1924

Electric Specialty Company
Stanford, Conn.

Dear Sir:

Upon arrival of your type 8000 generator I immediately coupled it to a Westinghouse 1 Hp. motor. After running it about two hours I connected it to my transmitter which uses three 50 gull tubes. Not only did it work but it put FORTYFIVE STABLE 1000 RADIUM, OCEANIC and FLORESC, ITALY.

I think the above statement shows how much I appreciate the generator.

My card from Italy reads as follows.

Radio 387A: Or sign had by very very 2m at 5.27 and 5.35 A.M. Both broad day-light. No Qs, Aug. 20. It was one of the loudest of 14 American sets had to A.M.

Sig.

F.B. Huddy
U 111 124

Since that time I have worked every district in the U.S. in one night, also three Canadian provinces.

Very truly Yours,
Bertie F. Barker
u3bba

P.S.

You may use this letter in conjunction with any of your advertisements as I stand by and for the ESO generators.

providing truthful instructions as to the various conditions likely to be met with aboard ship. But experience only can give that confidence and knack of "fitting-in" before one is accepted as a member of the "Sea-going Fraternity."

Wm. S. MARKS,
Opn. SS. Birmingham City.

FROM AN ENGLISH OPERATOR

Editor, Radio News:

Regarding the correspondence in your esteemed paper between 2LZ and 5XZ, I should like to correct some of their impressions, etc.—comparisons of English and American radio work.

Surely 2LZ was not serious when he stated that it was impossible to tune out 2LO in London, he has only to peruse the pages of "Modern Wireless," to note reports of sets there, on which this has been done.

Regarding English and American periodicals, the former can certainly hold their own. For instance, in the September issue of *RADIO NEWS*, appears an account of oscillating crystals, now with 2LF please note that an article on this subject appeared in the August number of "Modern Wireless," and also one in "Wireless Weekly" previous to this.

Another of your contributors, Mr. James Vinal, speaks of *The Work*. Does he know that 2LO is practically consistently received in the Mediterranean Sea (2,000 miles) on a crystal, and has been heard as far down as Persia? Also 2LO has come built in Calcutta and South Africa, on a Marconi set, of which, still another of your correspondents, Mr. Howe, does not seem to have a great opinion.

Mr. Howe has certainly some receiver if he can only get British broadcasting up to 500 miles.

Considering programs, the British stuff, in my estimation, is undoubtedly the best.

Tubes in England cost far less than they do in the States, for instance, the best bright emitters retail at 12 shillings, 6 pence and 10 shillings, for example; the Canadian Myers tubes, selling in the States for \$5, cost but 12/6. (\$3), in England.

Perhaps Mr. Howe will remember that there are also English operators sailing consistently to American ports, who are quite as well aware of American conditions as Mr. Howe seems to be unaware of English

Chief Operator,
R. F. ELLES,
S/S *Talitha*,
(English)

BRITISH vs. AMERICAN BROADCASTING

Editor, Radio News:

It has been my privilege to read extracts from your paper in which various correspondents have argued as to the relative merits of British and American broadcasting.

The line unfortunately taken by certain of your correspondents has been wholeheartedly to condemn British broadcasting in favor of America. The writers may or may not have been to America. In one case certainly a direct comparison was made; in the other case (a certain Mr. Mayer) I should very much doubt if the comparison had been made under the same conditions.

There are always to be found in all countries people who are ready to condemn their fellow-countrymen, and over here I have often run across Americans who have condemned American broadcasting, but they, at least, have had the decency not to publish their views in our English journals.

It would seem to me to serve very little useful purpose to make hasty comparisons, inasmuch as the conditions in the two countries are wholly different—a fact that none of your correspondents seem to have



Exclusive features give Erla Miniature Condensers high efficiency. Dielectric and resistance losses absolutely minimized. Compensating plate form. 3 to 41 plate—priced \$1.50 to \$5.50 each.




Unequal smoothness and sensitiveness bespeak the advanced design of Erla Precision Rheostats. Single hole mounting eliminates need for disassembly. 5, 25, or 40 ohms. Price \$8.10 each.



Built for permanent true running; with Bakelite knob shaped for sensitive touch; and highly elastic calibration. Erla dials better any made. Three sizes for 1/2, 1, and 2 inch shafts. Price, 50c to \$1.25.



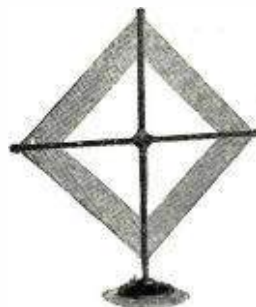Now approached in design, and perfect construction, Erla Synchronizing Transformers stand alone as an aid to maximum amplification, selectivity and tonal purity. \$5.00 each.



Adding to receiver efficiency is the advanced Erla Loop. Rigidly angled—completely folded—easy in rotation—beautifully finished. Standard and De Luxe models. \$7.50 and \$10 respectively.



CIR-KIT builds new Supereflex —Greatest of Erla Circuits

Erla led the radio amateur out of the wilderness of circuits. Erla initially introduced exclusive circuit ideas which made radio history, particularly because those ideas have uninterruptedly kept Erla circuits in advance of contemporary radio.

Remarkably significant is the fact that so many thousands of seasoned experimenters, once attracted to Erla circuits, consistently adhere to Erla. So there is a note of finality when Erla now announces the new Erla Supereflex Circuits. They represent highest development of the inherently superior Erla principles, acknowledged responsible for the most powerful circuits ever built, tube for tube.

Bringing these latest and finest circuits within the reach of everyone is the Erla CIR-KIT, effecting not only extreme economy, but also greatest ease of con-

struction. Only screwdriver and pliers are needed to transform any Erla CIR-KIT quickly and skillfully into the most efficient of radio receivers.

CIR-KIT provides you with everything including specially designed Erla Synchronizing Transformers, Erla Certified Capacity Condensers, Erla Cushion Sockets, and finally Erla famous Solderless Connectors, banishing all solder difficulties. Each unit and connection is unerringly located through full-size blue-prints; drilled, lettered panel; and stenciled baseboard.

With Erla CIR-KIT you yourself can confidently and proudly put into finished form the highest achievement of Erla radio engineers—Erla Supereflex Circuits. CIR-KIT receivers of one to five tubes are available, in loop and antenna types. See the Erla dealer, or write direct, mentioning your dealer.

ELECTRICAL RESEARCH LABORATORIES
Department C, 2500 Cottage Grove Avenue, CHICAGO

ERLA

Circuits of Certainty

SENSATIONAL PRICES ON GUARANTEED RADIO Sets and Accessories



\$57.95

with \$9.50 Loud-Speaker, \$6.00 Phones, 3 Dry Cells, 90 Volts, B Battery, complete Antenna, and 4 Dry Cell Tubes—Nothing else to buy.

\$69.95 COMPLETE

with all above equipment for use with

STORAGE BATTERY

Battery Compartment as shown \$4.45 extra.

Guaranteed Highly Selective Coast to Coast Range and Most Volume

at lowest prices. Use with or without aerial. Save about one-half. Completely wired and ready to install.

\$49.95 Complete for 3 tube set with \$9.50 Loud-Speaker, \$6.00 Phones, 3 Dry Cells, 67½ Volts, B Battery, 1 Tube and complete Antenna. \$41.95 with storage battery.

2-tube set complete with \$6.00 Phones, 3 Dry Cells, 45 Volts, B Battery, complete Antenna and 2 Tubes. \$44.25 with storage battery. **\$32.95**

\$19.95 for complete 1 tube outfit with 3 Dry Cells, \$6.00 Phones, 22½ Volts, B Battery, Tube and complete Antenna.

Sets can also be purchased alone. Also accessories. \$6.00 Phones for \$3.49—\$4.00 Tubes at \$1.00—B Batteries, \$1.42. Scores of other bargains.

Send order direct and pay on delivery or write for FREE literature to get all the details. Reference—The Atlas National Bank, Cincinnati, Ohio

THE MELLODYNE RADIO CO., Dept. A Cincinnati, Ohio

Send For
FREE
RADIO
100 Pages CATALOG You Need it!

Described full of radio sets and parts at reduced prices. At all levels of complete radio sets, parts and accessories.

LIBERTY M. O. HOUSE
Dept. 5752, 104 Liberty St., N.Y.C.

No letter needed—just write your own name and address. (If any new mailing, your out of 3rd year—NOW!)

MOVIES IN YOUR HOME

Our marvelous, beautiful MOVIE MACHINE will let you see 16 mm. films at home. We also have a special film of latest price—only a few days more. Write NOW for free catalog.

PARAMOUNT MFG. COMPANY
Dept. 24, N.Y.C.

DEALERS

WE CAN SAVE YOU MONEY!

Standard Guaranteed Lines. Send for latest Catalog Book on Quality Radio Apparatus.

RADIO MATERIAL SUPPLY COMPANY
52 N. Wells St. Dept. 110 Chicago

recognized. Americans who have been over here—and we have met many who are responsibly connected with American broadcasting—have on the whole expressed the opinion which I expected them to: namely, that British broadcasting was, at any rate, equal to American broadcasting. But of course the conditions on the technical side were entirely different.

The chief complaint against British broadcasting is that the signals are weak. If I were to enter into a foolish vituperative argument, I could point out that London has been heard in Rome at night, has been picked up in South Africa, that people dance to the Savoy bands in Ireland, that Cardiff has been heard in the Azores—in fact, I could give a list of information of this sort backed by written reports, but it seems to me that I would serve very little purpose.

Professional radio engineers are agreed that with a station employing 1½ k.w. power to the anodes of the oscillators it is not worth while listening to such a station at ranges much over 30 or 40 miles, as the listener is to have a sole interest in the program.

I know that many people will entirely disagree with this remark, and perhaps in America you have far better ranges than these. I am not talking about a station being heard, but about a station coming out of a local speaker in no way different from the voice of the announcer at the other end, undisturbed by atmospheric, humming or a background of mush.

In England, at any rate, our stations are no better than this, because we have concentrated not on power, but on quality, and we think that our quality is about as good as any in the world, and our view is confirmed by many persons who have visited all the broadcast organizations.

For this reason we have tried to cover the British Isles with broadcasting by a great number of stations. We have, as I said before, an entirely different problem, and we are able so to duplicate stations on account of our population being far greater over the whole country than that in America. I think I am right in saying that if and when our new 25 k.w. station is opened, something like 80 per cent. of the population of the British Isles will be able to receive broadcast on a crystal.

This is the problem, as we see it—to make broadcasting possible for all, and it would be interesting to compare figures as to crystal reception with America. I would ask your correspondents both on the other side of the water and on this to approach this matter of comparison in a somewhat more open frame of mind. It is so useless making irrelevant comparisons, if the conditions and very possibly the ideals of the two organizations are so widely different.

It always has been of the greatest interest to me to talk about broadcasting in America when I have come over here, and they one and all have confirmed me in my view that, seeing that the problems are so widely different, we have solved ours as adequately as they have solved theirs. In cases, he it whispered, they have said that we have done better, owing to a surfeit of control.

P. P. BURNLEY, M.I.E.E.,
Asst. Controller & Chief Engineer,
The British Broadcasting Company,
London, England.

MORE FROM MR. BAYES

Editor, Radio News:
I read with considerable interest your September issue, which only reached here in September, and not in August, as in the United States, and of the letters therein printed I will deal with 21.2 and 31r N're first.

I am sure I thank both gentlemen for their expert criticism of my "talking



And now the **Andrews Deresnadyne—** *successfully combines tone quality and selectivity with distance and volume*

Hitherto it has been possible to purchase in a radio set one of two groups of qualities—tone and selectivity on the one hand, and distance and volume on the other—but not both. Now the Andrews Deresnadyne 5-tube Radio Receiving Set, using the new Deresnadyne principle of the balanced plate circuit, for the first time successfully combines the two. It secures the finest tone and high selectivity with increased volume and distance.

The tone quality of the Deresnadyne has never in our belief been equalled by any radio set on the market. It brings to the home for the first time a reproduction of music really comparable to the original. In volume the Deresnadyne will give anything from a mute tone to a volume that fills a large hall. It is highly selective. It will go through a powerful local station to reach a weak distant station with only a few meters difference in wave length. This selectivity is secured by the remarkably low resistance of specially designed transformers. It secures great dis-

tance by conserving signal strength through unusually close transformer coupling. The Deresnadyne circuit stops the oscillation which produces whistling and distortion in the plate circuit, before it reaches the grid, which is extremely sensitive and where all adjustments are very critical. It is the only circuit which stops oscillation at its source, where it can be easily and efficiently controlled.

The Deresnadyne is extremely simple in operation and construction. It is easy to log. You can change from 1st to 2nd stage or turn off the set by simply turning the switch knob, eliminating jacks and plugs. A special feature is the Plate Balancer, which enables you, by simply turning a knob, to accentuate either tone quality or distance, as you wish. The case is genuine hand-rubbed mahogany.

Few sets have ever received the enthusiastic comments of radio authorities given the Deresnadyne. Robert J. Casey, head of the Chicago Daily News Laboratory says about it: "The circuit combines selectivity, range and quality in a degree that will astonish the old experimenter." Hear the Deresnadyne at your dealer's. Or write to us.

DEALERS: Order through your jobber. **JOBBER:** Exclusive rights in open territory may be secured by aggressive jobbers of high standing.

ANDREWS RADIO COMPANY • 327 S. LA SALLE STREET • CHICAGO

Andrews
Deresnadyne
DE-RES-NADINE • PATENTS PENDING
Radio Receiving Set

Price, without accessories

\$150



The Halldorson 4-tube set \$75.00

THE Halldorson 4-tube set for \$75.00 is one of the greatest values ever offered in radio receivers. Everything formerly found only in high-priced sets you'll now find here.

The set is tuned radio-frequency, easy to tune and operate. Constant range. Highly selective-large volume, with a clear mellow tone. Easily logged—a remarkable feature usually found only in 5-tube sets.

The workmanship and material are of the best—standard parts throughout—highly polished mahogany case. The panel is of insulated steel, in a beautiful stucco-ripple finish, with large handsome dials.

See this set at your dealer's today. If he cannot supply you, write direct for complete description.

Also the Halldorson 5-tube Radio Frequency Receiver. A superior set, unequalled for fine quality and all-around performance. A wonderful value at \$115.00.

Halldorson Radio Frequency Receiver

THE HALLDORSON COMPANY, 1772 WILSON AVENUE, CHICAGO

Hafner-Meter
for "A"
Batteries



\$1.00 Each

"Have a Hafner Handy"

Test your Batteries with

HAFNER HYDROMETERS

Specially designed instruments for testing both "A" and "B" batteries.

Floats have small glass heads to prevent sticking to the side of the tube.

They are also plainly marked for quick reading and will tell you at a glance condition of your battery.

Guaranteed Accurate

Can also be used to refill your battery with distilled water.

Hafner-Meter for "A" batteries.....\$1.00

Hafner Hydrometer for "A" batteries..... .75

Hafner "B" battery hydrometer..... .75

Inquire of your local dealer. If he cannot supply you, remit to us together with his name and we will see that you are supplied.

Hafner Manufacturing Company

3132 Carroll Ave.,

Chicago, Ill.


American," so much. Particularly 2LZ. I had the pleasure of doing a good bit of liaison work with your engineers in the war and generally made myself understood. As to "Hootleg", I heard it long before the Volstead Act came into force meaning, as you say, illicit. In a country where no receiving set can be fitted "a hootleg station" necessarily means an unlicensed transmitter and as such I took it to mean. Personally, were I financially able I should be only too pleased to entertain Mr. Gernsback as my guest, but being in a country where the war devastation in commerce has caused unprecedented depression, I have to be thankful I have a job paying \$25 per week so I can't do much international entertaining. I will, however, do whatever I can, if he cares to come, and can put him wise to DX merchants, if he chooses. Last winter I could always get four or five R.R.C. stations at two miles from 2LZ on a single circuit tuner with one tube, and on two tubes our office boys gets all but 6RM, so I must conclude that 2LZ is a poor hand. I hope for the sake of the transmitting fraternity his first is better. Why he should be proud of putting out mystery retransmissions of 2LZ on short wave I don't know. Capt. Ian Fraser, the totally blind flem, did it some time ago and gave his call sign and it was free from distortion. If 2LZ's reception is so poor, why bother to retransmit the received signals? They cannot have been very enjoyable. If you know how, you can pick up 2LZ on 94 meters or thereabouts, and it makes a useful test with short wave sets. 2LZ doesn't know, of course, that your correspondence column is a little behind hand, so will be unaware that my letter was written before the increased powers of 6 k.w. and 25 k.w. were authorized. As to the rebroadcasting stunt, what I meant in my original letter was to enquire, if a country where radio is dead can do it with special arrangements, why can't the only country (?) where it is alive, do it without.

As to Mr. Nitro and tuning dead on the allotted wave, doesn't Mr. Nitro know that the Hams do not, here and in the United States, have any allotted wave? They have an allotted wave *band* reference to an allotted wave are (in the minds of anyone who knows anything of the subject) necessarily limited to commercial and broadcast stations with fixed schedules.

Both gentlemen mentioned above seem to think that my criticism of your programs is based on the quality of the received signals. My criticism was intended against the programs themselves, i.e., the selected items for transmission, not the quality of the transmission, which owing to swinging, fading, etc., is often distorted when received here. I don't blame the distortion on the engineers of your big stations, but some of the little ones do need scratching up, now don't they?

To our friend the operator on the S.S. *Rondo*, I can only say that he is a first-class distorter of the truth. I suppose he doesn't realize that some of us may, by reason of business, come in daily contact with the Americans who visit us so often and he well aware of how often so many of them are (until they know us better), so full of bombast and self adulation. I have no peeve against the Yanks, as I have some very good friends and correspondents there but I have against people who lie about affairs in my country. How does Fred. Hurve account for the fact that all the R.R.C. stations are received in Geneva, Switzerland, on two tubes using a factory-made standard instrument, that 2LZ has been heard in Calcutta, India, in South Africa and the Argentine? His 320 miles is some exaggeration. Believe me. Taking the Harmsworth Encyclopedia as the latest authentic British information is pure foolishness, and he knows it. Was that the only paper he read?

I do like Mr. Howe; he must have con-

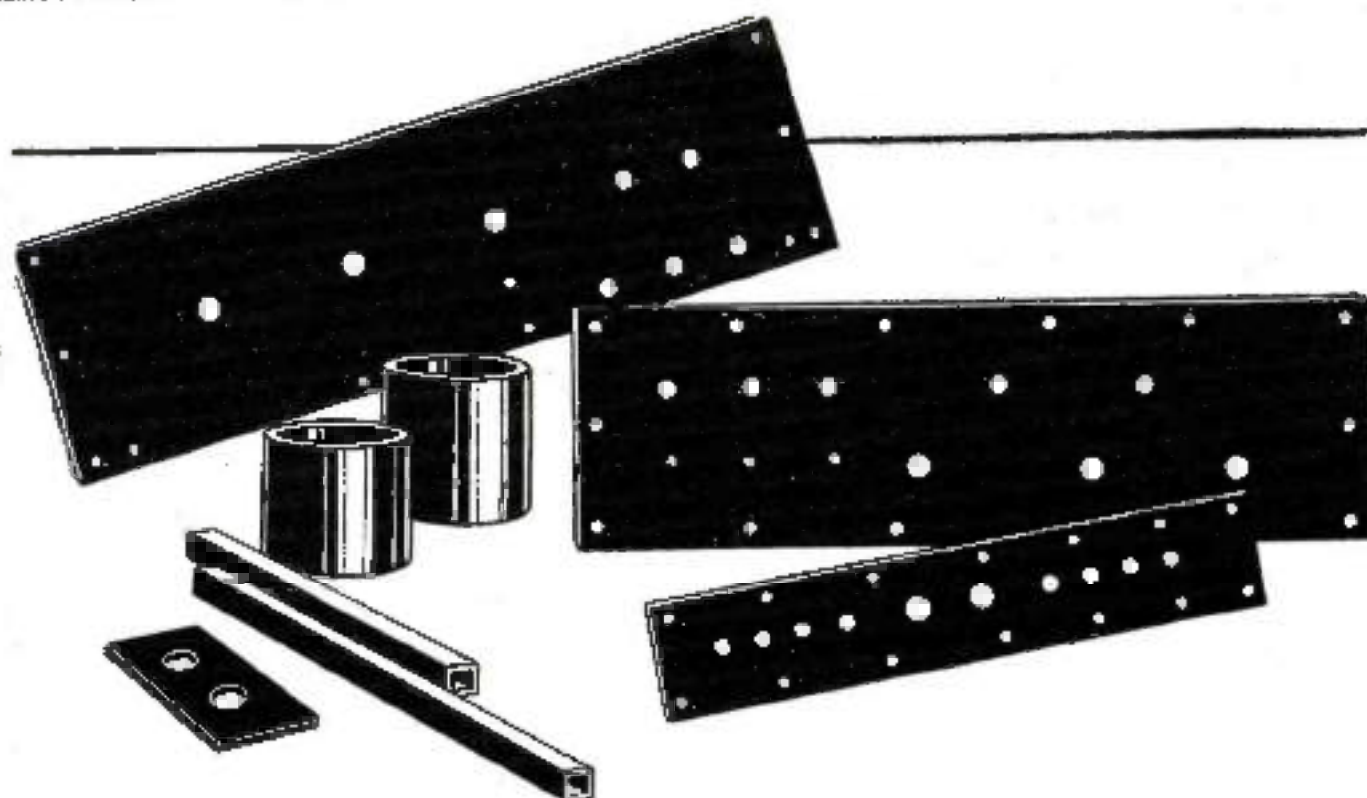

Why is Formica the leading radio insulation?

THE demand for Formica for radio insulation has forced the building of the largest plant in the world for the production of laminated bakelite — and the only plant in the world devoted exclusively to this one product. This year 60,000 feet of floor space have been added to assure everyone prompt service.

This volume has been built up because Formica production under close laboratory control has provided the most uniform, best looking, and most easily worked material. It is used by 125 leading radio manufacturers who have tested all materials and who know that Formica is best!

There are four beautiful finishes: Gloss black, dull black, walnut and mahogany. Formica will not sag under the weight of condensers and other instruments; it will not cold flow under the pressure of screws and binding posts; its insulating strength gets better with age.

It is being used by many manufacturers for front panels; base panels; terminal strips; transformer cases; condenser ends; for jack, head phone and loud speaker insulation.

Dealers: Formica advertising and sales promotion will be greater this year than before. No other product is so well known for quality.

THE FORMICA INSULATION COMPANY
4618 Spring Grove Avenue, Cincinnati, Ohio

Sales Offices

50 Church St., New York, N. Y.
122 First Ave., Pittsburgh, Pa.
1142 Granite Bldg., Rochester, N. Y.
415 Ohio Bldg., Toledo, Ohio

1210 Arch St., Philadelphia, Pa.
1326 Second Ave., S. Minneapolis, Minn.
385 Mission St., San Francisco, California
Whitney Central Bldg., New Orleans

516 Easton Bldg., Cleveland, Ohio
3 S. Clinton St., Chicago, Ill.
708 Tule Bldg., Baltimore, Md.
47 King St., Toronto, Ontario



FORMICA

Made from Anhydrous Bakelite Resins
SHEETS TUBES RODS



TRF-50

A handsomely carved cabinet—a most efficient 5-tube circuit with Unit Tuner—built in Magnavox Reproducer. The receiver you have been waiting for; study the details.

MAGNAVOX

Receiving Sets which establish an authoritative standard of excellence for the daily enjoyment of radio.

LONG identified with the most efficient radio reproducing and amplifying equipment, Magnavox has developed its new Receiving Sets under conditions insuring superior design, precision of manufacture, and a gratifyingly low cost.

Exacting tests prove that the Magnavox Receiver is not only the simplest to operate but one whose daily performance will satisfy the most discriminating.

Magnavox Radio Receivers, Vacuum Tubes, Reproducers, Power Amplifiers, and Combination Sets are sold by reliable dealers everywhere.

THE MAGNAVOX COMPANY, Oakland, California
 New York: 350 West 34th Street San Francisco: 274 Brannan Street
 Canadian Distributors: Perkin Electric Limited, Toronto, Montreal, Winnipeg

Receiving Sets

TRF-50 (as illustrated above)—is a 5-tube tuned radio frequency receiver with carved doors and built-in Magnavox Reproducer \$150.00



TRF-5 is identical with TRF-50 but enclosed in smaller cabinet without built-in Reproducer \$125.00



Type A and Type D—Six-volt storage battery amplifier and detector tubes with waxy base \$5.00



W.L. Douglas

\$5, \$6, \$7 & \$8 SHOES

BOYS AT \$4.50 & \$5.00

Women of fashion should know that our women's shoes are high-class, made in the most distinctive, up-to-date and exclusive styles, which appeal to those who desire stylish, comfortable and serviceable shoes at reasonable prices.



New Two Oxford for Women
Attractive pattern in light
Broom calf with seam welt.

W. L. DOUGLAS PEGGING

SHOES AT 7 YEARS OF AGE



New French Toe for Men
Smart style in light
Rabbit calf at a popular price, \$5.00

WEAR W. L. DOUGLAS SHOES AND SAVE MONEY

FOR 34 YEARS, W. L. Douglas' name and portrait have stood for quality, for economy and for satisfactory service. W. L. Douglas shoes are exceptionally good values. Only by wearing them can you appreciate their superior qualities. The exclusive, smart models, designed especially for young men and women, are leaders everywhere.

W. L. DOUGLAS \$7.00 SHOES are remarkably good value. Seldom have you had the opportunity to buy such high-grade shoes at this popular price. Shoes of equal quality, comfort and service are rarely found in other makes at our prices.

WHEREVER YOU LIVE demand W. L. Douglas shoes. They are sold in 120 of our stores in the principal cities and by over 5,000 shoe dealers. For economy and dependable value, wear shoes that have W. L. Douglas' name and the retail price stamped on the soles. The stamped price guarantees the value. If not for sale in your vicinity, write for catalog. W. L. Douglas Shoe Company, 172 Spark St., Brockton, Mass.

Thousands Now Know This
to be the Greatest Radio
Value Ever Offered

"Pacific Quintet" Super Het-Kit \$15

(45,000 cycle)
Complete Super-Heterodyne Receiver May Be Built For \$45.00

A remarkable value, made possible through huge quantity production. Build your own Super-Heterodyne, or have your dealer build it for you. Rebuild or convert your old set to a modern and advanced type Super-Heterodyne. All other parts required are standard. Hook-up print with complete and simple instructions packed with each "Pacific Quintet" kit. Foresight and Advanced Engineering Efficiency now bring the latest and most popular developments within a price range to suit the average pocket-book.

Send us your dealer's name and we will ship TO ANY ADDRESS upon receipt of \$15.00 or C.O.D.

Dealers & Builders
Write for literature
[Address blank]

BALDWIN-PACIFIC COMPANY

441 Pacific Building

San Francisco

Approved by Leading
Dealers, Jobbers and
Manufacturers Everywhere

**PACIFIC
RANGER
SUPER HET
KIT**

BALDWIN-PACIFIC CO.

Substitution
Guaranteed
Early Shipped
merchandise
built for test
work

"Pacific Quintet" Super-Het Kit
Consisting of 1 Pacific "Ranger" No. 10 (oscillator Coupler), 1 Pacific "Ranger" No. 25 Intermediate Frequency Transformer, and 1 Pacific No. 29 "Ranger" Filter Transformer



Wholesale
Radio
Equipment

Same Day Shipments

HUDSON-ROSS

Sells only nationally advertised radio apparatus.

Send for discounts.

123 W. Madison St. Chicago

ing is a little known sport. Indeed, most of the tube sets are not especially conducive to "DX." I have had two German sets, one with three tubes and the other with five. With the first I could hear the Stuttgart broadcast station located a mile and a half away moderately well, and with the second not quite so well; as for any other broadcasting, not a peep! I do not mean to imply that there are not a good many German sets with which one can hear London and Paris and other "DX" to the extent of 500 miles or so, but it may be admitted that my first experience was a little discouraging; so I resolved upon the typically American expedient of building my own. With a few parts screwed to a drafting board, I now manage to pull in most any of the European stations which use a respectable transmitting power. For Europe, 500 watts is to be considered very respectable.

A few words then, as to European broadcasting. The two most important stations are Radiola at Paris and London 2LO. In the August issue of Radio News, the power of Radiola is given as 15 kw., under the title, "The New French Broadcast Station." It is true that the equipment provides for this amount of energy, but as a matter of fact only 1.5 to 3 kw. are actually used. I am located only about 300 miles from Paris, but hear Radiola scarcely louder than London 2LO (Chelmsford transmitter) 450 miles distant. Chelmsford, by the way, seems to be almost unknown in the U. S. This is a transmitter at the Marconi works near London which transmits the programs of 2LO with an energy of something like 5 kw., at a wave-length of 1,600 meters. This new sender is vastly more powerful than the one using 365 meters, which is occasionally heard in New York. At 365 I get London just loud enough to be comfortably followed with the phones, but at 1,600 meters, the same program may be heard on the loud speaker a block away. This bit of information ought to be of great interest to all DXers. 2LO sends daily, almost continuously from 4 to 11 p. m. often until midnight. There is always a pause between 7.30 and 8. Chelmsford appears to be in use only from 8 o'clock on. It should be remembered that London and Paris as well, are six hours ahead of New York. Radiola sends from 12.30 to 2, from 4.45 to 5, and from 9 to 10.45, using a wave-length of 1,780 meters. The Eiffel Tower, at 2,600 meters, gives a concert daily at 6.15, which comes in here just about as strong as Radiola. American jazz is the popular form of music in London and Paris, so don't be surprised to hear familiar melodies floating in at these wave-lengths. The German stations use only about 500 watts, and would scarcely be audible in America. Frankfurt (90 miles), Munich (120 miles), and Berlin (300 miles) all come in with about the same strength as London on 365 meters. Berlin is reputed to use something like 1.5 kw., however. The stations are all under the control of the Post-Office Department, and are supported by the contributions of the licensed listeners, which are collected at the rate of 2 marks (50 cents) monthly by the letter-carrier. Naturally, there are *Schwarz-Hörer* ("black listeners") who do not pay their share, but the penalty is fine and imprisonment. The system works quite well, in general, and the programs are good. As a general thing, only receiving sets approved by the postal authorities and guaranteed not to radiate or go above a wave-length of 700 meters are permitted. However, an experimental license to build what you like is obtainable on joining an approved radio club and passing an examination on the technical side of radio. The authorities are, above everything, bent on keeping off the speaking nuisance. Experimenting with regenerative sets is quite verboten in the periods when the local sender is in operation. The wave-

Insure your copy reaching you each month. Subscribe to Radio News—
\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



Anti-capacity JACKS



Anti-capacity SWITCHES

Lower-Loss
VernierVARIABLE
CONDENSERS

Lower-Loss PHONE PLUGS



Lower-Loss

RHEOSTATS



Lower-Loss

SOCKETS




Lower-Loss

VARIO-
COUPLERS

Lower-Loss GRID LEAKS



Lower-Loss

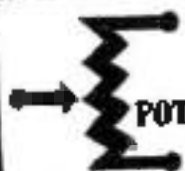INDUCTANCE
SWITCHES

Lower-Loss

POTENTIOMETERS

NO SOLDERING—LESS DRILLING—SCIENTIFICALLY BUILT

For Your New Hookup—

Build with less work and have a better set.
Build with JOS. W. JONES RADIO PARTS.

Less drilling—no soldering—contact by simple binding posts.

Whatever the hookup, Jos. W. Jones parts will increase its efficiency.



\$1
Double Circuit
JACKS

JOS. W.
JONES

Anti-
Capacity



\$1
"A" Battery
SWITCHES

Jos. W. Jones Jacks—made for radio use only—have no long parallel leads, and so eliminate capacity effects. Binding posts make connections simple—no soldering. Jos. W. Jones switches are also anti-capacity. No soldering. The little red button shows outside the panel.

For Better Results Build With JOS. W. JONES

Jacks	Switches	Variable Condensers	Phone Plugs
Vario Couplers	Rheostats	Potentiometers	Grid Leaks
Inductance Switches	Sockets		


JOS. W. JONES

TRADE MARK.
"IMPROVED"

radio parts


JOS. W. JONES RADIO MFG. CO., Inc., 40-42-44-46 W. 25th St., New York
(Formerly Radio Engineering Co.)

Headed by JOS. W. JONES—for 28 years a successful engineer
and builder of precision instruments.



**Weston
Radio Plug**
75 Cents Everywhere

**Weston
All-Purpose
Voltmeter**



Insist on getting a Weston Plug—the original full automatic Radio Plug that defies imitation in design and quality of workmanship. There will be a sense of both satisfaction in possessing one of these plugs. Only two seconds to change from head-phones to loud speaker. No tools required. Simply necessary to shove in telephone terminals to connect. To disconnect press the little plungers and remove the terminals.

A double range voltmeter with ranges of 7.5 and 150 volts arranged for either portable use or switchboard mounting. Built by America's pioneer maker, the recognized instrument authority the world over.

Get the best results from your set and the resulting satisfaction by adjusting the filament voltage with an accurate and dependable voltmeter and when this is done it will then only be necessary to tune in for the station desired.

Will save your tubes, improve reception and will save discharging toxic "B" batteries which have not outlived their usefulness.

WESTON ELECTRICAL INSTRUMENT CO., 173 WESTON AVE., NEWARK, N. J.

Electrical
Indicating
Instrument
Authorities
Since 1888

WESTON

STANDARD - The World Over

Burnt-Out Tubes Replaced



All Standard Types

Burnt-out, Defective or Broken Tubes of any brand or make whatsoever will be replaced by a brand new Royaltron Tube, at a cost of only \$2.25. Take this advertisement with your old tubes to any ROYALTRON dealer, or send them direct to us with \$2.25.

\$2.25

Special Offer on New Royaltrons

If you have no defective tube, send us this ad with the name of your nearest dealer, and we will send you a new tube, any type, for \$2.40. This offer limited to 5 tubes to one customer.

It is with the object of advertising the MERITS of ROYALTRON Tubes, that we make this above special offer. ROYALTRON TUBES are regularly priced at \$4.00. "A ROYALTRON USER NEVER CHANGES"

ROYAL MANUFACTURING CO.

206 BROADWAY Dept. N NEW YORK

Special Precondition to Distributors, Dealers and Radio Clubs

Manufacturers of Radio Parts (No Sets)

As large Wholesalers only and carrying stock in eight largest Cities in Australasia, we can give standard lines exclusive representation. Send us your catalogue and samples by Parcel Post, which we will pay for or return.

UNITED DISTRIBUTORS Ltd.
Sydney, Australia

Cable Address: "SUPERIOR"

Representatives: United Manufacturers & Distributors Co., 1045 Chicago Ave., Chicago, Ill.

RADAK

RELIABLE RECEIVING SETS

Licensed Under Armstrong Patent
L113,149

BUILT BY AMERICA'S OLDEST
MANUFACTURER

Clapp Eastham Co.
107 Main St. Cambridge, Mass.

lengths used are between 390 and 500 meters. Berlin sends on 430 and 500 meters. There are altogether in Europe some 50 broadcast stations, with wave-lengths ranging from 250 to 3,200 meters.

Here I come to one of the chief problems which faces the radio enthusiast who will listen to European programs, that of covering the wide wave-band involved. Practically no attention appears to be paid to this problem in the modern American hook-ups. Anyone wishing to hear the higher powered European stations must be prepared to cover wave-lengths between 1,500 and 3,000 meters. The discussions in Radio News of an international language for radio are strong evidences that program broadcasting is taking on a world aspect. But no less important than a cosmopolitan language is a wide wave range for all receiving sets of international radios. There is one rather high powered German station known as Königs-wusterhausen which even sends on a wave-length of 4,000, giving stark exchange and similar reports almost hourly throughout the day. What is really needed for international broadcast receiving is a highly sensitive set with a range of from 100 to 4,000 meters. Of course, the set must be highly selective, for the interference from high power code stations on the longer waves is often very thick. I know of an arrangement which is practical and convenient for covering efficiently the international wave-band. If anyone reading these lines does, I should be most glad to hear from him. Up to the present I have simply employed two stages of R.F. tuned impedance amplification, whereby a considerable portion of the joy of hunting for different stations consists in plugging in and out a set of honeycomb coils. Not less than 15 or 20 coils are required to do the job right. This is not what I call practical. Besides, the arrangement is quite unsatisfactory to tune in, owing to three condenser controls and the aggravating instability of such an unneutralized system. I am at present experimenting with a Super-Electrode tube hook-up, but do not know whether this system can be persuaded in any practical way to go up and down the scale as required. I hope to hear from readers who have worked out anything practical along this line. I am aware that there are some simple hook-ups which will do the job, but what is required is an extremely sensitive multi-tube set which will work on a long red do trans-Atlantic broadcast receiving.

There certainly is a tremendous fascination in international receiving. About 10:45 I hear Radiola close down with a "Bon soir Mesdames, bon soir Mesdemoiselles, bon soir Messieurs," in suave Parisian accent. A little later the tones of "Deutschland, Deutschland Über Alles" may be heard ringing in from Berlin. Then I switch over to England, perhaps just in time to hear "God Save the King" and an engaging, "Good night everybody, good night." Three times a week at least, London gives us dance music from the Savoy Hotel, generally until midnight, when the station switches over to Big Ben and we hear the chimes and then the ponderous tones of the famous old clock pounding out the hour of 12. Then all is quiet on the air, except for a little station away off somewhere which uses an un-understandable tongue and keeps on going until about 12.30 o'clock.

By the way, don't take offense at the "Deutschland Über Alles" from democratic Germany. This much maligned song had a most democratic origin, and the opening line is as innocent in spirit as "The Stars and Stripes Forever."

S. McCLATCHEY,
Lenzhalde 45, Stuttgart, Germany.

Atlas

TRADE MARK

RADIO REPRODUCTION speaker



THE material of the horn itself plays an important part in the faithfulness of Atlas Radio Reproduction. The magnified cross-section below shows how the resilient core absorbs the vibrations of the horn material; while the rigid surface conserves the sounds you ought to hear—as you want to hear them.



Multiple Electric Products Co., Inc.
36 Spring St., Newark, N. J., Dept. F

New York, Boston, Philadelphia, Baltimore,
Pittsburgh, Detroit, Chicago, St. Louis, Denver,
550 Howard Street, San Francisco.

Martens Wireless Telegraph Co. of Canada Ltd.
Sole Canadian Distributors



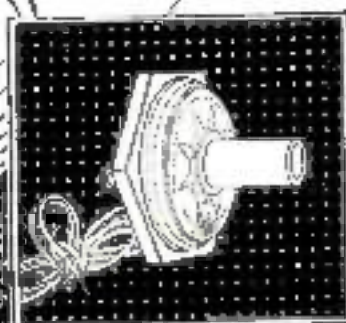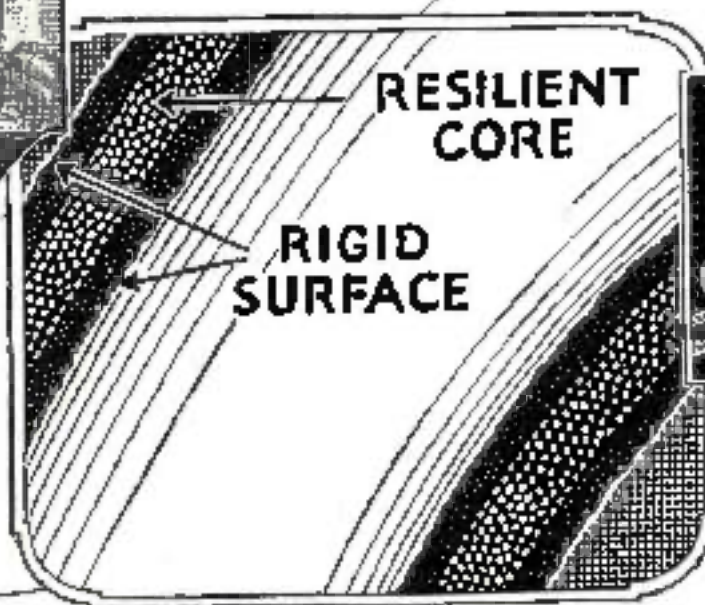New Atlas speaker with the exclusive and strikingly beautiful bronze-brown ripple-finish.



Atlas unit, complete with attachment coupling, to fit all standard phonographs.

Pure, clear tones from your speaker, must start with your transformers

You want more than noise from your loud speaker.

You want pure tones, clear, mellow reproduction.

But no speaker can be better than your A. F. transformers.

And any speaker will be improved when you use transformers that are designed for loud speaker use!


Transformers that produce the greatest possible amount of amplification unfortunately also introduce imperfections in the tone. And the speaker magnifies such imperfections.

Fortunately, however, when the tone is clear, you don't need anywhere near so much volume of sound.

In designing MAR-CO transformers, an amplification ratio has been used, which provides the most volume that is consistent with absolute purity of tone. And, of course, they are built, like all other MAR-CO parts, with the famed MAR-CO precision that stops leaks and conserves radio energy!

So, now, those who value tone purity highly, will use two and sometimes three stages of MAR-CO amplification this Fall, and replace squeals with music!

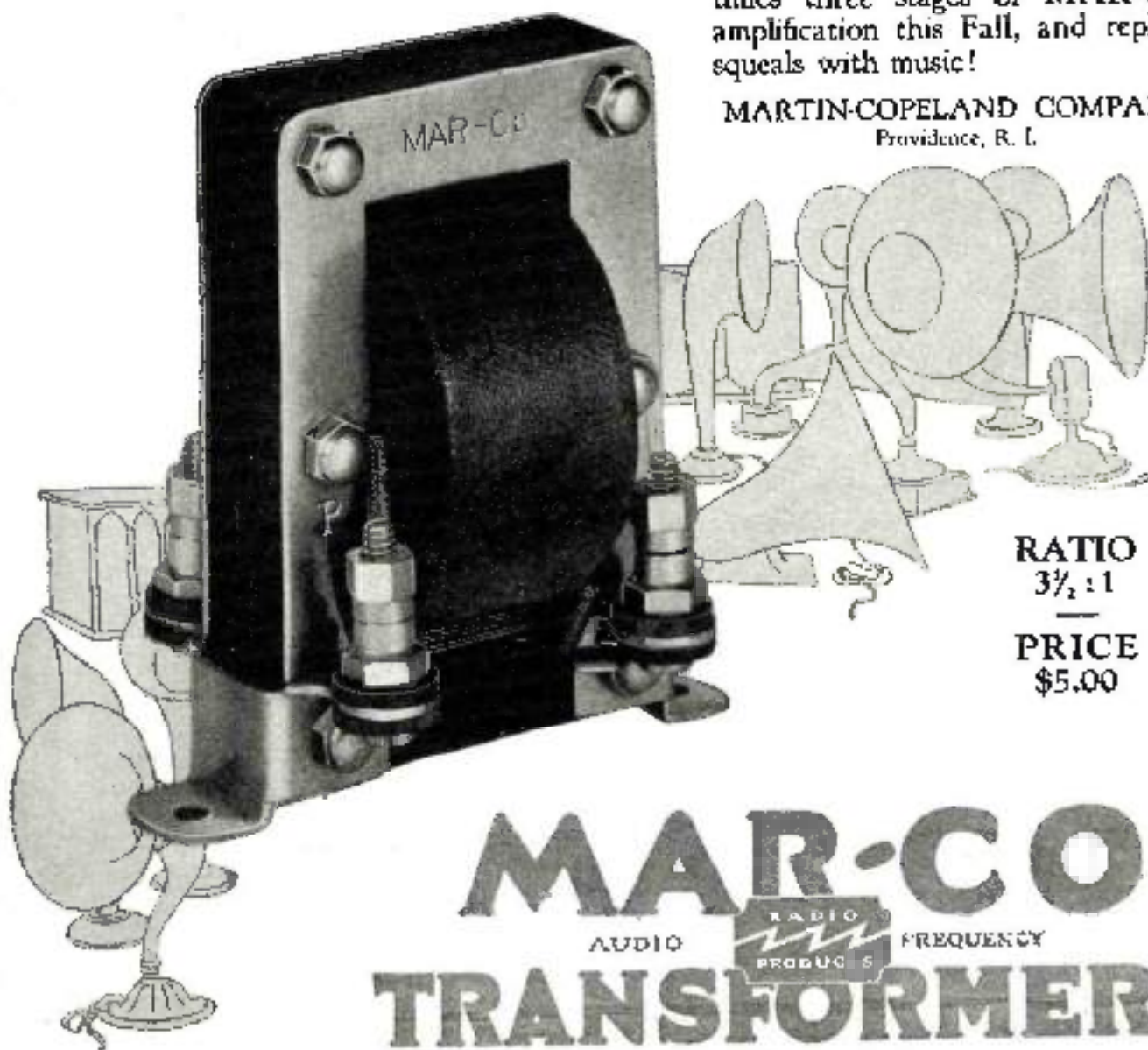MARTIN-COPELAND COMPANY
Providence, R. I.



RATIO
3½ : 1
PRICE
\$5.00

MAR-CO
AUDIO  FREQUENCY
TRANSFORMERS

Radio Without the Horn!



Goodbye to the
Old-Fashioned
Horn Speaker!


A Vastly Better
Reproduction
With this New
Radio Console!



"Our old horn speaker never gave tones like this! An artistic addition to the living room—everything in its place—it's a joy!"

New Console Has
Its Own Perfect
Loudspeaker!

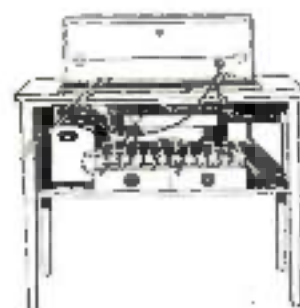Ample Space for
All the Rest of
Your Outfit!



HERE is something that enables you to enjoy radio in the home without the clutter of unsightly apparatus that plays havoc in the decorative scheme of your living room! The horn speaker is out of date and out of place in radio for the home. This console with its in-built loudspeaker is scientific and sightly.

A Truly Wonderful Tone

It does a better job of reproducing, for it has the best unit of all that have been tried and its sound-box is of resonant wood instead of metal, fibre, or composition.

The appearance of a Windsor loudspeaker console is a delight. Its convenience is a joy. A piece of real living room furniture of pleasing lines and finish—and it accommodates all the miscellany of equipment which hitherto had no place except on table tops, shelves or floor. Ample space on top for any set, with plenty of elbow room in front. Nothing in sight but the dials. Everything else goes inside—from behind in spaces cleverly designed to hold the largest batteries and outfit—besides the self-contained loudspeaker—all unseen and protected from dust or disturbance.

Dealers!

The sale of these consoles has already reached estimated 75,000 units. They are selling in surprising quantities in 2000 smaller stores where there is due to the low price on the floor. It is a convenience and a value not to be duplicated.

We are in for accounts and particulars of our catalogue a very long campaign.

You Need This Console Whatever Your Present Outfit Is

It makes no difference what kind of radio outfit you have—this console was designed for your use. The graceful exterior of this console gives no hint of its inner utility, for it is a simple and effective piece of furniture in every line. But a glance at the interior reveals a most ingenious arrangement of the in-built loudspeaker with space either side and in front. These spaces are ample for the largest A battery,

and the largest wet B batteries and the largest charging outfit. It is 38 in. long, 18 in. deep, and 29 in. high. Notice the artistic grill that conceals sound box, and the provision of "knee room" beneath. Made in mahogany or walnut finish, and the price is only \$40! (West of the Rockies \$42.50.)

Investigate!

Dealers everywhere are now showing the Windsor loudspeaker console, and have them for immediate delivery to your home. If you haven't already seen this remarkable contribution to radio enjoyment and convenience, write us now for the name of a nearby store

where you may view it. We will also send you complete information. Remember, this console gives you not alone a marvelously faithful reproducing unit and sound-box, but an altogether new beauty and utility in the provision for your entire radio outfit. Mail coupon or postal.



\$40

Loudspeaker Included
West of the Rockies \$42.50

Windsor Loudspeaker Console

Windsor Furniture Company
1422 Carroll Ave., Chicago

Please furnish pictures and full details, also name of nearest dealer who has the new Windsor loudspeaker console.

Name

Address

4B21

LIBERTY TRANSFORMERS


give the amazingly clear tone
of this remarkable set



AUDIO
FREQUENCY
base mounting type.

Ratio	Price
3 to 1	\$4.50
5 to 1	4.75
9 to 1	4.75

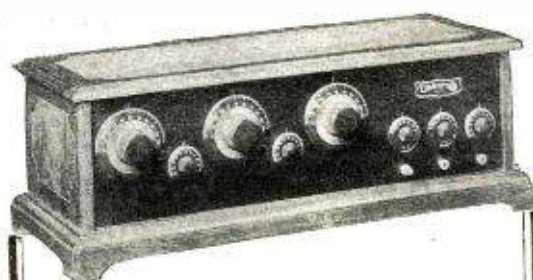Amateur set-builders and manufacturers can obtain equal tone quality by using Liberty Transformers




LIBERTY Sealed Five

5-tube tuned radio frequency receiver. In handsome solid walnut two-tone cabinet\$100.00
(Less accessories)

Equals any original or reproduced music for clear tone. LIBERTY clear tone transformers combined in this perfectly balanced set make it astonish all who hear it.



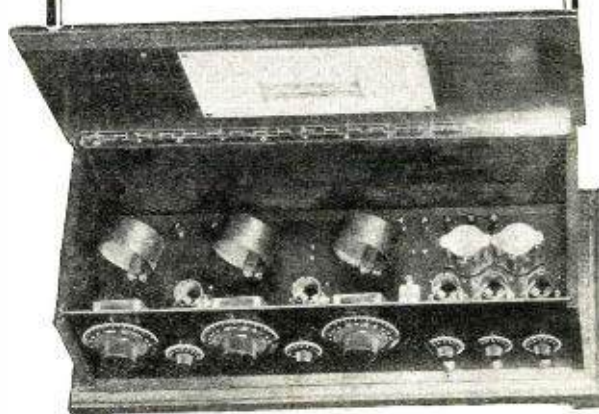(Write for booklet "Choosing Your Radio"—describes the LIBERTY Sealed Five.)



Obtain any of these guaranteed products from your dealer or post paid from us at list price.

LIBERTY TRANSFORMERS

They make any good set better

Your money back if they fail!


These transformers are so good because we take the time to make them properly—and have the machinery to do so. Coils are all wound perfectly. Insulation is ever-sure. Silicon steel laminations. Pure bakelite tops. No transformer—at any price—possesses an essential feature not found in LIBERTY TRANSFORMERS.



Panel Mounting Type
(price \$4.50 for
base mounting type
shown above)

LIBERTY
TERMINAL
LUGS

Per Dozen ... 1.00
Per 1,000 ... \$1.00

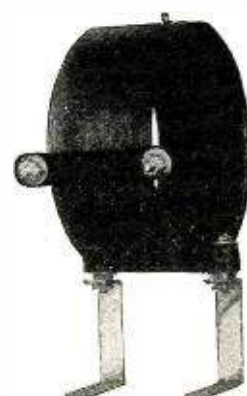

[Air-Core]
Radio frequency
transformer\$1.50

Write for folder.

Liberty Transformer Co., Inc.

555 N. Parkside Ave., Chicago

Be A Master OF THE Air



Pleasant Home Study

During the next few months you can, by devoting a few hours each week in pleasant home study, qualify yourself to get into the biggest paying field of all time. My practical, understandable course of instruction enables you to be a Master of the Air. Every problem in radio becomes an open book to you. Be a Master of the Air and you will be a master of your future.

\$3,000 to \$10,000 a Year as Radio Expert

15,000 ships, hundreds and hundreds of Radio stations, with new ones springing up every day, are all keenly competing for the services of the radio-trained man. So enormous is the call for the radio expert that the man who knows his business in this field is in a position to command the size of his salary. The kind of work, in Government or private service, there are boundless fine paying opportunities for the man who understands radio problems and how to solve them.

RADIO is Power —and Power is Cash

I show you how to construct, install, operate, repair and sell radio equipment. Instead of being a spectator in this big game with big makes, you become an active player. I qualify you to handle every branch of radio. There is nothing theoretical or practical that is not presented to you in complete, concise form. You are standing face to face with the greatest money-making chance ever presented in 1934. Will you turn your back on it or will you decide now, once for all, that you will get your share of the millions being divided among radio-trained men? Right in your own neighborhood you can make easy money. Neighbors and friends will gladly give orders for sets and pay for advice on radio problems.



FREE 1000 Mile Radio Outfit

This set, when completed, has a range of over a thousand miles. I give it free with my course. I give you practical training by having you work on this set. The knowledge you gain is not mere book knowledge, but is worth, practical experience. When you have finished my course, you can sell this set at a price that will more than pay the cost of the course.

QUICK PRACTICAL TRAINING

Everything in my course is clearly and simply stated so that you can easily understand every point I bring out. No previous experience or education is required. I give you fundamental and practical training in every angle of radio. There is no time to lose. Now is the best time to get the other fellow by. Mail coupon today and get full information on my course, also details of the thousand mile set that I give free.

A. G. MONAULT, Radio Engineer
RADIO ASSOCIATION OF AMERICA
 4513 Ravenswood Ave., Dept. 1512, Chicago, Ill.



A. G. MONAULT, B.S., M.E., Head of the Radio Association of America, Graduate Electrical Engineer, University of Wisconsin, Fairbury, Idaho Institute, and U.S. Government, Arthur J. Wallace, and Thomas of Modern Radio.

I give my present situation to every student online and offline. Your technical knowledge and business are guaranteed by me. I have built you at every stage of the course, guiding you directly to your goal to be a Radio Engineer in the big big class. My course prepares you to successfully pass the examination for Commercial License.

MAIL COUPON

A. G. MONAULT, Radio Engineer,
 Radio Association of America,
 4513 Ravenswood Ave., Dept. 1512, Chicago
 Please send me details of your Home Study Course—also your Free "Radio Facts" and information on how I can get a FREE 1000 mile Radio Set.

Name
 Address
 City State

Special Library of Information

RADIO PATENTS and TRADE MARKS

JOHN B. BRADY

Patent Lawyer

Quincy Building Washington, D. C.

Cable address: RADIOPAT Telephone: Main 4806



PATENTS

DON'T LOSE YOUR RIGHTS
 Before disclosing your invention to anyone and let the clock turn "EVIDENCE OF CONCESSION" to the patent and trademark lawyers.
LANCASTER & ALLWINE
 208 1/2 West 11th St., Chicago, Ill.
 570 Grand Bldg., Washington, D. C.
 Attorneys at Law "Evidence of Concession"

10 cents will bring you one can of ALLEN'S SPECIAL RADIO SOOTHING PASTE. If you mention this advertisement, a limited number of Radio Sets on "How to Build Radio Sets" will be given free to early replies.

L. B. ALLEN, Inc.
 4564 N. Lincoln St.
 CHICAGO, ILLINOIS

STRAIGHT LINE CONDENSERS

(1934) Mr. Solomon Eagle, Kwiguk Slough, Alaska, 9583

Q. 1. What is the main difference between a line telephone receiver and a regular loud speaker?

A. 1. The line telephone receiver is not required to respond as truly to such a wide range of frequencies as the loud speaker, also, the resistance of the line receiver is considerably lower. The usual resistance of line receivers is only 25 to 50 ohms, while loud speakers operating directly in the plate circuit of the tube are wound to resistances between 1,000 and 4,000 ohms. Where line receiver diaphragms are considered satisfactory, if made of ordinary ferro-type iron, loud speaker diaphragms must be of exactly the right material and dimensions, or distortion of certain frequencies will result. The physical construction of the loud speaker case and parts is designed with exactness, down to the minutest detail, greatly exceeding the thought expended on the ordinary line receiver. But each unit suits its particular purpose in a quite satisfactory manner.

Q. 2. What is a straight line condenser?

A. 2. A condenser whose value varies directly according to the position of the plates. A condenser may be calibrated, or its curve plotted, in one of three ways, according to wave-length, capacity or frequency. A condenser having a straight line calibration for frequency will not have a straight line according to wave-length. A condenser having a straight line according to capacity cannot be of the straight line type for either of the other two. No two of these curves can be the same. When a condenser is stated to be of the straight line type, no information is given, until the statement is completed by the words, "for wave-length," or "for capacity," or "for frequency."

Q. 3. What are the advantages and disadvantages of straight line condensers?

A. 3. Condensers with decentered plates, or their equivalent, have a straight line for capacity. The value of this is mostly in work where it is desirable to know the capacity at each setting of the pointer. The capacity will be proportional to the scale readings. In tuning stations, the stations will be lumped at the lower end of the condenser, making tuning more difficult as the short-wave lengths than if the condenser design were changed so as to have a straight line variation for wave-length. When the latter is the case, the dial degrees will be proportional to the wave-length and there will be a certain number of degrees per degree of variation. Occasionally, it is desirable to have a condenser so designed as to have straight line calibration for frequency. Knowing the frequency of the stations, the location of the correct tuning point is readily determined, since the dial variations will be proportional for the variations in frequency. The practice of referring to a station's frequency, rather than its wave-length, is becoming more general and condensers designed for straight line frequency variation will be in greater demand.

W. E. TRANSMITTING TUBES

(1934) Mr. A. E. McCullough, Akron, Ohio, 9584

Q. 1. Can honey-comb coils be used to advantage in the construction of vacuum tubes for an Autophase receiver?

A. 1. By connecting two honey-comb coils in series, each of about 10 to 50 turns and sliding one across the other, a variable action will be had which will be satisfactory. The wave-length range of such a construction is rather limited and it is doubtful if results will compare very favorably with those secured through the use of a standard vacuum tube of current design. Of course, a high natural inductance and low natural capacity is thus secured, but the usual honey-comb construction does not permit a very wide variation between maximum and minimum.

Q. 2. What general information is available on the Western Electric transmitting tubes?

A. 2. The 50 watt "C," or 212-A tube, has the following characteristics: It fits a standard 50-watt socket; the filament is oxide coated and is kept constant at 1.4 amperes; the filament voltage varies; the screen voltage is between 0 and 9.8. It is not advisable to operate the tube with more than its open-circuit voltage of 750 on the plate although the maximum permissible potential is 1,000 volts. The grid bias voltage varies between -10 volts and -50 volts. The plate current is 35 milliamperes, with a grid voltage of -20 volts and a plate voltage of 750. The voltage amplification is 11 to 11 and the impedance between plate and filament is 1,500 ohms.

The 250 watt 212-A, or "T" tube, has these characteristics: A special four-pin socket is required; constant filament current, 6.25 amperes; filament voltage, 9 to 9.8; grid voltage, -35 to -60 volts; plate voltage, 1,000 to 2,000, with best operation at 1,500 volts; with a grid bias voltage of -60 and a plate voltage of 1,500, the voltage amplification is 15 to 17 and the impedance is 2,000 ohms. Do not impress the supply on the plate until the tube has been heated for five minutes. The filament may be turned out if the full plate voltage is then applied; unheated the voltage should be applied at first. If de

THE NEW SUPER-HETERODYNE MODEL C-7

Important Today

THE EXPERIMENTERS INFORMATION SERVICE, Inc., has been recommending the Super-Heterodyne method of reception since the early part of 1922. In February, 1923, a Super-Heterodyne of our design was installed on the S.S. *Western* of New York, N. J., in the cabin of Dr. Horatio Belt. On the voyage to Rio de Janeiro, Brazil, at a distance of 3,000 miles, southeast of New York, the entire Circulator light was received from WJZ, with sufficient audibility for the entire cabin full of passengers to hear the boat, blow by blow, plainly. At 3,300 miles southeast of New York, an entire evening church service was received from Pittsburgh. At that time there was not another single firm advertising or advocating the Super-Heterodyne. Since then Mr. A. Arceus, Engineer, Travijsa Elec de Arequipa, Arequipa, Peru, has reported consistent reception from KDKA, WDAP, WEAF, WGY and others, at a distance of over 5,000 miles, using a Model "C" Super-Heterodyne. The Pratt & Blake Corp., of New York City, sent a Model C to Rio de Janeiro which received American broadcast station at a distance of over 7,000 miles.

Practically all concerns now featuring Super-Heterodyne have copied our original Model C design, and to prove again that we are far in advance of competition, we present this Improved Model C-7 Super-Heterodyne as the *Most Sensitive, Most Selective*, and finest reproducing Broadcast Receiver that can be built.

7 Tubes Give the Results of 10

The Reason:—When regeneration is added to a one tube non-regenerative receiver the increased amplification is about equal to adding two stages of tuned audio frequency amplification. Hereinfore it has been impossible to add regeneration to the 1st Detector of a Super-Heterodyne and accordingly this has been a big loss.

The new Model C-7 Super-Heterodyne has a special 1st Detector circuit with a split antenna inductance so arranged that normally the detector will oscillate continuously. However, in addition, a neutralizing condenser is inserted in the circuit which gives absolute control of the oscillations to such an extent that the circuit can be adjusted to just below the oscillating point, as this adjustment gives the maximum regenerative amplification. The new circuit has a bias potential on the 1st Detector grid, in place of the usual grid leak and condenser, and this allows infinitely weak signals to be regenerated and heterodyned through the radio frequency amplifier, which an ordinary grid leak and condenser would block. On a weak signal the difference in sensitivity is very noticeable. Using a 22-000 ohm antenna in the suburbs of New York loud speaker reception has been obtained from KISL, Oakland, California. A normal range of 2000 miles is easily obtained on an average small antenna at night under average conditions.

EXPERIMENTERS INFORMATION SERVICE, INC.

476 Broadway, New York City

Designers of the Highest Class Radio Apparatus in the World

New Book, "Modern Radio Reception," by Charles R. Leutz, over 250 Pages, over 150 Illustrations, Fully Bound, \$3.00 Postpaid

"The Rolls-Royce of Reception"



MODEL C-7 SUPER-HETERODYNE

Wave-length Range: 200 to 575 meters. Dimensions: 40 in. x 8 in. x 7 in.
Tube Arrangement: Regenerative Detector, Oscillator, 2 Signal Radio, Detector, 2 Super Audio.

General Information

ANTENNA: Single wire, all on 150 feet long. Provision has been made for use of either a short or long antenna. Inductor unit—3 works very satisfactory.

TUBES: 7 Radiotrons UV281A or C201A, requiring one 6 volt storage battery and one 90 volt D Battery either dry or storage.

DRY CELL TUBES: Radiotrons UV199 or UV200 may be used if desired, but the results obtained with dry cell tubes are not as satisfactory as with the Radiotrons UV281A or C201A.

LOOP: As a loop takes considerable space and is objectionable looking and furthermore an inefficient collector, no provision has been made for loop reception. Local reception can be had without antenna or ground. An indoor antenna 30 to 40 feet long is suggested in place of a loop.

SELECTIVITY: The degree of selectivity is so high that distant stations can easily be tuned in through the local stations. For example, with a C-7 located five miles from WJZ, operating on 485 meters, WJZ Pittsburgh on 462 meters can be tuned in without interference with WJZ.

TUNING: There are only two tuning adjustments, one for the detector circuit and one for the oscillator. Each station has a definite point on each dial and will always be found at these calibration points. Individual Verniers are provided for each dial. A third Vernier controls the volume.

CONSIDERATIONS: The second harmonic feature could be used with a view to eliminating aerials but we feel that the many advantages of having a separate oscillator more than compensate for the extra tube. For a similar reason we have refrained from Kellering the circuit to reduce the number of tubes.

STANDARDIZATION: All the component parts specified are readily obtainable on the market through high-class dealers.

PARTS: The parts specified in this design are all selected with expert consideration with a view to giving the maximum results obtainable. While it may appear that certain other parts could be used to economize we strongly recommend that you take advantage of our engineering experience and follow the specifications in the design.

Original Blue Print showing all data, diagrams, circuits, details, etc., \$1.00, postpaid

The New RECEPTRAD

GRIFT DOUBLE SELECTOR

MULTIFLEX KIT

The Perfect 4 Tube Circuit—Loop Operating



This wonderful circuit uses four tubes and has two stages of radio frequency, a crystal detector and three stages of audio frequency. Developed by the Research Engineers of the Radio Receptor Company, working under the direction of Victor Greath, of Super Heterodyne fame. The tone quality is really captivating. No station too far away to be brought in completely—whenever and wherever wanted—with good, clear volume. It can be described by any one in a few hours. For simplicity and ease of tuning, as well as power and quality of reception, it is far superior to a 5-Tube Neutrodyne.

Read the article on the Multiflex by E. C. Victor Greath in this issue. Let's intercept. Write for circular K3, giving complete information.

\$29.50

Containing principal parts

\$50.00

Including all parts

RECEPTRAD
PRODUCTS

RADIO RECEPTOR CO.
59 BANK STREET
NEW YORK

KIC-O "B" Battery and Charger

—the Ideal Christmas Gift

Nothing gives more pleasure or lasting satisfaction to the radio fan than this outfit of KIC-O "B" Battery and Charger. Battery is of the well-known alkaline type, giving constant current and long life. Heavy glass jars are completely enclosed in a highly finished cabinet which is practically water tight.



KIC-O Multi-Polar Double Potential! Chargers recharge storage "B" Batteries quickly and economically. They use both halves of the A.C. cycle and operate from the ordinary electric light circuit. Fully guaranteed.

KIMLEY ELECTRIC COMPANY, Inc.
2665 MAIN STREET, BUFFALO, N. Y.

KIC-O BATTERY

For instance, total type with electrolyte in multi-type without electrolyte

Type	Volume	Price
P2	140	\$32.00
C2	140	28.00
T2	140	25.00
C2D	140	22.00
P2D	140	18.00
C2D	140	15.00
P2D	140	12.00
C2D	140	10.00
P2D	140	8.00
C2D	140	6.00

KIC-O Chargers
KIC-O Special Charger Chassis \$7.50
Type K-1 Single charging 1.50
Type K-2 Single charging 1.50
Type K-3 Multi-charging 3.00

GUARANTEE
Your money back on any KIC-O Battery if not satisfied within 30 days trial. Write for full information on "A" and "B" Batteries.

Only the World's Best Arms



LUGER PISTOL
Barrel 4, 5, 6, 7 and
8 inch. Muzzle
velocity, long barrel, higher scores than both
Mannlicher, Vetterli and all other arms. Call
for it at once. **PACIFIC ARMS CORPORATION**
110 N. Lombard St. San Francisco, Calif.

MORE PROFITS

To Dealers Who Buy Nationally
Advertised Radio Goods from Our
Bargain Catalog! Write for It Today!
AMERICAN RADIO MFG. CO.
Dept. 6 WEST 14th ST. KANSAS CITY, MO.

Include your copy reaching you each month. Subscribers to Radio News—\$2.50 a year.
Experimenters Publishing Co., 35 Park Place, N. Y. C.

used, a high grid bias may be employed to reduce the plate voltage. As this bias voltage is reduced in normal, the plate voltage will increase. The grids and plates of these tubes are made of metallic nickel which has been coated with black nickel oxide. It is very important that the plates are not heated beyond a faint red at the center.

Q. 3. What is the maximum transmitting range of an oscillating receiving set using a UV-201A tube?

A. 3. The results of several tests made is dependently indicate that there is no difficulty in transmitting by phone and code for a distance of 15 miles. This is a concrete example of the great interference that can be caused by a receiving set in the operating conditions.

BATTERY TESTING

(7062) Mr. P. Cherubini, Rome, Italy, asks:
Q. 1. Should my 28 volt "H" battery, and electrolyte, be tested with an ammeter?

A. 1. An ammeter should not be used for testing batteries. It is sometimes desirable to test storage batteries with a special ammeter, but a voltmeter is the safest instrument to use. Do not permit the voltage to drop lower than 1.6 volts per cell. A hydrometer is usually used for testing storage batteries, but there is too little electrolyte in "H" battery cells for it to be used there.

Q. 2. Should an Edison alkali electrolyte battery be tested with a hydrometer?

A. 2. The specific gravity of this battery changes but little between charge and discharge. Use a voltmeter.

Q. 3. What is the correct speed for drilling small holes in bakelite?

A. 3. A little oil or small drills rotating at about 1,200 r.p.m. will be correct.

BAKELITE

(1202) Mr. Santiago Ventura, Sagua la Grande, Cuba, asks:

Q. 1. Kindly describe the general construction of Bakelite.

A. 1. The reaction of formaldehyde and carbolic acid, under certain conditions, produces a resin-like material. Alcohol or acetone will dissolve this compound. This compound, which has been termed synthetic resin will first melt, upon the application of heat, but the heat produces a chemical change that causes the liquid to harden. Once hardened, it cannot be softened, not even by the use of the common solvents. Once permanently hardened, it becomes infusible, insoluble, and impervious to oil or water. It has become "chemically inert." There is no gradual deterioration, such as we see in the rusting of iron, the softening of asphalt compositions, or the sulphur "blow" in rubber.

Q. 2. How is it possible to mould bakelite?

A. 2. Powdered bakelite is mixed with some binding ingredient, such as glue, wood pulp, asbestos, or wool "flour." This powder is "plastic moulded" by being put in a heating press exerting a 2,000-pound pressure per square inch. The chemical change referred to above then takes place, the compound first melting and conforming to the mould form, and then hardening permanently.

Q. 3. What is the specific gravity of bakelite?

A. 3. Approximately 4.5 to 5.5.

TRANSFORMER SPACING

(2064) Mr. J. S. Skinner, Jr., Gatun, C. Z., Panama, asks:

Q. 1. Would it be advisable to use a push-pull amplifier instead of the regular vacuum tube amplifier in a Neutrodyne set?

A. 1. Greater clarity and somewhat greater volume would result. While it would mean greater expense for materials and upkeep, the labour of its construction, and the use of additional space in the cabinet, we believe the results would be worth it, if the work were done carefully and the transformers and wiring not crowded.

Q. 2. How was it possible for WREX, at recently stated by the press, to broadcast with a power of 5 K.W., when the legal limitation is 1 K.W.?

A. 2. This was permitted under the special license held by that station.

Q. 3. What is the correct spacing distance for intermediate frequency transformers?

A. 3. This depends upon the design of the transformers. Placing them end to end, as you suggest, is even more undesirable than placing them side by side. If placed side by side, the spacing may easily be about three inches. The best procedure is to put the coils at right angles.

TRANSFORMER CONNECTIONS

(2065) Mr. John Fennel, Racine, Wis., asks:
Q. 1. What size honey-comb coils are required to receive 5,000 to 8,500 meter wavelengths?

A. 1. The wave range of the average vacuum coil is 5,000 to 8,500 meters, when shunted by a variable condenser of .001 mfd. capacity. This coil will be about right for the primary. Use a 600-turn coil, wave range, 4,000 to 12,000 meters, for the secondary. The tapper may be between 400 and 600 turns. For those who do not mind the extra work entailed in tuning, a third variable condenser connected in parallel to

Table-Talker



What greater gift?

Joy for the holidays—for all the year. Joy for the fellow who gets the gift—and for the family. Give it all—give a Table-Talker.

You're sure of its tone. Sure that it will always be loud yet pleasant, because its horn is matched to the unit. It reproduces every word, every note with vivid clarity—it makes the joys of radio real!

\$10
It needs no extra
batteries

Brandes



*The name
to know in Radio*

Copyright © C. Brandes, 1934





TABLE NO. 31

Refrigerator Table 27" x 31" x 24"
Latched 2 days in
factory \$42.50

MBG RADIO CABINETS

For your RADIO SET


Get an MBG Cabinet for your set today. Any size you need at ridiculously low prices. All our cabinets are strongly made from beautifully grained Douglas Fir. Shipped in the natural wood with full instructions for staining at home to harmonize with 24 standard wood finishes. Make your radio set an attractive piece of furniture at low cost.



SPECIFICATIONS AND PRICES

Panel To 9" x 17" deep	\$1.50
Panel To 12" x 17" deep	1.80
Panel To 15" x 17" deep	2.00
Panel To 18" x 17" deep	2.20
Panel To 21" x 17" deep	2.40
Panel To 24" x 17" deep	2.60
Panel To 27" x 17" deep	2.80
Panel To 30" x 17" deep	3.00
Panel To 33" x 17" deep	3.20
Panel To 36" x 17" deep	3.40
Panel To 39" x 17" deep	3.60
Panel To 42" x 17" deep	3.80
Panel To 45" x 17" deep	4.00
Panel To 48" x 17" deep	4.20
Panel To 51" x 17" deep	4.40
Panel To 54" x 17" deep	4.60
Panel To 57" x 17" deep	4.80
Panel To 60" x 17" deep	5.00
Panel To 63" x 17" deep	5.20
Panel To 66" x 17" deep	5.40
Panel To 69" x 17" deep	5.60
Panel To 72" x 17" deep	5.80
Panel To 75" x 17" deep	6.00
Panel To 78" x 17" deep	6.20
Panel To 81" x 17" deep	6.40
Panel To 84" x 17" deep	6.60
Panel To 87" x 17" deep	6.80
Panel To 90" x 17" deep	7.00
Panel To 93" x 17" deep	7.20
Panel To 96" x 17" deep	7.40
Panel To 99" x 17" deep	7.60
Panel To 102" x 17" deep	7.80
Panel To 105" x 17" deep	8.00
Panel To 108" x 17" deep	8.20
Panel To 111" x 17" deep	8.40
Panel To 114" x 17" deep	8.60
Panel To 117" x 17" deep	8.80
Panel To 120" x 17" deep	9.00
Panel To 123" x 17" deep	9.20
Panel To 126" x 17" deep	9.40
Panel To 129" x 17" deep	9.60
Panel To 132" x 17" deep	9.80
Panel To 135" x 17" deep	10.00
Panel To 138" x 17" deep	10.20
Panel To 141" x 17" deep	10.40
Panel To 144" x 17" deep	10.60
Panel To 147" x 17" deep	10.80
Panel To 150" x 17" deep	11.00
Panel To 153" x 17" deep	11.20
Panel To 156" x 17" deep	11.40
Panel To 159" x 17" deep	11.60
Panel To 162" x 17" deep	11.80
Panel To 165" x 17" deep	12.00
Panel To 168" x 17" deep	12.20
Panel To 171" x 17" deep	12.40
Panel To 174" x 17" deep	12.60
Panel To 177" x 17" deep	12.80
Panel To 180" x 17" deep	13.00
Panel To 183" x 17" deep	13.20
Panel To 186" x 17" deep	13.40
Panel To 189" x 17" deep	13.60
Panel To 192" x 17" deep	13.80
Panel To 195" x 17" deep	14.00
Panel To 198" x 17" deep	14.20
Panel To 201" x 17" deep	14.40
Panel To 204" x 17" deep	14.60
Panel To 207" x 17" deep	14.80
Panel To 210" x 17" deep	15.00
Panel To 213" x 17" deep	15.20
Panel To 216" x 17" deep	15.40
Panel To 219" x 17" deep	15.60
Panel To 222" x 17" deep	15.80
Panel To 225" x 17" deep	16.00
Panel To 228" x 17" deep	16.20
Panel To 231" x 17" deep	16.40
Panel To 234" x 17" deep	16.60
Panel To 237" x 17" deep	16.80
Panel To 240" x 17" deep	17.00
Panel To 243" x 17" deep	17.20
Panel To 246" x 17" deep	17.40
Panel To 249" x 17" deep	17.60
Panel To 252" x 17" deep	17.80
Panel To 255" x 17" deep	18.00
Panel To 258" x 17" deep	18.20
Panel To 261" x 17" deep	18.40
Panel To 264" x 17" deep	18.60
Panel To 267" x 17" deep	18.80
Panel To 270" x 17" deep	19.00
Panel To 273" x 17" deep	19.20
Panel To 276" x 17" deep	19.40
Panel To 279" x 17" deep	19.60
Panel To 282" x 17" deep	19.80
Panel To 285" x 17" deep	20.00
Panel To 288" x 17" deep	20.20
Panel To 291" x 17" deep	20.40
Panel To 294" x 17" deep	20.60
Panel To 297" x 17" deep	20.80
Panel To 300" x 17" deep	21.00
Panel To 303" x 17" deep	21.20
Panel To 306" x 17" deep	21.40
Panel To 309" x 17" deep	21.60
Panel To 312" x 17" deep	21.80
Panel To 315" x 17" deep	22.00
Panel To 318" x 17" deep	22.20
Panel To 321" x 17" deep	22.40
Panel To 324" x 17" deep	22.60
Panel To 327" x 17" deep	22.80
Panel To 330" x 17" deep	23.00
Panel To 333" x 17" deep	23.20
Panel To 336" x 17" deep	23.40
Panel To 339" x 17" deep	23.60
Panel To 342" x 17" deep	23.80
Panel To 345" x 17" deep	24.00
Panel To 348" x 17" deep	24.20
Panel To 351" x 17" deep	24.40
Panel To 354" x 17" deep	24.60
Panel To 357" x 17" deep	24.80
Panel To 360" x 17" deep	25.00
Panel To 363" x 17" deep	25.20
Panel To 366" x 17" deep	25.40
Panel To 369" x 17" deep	25.60
Panel To 372" x 17" deep	25.80
Panel To 375" x 17" deep	26.00
Panel To 378" x 17" deep	26.20
Panel To 381" x 17" deep	26.40
Panel To 384" x 17" deep	26.60
Panel To 387" x 17" deep	26.80
Panel To 390" x 17" deep	27.00
Panel To 393" x 17" deep	27.20
Panel To 396" x 17" deep	27.40
Panel To 399" x 17" deep	27.60
Panel To 402" x 17" deep	27.80
Panel To 405" x 17" deep	28.00
Panel To 408" x 17" deep	28.20
Panel To 411" x 17" deep	28.40
Panel To 414" x 17" deep	28.60
Panel To 417" x 17" deep	28.80
Panel To 420" x 17" deep	29.00
Panel To 423" x 17" deep	29.20
Panel To 426" x 17" deep	29.40
Panel To 429" x 17" deep	29.60
Panel To 432" x 17" deep	29.80
Panel To 435" x 17" deep	30.00
Panel To 438" x 17" deep	30.20
Panel To 441" x 17" deep	30.40
Panel To 444" x 17" deep	30.60
Panel To 447" x 17" deep	30.80
Panel To 450" x 17" deep	31.00
Panel To 453" x 17" deep	31.20
Panel To 456" x 17" deep	31.40
Panel To 459" x 17" deep	31.60
Panel To 462" x 17" deep	31.80
Panel To 465" x 17" deep	32.00
Panel To 468" x 17" deep	32.20
Panel To 471" x 17" deep	32.40
Panel To 474" x 17" deep	32.60
Panel To 477" x 17" deep	32.80
Panel To 480" x 17" deep	33.00
Panel To 483" x 17" deep	33.20
Panel To 486" x 17" deep	33.40
Panel To 489" x 17" deep	33.60
Panel To 492" x 17" deep	33.80
Panel To 495" x 17" deep	34.00
Panel To 498" x 17" deep	34.20
Panel To 501" x 17" deep	34.40
Panel To 504" x 17" deep	34.60
Panel To 507" x 17" deep	34.80
Panel To 510" x 17" deep	35.00
Panel To 513" x 17" deep	35.20
Panel To 516" x 17" deep	35.40
Panel To 519" x 17" deep	35.60
Panel To 522" x 17" deep	35.80
Panel To 525" x 17" deep	36.00
Panel To 528" x 17" deep	36.20
Panel To 531" x 17" deep	36.40
Panel To 534" x 17" deep	36.60
Panel To 537" x 17" deep	36.80
Panel To 540" x 17" deep	37.00
Panel To 543" x 17" deep	37.20
Panel To 546" x 17" deep	37.40
Panel To 549" x 17" deep	37.60
Panel To 552" x 17" deep	37.80
Panel To 555" x 17" deep	38.00
Panel To 558" x 17" deep	38.20
Panel To 561" x 17" deep	38.40
Panel To 564" x 17" deep	38.60
Panel To 567" x 17" deep	38.80
Panel To 570" x 17" deep	39.00
Panel To 573" x 17" deep	39.20
Panel To 576" x 17" deep	39.40
Panel To 579" x 17" deep	39.60
Panel To 582" x 17" deep	39.80
Panel To 585" x 17" deep	40.00
Panel To 588" x 17" deep	40.20
Panel To 591" x 17" deep	40.40
Panel To 594" x 17" deep	40.60
Panel To 597" x 17" deep	40.80
Panel To 600" x 17" deep	41.00
Panel To 603" x 17" deep	41.20
Panel To 606" x 17" deep	41.40
Panel To 609" x 17" deep	41.60
Panel To 612" x 17" deep	41.80
Panel To 615" x 17" deep	42.00
Panel To 618" x 17" deep	42.20
Panel To 621" x 17" deep	42.40
Panel To 624" x 17" deep	42.60
Panel To 627" x 17" deep	42.80
Panel To 630" x 17" deep	43.00
Panel To 633" x 17" deep	43.20
Panel To 636" x 17" deep	43.40
Panel To 639" x 17" deep	43.60
Panel To 642" x 17" deep	43.80
Panel To 645" x 17" deep	44.00
Panel To 648" x 17" deep	44.20
Panel To 651" x 17" deep	44.40
Panel To 654" x 17" deep	44.60
Panel To 657" x 17" deep	44.80
Panel To 660" x 17" deep	45.00
Panel To 663" x 17" deep	45.20
Panel To 666" x 17" deep	45.40
Panel To 669" x 17" deep	45.60
Panel To 672" x 17" deep	45.80
Panel To 675" x 17" deep	46.00
Panel To 678" x 17" deep	46.20
Panel To 681" x 17" deep	46.40
Panel To 684" x 17" deep	46.60
Panel To 687" x 17" deep	46.80
Panel To 690" x 17" deep	47.00
Panel To 693" x 17" deep	47.20
Panel To 696" x 17" deep	47.40
Panel To 699" x 17" deep	47.60
Panel To 702" x 17" deep	47.80
Panel To 705" x 17" deep	48.00
Panel To 708" x 17" deep	48.20
Panel To 711" x 17" deep	48.40
Panel To 714" x 17" deep	48.60
Panel To 717" x 17" deep	48.80
Panel To 720" x 17" deep	49.00
Panel To 723" x 17" deep	49.20
Panel To 726" x 17" deep	49.40
Panel To 729" x 17" deep	49.60
Panel To 732" x 17" deep	49.80
Panel To 735" x 17" deep	50.00
Panel To 738" x 17" deep	50.20
Panel To 741" x 17" deep	50.40
Panel To 744" x 17" deep	50.60
Panel To 747" x 17" deep	50.80
Panel To 750" x 17" deep	51.00
Panel To 753" x 17" deep	51.20
Panel To 756" x 17" deep	51.40
Panel To 759" x 17" deep	51.60
Panel To 762" x 17" deep	51.80
Panel To 765" x 17" deep	52.00
Panel To 768" x 17" deep	52.20
Panel To 771" x 17" deep	52.40
Panel To 774" x 17" deep	52.60
Panel To 777" x 17" deep	52.80
Panel To 780" x 17" deep	53.00
Panel To 783" x 17" deep	53.20
Panel To 786" x 17" deep	53.40
Panel To 789" x 17" deep	53.60
Panel To 792" x 17" deep	53.80
Panel To 795" x 17" deep	54.00
Panel To 798" x 17" deep	54.20
Panel To 801" x 17" deep	54.40
Panel To 804" x 17" deep	54.60
Panel To 807" x 17" deep	54.80
Panel To 810" x 17" deep	55.00
Panel To 813" x 17" deep	55.20
Panel To 816" x 17" deep	55.40
Panel To 819" x 17" deep	55.60
Panel To 822" x 17" deep	55.80
Panel To 825" x 17" deep	56.00
Panel To 828" x 17" deep	56.20
Panel To 831" x 17" deep	56.40
Panel To 834" x 17" deep	56.60
Panel To 837" x 17" deep	56.80
Panel To 840" x 17" deep	57.00
Panel To 843" x 17" deep	57.20
Panel To 846" x 17" deep	57.40
Panel To 849" x 17" deep	57.60
Panel To 852" x 17" deep	57.80
Panel To 855" x 17" deep	58.00
Panel To 858" x 17" deep	58.20
Panel To 861" x 17" deep	58.40
Panel To 864" x 17" deep	58.60
Panel To 867" x 17" deep	58.80
Panel To 870" x 17" deep	59.00
Panel To 873" x 17" deep	59.20
Panel To 876" x 17" deep	59.40
Panel To 879" x 17" deep	59.60
Panel To 882" x 17" deep	59.80
Panel To 885" x 17" deep	60.00
Panel To 888" x 17" deep	60.20
Panel To 891" x 17" deep	60.40
Panel To 894" x 17" deep	60.60
Panel To 897" x 17" deep	60.80
Panel To 900" x 17" deep	61.00
Panel To 903" x 17" deep	61.20
Panel To 906" x 17" deep	61.40
Panel To 909" x 17" deep	61.60
Panel To 912" x 17" deep	61.80
Panel To 915" x 17" deep	62.00
Panel To 918" x 17" deep	62.20
Panel To 921" x 17" deep	62.40
Panel To 924" x 17" deep	62.60
Panel To 927" x 17" deep	62.80
Panel To 930" x 17" deep	63.00
Panel To 933" x 17" deep	63.20
Panel To 936" x 17" deep	63.40
Panel To 939" x 17" deep	63.60
Panel To 942" x 17" deep	63.80
Panel To 945" x 17" deep	64.00
Panel To 948" x 17" deep	64.20
Panel To 951" x 17" deep	64.40
Panel To 954" x 17" deep	64.60
Panel To 957" x 17" deep	64.80
Panel To 960" x 17" deep	65.00
Panel To 963" x 17" deep	65.20
Panel To 966" x 17" deep	65.40
Panel To 969" x 17" deep	65.60
Panel To 972" x 17" deep	65.80
Panel To 975" x 17" deep	66.00
Panel To 978" x 17" deep	66.20
Panel To 981" x 17" deep	66.40
Panel To 984" x 17" deep	66.60
Panel To 987" x 17" deep	66.80
Panel To 990" x 17" deep	67.00
Panel To 993" x 17" deep	67.20
Panel To 996" x 17" deep	67.40
Panel To 999" x 17" deep	67.60
Panel To 1002" x 17" deep	67.80
Panel To 1005" x 17" deep	68.00
Panel To 1008" x 17" deep	68.20
Panel To 1011" x 17" deep	68.40
Panel To 1014" x 17" deep	68.60
Panel To 1017" x 17" deep	68.80
Panel To 1020" x 17" deep	69.00
Panel To 1023" x 17" deep	69.20
Panel To 1026" x 17" deep	69.40
Panel To 1029" x 17" deep	69.60
Panel To 1032" x 17" deep	69.80
Panel To 1035" x 17" deep	70.00
Panel To 1038" x 17" deep	70.20
Panel To 1041" x 17" deep	70.40
Panel To 1044" x 17" deep	70.60
Panel To 1047" x 17" deep	70.80
Panel To 1050" x 17" deep	71.00
Panel To 1053" x 17" deep	71.20
Panel To 1056" x 17" deep	71.40
Panel To 1059" x 17" deep	71.60
Panel To 1062" x 17" deep	71.80
Panel To 1065" x 17" deep	72.00
Panel To 1068" x 17" deep	72.20
Panel To 1071" x 17" deep	72.40
Panel To 1074" x 17" deep	72.60
Panel To 1077" x 17" deep	72.80
Panel To 1080" x 17" deep	73.00
Panel To 1083" x 17" deep	73.20
Panel To 1086" x 17" deep	73.40
Panel To 1089" x 17" deep	73.60
Panel To 1092" x 17" deep	73.80
Panel To 1095" x 17" deep	74.00
Panel To 1098" x 17" deep	74.20
Panel To 1101" x 17" deep	74.40
Panel To 1104" x 17" deep	74.60
Panel To 1107" x 17" deep	74.80
Panel To 1110" x 17" deep	75.00
Panel To 1113" x 17" deep	75.20
Panel To 1116" x 17" deep	75.40
Panel To 1119" x 17" deep	75.60
Panel To 1122" x 17" deep	75.80
Panel To 1125" x 17" deep	76.00
Panel To 1128" x 17" deep	76.20
Panel To 1131" x 17" deep	76.40
Panel To 1134" x 17" deep	76.60
Panel To 1137" x 17" deep	76.80
Panel To 1140" x 17" deep	77.00
Panel To 1143" x 17" deep	77.20
Panel To 1146" x 17" deep	77.40
Panel To 1149" x 17" deep	77.60
Panel To 1152" x 17" deep	77.80
Panel To 1155" x 17" deep	78.00
Panel To 1158" x 17" deep	78.20
Panel To 1161" x 17" deep	78.40
Panel To 1164" x 17" deep	78.60
Panel To 1167" x 17" deep	78.80
Panel To 1170" x 17	

Stations You Never Heard Before

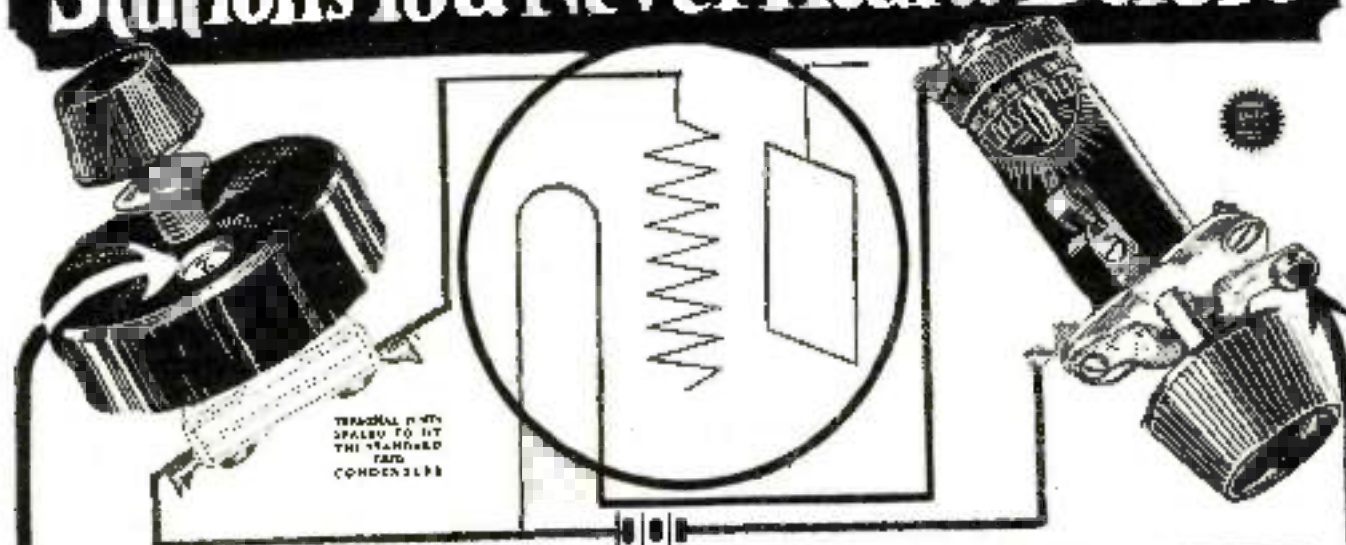

-thru scientific tube tuning

The most important (and most neglected) tuning unit on your set is the tube. It is the one thing you can adjust to bring weak stations to audibility—to eliminate distortion on local programs. Coils and condensers are easily tuned to incoming waves, but wave-length isn't everything. The antenna gets distant broadcasters but their signals never reach the phones unless you tune the tube to the different characteristics of the weak, distant stations. Here are two instruments distinctly designed to improve reception through their ability to control tube action—FIL-KO-LEAK to tune the grid by securing correct grid bias—FIL-KO-STAT to tune the plate-filament circuit by its control of electronic flow. Together they assure you maximum audibility, clearer signals and freedom from oscillations and other tube noises. They bring in stations you never heard before.

FIL-KO-LEAK \$2
SCIENTIFICALLY CORRECT
VARIABLE GRID LEAK
Individually Calibrated
In Cases \$2.75

You will get stations you never heard before with Fil-KO-Leak. Clear up distortion and increase volume. You can "log" your Fil-KO-Leak as you do your other tuning units. Each Fil-KO-Leak is individually hand calibrated over the operating range of all tubes $\frac{1}{4}$ to 5 megohms. Set it for specified resistance and adjust it for best results. Resistance read in megohms through panel peep-hole. (Base-board mounting furnished.) Resistance element constant, accurate, not affected by atmospheric conditions, wear or jarring. Assures smooth, gradual control of resistance and correct grid bias. Unconditionally guaranteed!

FIL-KO-SWITCH
SCIENTIFICALLY CORRECT
"A" BATTERY SWITCH

Simple
Sturdy
Sure



50¢
In Cases 24¢

150 stations were logged on a Fil-KO Stat equipped set, at Harrisburg, Pa., using a 1 meg. fixed grid leak. A calibrated Fil-KO-Leak was substituted for the fixed leak and in two nights 27 new stations—never heard before—were added.

The "DX Booklet" on "Improved Reception Through Scientific Tube Tuning" sent on receipt of 2c postage.

FIL-KO-STAT \$2
SCIENTIFICALLY CORRECT RADIO RHEOSTAT
with Battery Switch
In Cases \$2.75

Tune your tube filament with Fil-KO-Stat and receive stations you never heard before, get greater distance, louder signals, sharper tuning, freedom from tube noises. Fil-KO-Stat is the only rheostat that permits adjustment over the entire operating range of all tubes and enables you to get maximum audibility in phones or loud speaker. And now the improved model is fitted with battery switch that attaches to the regular mounting screws. Distinctly signals "on" and "off" and enables you to break circuit without changing Fil-KO-Stat adjustment. Fil-KO Stat fits any type tube in any hook up. Unconditionally guaranteed.

Joseph J. Scott of Ottawa writes, "Among the fifty-four new stations I tuned in with my Fil-KO-Stat was 6KW, Trinidad, Cuba, which I consider exceptional as it is only a small 100 watt station." And we have hundreds of other testimonials on file!

FIL-KO-ARRESTER
SCIENTIFICALLY CORRECT
RADIO LIGHTNING ARRESTER

with the
\$100
Guarantee



\$150
In Cases \$105



DISTRICT SALES OFFICES
NEW YORK: 100 W. 40th St.
CHICAGO: 100 N. Dearborn St.
PHILADELPHIA: 100 N. 3rd St.

MADE AND GUARANTEED BY
DX INSTRUMENT CO.
HARRISBURG, PENNSYLVANIA

DISTRICT SALES OFFICES
NEW YORK: 100 W. 40th St.
CHICAGO: 100 N. Dearborn St.
PHILADELPHIA: 100 N. 3rd St.





Model S Audiophone \$25

Non-metallic Horn 14 1/2" diameter. Velvet mat finish of mottled bronze and gold classic base.



Both Must Be Musical Instruments

IF you are to enjoy the rich resonance of an old German violin, your loud speaker must also be a true *musical* instrument. So designed and powered as to respond as faithfully to the inspiring crescendos of a Wagner opera as to the whispers of a Moonlight Sonata.

The new Bristol AUDIOPHONE does that. With its joyous, open-throated non-metallic horn, and its finely adjusted transformers, it is on a musical plane with the noblest instrument or voice at your favorite station.

In addition to Model S, shown here, the Bristol line includes Model L, \$20, Baby Grand, \$15, and the "Baby" at \$12.50. Send for Bulletin No. 3011 and 3017-S, mentioning name of your dealer.


THE BRISTOL COMPANY
Waterbury, Conn.

BRISTOL AUDIOPHONE

TRADE MARK REG. U.S. PAT. OFFICE

LOUD SPEAKER

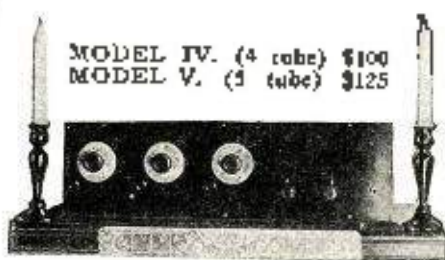MODEL IV. (4 tube) \$100
MODEL V. (5 tube) \$125



BILTMORE MASTER REFLEX

Sensitivity:—Five stages of radio frequency amplification, detector, and two stages of audio frequency amplification in Model V, and four stages of R.F. detector and 3 of A.F. in Model IV, make the BILTMORE MASTER REFLEX sensitive to signals in this respect, very far surpassed by any standard receiver. These models have many other good features: automatic loudspeaker operation, using only an "on-off" switch. The BILTMORE ensures the loudspeaker as always heard only on the phone with other amplifiers.

Tone:—A fixed circuit detector and perfect design are responsible for the wonderful quality of reception on the BILTMORE. There is no howling and humming in any the enjoyment of a program.

Reliability:—In its basic design, it is of the rugged of radio frequency amplification and tuned. The very best low loss condenser and low loss speed R.F. transformers are used, resulting in an unflinching performance. It is built to last and the most liberal maintenance, after one makes it listen to a distant station.

Accessories:—A Tauton Mechanical Motor, nickel plated metal parts, white and mahogany dials, and a

heavy hand-cranked rotating cabinet give the receiver a wonderfully beautiful appearance.

Appearance:—The receiver is made from the very best materials with its own design, brilliant brass, polished metal, stainless steel, and nickel-plated, aluminum-lined 160 to 1 copper-recessed, and extra coils and audio frequency transformers.

Operation:—The operation of the receiver is simplicity itself. The three dials have the same action for any set dialing, which setting is almost the same for that station. Consequently, when the receiver is set to receive the way one normally is, it is a matter of a few seconds to select any desired station while music, broadcast, or other station is in operation. All connections are made permanently to the rear of the cabinet, and the coupling of a switch provides the receiver for reception. The only necessary requirement is a clear indoor wire and a ground.

Write today for literature on both models at this wonderful receiver.

If your dealer is not yet supplied, write us for name.

The Biltmore Radio Company

Dept. N,
Boston 30, Mass.

AMAZING VALUE IS THE MARTINOLA ^{AT} \$85.00

Superior
Workmanship
Throughout



Easy
to
Operate

A five tube radio frequency set, STABILIZED so that the peak of amplification is obtained on weak and strong broadcasting.

SOLD ON A MONEY BACK GUARANTEE

Write today for literature

PHONE
4828
STUY
4829
6004

THE VIBROPLEX CO., Inc.
629 BROADWAY
NEW YORK

Cable
Address:
"VIBROPLEX"

SURE-TIGHT CONNECTORS



Phone Connector



Wire Clip



Lead Tip

These three types of connectors are a little different. It is particularly true of the wire clip and lead tip, which are made of different materials.

Excellent for use in the most difficult conditions.

These connectors are made of the best materials and are sold at a low price, only 10c each.

As you will see, if your dealer doesn't have them, just order direct.

ILLINOIS RADIO CO.
Springfield, Ill.

RADIO TUBE EXCHANGE

We Repair All Standard Makes of Tubes

W.F. 11 or 12
U.V. 199 or C-299
C-11 or 12
U.V. 201A or C-301A
D.V. 1 or D.V. 2
U.V. 240 or 101
C-300 or 101

\$2.00

U. V. 202 Replaced, \$3.00
All tubes guaranteed to do the work.
RADIO TUBE EXCHANGE
200 Broadway NEW YORK CITY, N. Y.
All Mail Orders Given Prompt Attention
Orders Sent Parcel Post C. O. D.

The mass of a proton is approximately equal to that of the hydrogen atom, the mass of the electron being by comparison negligible. In the atomic nucleus there are more protons than electrons, so that the nucleus has a positive charge; this is ordinarily neutralized by a certain number of surrounding electrons. The electrons in the nucleus are called nuclear electrons, and the surrounding ones are called planetary electrons, since they revolve round the nucleus after the manner of the planets round the sun. Now the first important point for our present purpose is that the planetary electrons are comparatively loosely held. There are many methods by which we may detach one or more of these electrons from an atom, or "ionize" the atom as the process is called. One simple method is to heat the substance, when many of the atoms will part with planetary electrons. These are the electrons which we make use of in the tube; being easily detached they may be made to leave the parent substance with a small velocity, which makes them easy to control. Furthermore under the conditions in the tube, practically no other rays but the electrons are emitted, and we are not troubled with a mixture of rays requiring different controls.

On the other hand, the protons and the nuclear electrons are very tenaciously held, and they must develop large amounts of energy before they can escape from the atom. These are the particles which form the alpha and beta rays from radioactive substances. Their velocities are very large compared with the velocities of thermions from hot filaments; for example, the velocity of emission of electrons from a heated filament may be about 6 inches per second, whereas that of the beta rays may be 100,000 miles per second.

Thus our first difficulty in attempting to make use of a radioactive substance as a source of electrons is that the electrons issue forth with such a high velocity that they cannot conveniently be controlled. And there are many other difficulties. The emission may consist of a mixture of negative and positive charges, the positive being even more unmanageable than the negative. The gamma rays complicate matters, and secondary rays are produced by the impact of the primary rays upon surrounding objects. The total emission from a convenient amount of radioactive substance may be too small to be of practical use, and there are still further difficulties—the production of gas, the cost, and so on—into which we cannot at present enter.

But our knowledge of radioactivity is rapidly progressing. New radioactive substances may be discovered; induced or indirect activity may prove available, or methods for the control of the activity be found. Again, development may come along the lines of the cathode ray experiments, or it may come in some hitherto untried direction.

To some these may seem fantastic speculations. But how many times, particularly of recent years, have we learned the wisdom of reserving judgment in scientific matters. It is as unsafe to dogmatize in the negative sense as in the positive, and the tapping of the intra-atomic energy may yet be added to the list of the greatest achievements of science.

HAD BIG EARS

She (reading newspaper): "Woman born without arms gains college and musical education; is adept at domestic tasks." How without arms! How could she play an instrument?"

He: "Couldn't she play by ear?"—Joseph M. Stroughan.

Insert your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Reprinters Publishing Co., 55 Park Place, N. Y. C.



FADA

Improves the 5-tube Neutrodyne

YES, sir! We've made it better in every way. Improved its looks, improved the circuit, eliminated unnecessary detail in making, and incorporated the latest and best ideas in Neutrodyne efficiency. Letters from ten thousand FADA boosters have helped us work out the new and improved FADA 5-tube Neutrodyne. We've put all binding posts in the rear, simplified the wiring and beautified the panel arrangement. Two stages of radio frequency, detector and two stages of audio frequency amplification (using the new FADA Audio Transformers) make this new FADA Neutrodyne about the best looking and most dependable radio receiver anyone can make. Your dealer

sells the new FADA knock-down set of Neutrodyne Receiver Parts No. 169-A for \$72. Look for it in his window. With every one goes the new and enlarged edition of

"How to Build FADA Neutrodyne Radio Receiver"

This is the latest and most up-to-date 76-page text-book on Neutrodyne. 38 pages of pictorial description, 44 illustrations, 30 pages of receiver trouble shooting in general and a fine, big full-size picture wiring diagram. This picture wiring diagram alone is worth the price of the book. Book sold separately on receipt of price—use coupon below.

F. A. D. ANDREA, Inc., 1581 Jerome Ave., New York



F. A. D. ANDREA, INC.
1581 Jerome Ave., N. Y.

Gentlemen: Enclosed find 75 cents for which send me the new FADA book, "How to Build FADA Neutrodyne Radio Receivers." #1

Name
Street or R. F. D.
City
State



**O'NEIL
AUDIPHONE**

Large Speaker

Designed on
Phonograph
Principle

AUDIPHONE Features

Air-gap Adjustment made with Armature by vernier accessible placed on speaker base: Synchronizes Speaker with Broadband Receiver and individual local receiving conditions.

Laminated Electro Magnet (voice core) Intensifies the magnet field.

Large Permanent Magnet of best quality aged and scientifically tested for permanency.

India Mica Diaphragm—best quality. The best phonographs have it.


Heavy die-cast Assembly Plate: Resists self contained vibrations. Coil is designed to resist short circuit—is space wound with extra heavy enameled No. 40 wire, layer insulated, vacuum treated and impregnated with anti-moisture compound.

Durably constructed to withstand abuses in transportation—plays pure

Requires no extra battery.

Apace with Radio Progress The 3-Way-Control Balanced Armature

(An Exclusive Patented Feature)

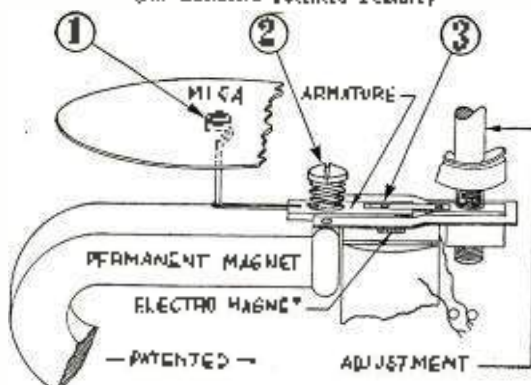

THIS "three-way-control balanced armature" is the big difference between all "loud speakers" and the O'NEIL AUDIPHONE. There can be no blast or chatter because the mica diaphragm of the Audiphone can be actuated **ONLY** by electrical impulses. The diagram illustrates how the armature is balanced in three directions. The large permanent magnet affords a real foundation for sensitivity, amplification and the full range of broadcast impulses. The Audiphone is not an earphone type Loud Speaker. This is real progress, real achievement. Hear the Audiphone at your dealer's.

Price— with 14 inch bell Horn **\$28**
with 12 inch bell Horn **\$25**

Sold with an Absolute-Satisfaction-or-Money-Back Guarantee. At your Dealer's or Direct upon receipt of purchase price and your dealer's name. Write for Literature.

O'Neil Mfg. Co.

719 Palisade Ave., West New York, N. J.

Some Loop Aerial Circuits

(Continued from page 936)

and the loop-aerial should be mounted well away from the experimenter, as otherwise his movements in its proximity will interfere with the tuning. The regeneration-control is wonderfully smooth. Stations at 100 miles, as well as local 10-wattlers, can be read in a favorable location. The radio-choke is the customary coil of about 200 to 300 turns of any convenient size and build, but of fairly low distributed capacity.

Developing this into a reflex circuit, of the general type already described by the writer for an Ultrasonic circuit, we get Fig. 2. As there is plenty of power available now, and stability is all important, the writer prefers to use the reliable and trouble-proof carborundum crystal, without potentiometer. The connections should be made as shown, the crystal being next to the O.P. and the contact spring (the writer uses a plain piece of tinned iron: "tin") near to the feedback-condenser end of the loop. As the transformer has an R.F. potential relative to earth, it should be well insulated the connection via a grid-bias cell being taken to the lowest point of the "A" battery through a radio-choke of the same type as that used in the plate-circuit. This can be avoided by making the slight modification indicated in Fig. 3—which suggests dimly certain American reflex circuit arrangements. Either of these gives most excellent reception of local broadcasting in an outer suburb with careful tuning; and is easily controlled. Distant stations can be read at comfortable strength, searching in the reflex arrangement being unusually easy.

Loud-speaker reception in the vicinity of the local station is given by No. 4, where a stage of power amplification is provided, with extra "B" battery and proper grid-bias on each tube. As different grid-bias will be needed on the two tubes, the No. 2 circuit is used for the first tube. As indicated, excellent loud-speaking is reached with this circuit up to a dozen miles, using a good tube and a L.S. or small power tube and 100 to 300 volts "B" battery on the plate of the second tube.

The same general principle has been applied by the writer to an Armstrong single-tube super or "flivver" circuit with admirable results. Tuning for wave length was fine, but the rage for a particular loop-aerial without variable tapings was unusually great, while signal-strength was satisfactory on a very small loop, several of the distant stations being easily readable under favorable circumstances.

Oscillations

(Continued from page 917)

decent and also men, are not ones for whom I plead new law administering. With other radio laws, Hon. Sir, should be coupled one which are intended for bootlegger of radio parts and sets which accumulate huge fortune from ignorant, helpless, peopl. which are hurried up with hasty desire to secure parts for radio sets.

These proposed law should provide means for arresting such sharks of decent commerce, and also punishing sex. Minimum small punishment for such cheating should be hanging till dead by thumb, tongue, nose,

"199" CUSHION SOCKET

SOCKET FLOATS ON RUBBER

Rubber Cushion Base



PATENTED DESIGN

MODEL B "199"

Model A for Standard Base Tubes, \$1.25; Model B for Small Base Tubes UV-199, \$1.00 postpaid. Send checks or money orders.

DEALERS—Write for circular and discounts.

ILLINOIS RADIO CO., Springfield, Ill.

An Ideal Gift



NOTE: With gold case which is built into leatherette covering case. 18 karats in color. Delivered in original box everywhere.

Price \$1.00 Postpaid

THE KEYSTONE PRODUCTS CO.
308 Cardiac Ave., Hazel, Pa. 15115.

GOLDEN-LEUTZ

PLIODYNE-6

TRADE MARK REG.

"The Perfect Broadcast Receiver"

A NEW SUPERIOR BROADCAST RECEIVER
SIMPLE-LONG RANGE-HIGHEST QUALITY
NON RADIATING - NON REGENERATIVE


*Two Stages Tuned Radio Frequency-Detector
and Three Stages of Audio
Frequency Amplification*

\$95.00

Completely Constructed
Without Accessories
Transportation Prepaid



PLIODYNE 6
Front View Showing Simplicity of Control

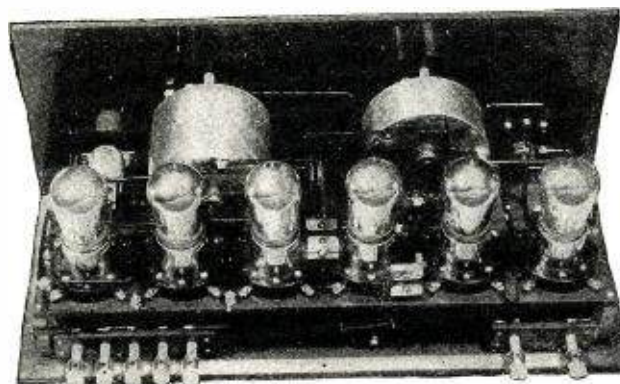

PLIODYNE 6
Interior View Showing Compact and Efficient Design.

A New Marketing Plan

Rather than sell this high grade receiver to wholesalers at \$190.00 less 50% discount we are going to sell it direct to you at wholesale, saving you \$95.00 and at the same time giving you the finest set that can be bought for twice the amount.

Inspect the "PLIODYNE 6" At Our Expense

We will send the "Pliodyne 6" C. O. D. transportation prepaid with privilege of inspection. If it does not appeal to you as the finest medium priced broadcast receiver you ever saw, return it to us at our expense. *Otherwise take advantage of*

A FREE TRIAL

Accept the C. O. D. and try the "Pliodyne 6" for five days. If you are not satisfied in every way return it at our expense and we will return your money.

Our Guarantee

We guarantee every Golden-Leutz "Pliodyne 6" to be the finest broadcast receiver that can be manufactured using 6 tubes or less and to be satisfactory to you in every way and to reach you in perfect condition.

You take no risk whatever in sending us your order for unless you are completely satisfied with the receiver and with your saving you may return the receiver to us and we will refund your money.

GOLDEN-LEUTZ, Inc.
476 Broadway, - - - New York City

Licensed under Farrand Agreement and U.S. Patent No. 1,914,003

NOTE.—We reserve the right to withdraw the Free Trial Offer if our Factory Production is exceeded. Golden-Leutz, Inc.

XMAS GIFTS ON CREDIT

10 MONTHS TO PAY

Sweet's
Diamond and
Gift Book
Send for Your
Free Copy Today

It shows a wonderful selection of Diamonds, Watches and Jewelry, Silverware, Ivory Ware, Toilet Articles and Novelties—all suitable for Christmas gifts. Make your selections today on our Easy Confidential Payment Plan—one-fifth after you receive and examine your purchase and the balance in ten easy monthly payments.



OUR CHALLENGE If you do not find that our price on any diamond ring is at least 10% lower than that of any other concern, either cash or credit, we will gladly refund your payment in full, if you return the ring within two weeks. Send today for your Diamond and Gift Book—IT'S FREE.

THE HOUSE OF QUALITY
L.W. SWEET INC.
1060 BROADWAY, NEW YORK

or other prominent part of physiognomy of such persons.

If gentlemen for such job are desired, I will be pleased to apply for such position, and can be secured at undersigned location at reduced salary.

Sensitively,
CHIN CHEN CHOW,
Shanghai, Ariz.

The Behavior of Radio Waves and the Heav- side Layer

(Continued from page 899)

light would be fatal both to animal and vegetable life. The radiation from so extremely hot a body as the sun is of a very violent character, having all the deleterious qualities of X-rays, and others in addition. So filtered sunlight constitutes a powerful ionizing agent. Also it appears that the sun itself shoots off free electrons, mingled probably with positive particles. These, according to Arrhenius, would be sorted out by the earth's magnetism, the positives falling mainly at the tropics, the negatives being deflected to the Poles, where they give rise to aurorae, the opposite charges ultimately recombining with recognized atmospheric effects and earth currents and other disturbances.

Sunlight is one of the main causes, therefore, which may give us a fairly sharply bounded conducting stratum in the atmosphere; though it may be corrugated and otherwise disturbed by heat effects. And this layer it is which has been treated as the main reflector or whispering gallery responsible for keeping the waves traveling around the curvature of the earth, and partially preventing their escape into space.

Mr. Feiler has dealt with the theory of an ionized atmosphere very thoroughly. And on the whole this Heaviside layer has been felt fairly competent for its work, though admittedly the whole subject demands extensive observation and record of experience before the theory can be considered in any respect complete. Like all meteorological phenomena it is complicated by a multitude of causes and no one simple theory can adequately cover the ground.

In one of the interesting and instructive radio articles which Professor Howe contributes to the *Lancet* paper "The Electrician" once a month, he comments (in the issue of June 13, page 720) on what he calls "the overworked Heaviside Layer" in the upper atmosphere, and on the criticism of it by Professor Guinchant of Bordeaux. This gentleman objects that the layer is not sufficiently conducting for low E.M.F.s, unless it is ionized; and he claims that the sun cannot ionize it, for two reasons: First, because a constant supply of electrons would soon overcharge the earth and deplete the sun; much as a thoroughly insulated filament in a vacuum tube could not continue to do its work properly. And secondly, because ultra-violet light can only ionize things when it encounters dust or solid particles. But I suggest that Professor Guinchant overlooks the exceedingly high frequency of some of the radiation likely to be emitted by a body at the temperature of the sun. Some of it would be X-rays, competent to ionize even nitrogen atoms; and anyhow there is no doubt that the inner atmosphere is ionized; the Aurora is sufficient evidence of that.

The problem of the transmission of waves around the world is a most interesting and difficult one, and certainly the last word on it has not yet been said. But few acquainted with the facts can doubt that the atmosphere is largely responsible for the possibility. It must be the main deflector for world trans-

MODERN RADIO RECEPTION

A New Book
by
Charles R. Leutz

264 Pages, 150 Illustrations
Fully Bound

Partial List of Contents

Radiolu Super-Heterodyne Diagram
Western Electric 4 B Receiver
Model C Super-Heterodyne
Model C 7 Super-Heterodyne
Long Distance Reception
Short Wave Reception
Long Wave Receivers
Mikodynes and Super-Mikodynes
Laboratory Equipment
Broadcast Transmitters
High Efficiency Amateur Transmitters
Model L Super-Heterodyne

and
Everything of importance relating to
Broadcast Reception.

Price

\$3.00 Postpaid

**Experimenters
Information Service**

Incorporated

476 Broadway
New York City

PATENTS WHITE for one Three Guide Books and "REC-ORD OF INVENTIONS" volume disclosing inventions, Send model or sketch and description of your invention for Examination and Instructions. Electrical rates a specialty. Highest references, reasonable terms, prompt attention.


No charge for the above information.

VICTOR J. EVANS & CO.
919 NINTH ST., WASHINGTON, D. C.

NATIONAL CAPITAL VIEWS
Takes the beautiful interesting Post Card Views of Washington, D. C. Public House and Capitol View included; using the best. **CAPITAL VIEWS**
528 Board Street, N. W. Washington, D. C.

The Greatest Advance yet made in **RADIO**

Marshall
3-4
and 5
Tube Sets

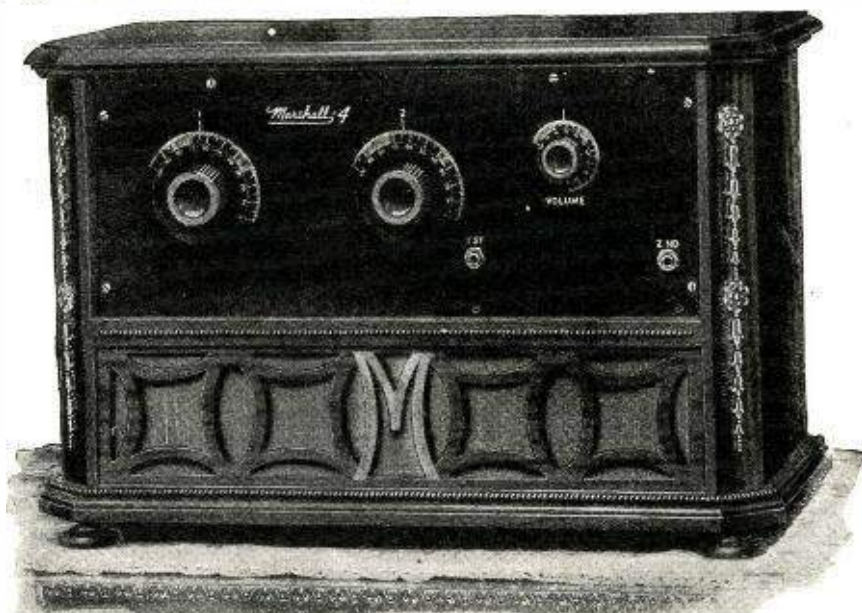

Receiver
and Loud
Speaker in
Combina-
tion Cabinet
of Solid
mahogany

**This Beautiful
Marshall 4 Tube
Non-Oscillating Receiver**
Complete with all accessories

**only \$5⁰⁰
DOWN**

WRITE TODAY for full particulars of this most exceptional offer. Marshall Sets embody the very latest improvements known to radio. The wonderful new principle involved is proving the sensation of the 1924-25 radio season. Zero Coupling—the problem which radio engineers have been working on for years—has at last been solved. As a result, the Marshall has no need for neutralizing condensers or other make-shift methods of avoiding internal oscillations which invariably reduce efficiency. The Marshall Tuned Radio Frequency Receiver brings to radio a new degree of musical quality. Its selectivity will delight the experienced radio operator. Yet it is so easy to tune that the novice will handle it like an expert.

Easy Monthly Payments—2 Weeks Free Trial

This is the remarkable offer we are prepared to make you. Two weeks to prove that the credit you select is everything we have said for it. If it doesn't make good our claims, back it comes, and your deposit will be cheerfully refunded. But if it fulfills all your expectations, you may pay for it in easy monthly installments. You don't risk a cent when ordering from us. You must be satisfied, or we don't do business. Is it any wonder that radio buyers the country over are rushing to take advantage of such an offer? If you are interested, spare no getting your order in early, while prompt shipment can be made. Everyone predicts a serious shortage of radio supplies this season. Send for full particulars today.

Beautiful Solid Mahogany Combination

Compare the beautiful Combination Cabinet, pictured above, with the usual radio set and horn. Here the receiver and Loud Speaker are combined in a single mahogany cabinet. Do it this winter, we also have the Receiver in a separate cabinet of solid mahogany. These cabinets are the work of a master designer—finished of solid mahogany. They will harmonize with the surroundings of any home. As fine as the finest. These Marshall sets are verily the best in price. Compare them with others which will tell for themselves. This receiver you can order a Marshall credit on the order form and pay for it on very easy terms.

Complete Outfits If Desired

In buying from Marshall, you have the choice of a set complete with all accessories, or the set alone. You have choice of dry cell or storage battery outfit. Unless you already own the accessories, you can buy them from us at less than market prices, with your set, on easy terms. Your outfit will come all ready to get up and operate within a few minutes—saving time and trouble—and saving money, too.

MARSHALL RADIO PRODUCTS, INC.

Marshall Blvd. and 19th Street, Dept. 59-49 Chicago

Send Coupon for Special Offer!

If you have any idea of buying a radio set this year, don't let this chance slip by. Our terms and liberal guarantees have set a new pace in the radio business. The low prices we will make you on a 3, 4, or 5 tube Marshall set will surprise you. A letter, postcard, or just coupon will do. But send it today.

We also have a most favorable offer for radio dealers. Write

Marshall Radio Products, Inc.

Marshall Blvd. and 19th St., Dept. 59-49 Chicago

Please send me your special offer price, terms and full description of Marshall Radio Cabinets. (Check 1 set change and bill on receiving your first payment, as per order form and 47 a.)

.....3 Tube4 Tube5 Tube (Please check)

Name
Address



Far Better Reception Or your Money Back!

MAIL THE COUPON AT ONCE for a pair of Karas Harmonik Audio Frequency Transformers. Purchase is that new radio set you are building or get them as your outlet in place of the transformer you are now using. Try them out—test them thoroughly for two days. If you don't enthusiastically agree that they give you the most delightful radio reception you have ever heard send them back and we will return your money at once!

That's Our Special
Introductory Offer!

KARAS HARMONIK \$7.00

Those who are now using Karas Harmonik Transformers in their radio sets tell us: "If we could hear better in all radio sets, we would be regular customers of Karas Harmonik Transformers. They would all want Karas Harmonik Transformers, at once. But there is only one way to fully realize the delightful, clear, loud, full-bodied sound of Karas Harmonik, and that is to actually hear them! That is why we make this amazing trial offer."

We are making the deal with Karas Harmonik

just as fast as we can. In the meantime we are making the "Proof By Trial" offer direct to you, discriminating and particular radio reception at a very low price. If you already have received the enjoyment of Karas Harmonik, it is not to be had for less than this offer.

We might give you a pair of Karas Harmonik Transformers, but you must give us your word, in writing, that you will use them for at least 30 days. If you do not like them, we will refund your money. If you do like them, we will give you a pair of Karas Harmonik Transformers at once. If you do not like them, we will refund your money. If you do like them, we will give you a pair of Karas Harmonik Transformers at once.

Karas Electric Co.,
4040 N. Rockwell St.,
Dept. 57-48
Chicago, Illinois

Send No Money With this Coupon

Enclosed find the coupon for a pair of Karas Harmonik Audio Frequency Transformers. I will pay the balance of \$3.00, plus postage, on delivery. It is understood that I am privileged to return the transformers for a full refund within 30 days if they do not give exactly satisfactory results, and my money will be refunded at once.

Name _____
Address _____
City _____
State _____
Zip _____
I have read with interest and satisfaction the advertisement for Karas Harmonik Audio Frequency Transformers and I am convinced that they will give me the most delightful radio reception I have ever heard.

Indure your copy reaching you each month.
Subscribe to RADIO NEWS — \$2.50 a year.
Superintendent Publishing Co., 51 Park Pl., N. Y. C.

mission. If it is ever found that short waves are able to go around as well as long ones,—and some recent statements suggest that facts are trending in that direction; as then the whole question—I do not say it will have to be reopened, for it has never been closed—but the whole question will enter on a new phase.

The way in which natural conditions seem to assist long-distance radio communication, and as it were unexpectedly to lend a helping hand, is rather remarkable. It is generally said that the perfect adaptation of ways and means to ends, which we frequently encounter in the operations and processes of live things, must be due to their long continued adaptation through the ages, and survival of the fittest. But that explanation cannot be applicable to a recent innovation like radio telegraphy; and it is interesting to find in the earth's atmosphere a favorable agent which indirectly promotes radio communication, even at enormous distances, and thus lends itself to the convenience of man, although the very recent inception and development of the process cannot have allowed any time for adaptation and survival.

A Marine Radio Operators' Association


(Continued from page 951)

The mates and engineers have their associations, which are to be commended. However, in contrast to the radio operator, in some places they are over-represented with more than one association. Some of the mates or engineers belonging to more than one are sometimes "on the fence" when certain issues develop. So it would be best for the operators to let their plight be an example and when they do unite, all belong in one organization.

When considering a Marine Radio Operators' Association, the following self-evident truths should receive some thought. Consider an increase of personal efficiency as a basis for the organization and stabilization of the profession; for betterment of the profession for present and future time. The profession can be bettered, and with a clean association as an agency, the present rights, position and remuneration can be maintained, thus granting basis for future advancement. In Mr. Fyle's article, September issue, he states: "Very likely the operators on the lakes or on salt water doing the work mentioned, do it because if they protest they have no one to back them up." When a steamship company cannot get an operator for a certain vessel they are bound to investigate the why and wherefore and probably will, in a very short time, correct the existing condition in that particular case.

An association for the marine operator must state an official organ to produce and give growth to the fraternal spirit which must exist. The "Tappa Kee" Fraternity is described briefly in this department in the September issue, in which article it is stated, "Were it not for the strong fraternal spirit of these men it would be difficult indeed to keep in touch with them." Due to shifting around or changing of crews, the operator has no opportunity for organizing personally and the bonds of the Association must be through letters and an official organ. The organ must be kept up and besides being instructive it must serve as the outlet for the human and personal element found in the profession.

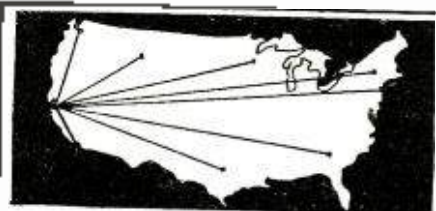It is evident that an honest, good, clean association for the Marine radio operators of this country could exist. Instead of "Why Not?" the question really is: "What is the most practical way to form such a 'Marine Radio Operators' Association'?"



ON ONE TUBE

FREE BOOKLET with the story. California users of CROSS COUNTRY CIRCUIT hear Atlantic Coast, Canada, Cuba, Mexico and Hawaii. Atlantic Coast users hear England to California. Our new play makes this act easiest and cheapest to build. One hour puts a operation. One tuning control. No soldering. Any service can do it. BIG BOOKLET FREE or complete instructions for 25 stamps or coin.

WHAT USERS SAY

EAST—Am more than pleased with the parts ordered from you. The first night I hooked it up and received Omaha. Since then Minneapolis and Los Angeles. It works better without disconnection than most sets with two stages.
—Donals, S. C.
WEST—I am sending you a list of some of the stations heard on one tube: WFL, WGY, KDKA every night. WJZ, WJL, WTAM, WLW every night. CFAC, CHCR. Not long ago I purchased another set of parts from you and first night got WGH, Buffalo, and KDKA.

NORTH—Received parts for today. If I have some results with these that I had with last will be wanting more. I am 1,250 miles from nearest station and have picked 36 to date. Chicago, Havana, Mobile, New Orleans and TWO IN ENGLAND.—Lansburg, Canada.
Vesco Radio Shop BOK BN-117 OAKLAND, CALIF.

PATENTS

To the Man with an Idea

I offer a comprehensive, experienced, efficient service for the prompt, legal protection and the development of his proposition. Send sketch, or model and description, for advice as to cost, success through prior United States patents, etc. Preliminary advice gladly furnished without charge. My experience and familiarity with various acts frequently enable me to accurately advise clients as to probable patentability before they go to any expense. Holder of valuable information and form for proper disclosure of your idea free on request. Write today.

RICHARD B. OWEN

PATENT LAWYER
2000 Building, Washington, D. C.
2126A Westview Bldg., N. Y. City

Six Tools in One

\$1.25

A radio socket wrench that fits every round and hexagon radio nut.




Sockets ranging from 1/4" to 3/4"

How it works

Place socket of required size on end of shaft with slot not in line with lugs on shaft.

Buy it from your dealer or direct from us

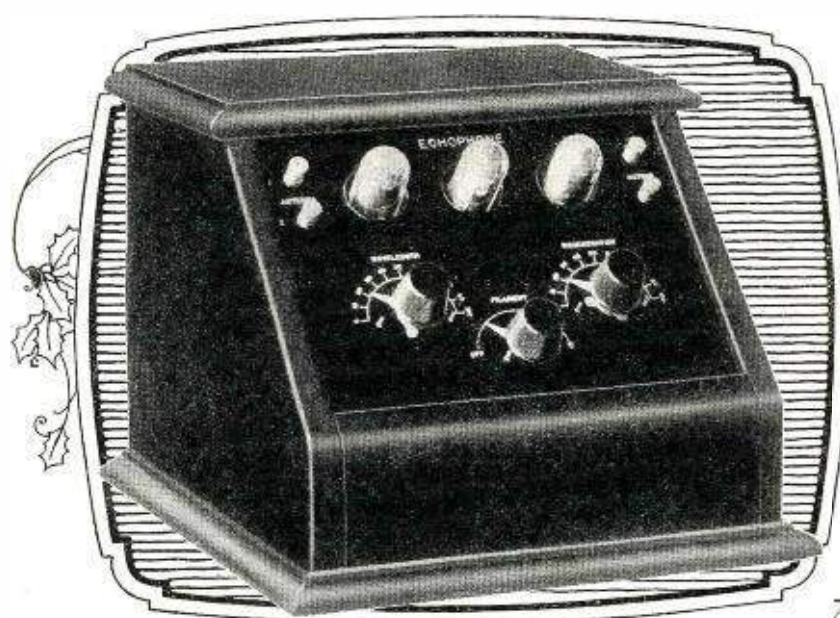The FAY COMPANY, Elyria, Ohio
Screw Machine Products



The Echophone "V-3"

*The Super-Volume
3-Tube Regenerative*

Without Tubes and Batteries

\$50.00



The Ideal Gift

Distinctively Superior Yet Moderately Priced

WHEN you give your family the Echophone "V-3" for Christmas you are giving them radio entertainment of a noticeably finer quality than is afforded by any other three tube receiver on the market.

For here is a machine that brings "real music" into your home—that reproduces even the loudest and low pitch tones, all voice modulations exactly as they are when they enter the microphone a half mile or eighteen hundred miles away. The Echophone "V-3" as a receiving set any novice can operate. It has only two tuning controls which once set brings in only the stations wanted. Operates with dry cell batteries, which fit into the handsome Adam Brown finished self contained cabinet.

As comparison readily reveals, such performance is available at moderate cost only in the Echophone "V-3." It is the result of special construction features and the use (through license obtained under U. S. Patent No. 1,123,149) of Armstrong's famous regenerative circuit.

For those who want the ultimate in radio reception there is the Echophone "F-5." The 5-tube combined radio and audio frequency set that assures loud speaker reception of distant stations from either loop, indoor or outdoor aerial.

Ask your dealer about these sets today. Meantime send for our descriptive folder. Address

The Armac Radio Company, Agents

1120 N. Ashland Ave., Chicago, Ill.

Manufactured by THE RADIO SHOP, 1120 N. Ashland Ave., Chicago, Ill.
Long Beach, Cal. Sanapole, Cal.



ECHOPHONE "F-5"

Without Tubes and
Batteries

\$110.00

ECHOPHONE

Storage Battery Results at Dry Cell Cost

Dealers: Get in Touch
With Your Jobbers.

THE ARMAC RADIO CO.
1120 N. Ashland Ave., Chicago, Ill.
Please send folder describing fully the Echophone
"V-3" and the Echophone "F-5." My Radio dealer is

Name
Address



Information Wanted about the **CONTINENTAL LO LOSS CONDENSER**

We are much interested in the many reports of distance and efficiency that come to our office regularly from enthusiastic users of Continental Lo Loss Condensers.

P O Z-Germany

is the record of a U. S. Radio Official in Baltimore, who hears that station regularly on 75 meters. Others tell of wonderful reception on both long and short wave-lengths with every possible kind of hook-ups. Have you got the POZ record hear? Write us.

Continental Lo Loss Condensers are made in the following sizes. All capacities are exact.

15 Plate—Capacity .00025	\$3.50
18 " " .00015	5.75
25 " " .0005	6.00
45 " " .001	7.00

Prices without Varner \$1.00 each

At your dealer's or write us direct

GARDNER & HUSBURN, INC.

PEREGRINE, ILL.

Sales Dept., 612 Widener Bldg.
Factory, 2300 Washington Ave.

Automobile Makes 27 Miles on Air

An automobile goes 27 miles on air by using an automatic device which was installed in less than 5 minutes. The automobile was only making 30 miles on a gallon of gasoline but after this remarkable invention was installed, it made better than 57. The inventor, Mr. J. A. Stramsky, 4129 Eleventh Street, Pukwana, South Dakota, wants agents and is willing to send a sample at his own risk. Write him today.—Adv.

Include your copy reaching you each month.
Subscribe to RADIO NEWS—\$2.50 a year.
Continental Publishing Co., 33 Park Pl., N.Y.C.

ling into port. Aviators, whose lives depend upon good atmospheric conditions, trust implicitly in these forecasts. Contractors in distant places vary their work when the voice from the air says—"rain." Fishermen who leave shore in the early hours of the morning, long before papers are available, obtain the predictions by radio about 10 p. m. They obtain the latest information when at sea by the same means. Orchardists, mechanics, fruit growers, at home and in the tropics, snowmen, resort managers, railroad and automobile touring campers, and many others, all bear heavily the results of unfavorable weather, and there is no extensive method by which they can obtain weather forecasts other than the night weather broadcasts. So, when the announcer simply reads a short telegram of weather predictions, you will know that thousands will either rejoice or sorrow at his words.

HOW IT IS DONE

As an example of the manner and speed with which this work is expedited, we will take station KDKA, at Pittsburgh, Pa. The Weather Bureau observer at Pittsburgh telegraphs his observation report to Washington at 8 p. m., and then goes home and turns in. At 9:30 p. m. the announcer at KDKA receives the telegram containing the forecasts for Pennsylvania, New York, Ohio, Indiana, Michigan, West Virginia, Virginia and Maryland, which he broadcasts at 10 p. m., immediately following the time signal. The Observer can hear the forecast within two hours after he made his observations, upon which the forecasts are based. Hundreds of thousands listen to this particular service every night, many living in remote and inaccessible regions. This is a service that is typical of all the other broadcast stations.

The broadcasting co-operative system of the Weather Bureau includes 115 of the best and most powerful radio stations in the United States.

Why Radio News Favors Esperanto


(Continued from page 937)

rain; they have no chance; but if they desire to be exclusive, all very well, but then of course their pet lingo is eliminated from the entries in the International Language race. For any language to be International, it must be universally employed or it is of no service to the peoples of the earth.

For instance—the Continental Code used for radio communication may not be the best, but since everybody uses it, it is possible for operators of different nationalities to copy any message sent in any language, since each group of dots and dashes represents the same letter.

Now, as to the point of the desirability of the two mentioned languages, it has some advantages over Esperanto as a technical language, but fails in some other respects. We advocate Esperanto because it has admirably filled the requirements demanded of it and has by far the greatest number of followers, about twice the number of adherents as it. This means that should you take up the study of Esperanto, and it is a very easy language to master—there are quantities of people all over the world with whom you could communicate, while on the other hand should you learn this or one of the other tongues, you would be in the same boat as a person who can speak Latin fluently. You would have learned a language for which you had little use. You would be greatly disappointed because of its lack of serviceability. Esperanto, at the pres-

One Radio Book Everyone Reads

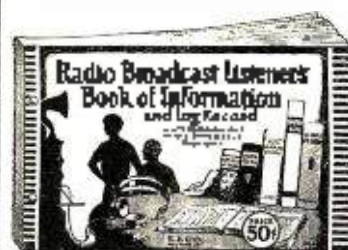

The Radio Broadcast Listener's Book of Information and Log Record

Is not only a complete, practical book of those essential Radio facts that everyone who owns a radio should know, but it is also a handy log record for those who want to keep a record of the stations they receive. The book is enclosed in a handsome two-color cover, bound in loose-leaf fashion, so that new pages can be inserted if necessary. It contains 60 pages, each one containing information more valuable than the last. The following is a brief summary of the information contained in this book:

Information for the Broadcast Listener:
Various Table, Meter wave length:
Radio Station, Wavelength chart:
Station log sheet

Complete list of Broadcast Stations in the United States, giving Name, wave length, and Time of Broadcast each day of the week.
Log sheets for recording the date, time, and of the stations you receive in your region.

Postage **PRICE 50¢** Paid

CONRAD CO.—Selling Agents
233 FULTON STREET
NEW YORK CITY

E.I. Company

Loud Speaker with one tube!

"This makes the cheapest set I know of for working a loud speaker with 11 or 20 tubes of a good broadcasting station," says H. M. Davis in "Radio to the Home." And many more are doing the same at home. With loud-phones Kelcoil brings to all DX listeners—LOUDER and CLEARER. Works in any broadcast hook-up. Most good dealers have the Kelcoil. If yours hasn't, we'll send you a Kelcoil C. G. H. parcel post. Mention dealer's name.


Users Tell Us: "Pardon Court say night." "Have heard in all regions." "Far exceeded my expectations." "Best of all kind an article."

We See Much Ups. Send the 50 tubes with Kelcoil for a week, and we'll refund the cost.

Dealers—Distributors—Write today for attractive proposition on this exciting set.

4500 RADIO PRODUCTS CORP.
440, A Division of Kellogg.

KELCOIL THE TUNING WONDER

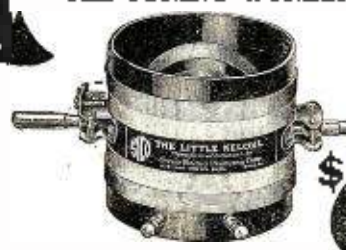

\$6



Dielectric!

A red stripe Bakelite-Dilecto panel has more dielectric resistance than is ever required in radio. It affords absolute insulation.

bakelite Dilecto

(Distinguished by its Red Stripe)

The U. S. Navy and Signal Corps have used Bakelite-Dilecto successfully for ten years. Makers of the largest radio sets favor it. Most practical material for amateurs' use. Use it for your next panel. Tell it by its red stripe.

The Continental Fibre Company

Factory: Newark, Delaware

Service from:

NEW YORK Woolworth Bldg.	SAN FRANCISCO 25 Fremont St.
CHICAGO Wrigley Bldg.	LOS ANGELES 407 S. Hill St.
PITTSBURGH 301 Fifth Ave.	SEATTLE 1041 4th Ave. So.

Tubes Repaired

Only middle west tube service station

8 hour service. No extra charge for broken glass.

WD-31, WD-32, C-31, C-32

UV-201, C-301

UV-201-A, C-301-A, UV-198, C-298

All styles DeForest

UV-250, C-300

Business in quantities of six or more. May be had in assorted styles. We pay the postage.

Dey's Radio Service

Dept 8, 5947 Superior St., Chicago, Ill.

\$2.25

Enter your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 53 Park Pl., N.Y.C.

ant time, is being used extensively throughout Europe and is helping to do much in the way of stimulating commerce as well as good will between the nations. If we learn Esperanto, we can talk to these people; if we learn one of the other tongues, we cannot talk to them. It is the logical thing for the people of the United States to select Esperanto as the International Language. The sooner the others are forgotten, the better, and the nearer all the nations of the world will be to a mutual understanding, that for which we are working and which is impossible without a common tongue.

In conclusion, we repeat Radio News favors Esperanto as the International Language for the reason that it is the most widely used and is too strong to break down. It can be weakened by the building up of it, but then we are back in the same old rut, two Universal Languages, two factions and ever so slight a gain in the direction of the desired goal. In such a case "each to his own language."

Following is an article published by Dr. Pierre Corret, president of the Internacia Radio Asocio (International Radio Association), in the "International Language" magazine in which he clearly explains why Esperanto is the International Language to use for radio communication.

The Morse code, which is used for telegraphy, with wires or without, is international. It is, therefore, easy for a telegraphist to receive a telegram in a language which he does not know. The apparatus as it were, "dictates" to him letter by letter. It is only necessary for him to write down the letters one by one as he receives them, and there is no necessity for him to understand the meaning of the words and sentences, which he writes. The multiplicity of languages, therefore, is not a very serious bar to telegraphy if the operator has only in view automatically telegrams not addressed to him personally.

But it is quite another matter when he has to abandon this merely mechanical role and enter into direct relations with his correspondent. If two parties using the telegraph have no language in common, it is impossible for them to achieve mutual understanding. And this state of things is fairly frequent in the case of radio. For in that field one is liable at any moment to get into touch with a telegraphist whose language is different from one's own.

In order to facilitate international communication, the London Conference on Radio Telegraphy accepted 40 or so conventional groups of letters, beginning with "Q," by means of which information may be asked or given as to the service, usually between ship stations. Thus, QRA? means: What is the name of your station? QRD?: Where are you going? QRE?: Where do you come from? QRK?: Do my signals come through properly? QRX: Must I wait? and so on.

There exists also a maritime "International code of signaling" by means of which certain set phrases may be exchanged. DAY means: I am busy; QMP: What has happened? DOQ: What do you advise? KWP: Send a description; QOY: Are you in good health? UCT: I am ill; TMV: What will you want...

But these means are wholly insufficient when it is necessary to telegraph something outside the scope of these prearranged phrases, or when those telegraphing have no language in common. The following for example was written to me a few months ago by a British radio-telegraphist (notwithstanding the fact that his language is one of the most widely known):

"There are few English or American stations that understand any other language than English, and French or

Announcing The SILVER-TONE A New Audio Frequency Transformer Ratio

7-1 3-1

1st Stage

2nd Stage

Better and clearer reception you ever experienced, the last word and achievement in radio.

BUY A PAIR—THEY ARE MATCHED

Money Back Guarantee

\$3.75 Each \$7.00 a Pair

Announcing the New Type 1-A Triplet Silvertron Tubes

BETTER THAN EVER

Long Life Clear Reception

\$3.50 Prepaid



Type 1-A (5-6 volts) operates as either Detector or Amplifier on 1/2 amp. filament consumption. The Ideal Tubes for Neutrodyne and Super-Heterodyne.

Type Detector 12 1/2 volt
The Silver Tube with the
Golden Voice

**A SUPER
VACUUM TUBE
for
\$3.50**

GIVE WONDERFUL AND CLEAR RECEPTION
Operates as either detector or amplifier on 1 1/2 volts. When detecting specify 11 detector or amplifier tube is preferred. Full standard socket. Filament consumption 1/5 of 25 amperes. Guaranteed to give entire satisfaction, or money refunded. Sent parcel post prepaid carefully packed to any address on receipt of \$3.50.

DEALERS and JOBBERS
Write for Discounts and Circulars.

New York Radio Company

71 West Broadway
New York City, N. Y.

De Luxe Extension Cord and Plug



25 Feet
Extension

Reversible
Plug

Adapted to every make of Loud Speaker—Phonograph Attachments—Head Phones.

Sold at all reliable Radio Stores.

Price \$2.00 Complete


Newarkians

DE LUXE SALES CO.

112 Trinity Place New York City
If Ordering Direct Mention Dealer's Name.

Enter your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 53 Park Pl., N.Y.C.

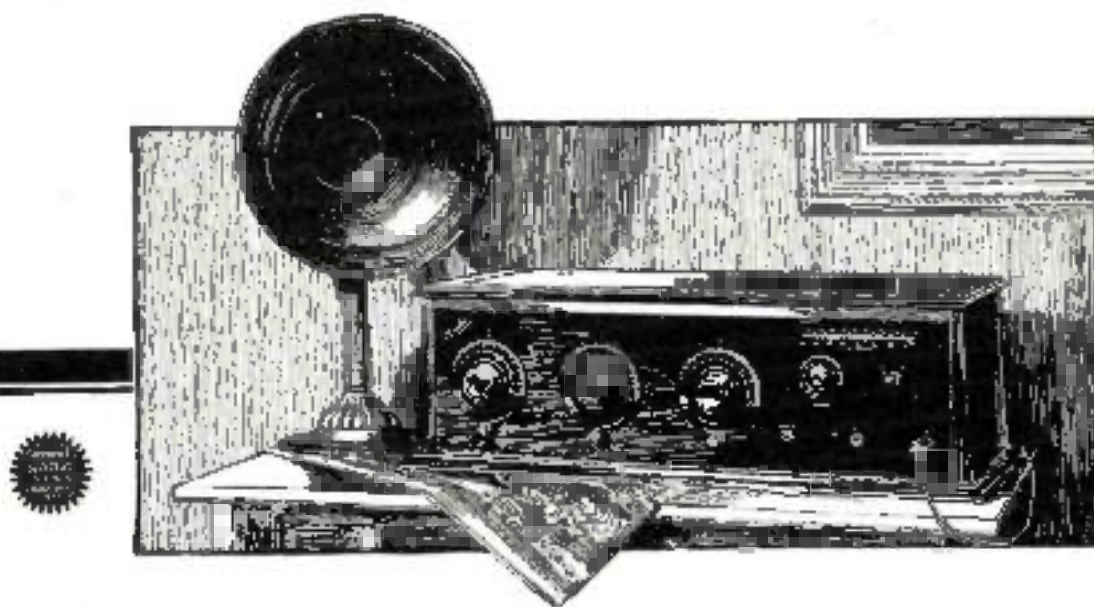A New Way to Get Supreme Purity and Sweetness of Tone



—the Pfanstiehl Model 7 Receiver

A 5-Tube Receiver using the new system of tuned radio frequency

AN entirely new stage of radio development has been reached by the Pfanstiehl non-oscillating system. Radio has not been entirely satisfactory hitherto. It has been more or less of a scientific toy, furnishing excitement for the radio fan rather than dependable enjoyment for the home. People now want trouble-proof service and purity of tone. The new Pfanstiehl meets those requirements, as they have never been met before, by avoiding complications. It is surprisingly simple, trouble-proof, gives a clear, natural tone at any distance. Internal noises have been absolutely eliminated.

The Pfanstiehl Non-Oscillating System a Revolutionary Improvement

Hitherto radio has been advancing along the line of more and more complication to get a higher sensitiveness. As amplification increased, internal noises developed. These were due to stray oscillations throughout the receiver which had to be choked down or neutralized by extra condensers, stabilizers and wiring—complications which get out of order and need adjustment. This was not the way to make radio a dependably enjoyable instrument for the home. It was not simple enough.

Simple—and Clear as a Bell

What Pfanstiehl did was to design a non-oscillating system, which gets rid of all stray oscillations—keeps

them out. There is no need of choking or neutralizing devices. You can change tubes as often as you like. No adjustments are needed. *The absence of such devices greatly improves purity and sweetness of tone.* Speech and music are naturally received and reproduced. In this respect distance makes no difference. There is no distortion, however great the amplification. Tuning is so sharp that wave lengths can be distinctly and separately received less than eight meters apart.

The "Station Finder"

is another big Pfanstiehl improvement that takes the guesswork out of tuning. This consists of three large dials which tune the three successive circuits. Therefore, these dials are turned identically, or to the same number, for any given station. This means that to receive on any one "wave length" you need to know but one number. That number is given by the "Station Finder" on the right-hand upper corner of the panel. On its lower scale, read the "wave length" of the station desired. (This information is obtained from the daily papers in the newspaper.) Directly above the "wave length" read the number at which the three large dials are all to be set to secure reception.

DEALERS: Exclusive local franchise open to strictly high-grade dealers in a number of desirable territories. Act quickly. Write for the Pfanstiehl Proposition.

PFANSTIEHL RADIO COMPANY

Highland Park

20 S. Second Street

Illinois

Pfanstiehl



Catch Everything in the Air!

Keep your radio batteries charged — and you won't miss a thing

APCO Battery Charger does the trick over-night for less than 10c per battery. It's noiseless, clean, compact. Connects with ordinary light socket as easy as an electric "flap." Write for interesting circular and nearest dealer's name.

Apco Mfg., Co.
Chapman St., Providence, R. I.



APCO BATTERY CHARGERS

for "A" and "B" Batteries



NU-TRO TUBES

ALL TYPES
GUARANTEED

Dealers, Write for
Special Trial Offer

C. A. W. LABORATORIES
Sole - 425 Chestnut Street
PHILADELPHIA, PA.

WALNART

"TROUBLE-FREENESS"
RADIO PRODUCTS

Italian ships accordingly often have difficulties with these stations. I myself experienced this when traveling to the Argentine. I was then on the English ship *Denzirton* bound for Buenos Aires. On meeting an unknown ship I hailed, asking: QRA? What is the name of your station? It replied QRA *Argentine ship, Estero*. I then continued QRD? QRF? Where are you going? Where do you come from? The reply was: QRD Cadiz, QRF Montevideo. I gave this information to the Captain who said: Ask what weather they have had since leaving Montevideo. Here my trouble began. I could not speak Spanish, therefore I asked in English, What weather have you had? The ship replied something in Spanish which I could not understand. One of our Officers knew a little French and he translated the sentence into French. I sent it to the *Estero* and received the same reply as before. They could not understand my question. I asked in Esperanto with the same result. It was impossible to continue the conversation.

It is a matter of common knowledge that experiments in trans-Atlantic transmission are at the present time being made on a short wave-length. Experience has proved that reception may be obtained at very great distances. European and American amateurs have succeeded in getting into two-way communication with wave-lengths of 200, 100, and even only 40 meters, with comparatively small power. Once when experimenting at my own transmitting station SAE, on a 200-meter wave, I got into touch with the British Station 20B. Unfortunately, the man at 20B, who was a very skilful experimenter, knew no French at all, and I myself am quite unable to use English. After the interchange of a few words in English and French with difficulty, and only partial understanding on each side, the station 20B finally informed me that it did not wish to waste my time any longer and thus the interesting experiments which without the barrier of language we could have made, had to be abandoned.

Over the whole vast territory of the United States, where there is one common language, amateurs relay telegrams to far distant places. In Europe the position is quite different. Even a comparatively weak station has within its range countries where many different languages are spoken. As Mr. H. A. Epton very truly remarked in the "Wireless World," for amateurs who wish to get into touch with only one country, it suffices to learn the language of that country (although the study of even that one language may be a long and difficult process). But for those who wish to be in touch with many countries, for example, Denmark, Holland, Czechoslovakia, Germany, Spain, etc., it will manifestly be necessary to find some solution other than the learning of a multitude of languages.

In the case of radio telegraphy the diversity of languages is only a comparatively minor inconvenience—for it is not always necessary that the message should be understood at the moment—in radio telephony, on the other hand, the case is quite different. A telephone message which is not at once understood by the listener himself, mistakes its aim and is completely lost.

In many countries there are now to be found radio broadcast stations, which transmit not only concerts, but also speeches and other communications, each using its own national language.

These concerts and communications are heard at distances far beyond the frontiers of the country concerned. And though it is possible to enjoy music internationally, it is



No phonograph parts to be removed—Drop sound-box needle on Dulce-Tone

\$10 makes your talking machine the finest of loud-speakers. Link your radio to your talking machine with a Dulce-Tone. Reproduce radio broadcasting with deep, rich clarity. Small, unobtrusive, convenient. Does not require removal of any parts. A separate device—NOT an attachment. \$10 complete at radio and talking machine stores, or direct, if obtainable locally.

THE TEAGLE COMPANY
1125 Queen Ave. Cleveland, Ohio

Dulce-Tone

Radio Talking Machine Speaker



LANE 100 Volt

Non-Acid Storage

"B" BATTERY

NO MUSS NO SPILLING—CLEAN, ATTRACTIVE

Makes a wonderful improvement in your radio set. Gives it more depth and power. Makes listening a real pleasure. Give a clear reception of every word and every expected note. No more cracked and noisy sound. Take the full work out of your battery.

Life of Battery Unlimited

LITTLE OR NO REPAIRS EVER NECESSARY

No deterioration—no acid, no gas, no change—no leakage—no trouble—no need for over-charge. Outlasts the best of the old type without replacement.

PANEL SWITCHES Give instant and correct voltage

A direct and necessary improvement on batteries. Instantly correct voltage and all the advantages of perfect reception. Allow for charging in several ways. Complete hardware. \$25.00. At your dealer's or direct. U.S. \$25.00.

Write for Proposition to Dealers and Jobbers.
LANE MFG. CO., ONE, 10 2941 W. Lake St., CHICAGO

The "LINCOLN"

Enclosed Fixed
Adjustable
Detector


Kills your Reflex
Troubles

See List Price **\$1.50**

Manufactured by

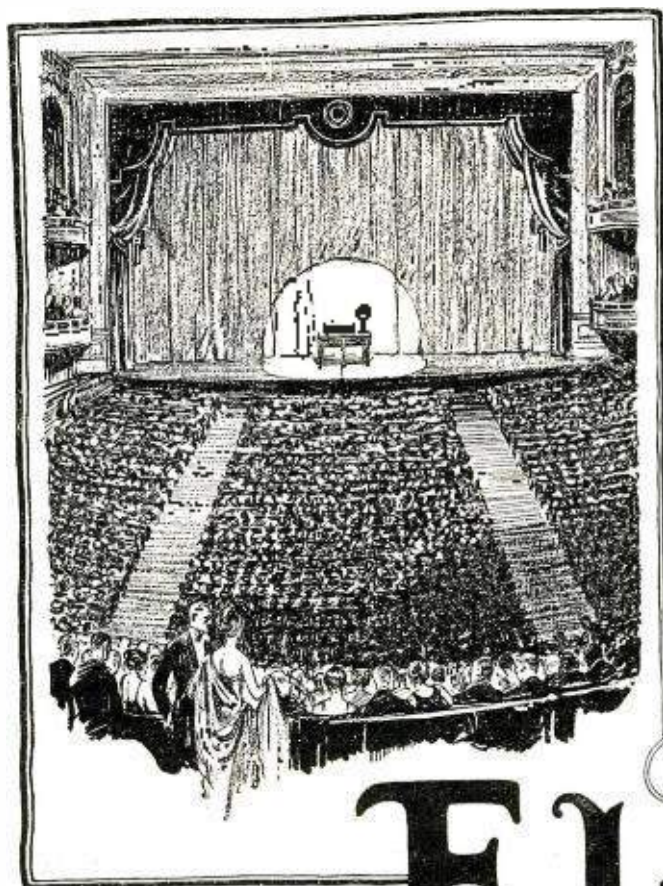The LINCOLN MFG. CO.
Dept. E-1 LOS ANGELES, CAL.





—and then
we heard

Electrola

The Musical Instrument of Radio

SUCH volume that it is necessary to warn users not to turn it on full—lest the loud speakers be thrown out of adjustment. A new tuned radio circuit—developed by the pioneer makers of radio parts in this country. Batteries and tubes will last from twice to three times as long. Marvelous selectivity. These are the high spots. The whole story in a booklet. Shall we send it? Jobbers: write for exclusive territory proposition.

The Famous Line of Kelford Radio Parts include a remarkable low loss condenser, a laboratory precision rheostat and an audio frequency transformer. These parts are more efficient because of our long experience—and at lower prices because of our facilities.

THE • AMERICAN • SPECIALTY • COMPANY

168 Holland Avenue, Bridgeport, Connecticut

America's Oldest Manufacturers of Radio Parts



**Better Your Signals
with
Stranded
Enamelled
Antenna**

It offers a greater receiving area for "skin surface" to the incoming wave than a single strand. Corrosion hinders the weak high frequency currents. The enamel coating prevents corrosion. This increases the range of your set.

If not at your dealer's, give us his name and we will send you a

**Free Folder Telling
How To Solder**

and also describing this Antenna; "Celastite," a new Spaghetti covered wire for radio sets; and a very high grade of Spaghetti Tubing.

THE ACME WIRE CO.
Dept. N., New Haven, Conn.

**ACME
WIRE**

Makes Better Sets



**Noiseless
Grid
Leak**

40c
each in any value
from 1c to 10

FRESHMAN SUPERIOR

Made of high resistance material incorporated throughout in one compact package. Unaffected by climatic conditions. Will not deteriorate. Clamps between solid knurled terminals ensuring rigid connection and free contact at all times.

At your dealer's, telephone and purchase price and you will be supplied postpaid.

Chas. Freshman Co., Inc., 104 3th Ave., N. Y.

Inquire your copy reaching you each month.
Subscribe to RADIO NEWS — \$2.50 a year.
Experiment Publishing Co., 53 Park Pl., N. Y. C.

otherwise in the case of speeches which are unintelligible for the majority of listeners.

Even music needs an International Language. In the days when Great Britain had no radio stations of its own, and British amateurs listened to Continental concerts, many of them used to write me asking if it would not be possible for the Eiffel Tower station to announce the titles of the musical items "in English also." Undoubtedly this solution of the difficulty would meet the needs of the British amateurs, but it would not in any way help the Spaniards, Italians, or Czechs, who also were listening.

It is unnecessary to labor the point any further, for it is obvious that communications broadcast in national languages are intelligible to only a small proportion of those who hear them, and very rightly Mr. Hugh S. Pocock, the Editor of the "Wireless World," has named Esperanto "The Key to World Broadcasting."

How few, for example, of the French amateurs, who, to use the current phrase "hear the British," are able to understand the speeches transmitted by the stations of the British Broadcasting Company! What is the proportion of British amateurs who understand the French discourses?

Even in the case of terminal experiments in radio, the language barrier stands in the way. One of the tasks of the experimenter which needs the greatest care is to reproduce to perfection the right modulation or timbre of the voice. An eminent engineer then in charge of the first experiments in radio at the Eiffel Tower once asked me to listen to the foreign stations, in order to report to him to what extent success was obtained in this respect. I could only reply: "You are asking me for something which is quite impossible, for even when an Englishman standing by me speaks in English, his 'modulation' sounds to me quite imperfect." In order to have the power of giving an expert technical opinion on the quality of telephonic transmission of a foreign language, it is absolutely necessary to know that language perfectly. As a matter of fact, British experimenters have often requested me by radio telegraphy to listen to their radio telephony. But in every case, even if they tried to speak my language (and in what a way! their transmission seemed to me poor. Without doubt direct speech with them would not have seemed much better!

It has often been said that the spread of the means of international communication will inevitably necessitate the adoption of an International Language. Railways, steamships, and aeroplanes, are the means referred to, but it is only to a comparatively small number of persons that they have brought home the need of an International Language. In the case of radio communication, and especially of telephony, the opposite is the case. There are thousands of persons at the present time who need only light up at home certain little lamps to get into direct communication with many different countries whose languages they do not know. They hear clearly, but understand nothing! If the saying is true, that necessity is the mother of invention, then there is no doubt that radio will bring about the definite adoption of an International Language, and that Esperanto, though scoffed at by some, and opposed by others, will very soon become the necessary handmaid of radio telephony.

The ever-increasing success of Esperanto has of course given rise to many imitations which are more or less noisily boomed. Each of these, of course, claims to be "better" than the original, and than all the others, as is usually the case with imitations. Their authors apparently have not realized the evil they do by discrediting in the view of the world the whole idea of

ARROW BATTERY

SLASHES Prices

Prices Smashed!

Quality Not Sacrificed

TO CONSUMERS ONLY

Here is real battery quality, guaranteed to you, at prices that will attract the entire battery-buying public. Order direct from factory. Put the Dealer's Profit in your own pocket. You actually save much more than half, and so that you can be convinced of true quality and performance, we give a

Written Two-Year Guarantee

Here is your protection! No need to ask for it. Our batteries right—and the price is the lowest ever made. Convince yourself. Read the prices!

Special 2-Volt Radio Storage Battery, \$2.75
Special 4-Volt Radio Storage Battery, \$4.00
2-Volt, 50 Amp. Radio Storage Battery, \$1.00
2-Volt, 60 Amp. Radio Storage Battery, \$1.00
4-Volt, 100 Amp. Radio Storage Battery, \$2.00
4-Volt, 120 Amp. Radio Storage Battery, \$2.25
4-Volt, 140 Amp. Radio Storage Battery, \$2.50

We ask for no deposit. Simply send name and address and \$2.50 wanted. Battery will be shipped the day we receive your order. Express C. O. D., subject to post establishment on arrival. Out guaranteed accompanied each battery. We allow 5% discount for cash or full with order. You cannot find better. Send your order today—NOW.

Arrow Battery Co.
1215 South Wabash Ave.,
Dept. 8 Chicago, Ill.

**A Pleasant Surprise Awaits the User of
the A. C. H. Sharp Tuner Dials**

WORM DRIVE



Why the A.C.H. is different

3 in. DIAL ——— 150-10-1
4 in. DIAL ——— 250-10-1

Money Back Guarantee

Price 1-inch dial... \$2.50 Price 4-inch dial... \$4.00
Regular Model 5/16 inch dial... \$2.50 each extra
EXTRA ADVANTAGE OF THE A.C.H.

1. Can be adjusted or returned from any instrument
2. Never lost or broken as are other dials.
3. Guaranteed to last as long as the owner desires.
4. Automatically locks instrument so no jar or vibration.
5. Dial grounded protected the last circuit in a station.
6. Special dial 2 graduations others ordinarily one.

Mail Orders Sent Promptly to N. & A.

A. C. HAYDEN RADIO & RESEARCH CO.
25 E. Butler St., BROCKTON, MASS., U. S. A.

MEN WANTED

EARN

\$35 to \$100 per Week

We offer excellent work to Chicago and find you. We give you an extra while you learn. We give you assistance while training—and GUARANTEE you an AUTOMOBILE job at \$100 per week and offer ready for it. Training required only 1 week. All automobile mechanics desired. \$2500 salary offered. We have 1000 of \$7,000 more. \$500 of which are now in hand—write for them now!

WRITE to Mr. FRED AUTO DRIVE and
Company, 1000 Broadway, 10th floor,
New York City.

Erwin Green, President

GREER

Automotive Engineering

224 E. Wabash Ave., Dept. 222, Chicago, Ill.

Insert your copy reaching you each month.
Subscribe to RADIO NEWS — \$2.50 a year.
Experiment Publishing Co., 53 Park Pl., N. Y. C.

At Last!

Radio That Satisfies

The Music Critic

THE DAILY NEWS SATURDAY
 Edition Standard, Ozone,
 Printed from "La Voix"



E. R. Rauland, Pres.
 Rauland Manufacturing Co.,
 2446 Cass St., Chicago, Ill.
 My dear Mr. Hackett:

THE
 CHICAGO DAILY NEWS
 (PROM. WASH.)
 August 6, 1924.

I must confess my great pleasure in examining the recent list of amplifying transformers in your catalogue, and in selecting, from different manufacturers, the one which seems to me to reproduce most exactly the artist's original sound. I was indeed gratified to learn, after the matter, that the feature which I had previously noticed as by far the most successful in reproducing, not alone the music, but even the very personality of the artist, was such other than your new "Rauland-Lyric" Transformer.

I am confident that music lovers everywhere will appreciate the satisfaction you have done to their enjoyment in the creation of this reproducing instrument.

Very truly yours,
 Maurice Rosenfeld
 Music Critic



Price, \$9.00

In placing his mark of approval upon Rauland-Lyric, Mr. Maurice Rosenfeld has invested Radio with a new beauty and dignity. His words carry positive assurance, to music-lovers and trained musicians, that they can now admit Radio to their field of appreciation and enjoyment, with the certainty that all voices and instruments will be reproduced with their original and distinctive Tone Quality.

Mr. Rosenfeld, a veteran among metropolitan music critics, selected Rauland-Lyric upon the sole basis of Tone

THE RADIO KEY BOOK contains a clear explanation of the most of the most of audio amplifiers and explains intelligible discussion of many other subjects in Radio. Sent for 20 cents, one per dozen.

Quality, from a group of the world's best audio transformers.

Karlson Hackett, famous critic of the Chicago Evening Post, pronounced Rauland-Lyric "a distinct advance in the musical quality of radio reproduction."

You can have, in your home, the amplifying instrument which has been commended by eminent critics.

Rauland-Lyric can be installed in your present set, or one that you may buy, to replace any ordinary audio transformer.

Ask your dealer.

RAULAND MANUFACTURING COMPANY
 Division of the Industry
 2446 Cass St. Chicago, Ill.

Rauland-Lyric




AN
 ALL-AMERICAN
 TRANSFORMER

The RADIO
 KEY BOOK
 E. R. Rauland



Precision
 Made for
 Reliability

ALL-AMERICAN

 <p>Standard Audio Frequency Transformers "An Answer for Reliability" Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35 (1000 to 100,000 cycles per second) Each set contains a complete set of instructions, a list of dealers, and a complete set of instructions for the use of the transformer at a price which is the lowest of its kind.</p> <p>Long Wave Transformers For highest reproduction of radio signals, 1000 to 10,000 cycles per second. Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35</p> <p>Power Transformers For Tone Quality in a Class of 10 to 1000 Watts. Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35</p>	 <p>Self-Tuned Radio Frequency Transformers "A Sound to See the Talk" Extremely amplifying, all frequencies within the radio range. Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35</p> <p>10,000 Cycle Transformer 10,000 cycles per second, 10,000 to 100,000 cycles per second. Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35</p> <p>Radio Frequency Coupler (Universal Coupler) - A complete set of instructions. Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35</p> <p>Universal Coupler Sets a new standard of efficiency in an amplifier circuit. Price \$10.15 - \$11.45 - \$12.75 - \$14.05 - \$15.35</p>	 <p>ALL-AMERICAN</p>
--	---	--

Largest Selling Transformers in the World

SUPER HETERODYNE

QUOTATIONS—from a few of the hundreds of letters we have received from enthusiastic purchasers of Pinkerton Kits,

DISTANCE—"I had Havana, Mexico City and Los Angeles all before 10 P.M. last night with ten New York stations all going full blast. This is the loud speaker using twenty-one inch loop only." N. Y. CITY.

SELECTIVITY—"No trick at all to pick up WLS 345 meters to WARD, 360 meters, to WGN, 370 meters, to WGY, 380 meters, to WDAR, 395 meters, to WJY, 405 meters. New Jersey.

"The surprising thing about this set is that the same station never comes in twice on the dial." Philadelphia.

PURE TONE—"Listening friends are amazed at the wonderful tone quality." N. Jersey.

"That is the cleanest tone instrument I have ever heard! It's just as if an orchestra were playing in the next room. It's much better than a phonograph." Mass.

EASY TO BUILD—"The tools I used are a screw driver, pliers and potting iron." Ill. "I put the large size diagram on the baseboard and each transformer stood on its own picture. The life size photo shows where to put each wire." New York.

"I got busy with the plans and kit at 7 P.M. At midnight I was listening to KHz on the best set I had ever heard. Expect to find a large order from a phonograph company." New Jersey.

LIFE-SIZE PHOTOS-PLANS—"I have never seen anything like this in any kit." N. Y.

"No, measuring or computing is easier to follow than a dress pattern." Penn.

"Like having a complete set before you. You can't go wrong." Del.

"No real fan who has or can 'bag, borrow or steal' two dollars (\$2.00) will fail to send for your life-size plans and photos on approval." New York.

COMPLETE PLANS \$2.00

4 Matched Transformers and Oscillator
Coupler \$12.50

Complete Kit \$40.00

All inquiries will receive prompt and personal answer. Write us your troubles!

PINKERTON RADIO CORPORATION

Super-Heterodyne Exclusively
1834 Broadway, New York

EVERYTHING IN RADIO

25% DISCOUNT

ANY RECEIVING SET
ANY SET OF PARTS
ANY ARTICLE OR PART
ANY TROUBLE

Give full details. Say exactly what you want. We will send anything C. O. D. We are your servants.

If you are not certain what you want, give full details and describe you wish and we will send the cheapest part, set of parts or receiving set for best results.

Prices lowest. No order too small or too large.

MAIL ORDERS ONLY

THE ALL RADIO CO.

412 North Clark St. Chicago, Illinois

INVENTORS

Who desire help in developing their inventions and have no money to pay for the same, write to the Inventors' Bureau, 1001 Broadway, New York City, N. Y. Established 1909.

an International Language, and giving to sceptics, for the sake of their personal whims, the impression that there exists a second Babel of International Languages beside that of the national languages. No, there must be one International Language, or none!

The radio field naturally has open to Esperanto. More than 40 radio stations in Britain, Czechoslovakia, France, Germany, U. S. A., etc., have already used Esperanto for transmitting purposes. For example, the British Broadcasting Company simultaneously broadcast from all stations the speech of H. M. the King of England on the occasion of the opening of the British Empire Exhibition at Wembley. An Esperanto transmission from station WGB in Newark, N. J., was perfectly clearly heard and understood in Japan, across the whole continent of America and the Pacific Ocean. "The American Radio Relay League" has just adopted Esperanto and has officially decided to recommend that language as the International Language of the International Amateur Radio Union.

Under the title "International Radio Association," there was founded on Jan. 1, 1924, an International Society which in the short space of only a few months has been joined by people in 30 different countries, and has national secretaries in Britain, Canada, Czechoslovakia, Denmark, France, Holland, Ireland, Italy, Jugoslavia, Spain and U. S. A. It aims at abolishing, by means of Esperanto, difficulties caused by the language barrier in the path of radio telephony, and at bringing radio users of different countries into touch with one another, even if they have not yet learned Esperanto. It further intends to publish, in Esperanto only, a radio magazine "Internacia Radio Revuo," by means of which, without the necessity of learning various foreign languages, radio-technicians can keep in touch with the work of investigators in other countries, and amateurs can read articles written by an international staff of contributors. This they will be able to do very easily after only a few weeks' study of Esperanto, and they certainly will not regret the small amount of time and effort expended for the purpose of learning the International Language.

INTERNACIA RADIO ASOCIACIO

(International Radio Association)

President

Pierre Corbet, 97 rue Royale, Versailles, France.

Secretary

Harry A. Epton, 17 Chatsworth Road, London, E. 5 England.

Corresponding Secretary

Chekostovakis—A. Pihle, Kremencova, 17, Praha, II.

Denmark—S. P. Lendorff, Dybbøsgade 35, Copenhagen, B.

France—C. Roussier, 4 Place de la République, Levallois-Perret (Seine).

Spain—S. P. Soter, tel.-telegrafista, Centro de Telegrafos, Valencia.

Ireland—S. P. R. A. McCormick, 5 Mount Eden Road, Donnybrook, Dublin.

Italy—G. Saggiari, Corso Vittorio Em. II, N. 6, Padova.

Jugoslavia—Nikola Lisac, Rogatica, Bosnia.

Canada—C. C. McFarquhar (CJ00), 163 University Avenue, Toronto.

Holland—Ir. J. B. G. Isbrücker, v. Beverningstraat 10, 's-Gravenhage.

United States—E. Jay Chaimby, 587 West 181st Street, New York City.

A SUPPORTER OF IDO

Editor, RADIO NEWS:

For many months I have enjoyed your prophecies as to the future of Radio (and

LARGEST RADIO STORES IN AMERICA

CHICAGO SALVAGE STOCK STORES

509 S. Dear St. CHICAGO, U. S. A. Dept. RN-6

We guarantee **RADIO**
our new 68-page
Catalog will save you money

on brand new fully guaranteed, nationally advertised radio apparatus. We buy up manufacturers' and government surplus stocks, rubber and dealer bankrupt stocks, etc. Our endowment buying power permits us to pay spot cash and get rock-bottom prices—even way below manufacturers' costs. That's why our catalog is crisscrossed with thousands of wonderful radio bargains. That's why we GUARANTEE to save you money.



Improved Your Tuning With E-Z-TOON (EASY TUNE) RADIO DIALS

Smooth Easy Movement. No coils, gears, back lash or lost motion. Easily installed. No holes to drill. No complicated adjustments. Take off old dial—slip on E-Z-TOON—tighten new set-screw.

3" Dials\$2.00
4" Dials\$2.25



E-Z-TOON Dials give that fine hair splitting adjustment that Radio fans have so long been hunting for. There are two dials in one, the ratio of the inner dial to the outer dial is 50 to 1.

E-Z-TOON Dials can be used on any instrument where a vernier adjustment is an advantage.

Ask your dealer to show you. If he cannot supply, write us.

Illustrated, subject matter mailed on request.

E-Z-TOON RADIO CO.
3234 W. Washington St., Indianapolis, Ind.

TELEGRAPH AND RADIO INSTRUMENTS



Open contact keys are recommended when it is desired to have a key with communication between contacts without the use of contact spring contacts.


Other types carried in stock
No. 1000 1/2 inch Key, Polished Brass Body.....\$1.00
No. 1001 1/2 inch Key, Polished Brass Body.....\$1.00

Send stamp for Telegraph Manual 25¢
Special Price to Dealers
J. H. MINNELL & CO., 72 Park Place, N. Y.

Ensure your copy reaching you each month. Subscribe to RADIO NEWS for \$2.50 a year. Experimenter Publishing Co., 51 Park Pl., N. Y. C.

Build Your Own Low Loss Receiving
SEND NO MONEY Set and Save 50% **Mail Coupon**
All Building Parts Furnished at Amazingly Low Prices

You know that the expensive part about building a receiving set is the wiring and assembling. The labor charges of high priced experts must all be included in a receiving set you buy all assembled ready to operate. But you save all this when you buy one of the Radio Shack's semi-assembled kits. You get all the parts, the wires, screws, panels drilled, sockets and a chart and directions to wire and assemble it. This is so plain and clear that you can put a set together so easily—so quickly that you will be surprised. Even though you know nothing at all about radio you can assemble one of these sets. The two semi-assembled sets shown here are the very latest Radio designs.

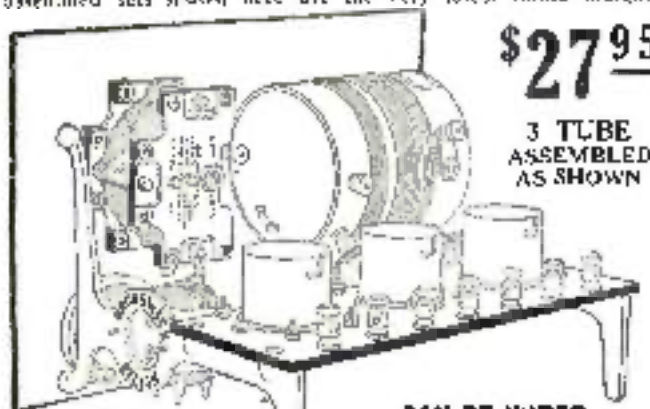

**CAN BE WIRED
EASILY QUICKLY**

THE NEW DE LUXE
AMBASSADOR

This kit enables you to build a set that will compare with any factory built set. The mounting brackets, one of the special new features, are the product of our own moulds and bear our name. The Low Loss Condensers used in this kit has been designed for use with this coil. The panel is Mahogany, engraved in gold, the dials also engraved in gold. All outside metal parts gold plated. The best value in radio today. Send no money—just mail coupon today. Written money back guarantee with every order.

WHAT THE AMBASSADOR KIT CONSISTS OF:

- [illegible]

ACCESSORIES

- [illegible]

**CABINET
FREE.**

Order Building Kit 489
Accounts Debit both to-
gether, and we will send
First Modern Finest
Cabinet FREE.



OPERATING OUTLET

- | | | |
|------------------------|------------------------------------|---------|
| 1 | Tireless Motor "Tenn" 700 cc. | \$19.50 |
| 2 | "Vell" and a Large "Valve" pump | |
| 3 | Batteries and Accessories | 6.00 |
| 4 | Motorcycle "Horn" Subsonic Battery | 11.25 |
| 5 | Motorcycle "Horn" | |
| 6 | Cord "P.C." Switch | 1.75 |
| 7 | Accessories | 4.31 |
| COMPLETE EQUIP | | |
| \$134.00 C.O.D. | | |

FREE

FINE MAHOGANY
LINEN CABINET

If you enjoy dining in, let our
dazzling Quilted beds together,
we will install Fire Kitchen
and French CABINET FREE.

**FREE BIG
RADIO BOOK**

Send for our big Radio Book, filled with standard radio parts at amazingly low prices. Just send name and address. Wanted FREE. Send to: R. A. Nunn, Radio Shack, Dept. RN12, 55 Vesey St., New York.


BRUNSWICK LOW
LOSS CONDENSER

A new low-key endeavor
so that did not. It had to
be a low-key, permanent
presence, positive contact
grounds, senior. If you
want the best on the
market, order. Get out.



Both sets have low-loss parts which mean that practically none of the program it receives is lost before it reaches you. When assembled you will have a set worth \$75 to \$850. Will operate any loud speaker clear, loud and distinctive. You don't need to send a penny in advance to get either of these sets—just put your name and address on the coupon below and mail it. Then when the semi-assembled set or entire arrives merely pay your postman the amount, plus the small carrying charges. If you are not delighted with it—return the set as sent to you and every cent of your money will be refunded. The Radio Shack, 55 Vesey St., Dept. RN12—New York, N. Y.

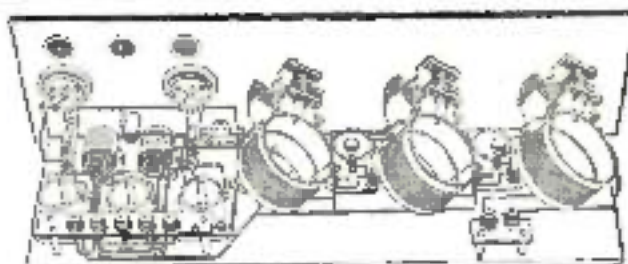5 TUBE KNOCKED DOWN KIT
DE LUXE COAST TO COAST
NEUTRODYNE **\$39⁴⁹**



**Genuine Licensed Hazeltine Parts,
Synchronized and Matched**

Think of getting a genuine *Neurodyne Radio Receiving Set* at this amazing low price! The "De Luxe" is a five tube hooked seven kit, consisting of genuine licensed coils and neonadons to build a genuine *Hazeltine set*. You can spend more money on another set, but you can't get better reception! Gather in broadcast from coast to coast. Loud, clear, powerful—delicate tuning—the superlative realization of months of preparation—new among Neurodyne sets—thousands in use. Send us money, just name and address on the coupon. Written money back guaranteed with each kit.

WHAT 5-TYPE NEUTRODYNE SET CONSISTS OF:

- [illegible]

MAIL THIS COUPON NOW—SEND NO MONEY

[illegible]

- (A) Airflow for Building Ducts \$27.95 ☐
 (B) Airhandler One along Ducts \$11.25 ☐
 (C) Non-saline Building Ducts \$29.49 ☐
 (D) Non-saline Operating Ducts \$41.40 ☐

Name
Address
City State Zip



Signor Marcello, as he appears today.
Signor Marcello is Secretary Chairman
of the Radio Institute of America.

Train for the big Jobs in Radio

There are big radio jobs waiting. Over 6,000 operators have already graduated from our school. But the radio industry is just in its infancy. There are more demands for operators than there are trained men to meet the demand.

Study at Home in Spare Time

Take a complete radio course, starting with magnetism and electricity, going straight through code and the practical operation of commercial radio. Take the same course, with the same careful grading and helpful guidance that resident students are getting. A few months' study will fit you for the U. S. Government operator's license. And you may have three weeks Post-Graduate study free in our New York Residence School.

Good Positions Are Assured
Our school is conducted by the Radio Corporation of America, the world's largest radio organization. This assures you not only first instruction and closest touch with the most recent radio practice, but also preference for prompt placement in a good position. The pay is excellent from the beginning. The opportunity is unlimited—and entirely in your hands.

Advanced Radio Course

Great popular demand by the advanced student and experienced amateur has led to the opening of an **ADVANCED HOME STUDY RADIO COURSE**, specializing in C. W., I. C. W., telephone and radio measurements. Investigate!

Radio Institute of America

(Formerly Marconi Institute)
Established 1909

324 Broadway, New York City

Indicate by a cross (X) the course you are interested in:

Radio Institute of America,
324 Broadway, New York.
Please send me full information about
radio opportunities today, and your
COMPLETE RADIO COURSE ☐
ADVANCED RADIO COURSE ☐

Name.....
Address.....

de-winkle" referred to in Mr. Lewis' article happens to conform to one of the principles of Chinese grammar, and this, together with a few more of the beautiful examples, led the Chinese to accept Esperanto as their International Auxiliary Language and probably accounts for the reason why there are 25,000 Esperantists against 12,000 Hists today. The 13,000 more Esperantists might also be those who became interested in Esperanto before 1907. Considering this, it appears that Esperanto has still been able to remain in the lead of the plagiarism Ho, and I cannot see where the public demands Ho, as was stated by Mr. Callaghan of "La Presse." Why does "La Presse" continue to publish its newspaper in the French language when the people want Ho? Why not give them Ho or else publish a paper in English which is surely the national language of Canada?

I also disagree with Mr. Lewis of the Cansley Radio Corporation, who says, "Esperanto does not lend itself to commercial use." I have secured orders not only from Switzerland, but also from China, Japan and Oceania. As far as getting orders from Switzerland is concerned I feel satisfied that I could have done this by using either French, German or even English. If the Cansley Corporation would avail itself of the opportunity to use Esperanto and the services of the 1,187 representatives of the Universala Esperanto-Asocio, they could distribute their products all over the world and with but little financial embarrassment.

Radio News certainly made a step in the right direction by accepting Esperanto as the International Auxiliary Language. I, from experience, have found that it is practical and satisfactory. If the common people are to be classified with the "intelligence of the majority" and I have the right to vote, my vote is cast for Esperanto.

WALTER A. DONNER,
1439 E. 65th St.,
Cleveland, Ohio.

ACKNOWLEDGMENT FROM ENGLAND

Editor, Radio News

I was pleased to read a most interesting article on the subject of an "Esperanto Radio World Language" by Mr. James D. Sayers in your issue of August, 1924. This article I consider to be one of the finest I have ever read on the subject of Esperanto, and both yourself and Mr. Sayers are to be congratulated upon it.

I am particularly pleased to note that Radio News has decided to accept Esperanto as the international auxiliary language. I presume that this decision was reached after due consideration of the subject from all its standpoints.

There is no doubt whatever that an international language for radio is an absolute necessity, and that, of course, there can only be one such language accepted. That Esperanto is the most suitable is a foregone conclusion, not only on account of its intrinsic superiority over all others, but also because of the strong footing it has obtained throughout the whole world. I have just heard that the A.R.R.L. has decided to support Esperanto, and to recommend its adoption by the International Amateur Radio Union.

This should convince all those who have not yet made up their minds on the subject that Esperanto is "the goods."

HARRY A. EYTON
Hon. Secretary
Internacia Radio-Asocio
London, England

ESPERANTO OR IDO

Editor, Radio News:

The October issue of Radio News has given a fair chance for a plea of Ido or Ho.

Consomello Radio Frequency Tuner Kit

The Perfect Tuner



For Tuned Radio Frequency Circuits

This kit is made up of three Consomello tuner units consisting of condensers, coils and slugs. This unit tunes both for capacity and inductance.

With each kit there is included complete instructions and panel chart for building a tuned radio frequency set consisting of two stages of radio frequency detector tube and one or two stages of audio amplification. Range of 200 to 600 meters.

A tuned radio frequency set built with Consomello tuners is quiet, doesn't re-radiate and is perfectly stable, not being in the slightest sensitive to body capacity.

This kit complete as described, \$15.00

Other Mazda Parts

We are manufacturers of a large line of radio parts, a few of which are listed here. Mazda Double Contact Socket.....\$1.00

Open Circuit.....30
Closed Circuit.....40
Double Circuit.....70
Element Control Single Circuit.....65
Element Control Double Circuit.....75

Plugs

Mazda Perfection.....60
Mazda St.....30

Rheostats

Ideal Graphite Jib.....1.25
Wire Rheostat, 5 ohms.....1.00
Wire Rheostat, 25 ohms.....1.00
Wire Rheostat, 50 ohms.....1.00
Potentiometer, 200 ohms.....3.25
Lead Speaker Radio Horn.....3.50

Condensers

17 Plate.....2.50
21 Plate.....3.00
43 Plate.....4.00

[List and series attachment included with each condenser]

Switches

Mazda Switch, barrel type.....60
Mazda Switch, pull type.....40

Write or direct if your dealer cannot supply you

The Mazda Radio Mfg. Co.

3036 Perkins Ave. Cleveland, Ohio

PANEL ENGRAVING For Manufacturers

A small but probably very important feature of your sets is the engraving on the panels. People buy attractive sets. Are you overlooking this?

Accurate machines and expert engravers. Largest facilities for this class of work.

Write now for quotations on job of 25 or more.

GEO. T. SCHMIDT

2800 Bell Place Ave., Chicago, Ill.

Insure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 55 Park Pl., N.Y.C.

All Esperantists, especially the Tele-experantists, have laid down the principle: "The best International Language is that one which represents the greatest facility for the greatest number of people, and this definition suffices to completely determine the solution of the problem."

Esperanto has half the amount of vocabulary of Latin, and as Mr. Roos makes a statement that "the Esperantists are satisfied with an easily spoken, but very difficult written system," he proves that Esperanto is the language which gives the greatest number of people the greatest facility.

As to the system of writing, few have found difficulty with Esperanto, for even children learn to read and write it within a very short time. There exists only one rule for spelling. Each sound is represented by one letter, and this letter always has the same sound. This makes its spelling obvious and easy, also pleasant. There are no silent letters. For this reason, ear and mouth get excellent training for reading, writing, speaking, singing, dramatic art, dictation and stenography.

This system has enabled a great number of blind people in different countries to master Esperanto and in carry on correspondence in Braille script.

The good lists make the world believe that Esperanto has Polish and Czechoslovak accents, because they describe the Slavonic peoples. Esperanto has not their accents, but entirely its own. The letters c, s, j, p, h, and u, are written with a little accent on the top. If these six letters are not to be written in printer's shape an "i" added to the first five will do, and the last one can go without it. It is true that the above mentioned peoples possess accented letters, but so do the French, Hungarians, Yugoslavs, Spaniards, Germans, Portuguese, Romanians, Lithuanians, Latvians, etc.

Of these letters it is chiefly the "j" which seems to offend the English eye! This is because the English read this letter like "g" in George, ginger, etc., but for this "g" Esperanto uses a "g" with an accent or "gh." The "j" in Esperanto sounds always and without exception like the English "j" in "hallelujah," for you say "hal-luh-lo-yah" and not "hal-luh-lo-jah." The Esperanto "j" sounds, therefore, like "j" in yes, you, year, etc. If this "j" follows an "a" like "aj" it sounds like "i" or "eye," if it follows an "o" it sounds like "oi" or "oin," if it follows an "u" it sounds like "ui" or "uin," if it follows an "e" it sounds like "ei" or "ein"; if it follows an "i" it sounds like "ii" or "i-in." What a moron one must be to consider Esperanto a system of difficult writing? Bulgarian shepherds, Dalmatian peasants, Polish tailors, and children have no trouble with Esperanto spelling. This was proven by the Chamber of Commerce at Los Angeles, Calif. for which its secretary Mr. Parrish, has been touring Europe to invite above mentioned people to California by the medium of Esperanto. His success was great.

Esperanto with its 16 fundamental grammatical rules and no exceptions has been easily mastered even by the "one-language" Englishman and American. It gave him a better comprehension of English, for practically all English words derived from Latin or Roman languages are found in Esperanto.

Mr. Roos claims that not the greatest number of people will decide which of the languages is to be internationalized, and before Esperanto should be that language, English could make the same claim. Every list up to this time has made it a business to blot out Esperanto and to ridicule it as much as possible. But English is not



A Perfect Radio Christmas Gift!

You, of course, desire to give the best you can afford and if any Mozart product comes within your price limit, you will always have the satisfaction of knowing you gave the best. You will enter into a little of what we enjoy from day today, as we continue to receive entirely unsolicited appreciations like the following:

"Baby Grand, received, and, saying that I was surprised is putting it very mild. Due to low B battery voltage, a \$25.00 speaker would not work, so hooked up the Mozart on a one tube Auto-Play, and secured KDKA, WHZ, WGY and several others with volume enough to fill the room. I then hooked it up to a two tube Crosley, resulting more volume with very satisfactory results.

"This is not a fair trial, as none of the B batteries registered over 16 volts, and to be exact, they were as follows: 16-14-15-14. Will say the tone was exceptional, very little distortion, if any, volume wonderful! And, will simply say that none of your claims are exaggerated, but are very modest and conservative.

"You have a product worthy of consideration, and the best all round speaker I have tried and I feel you are due this letter of appreciation, which you may use as the quality of your product deserves it."

(Signed) R. S. TILDEN,

(Atlantic Coast Line Railway Co.), Mayville, N. C.

PRICES

REPRODUCER COMPLETE

(No extra batteries required)

Model A, approx. 12" tall, black and gold crackle finish, gold plated unit	\$2.95
Model B, approx. 12" tall, heavily enamel, all black stain finish, gold plated	\$2.00
Model C, approx. 12" tall, black satin finish, nickel plated unit	\$0.95
Electric-Magneto set, with cord, nickel plated 11 1/2" speaker, any tone or phonograph	\$4.00
As above, with direct	\$5.00
Mozart Special Headset	\$4.00

ORDERS—If your dealer cannot supply, order direct.

TRANSPORTATION—Free shipments, strictly F.O.B. factory. Free on loan or store orders for cash items. C.W.D. or C.O.D. after order accepted and by mail deposit.

GUARANTEE—One year from date of purchase or money back, if not satisfied.

The MOZART-GRAND CO.

Manufacturers of Fine Instruments

Newark, N. J.

U. S. A.

scribers. There are two Protestant newspapers, *Die Regno* and *Kristana Espero*, a Bahai monthly, *La Unuigsa Tufikmanaro*, a single-tax bulletin, *La Veristo*, a police bulletin, *La Potestato*, a literary monthly, *Literaturo*, a monthly magazine for the blind, *Esperanto Ligilo*, and perhaps five others, issued entirely in Esperanto.

There is only one lido magazine in existence, *La Progreso*. And this appears irregularly.

Should the 20 broadcast stations introduce "Ido" and not allow Esperantists throughout the States to broadcast in Esperanto, it will follow, that many people will feel insulted by such an offense against Esperanto.

Mr. Roos says Esperanto cannot express "stolen from" and "stolen by." Please translate this into French "volée de" and "volée par," the same it is in Esperanto, "ŝtelita de" and "ŝtelita de!" But Mr. Roos is less a linguist than a fighter! The good Idiots had always to find fault with Esperanto but not with their own grammar which says: Aprilala, bazila, libelilo, patrola, expreskezo, gloriizeco, cinco, vilajo, humoralajo, linguala, where Esperanto uses: Aprila, bazila, libelo, patro, ekspresimo, glorigo, sciere, vilage, humoralajo, lingva. They were ridiculing the Esperantists for their fundamental, which is not a Bible nor a Talmud nor a Koran, but the Grammar on which it rests until governments come together and give reason for changing one or the other rule! But 217 operations which the Idiots wanted to perform on Esperanto has aroused all Esperantists.

Ido or Ilo, remains a jargon of Esperanto, an intermixture upon invention. Dr. René de Saussure at least says in his paper "Esperantido is a jargon of Esperanto" but the Idists and Ilots say this differently! Now you who don't investigate, learn the language of frauds! But Esperanto should remain pure for the pure!

D. A. KLACIN,
1 West 14th St.,
New York, N. Y.

(Correspondence continued on page 1068)


Calls Heard

(Continued from page 922)

[illegible]

EISEMANN

ELECTRICAL EQUIPMENT

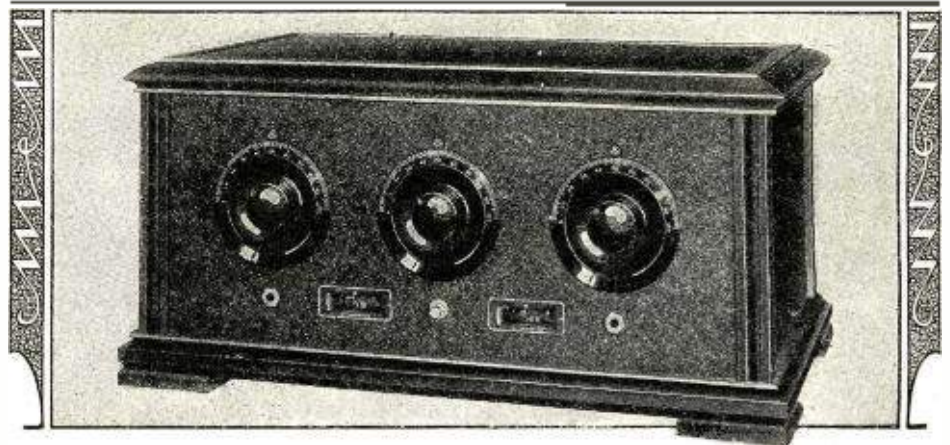

Choose Wisely!

SPECIFICATIONS

Current Transformers (CTs) used in radio frequency applications, detector and pulse circuits of radio frequency applications, electronic timing elements, etc. **SHIBUI** manufactures them in accordance with JIS standards.

Japan: Fine on all. Books presented for either use or for sale operation.

Useful: Enter number of
days

Complete use supplied for "A" and "B" burners.

අධ්‍යයනයකින්, හරිත පරිසරය සංරක්ෂණය කිරීමේ හා විකල්ප සම්පත් සම්ප්‍රදාය පිළිබඳව ප්‍රතිචාරය ලබාදීම.

Amos 7: 10-17, 24-27
28-33

Form: A hexagonal, white, uncoated tablet.
A partial body capcitor

1994, 1995, 1996, 2675, 26

Högskolan i Gäddede
 Högskolan i Gäddede
 Högskolan i Gäddede

Greases are: Single bearing,
low-Jack type roller.

Table 1. Suspended as cathodes
springs with absorbent
cathodes.

Culture: Nuboggar, traditional stone and bigbumb. A highly significant work of art.

Year	Percentage of Population 15 and Over with High School Diploma or Higher
1960	40
1970	55
1980	70
1990	85

Price, Without Tubes
and Batteries. \$125.00

EMANN -
General Office

— 0 . 7 .

IN selecting a broadcast receiver, it is well to distinguish between essential and non-essential considerations.

The circuit is important, insofar as it affects performance, but the mysterious trick names now so much in vogue are not.

Type 6-D combines the only three things that constitute true value—efficient performance, attractive appearance and fair price.

Speech and music are reproduced without distortion. Far distant stations are received with generous volume. The selectivity is extraordinary—even powerful, local broadcasting stations tune sharply. The 6-D is non-oscillating and non-radiating, with unvarying reception efficiency at high and low frequencies.

In appearance, the 6-D is strikingly attractive—a handsome mahogany cabinet, symmetrical panel layout and perfectly proportioned interior construction.

Be sure to examine the Type 6-D Receiver before you make a final selection.

Price, Without Tubes
and Batteries, \$125.00



For Sale by
Reliable Dealers

ELFEMANN · MAGNETO · CORPORATION

General Offices 165 Broadway, New York

DETROIT SAN FRANCISCO CHICAGO

Morrison
Loud Speaker

Was \$10.⁰⁰
Now
\$5



Model C

Exactly the same unit

Every one has heard about Morrison, the loud speaking unit that reproduces so faithfully and can be depended upon to give you an indefinitely. It is a pleasure to offer Morrison to America's fans at just half the former price.

Exactly the same unit that always sold for \$10.

Almost the first unit on the radio market, nothing like yet surpassed Morrison's well-known reproducing qualities. For simple operation and adjustment for long life and satisfactory enjoyment of radio, Morrison is the universal choice.

Own a Morrison and be sure.

The Morrison
TONER
Attached to your Receiving Set

—will give you a brand new thrill. For it performs a brand new radio feat—eliminates from radio everything but the broadcasting. With the Toner you can add another tube for three steps of Audio Frequency. Greater volume and finer tones result.

You'll never be without a Toner after you use it once.

2-COLOR RADIO CATALOG
Describe fully the Toner and the Unit—free on request.
If your dealer cannot fill your order, send request to Catalog.

Morrison Products are a money-back guarantee.

Morrison Laboratories, Inc.
339 E. Jefferson Ave., Detroit, Mich.

Morrison



SURE-FIRE D-X CRYSTAL



THE VALUE OF ALL OTHER
CRYSTALS IS JUDGED BY D. X.

Irresistibly superlative all over. Ideal on
radio circuits. Tantal sealed, guaranteed. En-
dorsed by N. E. Wain and Dr. Wain.

Sole. Mfg. or old dealers or sent postpaid.

Specialty Radio Co., 5 Hudson St.,oklyn, N. Y.
Radio L.S., Montreal, Can. Canadian Distributors.

NEUTRODYNE KIT

In 2 inch Heath component and Wain's transformers to
—and 1 million satisfaction for telephone. Will also be
T COMPLETE SATISFACTION of set all at as
Now 1/2. While order. Terms waived.

W. N. & W. E. CO.

Box 10 Box 10 Chicago

A Radio
Masterpiece

[illegible]

Canada—1hg, 1dd, 1ell, 1al, 2ax, 2fj, 3bu,
3cn, 3gk, 3ha, 3kg, 3kq, 3vh, 3wg, 3wy, 3znp).
See...

Please report on 2-wk intervals with ref to all who ask.

J. H. STRONG, JR. NO STATE ST.
ROSELAND, ILL.

C. W.:
 2pgm, 2cpi, 4mc, 3li, 6bvv, 5sk, 7m, 8dgo,
 3dsk, 8wy, 8z, 9vzu, 9ain, 9aia, 9aoc, 9ast,
 9bii, 9vzv, 9bhh, 9bds, 9bix, 9bci, 9gzy, 9vty,
 9cam, 9vcs, 9vy, 9cru, 9cdm, 9dc, 9dgo, 9dms,
 9dyv, 9eac, 9cln, 9em, 9eky, 9im, 9kz, 9mc,
 9vze, 9il.

W01 QSL all sides

0DHJ—CROWN POINT, INDIANA ONE

C.W.:
1acj, 1hic, 2aac, 2ann, 2azy, 2bpb, 2bwy, 2cbg,
2cpj, 2cuk, 2cpa, 2era, 2rwp, 10a, 2ra, 2agl, 2w
2bpy, 2bgg, 2awl, 2au, 2uct, 1chg, 1cw, 2u
2qaw, 2aww, 2ou, 2us, 2ux, 2ca, 2cg, 2cs, 2io
4lp, 4oa, 4ql, 4ka, 2agl, 2amb, 2amg, 2amh,
2np, 2ca, 2er, 2ic, 2lu, 2ka, 2la, 2nj, 2ok, 2wi
2awt 2lig, 2op. Too many sixes and nines
over 200.

1. *C. W.* — *zank*.
 From — *sek*, *bat*, *tsahul*, (*tsahut*, *tsahut*, *tsahut*;
chl, (*tschlan*, *tschme*), (*tscha*, *tschl*, *tscham*).
tschichan *C. W.* — *tsam*, *tsam*.

2CYX, 1104 CLAY AVE. IRONIX, N. Y.
 11ag1, 11ain, 11agp, 11aon, 11abn, 11ibcu,
 11hmg, 11bnq, 11bic, 11hgc, 11ciz, 11dm, 11ec
 11hlt, 11m, 11p, 11vq, 11rb, 11ves, 11vr,
 11y, 11z, 11ack, 11aih, 11aoj, 11amw, 11bmw,
 11dht, 11hvw, 11hvt, 11cur, 11erc, 11cpe, 11dgr,
 11hg, 11xa, 11d, 11dx, 11eg, 11g, 11gq, 11gr,
 11o, 11p, 11q, 11r, 11s, 11t, 11u, 11v, 11w, 11x,
 11y, 11z, 11aa, 11ab, 11ac, 11ad, 11ae, 11af, 11ag,
 11ah, 11ai, 11aj, 11ak, 11al, 11am, 11an, 11ao, 11ap,
 11aq, 11ar, 11as, 11at, 11au, 11av, 11aw, 11ax, 11ay,
 11az, 11ba, 11bb, 11bc, 11bd, 11be, 11bf, 11bg, 11bh,
 11bi, 11bj, 11bk, 11bl, 11bm, 11bn, 11bo, 11bp, 11bq,
 11br, 11bs, 11bt, 11bu, 11bv, 11bw, 11bx, 11by, 11bz,
 11ca, 11cb, 11cc, 11cd, 11ce, 11cf, 11cg, 11ch, 11ci,
 11cj, 11ck, 11cl, 11cm, 11cn, 11co, 11cp, 11cq, 11cr,
 11cs, 11ct, 11cu, 11cv, 11cw, 11cx, 11cy, 11cz,
 11da, 11db, 11dc, 11dd, 11de, 11df, 11dg, 11dh,
 11di, 11dj, 11dk, 11dl, 11dm, 11dn, 11do, 11dp, 11dq,
 11dr, 11ds, 11dt, 11du, 11dv, 11dw, 11dx, 11dy, 11dz,
 11ea, 11eb, 11ec, 11ed, 11ee, 11ef, 11eg, 11eh, 11ei,
 11ej, 11ek, 11el, 11em, 11en, 11eo, 11ep, 11eq, 11er,
 11es, 11et, 11eu, 11ev, 11ew, 11ex, 11ey, 11ez,
 11fa, 11fb, 11fc, 11fd, 11fe, 11ff, 11fg, 11fh, 11fi,
 11fj, 11fk, 11fl, 11fm, 11fn, 11fo, 11fp, 11fq, 11fr,
 11fs, 11ft, 11fu, 11fv, 11fw, 11fx, 11fy, 11fz,
 11ga, 11gb, 11gc, 11gd, 11ge, 11gf, 11gg, 11gh, 11gi,
 11gj, 11gk, 11gl, 11gm, 11gn, 11go, 11gp, 11gq, 11gr,
 11gs, 11gt, 11gu, 11gv, 11gw, 11gx, 11gy, 11gz,
 11ha, 11hb, 11hc, 11hd, 11he, 11hf, 11hg, 11hh, 11hi,
 11hj, 11hk, 11hl, 11hm, 11hn, 11ho, 11hp, 11hq, 11hr,
 11hs, 11ht, 11hu, 11hv, 11hw, 11hx, 11hy, 11hz,
 11ia, 11ib, 11ic, 11id, 11ie, 11if, 11ig, 11ih, 11ii,
 11ij, 11ik, 11il, 11im, 11in, 11io, 11ip, 11iq, 11ir,
 11is, 11it, 11iu, 11iv, 11iw, 11ix, 11iy, 11iz,
 11ja, 11jb, 11jc, 11jd, 11je, 11jf, 11jg, 11jh, 11ji,
 11jj, 11jk, 11jl, 11jm, 11jn, 11jo, 11jp, 11jq, 11jr,
 11js, 11jt, 11ju, 11jv, 11jw, 11jx, 11jy, 11jz,
 11ka, 11kb, 11kc, 11kd, 11ke, 11kf, 11kg, 11kh, 11ki,
 11kj, 11kk, 11kl, 11km, 11kn, 11ko, 11kp, 11kq, 11kr,
 11ks, 11kt, 11ku, 11kv, 11kw, 11kx, 11ky, 11kz,
 11la, 11lb, 11lc, 11ld, 11le, 11lf, 11lg, 11lh, 11li,
 11lj, 11lk, 11ll, 11lm, 11ln, 11lo, 11lp, 11lq, 11lr,
 11ls, 11lt, 11lu, 11lv, 11lw, 11lx, 11ly, 11lz,
 11ma, 11mb, 11mc, 11md, 11me, 11mf, 11mg, 11mh, 11mi,
 11mj, 11mk, 11ml, 11mm, 11mn, 11mo, 11mp, 11mq, 11mr,
 11ms, 11mt, 11mu, 11mv, 11mw, 11mx, 11my, 11mz,
 11na, 11nb, 11nc, 11nd, 11ne, 11nf, 11ng, 11nh, 11ni,
 11nj, 11nk, 11nl, 11nm, 11nn, 11no, 11np, 11nq, 11nr,
 11ns, 11nt, 11nu, 11nv, 11nw, 11nx, 11ny, 11nz,
 11oa, 11ob, 11oc, 11od, 11oe, 11of, 11og, 11oh, 11oi,
 11oj, 11ok, 11ol, 11om, 11on, 11oo, 11op, 11oq, 11or,
 11os, 11ot, 11ou, 11ov, 11ow, 11ox, 11oy, 11oz,
 11pa, 11pb, 11pc, 11pd, 11pe, 11pf, 11pg, 11ph, 11pi,
 11pj, 11pk, 11pl, 11pm, 11pn, 11po, 11pp, 11pq, 11pr,
 11ps, 11pt, 11pu, 11pv, 11pw, 11px, 11py, 11pz,
 11qa, 11qb, 11qc, 11qd, 11qe, 11qf, 11qg, 11qh, 11qi,
 11qj, 11qk, 11ql, 11qm, 11qn, 11qo, 11qp, 11qq, 11qr,
 11qs, 11qt, 11qu, 11qv, 11qw, 11qx, 11qy, 11qz,
 11ra, 11rb, 11rc, 11rd, 11re, 11rf, 11rg, 11rh, 11ri,
 11rj, 11rk, 11rl, 11rm, 11rn, 11ro, 11rp, 11rq, 11rr,
 11rs, 11rt, 11ru, 11rv, 11rw, 11rx, 11ry, 11rz,
 11sa, 11sb, 11sc, 11sd, 11se, 11sf, 11sg, 11sh, 11si,
 11sj, 11sk, 11sl, 11sm, 11sn, 11so, 11sp, 11sq, 11sr,
 11ss, 11st, 11su, 11sv, 11sw, 11sx, 11sy, 11sz,
 11ta, 11tb, 11tc, 11td, 11te, 11tf, 11tg, 11th, 11ti,
 11tj, 11tk, 11tl, 11tm, 11tn, 11to, 11tp, 11tq, 11tr,
 11ts, 11tt, 11tu, 11tv, 11tw, 11tx, 11ty, 11tz,
 11ua, 11ub, 11uc, 11ud, 11ue, 11uf, 11ug, 11uh, 11ui,
 11uj, 11uk, 11ul, 11um, 11un, 11uo, 11up, 11uq, 11ur,
 11us, 11ut, 11uu, 11uv, 11uw, 11ux, 11uy, 11uz,
 11va, 11vb, 11vc, 11vd, 11ve, 11vf, 11vg, 11vh, 11vi,
 11vj, 11vk, 11vl, 11vm, 11vn, 11vo, 11vp, 11vq, 11vr,
 11vs, 11vt, 11vu, 11vv, 11vw, 11vx, 11vy, 11vz,
 11wa, 11wb, 11wc, 11wd, 11we, 11wf, 11wg, 11wh, 11wi,
 11wj, 11wk, 11wl, 11wm, 11wn, 11wo, 11wp, 11wq, 11wr,
 11ws, 11wt, 11wu, 11wv, 11ww, 11wx, 11wy, 11wz,
 11xa, 11xb, 11xc, 11xd, 11xe, 11xf, 11xg, 11xh, 11xi,
 11xj, 11xk, 11xl, 11xm, 11xn, 11xo, 11xp, 11xq, 11xr,
 11xs, 11xt, 11xu, 11xv, 11xw, 11xx, 11xy, 11xz,
 11ya, 11yb, 11yc, 11yd, 11ye, 11yf, 11yg, 11yh, 11yi,
 11yj, 11yk, 11yl, 11ym, 11yn, 11yo, 11yp, 11yq, 11yr,
 11ys, 11yt, 11yu, 11yv, 11yw, 11yx, 11yy, 11yz,
 11za, 11zb, 11zc, 11zd, 11ze, 11zf, 11zg, 11zh, 11zi,
 11zj, 11zk, 11zl, 11zm, 11zn, 11zo, 11zp, 11zq, 11zr,
 11zs, 11zt, 11zu, 11zv, 11zw, 11zx, 11zy, 11zz,
 11aaa, 11aab,

A SUPPORTER OF ESPERANTO
Editor, RADIO NEWS:

As a regular reader of *RADIO NEWS*, as well as one who has for many years been interested in the question of an international language, I wish to congratulate you, and also to congratulate the friends of the international language movement, on the stand you have taken in favor of *Esperanto*. Your decision shows that you must have made more than a superficial investigation of the subject, as from the extravagant claims made by some of the would-be competitors of *Esperanto*, one might be led into believing that they were in use by millions of people, as their clientele, though very small, seems to be composed mostly of press agents, with their proverbial disregard for the small details of truth in their statements.

You will doubtless be bombarded with protests from the adherents of one of these in particular, called Ido or Ido, the followers of which seem to be the most voracious in their claims, but cannot produce any literature worth mentioning, as against a list of hundreds of books, which have been published in Esperanto, among which are many of the works of Shakespeare, Molière, Pushkin, Defoe, and other well-known and less well-known authors, including poems from many languages.

Your investigation doubtless revealed the fact that Ilo or Ido is an offspring of Esperanto, but you may not have been informed that, as is well known to those conversant with the facts of its origin, the *Wan* minister occupies a prominent place in its eschatology.

I was especially pleased with the article you printed from N. W. Frost of Cambridge, Mass. Mr. Frost is well known here, and you may be sure that any statements

ACCURATUNE
MICROMETER CONTROLS



for close tuning

Improved!
NO BACK LASH

No ordinary standards of tuning efficiency can be applied to the new improved Accuratune Micrometer Control. Special construction of this new model offers these superior advantages:

1. Eliminates all back lash.—Gears and gear train operation designed upon scientific engineering principles, producing quiet operation, eliminating all lost motion and back lash. The greatest advance in tuning devices. Increases the tuning efficiency over that of any known tuning device.
2. Fits all standard Condenser Shafts.—Accuratune Micrometer Controls fit all standard shafts and always operate parallel with panel.
3. Flush Panel Mounting.—Take all standard condenser shaft lengths and fit flush with panel. Eliminates the necessity of cutting off shafts before mounting dial.
4. Control 30:1 Ratio.—Permits infinitely close tuning with perfect ease. A practical compromise too low nor too high.

Accuratune Micrometer Controls tuning station after station you never tuned in before. Indispensable on all Super-Heterodynes. Price \$3.50. At your dealer's, otherwise send purchase price and you will be supplied postpaid.

ACCURATUNE
I.F.
MICROMETER CONTROLS

THE MYDAR RADIO CO.
9-F Campbell St., Newark, N. J.
Radio Ltd., Montreal—Cochran Harmonizers

[illegible]

he may make can be backed up by incontrovertible proof.

ERNEST F. DOW,
993 Watertown Street,
West Newton, Mass.

ESPERANTO INTERNATIONAL COMMUNICATION TONGUE

Esperanto has been adopted as the auxiliary international language in telegraphic intercourse by the League of Nations according to a cablegram from International Esperanto headquarters at Geneva. This is interpreted as applying to radio and cable communication, as well as purely telegraphic, by those familiar with the plans for its use in international communication. Recently the American Radio Relay League recommended this universal language as the most suitable for world wide communications by radio.

REGARDING MR. ROOS' ARTICLE

Editor, Radio News.

It seems that the Idiots care more about throwing mud into the eyes of people regarding Esperanto than in telling them something constructive about Idology. If you had read the Report of the General Secretariat of the League of Nations, as adopted by the Third Assembly 1922, you certainly would not permit such remarks about it. The League of Nations is too serious an institution to be made fun of.

Mr. Roos admits that Esperanto is easily spoken, but contradicts himself by adding "but a very difficultly written system." Isn't the easily spoken International Language just what the radio stations are demanding? The radio people cannot be blind to the fact that Esperanto is entirely practical for International Congresses and is the medium for millions of letters annually.

If Idology has claim for popularity, then what of Esperanto, Idiom-Neutral, Panroman, etc.? If the world suddenly becomes aware of a half dozen so called international languages, it necessarily will have to drop the subject because we will be in the same position as to which national language to use, French, English, German or Spanish. The world must use Esperanto for the present and the governments will in time see to it that it evolves along sensible lines. Otherwise, the great amount of work done in the past, along this line because of Esperanto, will be lost and a great apathy towards an international language will be the result, to the detriment of the international application of Radio.

On September 11, I gave a talk on Esperanto, in Esperanto, from station WHK at Cleveland, and received so many responses that we immediately organized a large class. This course will continue for 20 weeks. I am also arranging with one of the leading papers in Cleveland for placing radio Esperanto lessons in the paper and working out these lessons by radio. Will tell more about this after the date is set.

All this is going on in Cleveland in spite of the feeble and bombastic efforts of the one Idiot in Cleveland.

Our society is now making preparations to invade the National Esperanto Congress to Cleveland.

Have you seen the May number of the "International Language" published in London? Following are the broadcasts in and about Esperanto. These items will convince that Esperanto is already the language for radio.

Broadcasts in Europe in 1922—1
Broadcasts in Europe in 1923—9
Broadcasts in Europe in 1924—14
Broadcasts in America in 1922—3



*In fairness
to your receiving set*
—test this amazing
new loud speaker

The Dictogrand will reveal new and undreamed of possibilities in your radio reception. Dictograph Scientists of Sound have solved an important loud speaker problem in the Dictogrand—that of magnifying sound without changing the pitch or register.

Any horn-shaped sound carrier has a tendency to act as a megaphone—deepening tone and lowering register. You know this if you have talked through a megaphone. Thus, the identity of the artist's voice or instrument is changed. The violin sounds like the cello, the soprano like the contralto.

The Dictogrand embodies a remarkable articulating device and acoustically perfect horn which counterbalances this tendency. Every note and syllable—spoken, played or sung—is held in the original register.

Every instrument is clearly defined. Nothing is lost or garbled. Hence, greater sound range and faithful reproduction of the original rendition.

You're welcome to a five day trial. Dictogrand dealers will gladly place a Dictogrand in your home on five days' free trial—with no obligation to you whatever. Write for this liberal offer, giving radio dealer's name. In our reply, we'll include a supply of our famous and popular "Applause Cards," if you say so.

Dictogrand

TWO MODELS, UPRIGHT AND PORTABLE

DICTOGRAPH PRODUCTS CORP.
NEW YORK, N. Y.
Pacific Coast Agent, Leroy C. Bishop
3241 Pacific Mutual Bldg., Los Angeles, Calif.

Violin or Cello?

Does your loud speaker differentiate?

Can you tell the difference between a violin or cello, a cornet and a trombone, a bass and a baritone on your loud speaker? Important refinements in the Dictogrand have solved this tendency to "lower the register" so often apparent in radio rendition.



The Portable

Beautifully hand etched, 12 inch hard rubber bell mounted on non-vibrating metal base arm. Ebony finish. Attractive design. Small and compact.

Price \$24.50



The Upright

Beautifully hand-etched, 12 inch ebony finished hard rubber horn and bell securely mounted on metal base. Easily hooked in on any set without extra batteries.

Price \$25.00

DICTOGRAPH PRODUCTS CORPORATION,
220 W. 42nd St., New York City,
Dept. D-12.

Please tell me how to secure a Dictogrand on five days' free trial. Also send "Applause Cards."

Name


Address

Radio Dealer's Name



BELL Knobs and Dials

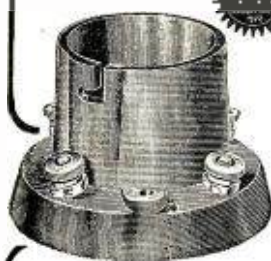are hand-
made molded
B a b e -
lites; made
for the par-
ticular radio
fun.
2" to 4" sizes
35c to 1.00 ea.
(also special
vernier
knobs)



Bell Round Socket

Sold brown
B a b e -
lites. Positive
contact.
Nickel plated
posts

Bell Round Socket.....45c ea.



Bell Square Socket

For panel or
base mount-
ing. Brown
B a b e -
lites. Double-
wipe contact. Nickel plated
posts.

Bell Square Socket.....60c ea.



UV-199 Socket

Black Bak-
elite Heavy
Double
spring con-
tact. Nickel
plated posts.

Bell UV-199 Socket.....45c ea.

Bell Sockets and Dials are packed in in-
dividual blue boxes. Look for the trade-
mark.

DEALERS: Write for circular and
attractive discounts.

Bell Manufacturing Co.

11 Elkins St. Boston 27, Mass.



KORACH TUNED LOOP

Tuning Feature
Directional
Can Be Folded
Collapsible

Patented this last year as low construction. Other makers
will charge you for it and it will be hard to get. Korach
patented feature gives you reliability and distance without
of fatigue with loop antenna. We want you to see for your-
self. No more at home for us.

GUARANTEE TRIAL OFFER

We will send this loop on the day's trial. You use
it for 10 days. If you like it, we will deposit with your
order. If you do not like it, we will return it to you.
No charge. Try it for 10 days. If not perfectly satisfied
we will return it to you. No charge. No more at home for us.
QUESTIONS ASKED. You take no risk. Our offer is
unlimited. No more at home for us.

KORACH TUNED LOOP MFG. CO.

309 So. La Salle St., Dept. 7, Chicago, Ill.

Full Particulars on Request

and Dealers who are asked: We will ship sample on
water for inspection and trial. Write today

Broadcasts in America in 1923—2

Broadcasts in America in 1924—16

If the Esperanto broadcasts have made
such a jump in 1924 up to May 7, the total
can well be imagined up-to-date. Get the
100 broadcast by comparison and you will
satisfy yourself as to which to choose.

The Idols stress the term "more scientific."
Where the 100 principle seems more sci-
entific in places, it is too cumbersome for fluent
speech. They make fun of the Esperanto
's. how about their numerous Q's? I
was a follower of 100 for a few years, but
now I have a greater appreciation of the
cathartics and internationally practical
Esperanto.

Have you seen the Esperanto publication
"Internacia Radio Revuo"? Are you aware
of the magnitude of "La Internacia Radio
Asocio" with headquarters in London, Paris
and New York City? These papers and
associations are facts, not dreams of "what
we will do."

Out of our membership of 68 there are
59 radio fans. We link up Esperanto with
radio.

STANLEY KOKENSKI,

Sec. The Cleveland Esperanto Society
3406 Meyer Ave., Cleveland, Ohio.

ESPERANTO AND 100

Editor, RADIO NEWS:

I do not know whether you intend giving
further space for controversy as to the
relation of Esperanto and 100. If so, may
I check the following item in Mr. Roos'
article in your October issue?

Mr. Roos says: "Let us all forget num-
bers and lump the entire opposing camps
on the best available statistics at 25,000
Esperantists and 12,000 100's"; he gives nei-
ther source nor data on which to justify
the final figure. My estimate of 25 to 1
on page 210 of your August number gave
the basis for the estimate. The importance
of the ratio to a radio fan seeking prac-
tical use is apparent. The test of actual
practical use has been made in Europe and
25 to 1 represents the resulting judgment
between the two projects after 15 years
of competition. Why, then, should we not
class 100 with the other minor projects
named? Possibly in North America, thanks
to the lack of competition in practical use,
250 to 120 may represent the opposing
forces, but why bother with an auxiliary
language for North America alone?

Passing from the realm of estimates to
that of fact, Mr. Roos declares, "Do not
let Esperantists tell you they have 4,300
words, they have about 2,800." I have had
for some two years the "Vortaro de la
Oficialaj Radikoj de Esperanto" by Th.
Carl, President of the Esperanto Lingvo
Komitato. It contains just 4,206 word roots,
all of which had been before accepted and
announced as official and are in regular use.

Esperanto may be "etymological hooch,"
but it does the work efficiently. It is "per-
haps possible" that some Esperantist may
be redundant barely possible that he may
escape that logical error. The Esperantist
is not likely to hesitate in translating
"shelilat de la listoj"; yet perhaps it is
only fair to confess that it is possible for
an opponent to make unclear phrases in
Esperanto if he seeks to. The use of the
abbreviations eliminates almost every excuse for
using "shelilat." The correct translation of
"The words were stolen by the —" would
be "La vortojn ŝtelis la —." As to
the attack upon Mr. P. Corret, President
of the Trans-Atlantic Tests Committee
(France), Vice-President of the French So-
ciety for Study of Wireless, President of
the Internacia Radio Asocio, and Vice-Pres-
ident of the International Union of Radio
Amateurs, that is not within my province.

Did Esperanto fail at the League of Na-
tions? The wise man will get his facts from



Spintite WRENCHES

Why not have a gift
that you want and really
need in your radio work? Ask
"the folks" in include 30c
kits in your Christmas list
this year. Or, if you have a
friend who is a fan, surprise
him with a set of these handy
little wrenches that make the
hardest hook-ups easy.

Radio men are stereotyped as
Chicago suits because they are
just like drop-forged in one piece
for long over and under action
So separate parts to get lost. The
wrench set on "Speed-Up" tools
for radio men also make them
holder gets into the work
24 jamming all the tools


Set of 3
Spintite

in most ap-
plicable
work (also
for a de-
stroy).


\$1.00

If your dealer won't
supply Spintite, order
from a direct. Don't
take a risk.

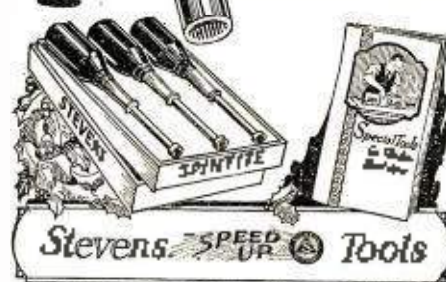STEVENS & COMPANY
Toolsmiths since 1829
375 Broadway, New York



Stevens SPEED UP Tools

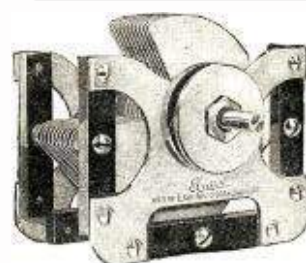

The new, remarkable ELRACO Low Loss Condenser

leads the field. Grounded rotor. Single
hole mounting. Brass plates. Practically
no loss. Correct in design and construction.

.00035 M.F. \$1.50 .0005 M.F. \$4.00
.00075 M.F. 4.75 .001 M.F. 6.50

Ask your dealer, or order direct
Satisfaction Guaranteed

ELGIN RADIO CORPORATION

Radio Division, The Elgin Tool Works, Inc.
65 N. STATE ST. ELGIN, ILL.

Geneva direct or from Radio News and the A. R. L. findings. The Poincaré government did succeed in blocking Esperanto in the Committee on Intellectual Co-operation, but the assembly promptly rejected the committee's report on the matter and sent the question back to the committee for further consideration. The Herriot government is now opposing Esperanto. Why torture Dr. Nitobe's word "objective" into "non-partisan"? The suppressed section in my opinion was not "objective"—i. e., statement of fact—but was "subjective"—i. e., arguement of fact—use of Esperanto at Geneva and in teaching everywhere—and therefore the section was outside the competence of the League Secretariat which compiled the report, "Esperanto as an Auxiliary International Language" (obtainable from any League agency, e. g., World Peace Foundation, 40 Mt. Vernon St., Boston 9, Mass., or through any Esperantist at 20 cents a copy, 37 pages).

Mr. Roos thinks that the "real test is the translation of technical and scientific works." Esperantists generally feel that Esperanto must not be made more difficult for the ordinary human being—by large dictionaries and excessive precision—in order to make it easier for the few scientists and technicians.

Yours for accuracy
NORMAN W. BROOK,
12 Ash St. Place,
Cambridge 38, Mass.

Copies to International Institute of Agriculture, Rome and its use of Esperanto in correspondence
United States Department of Agriculture
Bureau of Plant Industry
Washington

December 1, 1923.

Office of
Associate Chief of
Bureau
Dr. Asher Hobson,
American Representative
International Institute of Agriculture
Rome, Italy

Dear Dr. Hobson:—

I have recently been discussing with Dr. Cottrell of the Fixed Nitrogen Laboratory of this Department the progress of the International Auxiliary Language Association, and to indicate briefly the activities that are under way by those interested in the possibility of such a development I am enclosing a Report of Progress made by Dr. Cottrell to the Committee on International Language of the International Research Council in August and a report by a special Committee that is undertaking to provide more definite support for the investigation of the feasibility of using an auxiliary language.

I understand from Dr. Cottrell that for several years correspondence addressed to the Bureau of Standards in Esperanto is answered in Esperanto, and that certain other institutions have extended somewhat the same kind of support to the auxiliary language movement, and that the International Labor Office permits the release of certain of its information through a supplement to the Esperanto Journal. This supplement, I believe, is prepared for publication in Esperanto by Mr. Bruck, who is on the editorial staff of the International Institute.

I am now particularly campaigning for the use of Esperanto rather than any of the other proposed auxiliary languages, although I believe that at the present time Esperanto has been more widely used and has perhaps a larger number of supporters than any of the other proposed auxiliary languages. This has led Dr. Cottrell to make the suggestion which appeals to me as worthy of trial—in undertaking to answer correspondence on agricultural matters in Esperanto. If it is practicable and if the correspondents

It's Easy to Cut and Drill RADION PANELS

NO special tools are required. Common house tools will turn out a clean hole and a straight edge, with no chipping.

There are 18 stock sizes to select from—literally a size for every set. This means less cutting and little waste, sometimes a definite saving in real money.

Exhaustive research has shown that RADION excels other insulations in the important electrical and mechanical characteristics. It's worth while to ask for RADION Panels and Parts. Be sure to get only the genuine.

Do not accept inferior so-called hard rubber panels that are *not* RADION and that do *not* have the insulating values of RADION.

AMERICAN HARD RUBBER COMPANY
11 Mercer Street, New York

18 Stock Sizes

Mahogany and Black

3/16 x 6 x 7	3/16 x 7 x 21
3/16 x 6 x 10½	3/16 x 7 x 24
3/16 x 6 x 14	3/16 x 7 x 26
3/16 x 6 x 21	3/16 x 7 x 30
3/16 x 7 x 9	3/16 x 7 x 48
3/16 x 7 x 10	3/16 x 8 x 26
3/16 x 7 x 12	¼ x 8 x 40
3/16 x 7 x 14	¼ x 10 x 36
3/16 x 7 x 18	¼ x 20 x 24



Look for this stamp on every genuine RADION panel. Beware of substitutes and imitations!

RADION

The Supreme Insulation

PANELS



Dials, Knobs, Sockets, Insulators

**AMSCO Low Loss Condenser**

Designed especially for perfection in set building. A laboratory instrument.

AMSCO "Dublwindr"

Combination Rheostat and Potentiometer. Selected by E. M. Cockaday for use in his Improved Four Circuit Tuner, as described in the October Popular Radio.

AMSCO Double Rheostat

Designed to take the place of two Rheostats. Saves panel space and wiring.

Ask your dealer or write for catalog, literature and literature.

AMSCO PRODUCTS, Inc.
Brooklyn and Lafayette New York

BARGAIN CATALOG

FREE! 100 Pages!

Just send your name

Get it now!
Crammed full of information & offers of all kinds of wireless sets, parts and accessories. Includes a special "Knock-Out" Set, guaranteed and approved by Radio Broadcast Engineers, published by Doubleday, Page & Co., anything you may need to build or repair.

RADIO

This book tells how to build a set, how to tune it, how to make it work, how to make it sound, how to make it look, how to make it last, how to make it cheap, how to make it good, how to make it great, how to make it perfect.

Very interesting!

Write to: **Therby Mail Order House**
Dept. 4112 300 Liberty St., N.Y.C.

desire answers in that language, and possibly also to permit the Esperanto Journal to carry a supplement in that language summarizing points of interest that develop in connection with the work of the International Institute of Agriculture.

You will note that I am not suggesting the official adoption, or official recognition even of an auxiliary language but merely the experimentation with it in the hope of determining whether it has any useful place in the handling of correspondence or distribution of information on the part of the Institute.

Any comments or suggestions regarding this general subject that you would care to make I will be very glad to receive.

Very truly yours,
(signed) K. F. KELLERMAN,
Associate Chief of Bureau

(Copy)

Rome 16 Jan. 16, 1924

Institut International
D'Agriculture

Le Délégué

Des Etats-Unis-D'Amerique

Dr. K. F. Kellerman,

Associate Chief, Bureau of Plant Industry,

U. S. Department of Agriculture,

Washington, D. C.

Dear Mr. Kellerman:—

Since receiving your letter of December 1, I have made some inquiries concerning "Auxiliary Languages" and the extent of their use. I was surprised at the amount of recognition which Esperanto seems to have won. No one appreciates more than those engaged in foreign fields the present handicaps in international communication because of language difficulties. Hence, you will readily understand that I am a hearty supporter of any movement which gives promise to lessen these difficulties.

Upon inquiry, I find that our Mr. Bruck made definite proposals to the Administration here in the Institute that Esperanto be utilized in a limited way in the distribution of information pertaining to the Institute. I am enclosing a copy of the memorandum containing Mr. Bruck's proposals. As a result of these proposals Mr. Bruck was warned by the Delegate of France, who is also the Vice-President of the Institute, that any activity on his (Bruck's) part in promoting his proposal endangered his position with the Institute.

The language question in the Institute is now encumbered with unhealthy animosities. The nations preferring the English language have just terminated a winning fight to place that language on a par with French at the Institute. Although that question is settled, feeling still runs high on the part of the delegates.

Because of the known attitude of the Administration and because of the delicacy of the language question here, I do not believe it an opportune time to bring the matter up for discussion. You may rest assured, however, that I am personally in sympathy with the auxiliary language movement and shall keep your proposals in mind with a view to presenting them to the Permanent Committee should a more favorable opportunity present itself.

Yours truly,
(signed) ASHER HANSON,

Delegate of the United States of America.

P. S. I am sending a copy of this letter to others who have written me on the same question.

This will probably explain the attitude of CRAC and La Presse and it illustrates what happened in the Committee on Intellectual Co-operation.

"That
Musical
Pal of
Mine"



Come On Boys— Let's Hear You Play!

There's nothing like good music for happiness; and there's nothing like a Hohner for good music. Millions of happy boys and girls are now playing Hohner Harmonicas for entertainment, popularity and education.

Anyone can quickly learn to play a Hohner with the aid of the Free Instruction Book. Get a Hohner Harmonica today—50c up—and ask for the free book. If your dealer is out of copies, write M. Hohner, Inc., Dept. 198, New York City.

If you want a musical treat ask to hear Victor Record 19421, by Borrah Minniskie,

HOHNER HARMONICAS

TRESCOLA



Coast to Coast Radio

Received the Chicago Evening American, general price of \$150.00, 1,300 miles range.

Price \$22.50

Expendative, Licensed under American, G. A. Pat. No. 1,333,143

OUR AMAZING OFFER

For a short time only, send us your old crystal set and we will send you one of our \$25.00 beautiful sets for the small sum of \$12.50; add P. P. on 10 pounds. Circulars, 2c.

Tubes, Batteries, Phones, etc. extra.

TRESCOLA SALES Inc. Davenport, Iowa
P. O. Box 148

HUDSON-ROSS

Wholesale radio only.

One of the first and still in the lead.
Write for discounts.

123 W. Madison St. Chicago

A New Oscillator for Very Short Waves

(Continued from page 923)

condenser of .002 mfd. capacity, and must be able to withstand full plate voltage. A variable condenser that will stand full plate voltage is available that may replace the fixed condenser and will serve to make the adjustment much easier. By using a variable condenser having low losses, the maximum capacity need not be over .0005 mfd.

Fig. 2 gives a good idea of the arrangement used to get the shortest waves. The base of the tube has been removed and the chokes arranged to make the leads to the tubes as short as possible. A portion of the oscillating circuit is seen connected between the plate and grid terminals. This figure also shows the wavemeter which was calibrated from 4 to 25 meters by the method to be described later. The wavemeter consists of one turn of wire $4\frac{1}{2}$ inches square, a low loss condenser and a thermo-ammeter.

Fig. 3 shows a similar arrangement of the tube, but here the tube is used with its original base and socket. It was possible with this arrangement to get down to as low as 5 meters or to a small variable condenser is used to $4\frac{1}{2}$ meters. The following table shows roughly what should be expected using a 50-watt tube.

Western Electric 50-watt tube
Base on and in socket and stopping condenser of .002 mfd.

Length of inductance	Wave-length
7 inches	$3\frac{1}{4}$ meters
16 inches	$4\frac{1}{2}$ meters
$2\frac{1}{2}$ turn 5 in. in diam.	12 meters

Base removed and stopping condenser of .002 mfd.

Length of inductance	Wave-length
5 inches	4.4 meters
3 inches	3.9 meters
$1\frac{1}{2}$ inches	3.25 meters

With base removed and variable condenser variable down to .0001 mfd. 6-inch length of wire worked down to 3.1 meters.

Considerable care is necessary in the selection of tubes for this class of work and the following suggestions are given.

1. The tube must be a good oscillator at ordinary wave-lengths for it is obvious that if the tube is made to oscillate with difficulty at 200 meters it will seldom oscillate at 5 meters.

2. The wires leading to the plate, grid and filament should be separated as far as possible.

3. The connecting coil inside the tube connecting the seal and the plate or grid should be either small or absent, for either it will become red hot at short wave-lengths indicating a great loss in efficiency.

The radiating system ABCDE shown in Fig. 1 consisted of several feet of copper tubing supported on pyrex. The condensers C₁ and C₂ are made up of two circular copper plates 5 inches in diameter and they are so arranged that the distance between them may be adjusted at will and thus tune the circuit. The total distance (expressed in meters) from A to E via BCD should be from 50 per cent. to 80 per cent. of the wave-length used.

The wave-length for a definite adjustment was determined by the usual method using two parallel wires. Two parallel wires $\frac{1}{8}$ foot long and separated about four inches were stretched between insulators and coupled conveniently to the oscillator. One end was closed through a hot wire galvanometer or other indication device (a $4\frac{1}{2}$ -volt flashlight bulb will do) and a connecting bar slid along toward the open ends of the wire until an indication was obtained. (See Fig. 3.) This indication should be sharp if everything is working properly and should



THE EXECUTIVE

Smith, executive in an office, is called upon to make decisions which require applied Chemistry. If he does not know Chemistry, he may not collect the right raw materials or high priced compounds. A knowledge of Chemistry, well applied through our course, would save him many thousands of dollars.



THE BUSINESS MAN

Under testing and inspection, the man in the business world is called upon to make decisions which require applied Chemistry. If he does not know Chemistry, he may not collect the right raw materials or high priced compounds. A knowledge of Chemistry, well applied through our course, would save him many thousands of dollars.



THE PROFESSIONAL MAN

Every professional man needs a reliable knowledge of Chemistry. Whether he is practicing law, engineering, architecture, or any other calling, the man who knows all the latest progress in chemistry is better equipped to handle his business. The knowledge of Chemistry is a great asset in the modern world.



THE DAILY WORKER

Workers in our highly civilized world are called upon to make decisions which require applied Chemistry. If they do not know Chemistry, they may not collect the right raw materials or high priced compounds. A knowledge of Chemistry, well applied through our course, would save them many thousands of dollars.

CHEMISTRY

Insures Your Climb to Success

No matter what your vocation you can increase your Proficiency and earn bigger pay by a thorough training in Chemistry

TO be successful today is to know Chemistry! Every line of business, every branch of industry depends upon Chemistry in some form. You may not realize it, but your own proficiency in whatever work you are doing would be increased by a knowledge of Chemistry. In many lines such knowledge is absolutely essential. In others it is a guarantee of promotion and more money.

It is no longer necessary to enter college in order to learn this fascinating science. Our Home Study Course trains you just as thoroughly, and with the same assurance of success as those who took the longer way. And the methods are so simple that we can teach you no matter how little previous education you may have had. Many of our graduates now hold responsible positions or have successfully increased their incomes from part-time occupations as a result of taking our course. Hundreds of letters from students testifying to the benefits they have derived from our training are here for your inspection.

Remember that you do not need to study Chemistry with the idea of actually practicing as a chemist, although a great many of our students are taking our course with this object in view. If you want to know more about what Chemistry will do for you, if you want to know what our home study course offers, sign and mail the coupon today for FREE BOOK "Opportunities for Chemists."

DR. T. O'CONOR SLOANE Will Teach You Practical Chemistry in Your Own Home

The Chemical Institute of New York, of which Dr. T. O'Conor Sloane is Educational Director, was founded to fill the need of ambitious, high-minded men who realize and recognize the splendid future Chemistry offers them, but who cannot spare either the time or the money in actual college. Dr. Sloane, a leading authority on Chemistry, will teach you and will give you all the individual help you require. He will personally go over your papers, correct them, point out your faults and teach you in a practical and interesting way. No special education needed except the ability to read and write English. One student has characterized our program as "The course that takes the mystery out of Chemistry."

Easy Monthly Payments

You do not have to have even the small price of the course to start. You can pay for it in small monthly amounts—so moderate that you won't feel them. The cost is low, and includes everything, even the Laboratory Equipment—there are no extra charges. Our plan of easy monthly payments places a chemical education within the reach of everyone.

Laboratory Equipment Given To Every Student Without Additional Charge

We give to every student without additional charge his chemical equipment, including forty-eight pieces of laboratory apparatus and supplies, and forty different chemicals and reagents. These comprise the apparatus and chemicals used for the experimental work of the course.

Special 30-Day Offer

For a short period we are making a special offer that will be worth your while to take advantage of. Write for particulars, using the coupon below or simply a postal card. This will not obligate you in the least. Do not wait until tomorrow. Send the coupon now while you think of it.

The CHEMICAL INSTITUTE of New York, Inc.

HOME EXTENSION DIVISION IS

66-R W. Broadway, New York City

Sign and Mail this Coupon for FREE BOOK

CHEMICAL INSTITUTE OF NEW YORK, Inc.
Home Extension Division 12,
66-R W. Broadway, New York City.

Please send me at once without any obligation on my part, your Free Book "Opportunities for Chemists," and tell particularly about the Laboratory Equipment furnished to every student. Also please tell me about your plan of payment and your special 30 day offer.


NAME

ADDRESS

CITY

STATE

R.N.1224

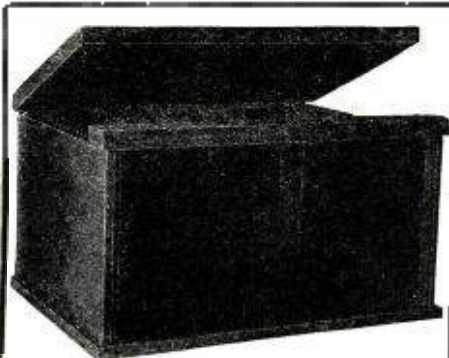

Radio Cabinets Strong and Rigid. Remember That We Pay Mail and Express Charges. It Makes Quite a Difference When Comparing Prices.

Specifications

Hardwood, rubbed mahogany finish. Top hinged, ends of top splined to prevent warping.

Panel size	Depth	Price
7 x 14.....	10.....	\$3.00
7 x 16.....	10.....	3.25
7 x 21.....	10.....	3.50
7 x 24.....	10.....	3.75
7 x 26.....	10.....	4.50
7 x 27.....	9.....	5.00
7 x 28.....	10.....	6.00

Mail and express prepaid east of Mississippi River.

We also make Radio Desks and Tables.
Send for free catalogue

The Southern Toy Company, Inc.
Dept. N. HICKORY, N. C.

Insure your copy reaching you each month.
Subscribe to RADIO NEWS — \$2.50 a year.
Experimenters Publishing Co., 52 Park Pl., N.Y.C.

sending a current of from 2,000,000 to 5,000,000 volts to the Crookes tube, to be placed at the apex of the tower.

ON PLAN OF SEARCHLIGHT

The tube would be mounted on a pivot, like a searchlight so as to be turned in any direction. The exact latitude and longitude of the New York receiver would be known and the point toward which to turn the lines of force could be found by nautical instruments.

Alongside the tower would stand a mast or pole of equal height capped by a metal globe. A current of low voltage would be sent up this pole, and as the high voltage X-ray current from the tower struck the globe, it would pick up and carry along the weaker current. The latter would be governed by a telegraph or telephone instrument.

HIGH POLE AND METAL GLOBE

At the New York end of the route would stand another 1,000-foot mast or pole surmounted by a metal globe, and as the X-ray current from Chicago reached it, the pulsations could be recorded by a telegraph sounder or heard by a telephone receiver.

Of course the lines of force would extend beyond the fast globe for a distance, but ultimately they would return to the original tube and complete the circuit. The telegraph or telephone instruments would both be grounded and the return circuit would be completed in the same way.

WOULD FOLLOW EARTH'S CURVE

While the lines of force are practically straight, yet the earth itself is a magnet and would deflect the current sufficiently to make it follow the curve of the earth's surface. Mountain ranges would not prove a bar to its progress.

The great initial cost would be the building of the tower and the poles, but aside from that, the equipment would not be expensive.

A BOOTLEG AERIAL

POULSEN TO DRUNK—"Come now, how did you get it?"

SOURCE RADIO FAN—"On a 'hic' beverage antenna, of course."

Contributed by Eugene Keler.

MODERN

"Push-Pull" Transformers Were First

can be offered the Radio public. Today they are recognized as the last word in quality amplification.



MODERN

"Super-Six" Reflex

This is the peak of all Reflex circuits. It works on a loop. Scores of laboratory tests were made before the MODERN Radio Frequency Transformer used in the "Super-Six" circuit were offered the radio world. The success and acceptance of this circuit have been instantaneous.

Full size wiring diagram and complete constructional bulletin mailed on receipt of 4¢ stamps. Be sure to specify whether you desire "Push-Pull" or "Super-Six" bulbless.

The Modern Electric Mfg. Co.

Builders of Transformers Exclusively

TOLEDO, OHIO

TRANSFORMERS

Radio's Greatest Value! Danodyne

**One Control; One Tube
1500 Miles—Loud and clear**

TURN the dial on the Danodyne and it's just like magic—station after station comes in. Even seasoned fans get the Thrill! Tunes sharp and sweet, and brings them in for 1500 miles and more.

Perfect Electrically and Mechanically

Nothing freaky or tricky about the Danodyne. It's an amazing development of a proven Radio principle brought to its utmost efficiency of operation. Each part made of finest materials—scientifically correct—and thoroughly tested before employed. The cabinet in the DANO "Jewel Box" is compact and beautiful. Try as you like, there's nothing to be bought to compare in value with the Danodyne.

DANO RADIO COMPANY
39 Liberty Street, Brooklyn, N. Y.



free

\$15 Complete Cabinet

Your copy of "Radio's Greatest Value" is waiting for you. It tells all about the Danodyne, explains how it is built, and puts a new and much more sensible value on Radio Sets and Essential Parts.

Send For It Today—Now!

No cost or obligation whatever involved. Ask for the booklet "Radio's Greatest Value." Write now to D. R. C.

In She Comes!

TIP YOUR whisker to almost any point of the NAA Meter tested crystal and the full flow of the low-pitched, clean, clear, steady, beautiful music will be yours. EVERY crystal tested and selected by specially trained electrical instruments to a point very beyond normal sensitivity. In addition, the Newman-Stern mounting is a perfect pendulum-cord assembly, provides for retuning and avoids damage to crystal by hot spots caused by poor design.

PERFECT FOR REFLEX

All all good holders and dust-free, in metal turned and anodized. If dealer can't supply, order direct and send dealer's name.

The Newman-Stern Co.
1742 East 12th Street
Cleveland, Ohio

Original source of special crystals in ref. and tested and largest producers.

Platters for Radio Repairmen in 10¢

New NAA Meter Tested Crystals



Nuggets of Sensitiveness



Why it is Better

"MASTER of Every Note in the Orchestral Range" is the proven claim of the Federal No. 65 Audio Frequency Transformer! Volume without distortion is the basis for the beauty of Federal Tone.

From its oversize locking nuts to its heavy brass mounting feet the Federal No. 65 Transformer incorporates the same engineering skill that has made Federal the recognized leader in electrical communication apparatus since 1890.

Insist upon Federal parts for your "pet" hook-up. There are over 130 standard parts bearing the Federal iron-clad performance guarantee.

FEDERAL TELEPHONE & TELEGRAPH CO.


Buffalo, N. Y.

Boston New York Philadelphia
Chicago Pittsburgh
San Francisco Bridgeburg, Canada



Federal

Standard RADIO Products

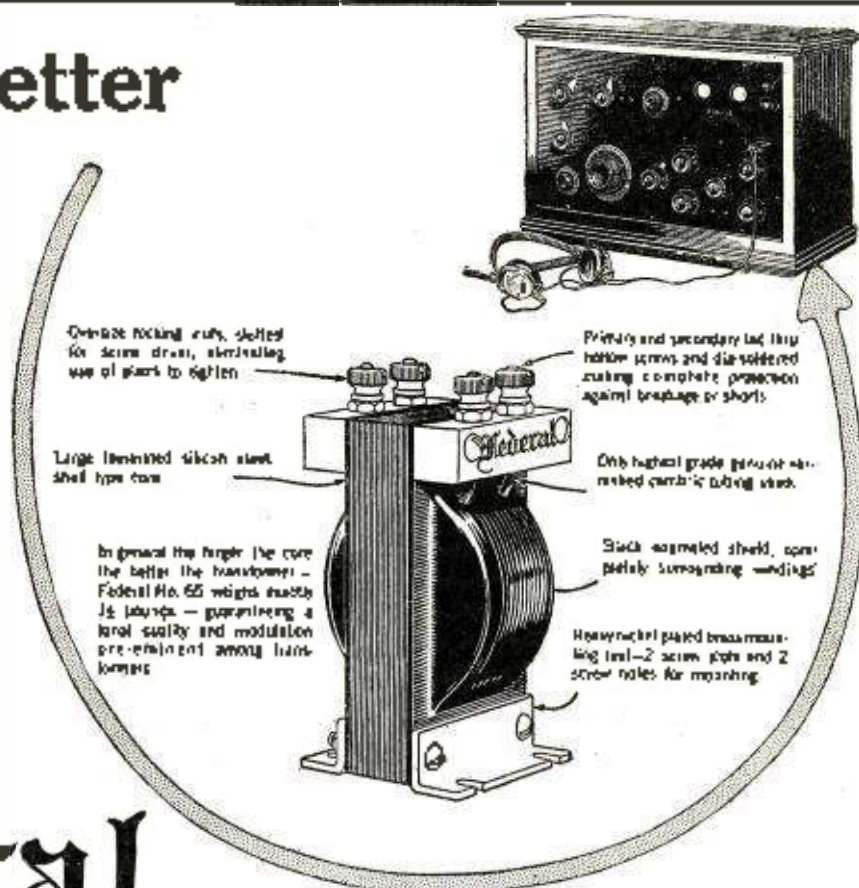

ROFFY CIRCUITS

Economy with Efficiency

This is the Keynote of all Roffy Hook-Ups

The much discussed theory and practice of Radio Frequency Amplification has been brought to its maximum efficiency, to date, by Mr. Roffy's research. Mr. Roffy has been able to leave the beaten track of circuits, by evolving a new and improved method of winding Radio Frequency Transformers; and applied this to the Roffy No. 7 and Super Roffy, already published in this magazine.

A beginner in the construction of Radio Circuits can follow the extremely simple instructions included with each carton of Roffy transformers; and build a set saving at least \$100.00 and in performance equaling or even surpassing the best factory built product.



ROFFY Transformers

\$6⁰⁰

Each

DEALERS AND JOBBERS are requested to write for attractive propositions.

STAMM-LAWSON
RADIO MANUFACTURING CO.

Sole Manufacturers of ROFFY Transformers

UPLAND

CALIFORNIA

-----USE THIS COUPON-----
STAMM-LAWSON RADIO MANUFACTURING CO.
Upland, California.
Please send me the very interesting and educational pamphlet describing in detail the principle and principle of Roffy Transformers and circuits. I am enclosing 4c to cover mailing cost.
Name.....
Address.....
City.....

RADIO READING COURSE



A Complete, Practical, 5 Book Course on Radio and Its Every Detail

All the technical details and a thorough explanation of radio operation, written in easily understood, non-technical language by a foremost radio engineer and lecturer. Over 100 electric drawings give you the knowledge to intelligently buy, design, build, service and maintain radio receiving apparatus. Tells you how to locate and correct troubles, how to make your apparatus more efficient and gives you a most useful knowledge of radio science.

SEND NO MONEY

On special arrangement you can own this 5 Book Course described in the art of the books for only \$1.47—if you act at once. Simply send us your name and address. Upon receipt pay the publisher only \$1.47 plus postage and the books are yours. The supply is limited so order at once.

From any of the hundreds of radio dealers and a complete radio library. To own this 5 Book Radio Reading Course is to have a library of radio science at your side, wherever you are, pointing the way. No matter what your interest in radio, take advantage of this attractive special offer and be the owner of the most useful 5 books.


CONSRAD COMPANY

233 Fulton Street, New York City

The Simplest Switch Stop

(Continued from page 941)

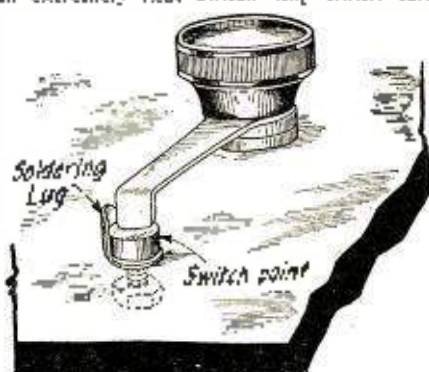As for the standard switch stop, sold on the market. All that is required is an ordinary straight soldering lug which is placed underneath the first and last switch points with its tip bent upright. This makes an extremely neat switch stop which com-



A simple switch stop made of a soldering lug fastened under the switch point.

pages favorably with any that can be bought. As the switch point will be raised slightly above the others, it may be necessary to file down the face of it in order that the switch lever may slide upon it smoothly.

—Contributed by James Wardell.

SILVER PANEL MARKINGS

The old methods of marking radio panels proving unsatisfactory, I finally hit upon the following method. This gives a very pleasing effect, more so than the plain white, and in addition is very simple and cheap.

First mix up some cold dope of acetone and celluloid. Then brush the mixture in to the mark to be filled, making sure all of the surface of the mark is covered. A toothpick will help here. While the dope is still wet, quickly dust some aluminum paint powder thickly over the spot, and rub it in well. Let the dope dry, then brush off all surplus matter, using a match in

Have you your EKKO Broadcasting Station Stamp Album?



Here's what every radio fan has wanted—a convenient, permanent and authentic means of recording all the stations you hear over your set. The Ekko Album contains spaces for a beautifully engraved stamp from each of more than 650 stations. These stamps are verified and prove your reception of the station.

Proof of Reception cards are furnished with the album. You send the card to the station, together with two cents, to cover cost of verified reception facts which prove to the station you have heard their broadcast. In return the station sends you their verified stamp as evidence of actual reception. The stamps are beautifully engraved in different colors and there is an individual stamp for every station showing the station call letters.

The album is 11 x 11 inches, handsomely bound in a two-color cover. It contains 10 pages with spaces for stamps of all recognized stations in the U. S. and Canada, arranged alphabetically by state and call letters. It also contains an alphabetical list of the official names and other interesting features of stations, as well as a convenient log.

See your dealer today and get a copy of the Ekko Album and start a collection of these stamps. You will find this a new and fascinating method of verifying the stations you hear. If your dealer cannot supply you, send check or money order to:

Price \$1.75

The EKKO Company

111 W. Monroe Street
CHICAGO

EASTERN LOW LOSS COUPLER



Designed by M. R. Sheper

Accclaimed a NEW STANDARD in tuning devices. Perfection in low loss tuners achieved—every feature a coupler should have. Absolutely no tuning used, no shunt or other coating on wires.

MINIMUM OF LOSSES
MAXIMUM OF EFFICIENCY
VOLUME—SELECTIVITY

Marvelous DX Reception

As your dealer or sent direct on receipt of purchase price.

Jobbers and Dealers Everywhere

—Manufacturer—

EASTERN COIL CORP.
22 WARREN ST. NEW YORK CITY

3500 M.A.
90 VOLT

Stop experimenting with dry cells,
hook on
SUPER-DUTHO
Rechargeable Storage
"B" BATTERIES
and note the
difference!

See your dealer or
send check with order

SHIPPED FULLY CHARGED • DRY • SOLUTION SEPARATE

PREPAID PRICES...
24 VOLT \$9
45 VOLT \$17
90 VOLT \$32

Dealers—Write for
special proposition

DUNKER-THOMAS Products Co.
1226 Folsom Street, San Francisco, California

Write for booklet on
Standard "B" Batteries

17661

Insert your copy reaching you each month.
Subscribe to RADIO NEWS — \$2.50 a year.
Experiment Publishing Co., 55 Park Pl., N. Y. C.



Edson Will Allow You \$4.00 for Your Old Headset

Another Edson achievement—the creation of a 4000-Ohm Edson Super DX Phone—enables us to make a most unusual offer.

SPECIAL OFFER: We will allow you \$4.00 each on your old headsets regardless of age, make, or condition—to apply at the purchase price of from one to four \$8.50 Edson Super DX 4000-Ohm Headsets. **YOU SAVE \$4.00** on each phone ordered by using the Special **EXCHANGE COUPON** below. Limit: four phones to a family at special introductory price. Simply mark your name and address plainly on the package containing your old headsets and send remittance by Money Order or Registered Mail, enclosing coupon below. Act quickly; quantity limited.

Partially repurchases the lowest and highest tone signals that come in on your receiving set. Fully guaranteed. Regular price \$4.50.



BOX, \$4.50, including phone plug

SPECIAL INTRODUCTORY PRICE WITH COU

DEALERS: Write for our wonderful selling plan.

Edson Radio Sales Company

Elmwood, Providence, R. I.

Special EXCHANGE COUPON

This coupon and your old headset entitle you to an allowance of \$4.00 each on from one to four 4000-Ohm Super DX Phones, valued at \$8.50 each. You pay only \$4.50 for each phone ordered.

(RM-32)

THE NEW ACORN COPPER RIBBON AERIAL

Enameled 3 New Features!



1. Weather-proof Enameled.
2. No-solder buckle.
3. Adjustable for length.

For greater distance and better tone, you must use the new, improved ACORN Enameled Ribbon Aerial. Not a strip of flat copper, but a Laboratory product in which resistance, capacity and strength have been calculated to produce best results.

PRICES DON'T BLAME YOUR RECEIVER

50 Ft.	\$1.75
75 Ft.	\$2.50
100 Ft.	\$3.25
150 Ft.	\$4.75

No radio set can give you more than the aerial receives. Nearly a million "ACORN" Ribbon Aerials now giving perfect results, under all conditions, with every type of radio set. Install this wonder aerial under our positive guarantee to refund your money if your reception is not improved at least 100%.

NOW AT MOST GOOD RADIO SHOPS

If your dealer cannot supply you, order direct from the manufacturer.

ACORN RADIO MFG. CO.

Dept. 605, 307 W. Lake Street
Chicago



ACORN ENAMELED WINDOW LEAD-IN

Now you don't have to drill through walls or windows to run your lead-in to your set. This flat, triple-insulated copper ribbon fits in under windows, set the wire it to be close right. Weather proof and electric insulation. Patented clip at both ends.

Only **35c**

any time least. The odds, however, "I guess that some of the realities of radio, on the other hand, seem almost as wild, and one of these is seeing by radio. This is no dream, but a fact that is being steadily perfected. Probably within five years radio audiences in remote cities will see the facial expressions as well as hear the words of the speaker."

Despite the recent development in the experimental use of short, directional waves, Doctor Hellingger does not contemplate that radio telephony will displace the long-distance wire telephone. "As to universal use of the radio to communicate between individuals, I think not," he asserts. "On the other hand, improvements in methods of concentrating the waves in a desired direction, increase in the restriction of the wave to its proper frequency, the use of much shorter waves than those employed at present, these and many other developments by the scientists in various laboratories will steadily increase the extent of the manifold service that radio can render."

"Eventually, every hospital in the United States will be equipped with radio," says the doctor. "This is the most beneficent use of radio. Besides the benefit to patients through providing entertainment, medical authorities testify to the actual therapeutic value of the mental relief thus afforded." The Bureau of Standards is extending valuable aid in the technical equipment of these hospitals. The system employed is the use of a single receiving set and a powerful amplifier to supply entertainment to all of the occupants of a hospital. Each patient is provided with receivers.

The increasing use of short waves or high frequencies and the elimination of spark transmitting equipment will relieve the ether of some of its interference and further contribute to the improvement of radio communication. Already, transmitting stations have installed auxiliary equipment and are employing high frequencies for transoceanic communication. The powerful sending station at St. Assise, France, is utilizing frequencies of the order of 3,000 to 4,000 kilocycles (100 to 70 meters) for transoceanic communication. This is an experimental undertaking, but there is likelihood of it being a permanent service.

Revolutionary

The "SELF ADJUSTING" Rheostat



\$1.10

Everywhere

Write for FREE Hook-ups

AMPERITE controls perfectly and automatically the current flow from battery to tube. No Rheostat knobs on panel to buzz. No wattmeter needed. No worry. One AMPERITE for each tube inside the set regulates current on thermo-electric principle. Simplifies wiring and operation. Facilitates tuning. Proven in use. Adopted by 50 set manufacturers. Be sure your set is equipped with AMPERITE.

RADIALL COMPANY

Dept. R.H. 4, 30 Franklin St., New York

AMPERITE

"means right amperes"


USE "RAGEMCO" TOOLS TO BUILD BETTER RADIO SETS



FR-701 RADIO TOOL SET

This is the handiest set of tools ever made for Radio Work by the makers of the famous "RAGEMCO" Tools. It contains the following: 1. Blade, 2 1/2 in. 2. Blade, 3 1/2 in. 3. Blade, 4 1/2 in. 659. Blade, 660 1/2 in. 660. Blade, 661

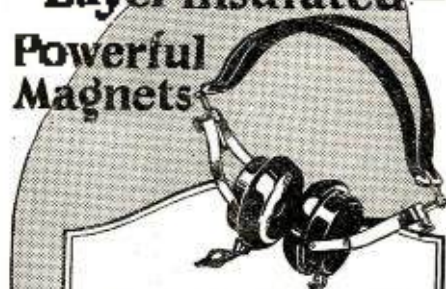Layer Wound and Layer Insulated - Powerful Magnets



Stromberg-Carlson Head Sets and Loud Speakers have powerful magnets and layer wound and layer insulated coils. Each coil has a wrapping of tough insulating material between layers. They stand up under the high plate voltages now prevalent for most speaker hookups.

Stromberg-Carlson Head Sets and Loud Speakers

operate with good standard tube receiving sets. They give abundance of sound and have the finest tonal qualities.

Ask Your Dealer

Stromberg-Carlson
Telephone Mfg. Co.
1060 University Ave.
Rochester, N. Y.



Stromberg-Carlson HEAD SETS AND LOUD SPEAKERS



FROM FACTORY TO USER

High Grade Radio Cabinets stand built and are looking like new when they leave the factory. They are completely finished. The inside of cabinets is painted. Fronts of cabinets are finished in lacquer. Walnut cabinets have continuous glass doors and the inside finish is painted. The inside of the door is painted. Walnut cabinets finished in French mahogany. Much cabinet finishing is done in Adams Brown mahogany. (Paint not included). See back of box for details.

Part	Price	Price	Price	Price
Panel	Door	No Door	Back	Back
7-1	1.75	1.75	1.75	1.75
7-2	2.25	2.25	2.25	2.25
7-3	2.75	2.75	2.75	2.75
7-4	3.25	3.25	3.25	3.25
7-5	3.75	3.75	3.75	3.75
7-6	4.25	4.25	4.25	4.25
7-7	4.75	4.75	4.75	4.75
7-8	5.25	5.25	5.25	5.25
7-9	5.75	5.75	5.75	5.75
7-10	6.25	6.25	6.25	6.25
7-11	6.75	6.75	6.75	6.75
7-12	7.25	7.25	7.25	7.25
7-13	7.75	7.75	7.75	7.75
7-14	8.25	8.25	8.25	8.25
7-15	8.75	8.75	8.75	8.75
7-16	9.25	9.25	9.25	9.25
7-17	9.75	9.75	9.75	9.75
7-18	10.25	10.25	10.25	10.25
7-19	10.75	10.75	10.75	10.75
7-20	11.25	11.25	11.25	11.25
7-21	11.75	11.75	11.75	11.75
7-22	12.25	12.25	12.25	12.25
7-23	12.75	12.75	12.75	12.75
7-24	13.25	13.25	13.25	13.25
7-25	13.75	13.75	13.75	13.75
7-26	14.25	14.25	14.25	14.25
7-27	14.75	14.75	14.75	14.75
7-28	15.25	15.25	15.25	15.25
7-29	15.75	15.75	15.75	15.75
7-30	16.25	16.25	16.25	16.25
7-31	16.75	16.75	16.75	16.75
7-32	17.25	17.25	17.25	17.25
7-33	17.75	17.75	17.75	17.75
7-34	18.25	18.25	18.25	18.25
7-35	18.75	18.75	18.75	18.75
7-36	19.25	19.25	19.25	19.25
7-37	19.75	19.75	19.75	19.75
7-38	20.25	20.25	20.25	20.25
7-39	20.75	20.75	20.75	20.75
7-40	21.25	21.25	21.25	21.25
7-41	21.75	21.75	21.75	21.75
7-42	22.25	22.25	22.25	22.25
7-43	22.75	22.75	22.75	22.75
7-44	23.25	23.25	23.25	23.25
7-45	23.75	23.75	23.75	23.75
7-46	24.25	24.25	24.25	24.25
7-47	24.75	24.75	24.75	24.75
7-48	25.25	25.25	25.25	25.25
7-49	25.75	25.75	25.75	25.75
7-50	26.25	26.25	26.25	26.25
7-51	26.75	26.75	26.75	26.75
7-52	27.25	27.25	27.25	27.25
7-53	27.75	27.75	27.75	27.75
7-54	28.25	28.25	28.25	28.25
7-55	28.75	28.75	28.75	28.75
7-56	29.25	29.25	29.25	29.25
7-57	29.75	29.75	29.75	29.75
7-58	30.25	30.25	30.25	30.25
7-59	30.75	30.75	30.75	30.75
7-60	31.25	31.25	31.25	31.25
7-61	31.75	31.75	31.75	31.75
7-62	32.25	32.25	32.25	32.25
7-63	32.75	32.75	32.75	32.75
7-64	33.25	33.25	33.25	33.25
7-65	33.75	33.75	33.75	33.75
7-66	34.25	34.25	34.25	34.25
7-67	34.75	34.75	34.75	34.75
7-68	35.25	35.25	35.25	35.25
7-69	35.75	35.75	35.75	35.75
7-70	36.25	36.25	36.25	36.25
7-71	36.75	36.75	36.75	36.75
7-72	37.25	37.25	37.25	37.25
7-73	37.75	37.75	37.75	37.75
7-74	38.25	38.25	38.25	38.25
7-75	38.75	38.75	38.75	38.75
7-76	39.25	39.25	39.25	39.25
7-77	39.75	39.75	39.75	39.75
7-78	40.25	40.25	40.25	40.25
7-79	40.75	40.75	40.75	40.75
7-80	41.25	41.25	41.25	41.25
7-81	41.75	41.75	41.75	41.75
7-82	42.25	42.25	42.25	42.25
7-83	42.75	42.75	42.75	42.75
7-84	43.25	43.25	43.25	43.25
7-85	43.75	43.75	43.75	43.75
7-86	44.25	44.25	44.25	44.25
7-87	44.75	44.75	44.75	44.75
7-88	45.25	45.25	45.25	45.25
7-89	45.75	45.75	45.75	45.75
7-90	46.25	46.25	46.25	46.25
7-91	46.75	46.75	46.75	46.75
7-92	47.25	47.25	47.25	47.25
7-93	47.75	47.75	47.75	47.75
7-94	48.25	48.25	48.25	48.25
7-95	48.75	48.75	48.75	48.75
7-96	49.25	49.25	49.25	49.25
7-97	49.75	49.75	49.75	49.75
7-98	50.25	50.25	50.25	50.25
7-99	50.75	50.75	50.75	50.75
7-100	51.25	51.25	51.25	51.25

Mounting boards all sizes in stock.

P.O. Box 1000, New York

Particular attention is given to the construction of the cabinet. The cabinet is built of solid wood and is finished with a high grade lacquer. The cabinet is built to last and is a beautiful addition to any home.

UTILITY SUPPLY COMPANY

27th Street

Manhattan, N.Y.

"Spark-transmitting equipment," observes Doctor Dellinger, "is being eliminated. This not only means greater transmitting and receiving ranges but interference is reduced. I think that owing to the cheapness of spark transmitting equipment it will be used on ships for many years to come, but eventually both spark and arc transmitters will disappear."

RESEARCH WORK

No research laboratory is doing more to realize the improvements and bring to a fruition the benefits foreshadowed in this interview than the Radio Laboratory of the Bureau of Standards. Radio frequency standardization, the testing of receiving sets to determine their relative selectivity and sensitivity, observations to determine the range of receiving equipment and the limiting factors attending broadcast reception, the testing of vacuum tubes, finding uses for and standardizing of very short waves or high frequencies and the application of radio as a life-saving agency at sea and for utilitarian purposes on aircraft, are among its manifold activities. For instance, a vibrating or shimmying machine has been designed for determining the relative ruggedness of receiving sets. A new method of primary radio frequency standardization has been developed, using cathode rays and a tuning fork. Means have been devised for guiding aircraft in flight and ships at sea by use of radio compasses on land. With respect to the testing of vacuum tubes, these questions are being asked and answered in this Radio Laboratory: How long is the life of various types of vacuum tubes? What is the power rating of a power tube? What is the effect of regeneration in radio receiving units? How can radiation be avoided in regenerative circuits?

How To Build a Battery Control Panel

(Continued from page 942)

elements and test tubes. It is necessary to split the battery in half for the purpose of charging, since it increases the charging rate. This is a feature which does not seem to be understood by many; when charging a battery, in order that the current may flow from the charger to the battery, the voltage of the charger should always be higher than the battery voltage, otherwise the current will not flow. The splitting arrangement is controlled by a D.P.D.T. switch, which acts as a series parallel affair, connecting the two halves of the battery in series when discharging, and in parallel when charging, so that the voltage across the negative and positive terminals is only 50 volts instead of 100. This switch is mounted on the battery panel, and not on the power panel as described in this article.

The "R" battery circuit is controlled by a D.P.D.T. switch as in the "A" battery circuit with the battery panel switch as described above. The middle terminals are connected directly to the negative and positive terminals of the battery, at which point the voltage is varied by the panel switch. On the upper part of the switch are connected the leads from the charger. The positive lead is clipped onto the exposed wire coming out of the transformer coil on top of the charger, when a 2-ampere Tungar is used, and to the wing nut with a 5 ampere size. The negative, black lead used in charging the "A" battery is also used in charging the "B" battery, connected to the upper negative side of the switch. On the positive is provided the 60-ohm resistance and a 5-volt 2-watt power lamp, both connected in series. The lamp serves as an indication that the battery is charging.

DUPLEX



"DR" Series

A compact precision vacuum tube of high value and extremely low price. Ideal for use in all types of radio sets. Buy now, before the price goes up.

"FR" Series

The highest quality low line vacuum tube. Used by inventors and manufacturers. Available in 100, 150, 200, 250, 300, 350, 400, 450, 500, 550, 600, 650, 700, 750, 800, 850, 900, 950, 1000, 1050, 1100, 1150, 1200, 1250, 1300, 1350, 1400, 1450, 1500, 1550, 1600, 1650, 1700, 1750, 1800, 1850, 1900, 1950, 2000, 2050, 2100, 2150, 2200, 2250, 2300, 2350, 2400, 2450, 2500, 2550, 2600, 2650, 2700, 2750, 2800, 2850, 2900, 2950, 3000, 3050, 3100, 3150, 3200, 3250, 3300, 3350, 3400, 3450, 3500, 3550, 3600, 3650, 3700, 3750, 3800, 3850, 3900, 3950, 4000, 4050, 4100, 4150, 4200, 4250, 4300, 4350, 4400, 4450, 4500, 4550, 4600, 4650, 4700, 4750, 4800, 4850, 4900, 4950, 5000, 5050, 5100, 5150, 5200, 5250, 5300, 5350, 5400, 5450, 5500, 5550, 5600, 5650, 5700, 5750, 5800, 5850, 5900, 5950, 6000, 6050, 6100, 6150, 6200, 6250, 6300, 6350, 6400, 6450, 6500, 6550, 6600, 6650, 6700, 6750, 6800, 6850, 6900, 6950, 7000, 7050, 7100, 7150, 7200, 7250, 7300, 7350, 7400, 7450, 7500, 7550, 7600, 7650, 7700, 7750, 7800, 7850, 7900, 7950, 8000, 8050, 8100, 8150, 8200, 8250, 8300, 8350, 8400, 8450, 8500, 8550, 8600, 8650, 8700, 8750, 8800, 8850, 8900, 8950, 9000, 9050, 9100, 9150, 9200, 9250, 9300, 9350, 9400, 9450, 9500, 9550, 9600, 9650, 9700, 9750, 9800, 9850, 9900, 9950, 10000, 10050, 10100, 10150, 10200, 10250, 10300, 10350, 10400, 10450, 10500, 10550, 10600, 10650, 10700, 10750, 10800, 10850, 10900, 10950, 11000, 11050, 11100, 11150, 11200, 11250, 11300, 11350, 11400, 11450, 11500, 11550, 11600, 11650, 11700, 11750, 11800, 11850, 11900, 11950, 12000, 12050, 12100, 12150, 12200, 12250, 12300, 12350, 12400, 12450, 12500, 12550, 12600, 12650, 12700, 12750, 12800, 12850, 12900, 12950, 13000, 13050, 13100, 13150, 13200, 13250, 13300, 13350, 13400, 13450, 13500, 13550, 13600, 13650, 13700, 13750, 13800, 13850, 13900, 13950, 14000, 14050, 14100, 14150, 14200, 14250, 14300, 14350, 14400, 14450, 14500, 14550, 14600, 14650, 14700, 14750, 14800, 14850, 14900, 14950, 15000, 15050, 15100, 15150, 15200, 15250, 15300, 15350, 15400, 15450, 15500, 15550, 15600, 15650, 15700, 15750, 15800, 15850, 15900, 15950, 16000, 16050, 16100, 16150, 16200, 16250, 16300, 16350, 16400, 16450, 16500, 16550, 16600, 16650, 16700, 16750, 16800, 16850, 16900, 16950, 17000, 17050, 17100, 17150, 17200, 17250, 17300, 17350, 17400, 17450, 17500, 17550, 17600, 17650, 17700, 17750, 17800, 17850, 17900, 17950, 18000, 18050, 18100, 18150, 18200, 18250, 18300, 18350, 18400, 18450, 18500, 18550, 18600, 18650, 18700, 18750, 18800, 18850, 18900, 18950, 19000, 19050, 19100, 19150, 19200, 19250, 19300, 19350, 19400, 19450, 19500, 19550, 19600, 19650, 19700, 19750, 19800, 19850, 19900, 19950, 20000, 20050, 20100, 20150, 20200, 20250, 20300, 20350, 20400, 20450, 20500, 20550, 20600, 20650, 20700, 20750, 20800, 20850, 20900, 20950, 21000, 21050, 21100, 21150, 21200, 21250, 21300, 21350, 21400, 21450, 21500, 21550, 21600, 21650, 21700, 21750, 21800, 21850, 21900, 21950, 22000, 22050, 22100, 22150, 22200, 22250, 22300, 22350, 22400, 22450, 22500, 22550, 22600, 22650, 22700, 22750, 22800, 22850, 22900, 22950, 23000, 23050, 23100, 23150, 23200, 23250, 23300, 23350, 23400, 23450, 23500, 23550, 23600, 23650, 23700, 23750, 23800, 23850, 23900, 23950, 24000, 24050, 24100, 24150, 24200, 24250, 24300, 24350, 24400, 24450, 24500, 24550, 24600, 24650, 24700, 24750, 24800, 24850, 24900, 24950, 25000, 25050, 25100, 25150, 25200, 25250, 25300, 25350, 25400, 25450, 25500, 25550, 25600, 25650, 25700, 25750, 25800, 25850, 25900, 25950, 26000, 26050, 26100, 26150, 26200, 26250, 26300, 26350, 26400, 26450, 26500, 26550, 26600, 26650, 26700, 26750, 26800, 26850, 26900, 26950, 27000, 27050, 27100, 27150, 27200, 27250, 27300, 27350, 27400, 27450, 27500, 27550, 27600, 27650, 27700, 27750, 27800, 27850, 27900, 27950, 28000, 28050, 28100, 28150, 28200, 28250, 28300, 28350, 28400, 28450, 28500, 28550, 28600, 28650, 28700, 28750, 28800, 28850, 28900, 28950, 29000, 29050, 29100, 29150, 29200, 29250, 29300, 29350, 29400, 29450, 29500, 29550, 29600, 29650, 29700, 29750, 29800, 29850, 29900, 29950, 30000, 30050, 30100, 30150, 30200, 30250, 30300, 30350, 30400, 30450, 30500, 30550, 30600, 30650, 30700, 30750, 30800, 30850, 30900, 30950, 31000, 31050, 31100, 31150, 31200, 31250, 31300, 31350, 31400, 31450, 31500, 31550, 31600, 31650, 31700, 31750, 31800, 31850, 31900, 31950, 32000, 32050, 32100, 32150, 32200, 32250, 32300, 32350, 32400, 32450, 32500, 32550, 32600, 32650, 32700, 32750, 32800, 32850, 32900, 32950, 33000, 33050, 33100, 33150, 33200, 33250, 33300, 33350, 33400, 33450, 33500, 33550, 33600, 33650, 33700, 33750, 33800, 33850, 33900, 33950, 34000,

The "A" and "B" battery lamps are quite important, as they prevent, by their indication, the charging of both batteries at the same time because the operator of the device should know that when lamp one is lighted he should not attempt to light the other by charging the second battery. More than one lamp should never be lighted at the same time.

The most interesting feature of this panel is the switching arrangement for measuring the voltage across each half of the battery separately. This is done by the aid of a series-parallel switch connected as shown in the wiring diagram, Fig. 2. Eight switch points are also needed for the purpose. The wiring is plainly shown in the diagram. When testing the first half of the battery the 50-volt connection becomes positive and when testing the second half, it becomes negative. The operation is very simple, the test of the first half of the battery is made when the switch is in a position as indicated in the diagram. The next position shows the test for the other half of the battery. In this case the two arms of the switch should be perpendicular. With this arrangement a 0-50 range voltmeter has been found best, because the percentage of error in reading a low-range scale is less than in a high-range one where the divisions of the scale are smaller.

Do not attempt to test the voltage across the battery while charging because the charging voltage is much higher than the battery voltage. The voltage of this battery immediately after shutting down the charge should be a little over its rated value, that is it should indicate on the voltmeter a little more than 50 volts. The normal voltage throughout most of the period of discharge should be about 46 volts for half the battery. When it drops to 35 volts it should be recharged.

The wiring diagram, Fig. 2, will give a very good idea of the layout. It shows clearly the entire wiring of the panel. The wiring of the Tungar charger is given to help the reader understand the entire circuit. The "B" battery panel wiring is also shown in the lower right hand corner of the diagram.

The photo of the panel, Fig. 3, will show how the apparatus is mounted on the panel.

The writer feels confident that any one who will build such a panel will find the maintenance of the radio receiving set more agreeable.

Experimental Technique

(Continued from page 921)

may copy a thousand in vain but the thousand and first may prove extremely valuable. Anyway, if they all prove nothing more than bulls, it will increase the fun of the thing and at the same time teach extreme care and workmanship and after all, workmanship of a high standard is the perfect joy.

So get rid of the sloppy habits and do the thing up brown. It will increase your range, see if it doesn't!—Jay Hollander

Radio Swindles

(Continued from page 915)

pressure it will test in resonance with the brain, but if there is pressure it will test below the capacity and indifference of the brain, and the Chiropractor will know the degree of INTERFERENCE (?) to the flow of life force.

If you have ever read any greater nonsense in your life than this, we would like to see it.

That the Neurophonometer will not only test nothing, but will do nothing else either, is absolutely certain. That it cannot do anything is for the simple reason first—that



So little to do—such great results

Never has there been entertainment, so much and so fine, that was so little trouble and expense as with radio.


Good programs without limit when that storage battery of yours is fully charged and ready. Perfectly easy and simple if you have the Tungar, which recharges the radio or auto battery overnight from the house current.

Sold by Electrical, Auto-accessory and Radio dealers.



Tungar is one of the truly scientific achievements contributed by the G-E Research Laboratories toward the wonderful development of electricity in America.

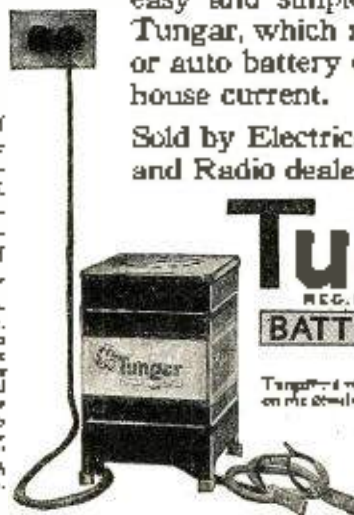Tungar Battery Charger operates on alternating current. Price, each of the Recharge (80 cycle) Charger—single complete, \$18.00, 5 complete complete, \$28.00. Special package for charging 30 or 20 cell "D" Storage Battery, \$2.00. Special package for charging 2 or 3 cell "A" Storage Battery, \$1.00. Both much more than worth the Tungar.



Tungar
REG. U.S. PAT. OFF.
BATTERY CHARGER

Tungar is registered trade mark—its found only on the genuine. Look for it on the name plate.

Merchandise Department
General Electric Company
Bridgeport, Connecticut

GENERAL ELECTRIC

418-12

REPAIRING

of all Styles of Amplifier, Detector or Power Tubes

You will like the working characteristics of our tubes, as they are absolutely correct in Vacuum and Filament

Send them in P.P. and have the satisfaction of knowing that your tubes are as efficient as scientific methods can make them.

5 Watt Tubes, \$3.50. All others, \$2.00

Send them today to

WAYNE RADIO TUBE LABORATORIES

2217 Lafayette St. (At Rear)

Pt. Wayne, Ind.

Insure your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Experimenters Publishing Co., 51 Park Place, N. Y. C.

cessively difficult, in spite of the use of modern methods, is the work of the physicist in his attempt through the analysis of rays to determine the structure of the atom radiating the wave, or when he seeks to reconstruct the linear formation of a crystal with the aid of Roentgen rays reflected from it. The determination of the ray transmitter simply through the characteristics of its transmitted signal is a comparatively simple matter compared with the identification of a ray in the field of physical radiation. While the radio operator is able to isolate the wave he is investigating, the physicist must deal simultaneously with a large number of rays, none of which he is able to eliminate.

The chief reason for this sensitiveness to every ray is the formation of the eye, which is primarily and solely the receiver of electro-magnetic oscillations. All the greatest of science's recent discoveries are dependent exclusively on electro-magnetic oscillations. The messengers from the most distant realms of space, as well as those delineating the operations of that smallest division of matter, the atom, are received by the eye as electro-magnetic oscillations. The eye is, of course, the most sensitive of our preceptive organs. According to the researches of Henry Morris Russell and Prentice Reeves,

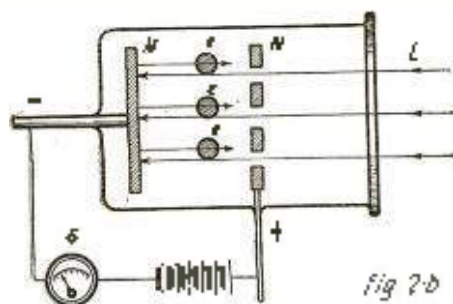


Diagram of the photoelectric cell: the light rays *L* set free electrons from the metal *C* which carries current through the galvanometer *G*.

the well practiced eye can appreciate light energy of the order of 10^{-16} watt as a true sensation.

We can, by simple comparison, make clear this extreme sensitiveness. The energy mentioned which gives the eye an appreciable sensation would need to be expanded over a period of many years, if its total power were to be able to raise one gram of water one degree centigrade. Another illustration is the fact that were the air perfectly clear from dust and moisture, the human eye could, ordinarily, perceive the image of a lighted candle at the distance of 62 miles. It is a well known fact that unaided the eye can perceive a sixth magnitude star.

Unfortunately the eye, while so extremely subtle a receiver of electro-magnetic rays, has at the same time, one great failing, i.e., it is extremely capricious with regard to surroundings. If one has been looking toward a bright light, a sense of fatigue results, causing an immediate loss of sensitivity. It also is extremely restricted in its range of effectiveness. The range of waves over which it acts is comparatively small including only those oscillations whose wavelength lies between .0003 and .0006 millimeters. The difficulty here is easily understood, when it is known that the modern physicist's investigations lead him into work covering waves ranging from 12½ miles in length down to 10^{-22} centimeters.

Luckily, we are able to assist the eye in this work with a number of artificial detectors of one sort or another which enable us to cover a great majority of these vibrations.

The first and one of the most important of these detectors is the photographic plate.

**"Oh boy,
that's
clear!"**

TRADE MARK REGISTERED



Out of the fog of uncertainties, doubts, experiments [and many superlatives and wild claims of superiority] has emerged Radync—developed by two of the powers of radio—men who were radio experts when the number of radio operators could be counted on the fingers of one hand. This simplified, balanced receiving set is now available to people everywhere—after having become the most popular set in California—an ideal place for testing under all conditions. It is as simple to operate as drawing a glass of water from a faucet. In long distance receiving it competes with all others under similar conditions; but it is clarity of reproduction that the inventors of Radync have been striving for—and have accomplished. As practical radio men they knew this is the one most desirable feature of radio. In price, Radync undersells other sets of similar construction [and less clarity] from \$20 to \$50—another big feature in its favor. There are a few other good sets—and a multitude of poor ones. Radync clarity is worth insuring upon. If your dealer cannot supply you with Radync, write to us.

Great Western Radio Corporation
SAN FRANCISCO

Sales Representatives:
Adams Pacific Agency Corporation
Kings Bldg., San Francisco
G.E. Thompson Co., 15 Huntington Ave., Boston
Sutton Electric Co., 90 Chambers St., New York
Simpson & Hadery
1401 Commonwealth Bldg., Pittsburgh
Wm. E. Wood, 1125 Pine St., St. Louis
Raymond Radio Service
1111 Chestnut St., Philadelphia
C.W. Howell & Co., 11 E. Van Buren St., Chicago
Brownlee Bros. & Co., Ogden

Radync
\$75
to
\$275



Increase your Range

From 15 to 100 per cent

Top eye, with top brand equipment, by using **SPRINGFIELD 16-STRAND BRAIDED ANTENNA**

Short, condensed wire for better results. Its extra large surface—twice that of ordinary wire—enables you to get greater distance and clarity. 25% less in your sight. In actuality 2 feet apart, gives better results than 20 feet of ordinary wire antenna. 10' for free booklet.

All dealers—send us \$2.50 for 100 feet. Cash and orders—write for prices and terms.

SPRINGFIELD WIRE & TUBE CO.
574 Taylor St. Springfield, Mass.
New York Office: 24 E. 42nd Street, Tel. Vanderbilt 6090

Springfield 16 Strand Braided Antenna

Insure your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



If it's a good hydrometer, it's a

Perfection HYDROMETER

A glance instantly gives condition of your battery.

Look for the name **PERFECTION** in the float. If the name **PERFECTION** is not on the float it is not a genuine **PERFECTION**.

Adjustments in nozzle prevent air passage and prevent clogging and leaking. Float studded to prevent sticking.

Every detail is perfected to give the Radio set owner the finest hydrometer obtainable.

\$1.00 At All Radio Dealers

Benco Manufacturing Company
243 W. 55 St., N.Y. City

Stop Tube Noises

BENJAMIN CLE-R-A-TONE SOCKET CLEARER RADIO TONE



Shock absorbing. Tube holding element "floats" on perfectly balanced springs. Takes up all jar and mechanical vibrations which interfere with clear reproduction. A vital necessity for loud used by leading makers of portable sets. Made of molded Bakelite. Underneath of base provided with smooth lugs for secure mounting. Contact springs keep tube prongs clean. In two sizes, for standard and UV-type, etc., tubes.

clear reproduction. A vital necessity for loud used by leading makers of portable sets. Made of molded Bakelite. Underneath of base provided with smooth lugs for secure mounting. Contact springs keep tube prongs clean. In two sizes, for standard and UV-type, etc., tubes.

RADIO-BATTERY SWITCH

Lightest and easiest switch made. Requires only 1/2 inch hole in panel. Requires no wiring. Only one adjustment necessary. The pushpull switch causes instant and positive contact. When it's in a well, avoiding accidental cutting in of battery.

Ask your dealer, or send us his name and address and we will supply you through him

BENJAMIN ELECTRIC MFG. CO.
120 S. Sangamon St., Chicago
247 W. 17th St. New York
580 Howard St. San Francisco

Assure your boys reaching you each month. See us in **RADIO NEWS**—\$2.50 a year. Zimmerman Publishing Co., 31 Park Pl., N.Y.C.

It is affected not only by the ordinary band of light to which we are accustomed, but by a band which lies below the ultra-violet. By only a sufficiently long exposure, sometimes running as high as a day, impressions of invisible light can be caught upon a plate which are much beyond the power of the human eye. This detection—as most others—has its defects. It is extremely sensitive to very short waves (Roentgen rays) but begins to fail when the higher bands are attempted. These oscillations jump about the red. It is also extremely difficult to bring the darkening of the plate into any dependable relation to the intensity of the light upon it.

A great step was made toward the enlargement of our knowledge concerning radiation through the invention of that great physical lawyer, in the construction of his bolometer. (See Fig. 1-A.) This instrument consists of an extremely fine strip of platinum which is heated by the rays which fall upon it. This heating has a very definite effect upon the resistance of the wire and so will give an appreciable change of an electric current passing through it. In the bolometer and the radio micrometer (See Fig. 1-B) we have two of the most sensitive measuring instruments known to man. With the former instrument there is no difficulty in measuring the heat falling upon the earth due to the light of the moon or that of a very distant star.

The modern physicist can predict even greater wonders than these, with instruments that far surpass those just mentioned in sensitiveness and at the same time are equally exact. I refer to the Audion bulb or the vacuum tube which is frequently used in the present day radio receiver and transmitter. As a detector of electro-magnetic light waves it has attained an extremely important position. For the development of its use in this connection, two German professors, Heter and Gerdel, have attained far-reaching results. The principle of the vacuum tube is, of course, understood by the readers of *RADIO NEWS*, as they are now fully acquainted with the peculiarities of electrons through their knowledge of these same tubes.

Every substance, as is well known, is composed of a great number of minute bodies, is electronic. When a metal is subjected to the effect of extreme heat, a large number of these tiny bodies are forcibly ejected from it, or literally, are called out into the surrounding space. We can also draw them out of a cold metal under certain conditions if light is caused to fall on the outer surface of the metal. The shorter these rays are the more profligate is the electronic emission and the hotter is the metal. The more intense they are the greater is the number of the electrons, derived from gases and impurities. The collision will set free more electrons and build up ions, which are in a condition to send an easily measurable electric current through the coils. The use of power fields and gas content has given to this appliance such sensitiveness that by its help one can follow the change of light of a distant double star.

If a light electron cell is combined with an amplifying tube or with the sensitiveness of the same cell, can be multiplied 15 million times and so at last we are able to note the sensitiveness of the human eye, but this cell has the advantage over the human eye in that it is free from all subjective sources of error and can give an exact and surprising estimation of the minimum light intensity. This electronic eye unfortunately shares with the human eye a lack of sensitiveness for long light waves.

Now we may compare the detector for light waves with the detector for wireless telegraphic waves. We will find as follows:



For All Batteries

Valley Battery Charger

For 2-volt peanut tube cells, for 6-volt A batteries and for 24-volt B batteries in from one to four units, the Valley Battery Charger is the one charger and the only charger which you need.

It plugs into the ordinary light socket like a fan or other household necessity, and is just as easy to operate. Takes about a dime's worth of current to bring your battery up to full charge.

It has a grained and engraved Bakelite panel which harmonizes with any radio set. Clear glass top shows the simple, patented working parts at all times. Scientifically planned and substantially made by experienced manufacturers of storage battery charging equipment.

At radio dealers everywhere. Further information furnished on request.

VALLBY ELECTRIC CO.
3137 S. Kingshighway, St. Louis, Mo.

FORMICA

RADIO PANELS

CUT PERFECTLY SQUARE WITH SMOOTH EDGES TO ANY SIZE

1/8" THICK 1/4¢ PER SQ. INCH
3/16" THICK 2¢ PER SQ. INCH
1/4" THICK 2 1/2¢ PER SQ. INCH

IN POLISHED BLACK, PATIOL, ANY OR WALNUT FINISH

ORDER SHIPPED SAME DAY RECEIVED

LET US DRILL AND ENGRAVE YOUR PANEL

SEND US A DRAWING OF YOUR PANEL AND WE WILL GLADLY FURNISH ESTIMATE

100 SIZES AND KINDS OF FORMICA SHEETS, TUBES AND HOODS CARRIED IN STOCK

Send For Price List

MANUFACTURERS JOBBERS and DEALERS

GET OUR PRICES ON MATERIAL AND CUTTING, DRILLING AND ENGRAVING PANELS IN LOTS OF 25 OR MORE

Small Pieces of Formica Sheet, Tube and Hood Cut to Size at Specialty Low Prices

STARRETT MFG. CO.
121 SOUTH GREEN ST. CHICAGO, ILL.

the subject, but she would show herself to be a little hurt, lending the impression that she considered Lee to be a bit selfish in his plans. The older sister too was sometimes explicit in her comments on the plans of her brother. None of them sympathized with or understood his ideals, the goal to which he was working.

There followed long soliloquies in which he attempted to get at the problem from every angle. He considered carefully the added advantages that would be given him by a second year of the purely technical work. There was always the DeForest scholarship upon which he might depend for help through the remainder of his work. He continued his correspondence with Tesla and came to the decision that he should stake everything upon the Great Inventor's acceptance of him into the laboratory.

The whole future would unfold itself to him in such mental wanderings. He could see clearly his state in 10 years. The vision was one of a great man in an experimental laboratory. He was dealing with little known phenomena. Problems were presenting themselves in such a manner as to be entirely new to the history of science. There was no one to whom he might turn for assistance in their solution. He would then consider the years spent in post graduate study of the finer, more technical, more abstract studies and be thankful that they had prepared him for just such an occasion as the one presenting itself. Such day dreaming would give him a great freedom of soul for his work. In his diary he would declare in the loftiest terms that he would not let his life's goal be scratched from him by the plans of relatives. Then the usually went to Lake Whitney or some of the other nature haunts he loved when bent upon deciding such a problem as he walked home the vision of the family would flash across his mind and the spirit of the clan would protest itself strongly upon him. The latest reportage would take the place of the former high righteous resolve. By the middle of the first post graduate year—the beginning of 1927—he had fully resolved to take the Ph. D. He did not mention the fact at home except at such times as it would be received with some show of co-operation.

Thus it was that the success of the Princeton Book and the possibility of his getting out a similar volume for the inter-collegiate book regions and for future Princes made it possible for him to get in a large amount of propaganda for the second post-graduate year. Even under these conditions Charles' attitude was one more of dignified consideration than hearty co-operation. And since he was with his family more than he was with his soul in some chosen tower of nature it was inevitable that the family should lend the greater weight to his decision. Therefore, he declared himself as willing to go to work within the additional year, if a place could be found for him in Tesla's laboratory. The "Great Inventor," however, had a complete staff for the coming year so he could not use DeForest's services immediately, but wrote a warm letter in response to DeForest's query, stating that he would possibly be able to use him a year later. Faced with the absolute, Lee took the situation right in hand and forced the remainder of the family to his will. He declared he would continue his studies in the face of every objection, even if he had to "hire a furnace another year and eat at Jackson's."

MORE PLANS

With his next year fully planned, he again slipped back into the regular routine of laboratory work, lectures and reading. The paper on the "Equation" as he called his Wheatstone Bridge application of the Great machine was duly read and appreciated by the Math Club. Following its presentation there he worked it into form and submitted

FAHLBERG
MADISON, WIS.

for
perfect
Conductivity
in Radio

Reddy
HOT

Soldering Furnace

(Burns Denatured Alcohol)

and TESTED SUPPLIES

Safe Soldering at Home

It is now possible for the amateur to do light, clean work in his home soldering than hitherto the poorest conducting path necessary in radio work.

Mr. E. D. Fahlgberg, Professor of Metallurgy at the University of Wisconsin and Metallurgical Engineer with Western Electric Company, has developed Reddy Hot, the complete and safe home soldering furnace that has class work demands. Reddy Hot will heat pure iron easily to solder in two minutes and it.


Safe—Non-Explosive—Portable

The complete Reddy Hot Soldering Furnace comes with the following: Large soldering copper, detachable handle—Fine soldering tip, detachable handle for delicate soldering—Reddy Hot Household Solder—Highest grade general purpose solder on market—Cap Reddy Seal—Non-corrosive Soldering Flux—Specially adapted for Radio—Cap Reddy Press—Air Ammonia—Keeps tip clean and bright—Cap Reddy Rub—Alcohol—Keeps for quick cleaning and polishing—Complete directions with each outfit.

Ask your dealer for the Reddy Hot Soldering Furnace and supplies. If not available we will send direct, but a short time only, on receipt of price.

E. D. FAHLBERG MFG. CO.
MADISON, WIS.

Illustration and Description:
Write for more literature
and Reddy Hot properties
and samples. This
plan comes at 12.

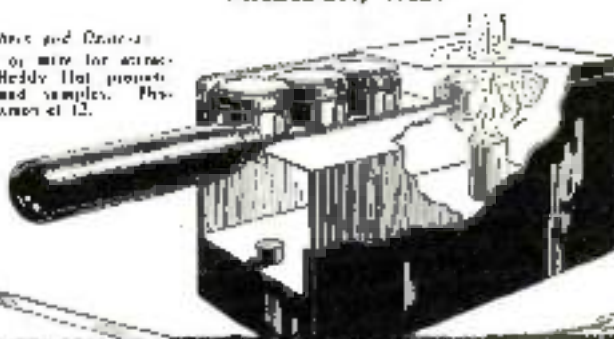

Price
\$1.50

E. D. FAHLBERG MFG. CO., Madison, Wis.

Send me prepaid one Reddy Hot Soldering Furnace for which I enclose \$1.50

My dealer's name is _____

Signed, Name _____

Address _____

RE-NU Radio "B" Batteries

Re-chargeable



Use Standard Standard 66's—50 Soldering—Male
Rechargeable—22.5—45 and 90 Cells
Send for free descriptive literature

STEINER BATTERY CO., Lancaster, Ohio



SOLDER WITH INSULATION


At Least 1,000 Miles More Distance

It is the chief reason if you can solder without
insulating the joints that you can solder.

If you are troubled by jointing—insulation—write
for your supply, read our "See Inside"

"HOW TO SOLDER RADIO SETS"

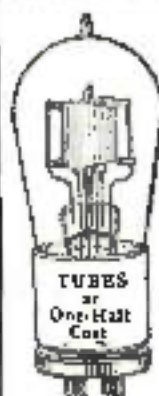Write for it
THE VALLEY FORD CHEMICAL CO.
Valley Forge, Pa.



Save 1/2 Cost of New Tube

Guaranteed Vacuum Tube
Repairs at Regular Prices

We try to maintain 24-
hour service.

All repairs guaranteed.
Tubes satisfactory or
money refunded.

Special discounts to
dealers.

Send order and bu-
red out tubes (must
be repaired tubes, returned
no col post, C.O.D.)

HARVARD RADIO
LABORATORIES

200 Old Colony Avenue
S.D. BOSTON, Mass.

Insure your copy reaching you each
month by Radio News—\$4.50
Harvard Publishing Co., 53 Park St.,

ing. This is good training for me, meeting business men.

This view is just another application of the previous one adopted both in his years at the museum and later at Shell. It seems that he demanded exactness more than anything else. The person who had any of the air of the dilettante was not for DeForest. His own training real and great grade combined with a lack of self-confidence in meeting others socially, all joined to make him a comparatively lone figure.

HUMAN NATURE

There was always something in the ordinary human equation that DeForest at this time never thoroughly understood. He realized this and strove to solve it. The most complicated thesis concerning the philosophical traits of Homo Sapiens were his delight. In such cases the conditions, the constants and the variables of the equation were thoroughly understood, for they were plainly set forth. It was like mathematics, physics or electricity; there were certain conditions given and certain laws by which to predetermine the results. With such problems DeForest was perfectly at home. He had a feeling, an instinct, which acted as a guide.

With the bulk of his fellow men, however, it was an entirely different matter. Never having had any great amount of social contact he had never become versed in the gentle art of pigeon-holing an individual upon first acquaintance. He was very real himself, and so, judging by the only standard he knew—himself—he expected others to fall into the same class. The results, as might easily be expected were many times disastrous. He had a pride that was nothing less than fierce. And it was invariably attacked in its most vulnerable spot, i.e., he was often laughed at.

He knew nothing of the generally used subtleties of society and business. Those bits of a society he isolated from time to time filled him with disgust. He could never consider a person who stooped to them as a friend.

It might have been one of Freud's compensations but nevertheless it was very true and very real that DeForest considered most social intercourse, as ordinarily indicated by the term "society," a complete waste of time. If it was a "compensation" it was because he felt a loss in not being able to join in it on account of deficiency in training. It is more probable, however, that his early formative years were so thoroughly given over to his chosen branch of work and knowledge that the other was completely crowded out. And since he never learned the rules of the "social game" he could never appreciate the value of the plays. He left him in very much the same position as the Englishman viewing an American baseball game for the first time. The whole thing appeared extremely silly.

Then his own reality and constant search after truth left him with an extreme distaste for the obvious (to him) superficiality and insincerity of the more socially inclined.

After each encounter with this philosophy which seemed to him so stupid he rushed back to his science with a refresh. And as time went on and the exposition of the whole of science's realm unfolded itself to him, he grew more and more to appreciate his mathematics, that wonder branch of science which acts as a guide to the other fields. At times he was actually ecstatic in its praise. Once such an occasion prompted him to declaim:

"The insight this mathematical study gives to the forms and laws of electrical (or of any natural) phenomena is wonderful. How this abstract generalizing can lead us to foretell most unexpected and startling results, about the real, final nature of which we can guess absolutely nothing is most mystifying. Yet how often are we thus diverted to the

Authorities Agree On the GEN-WIN Low Loss Tuner with the Silver Plated Primary

REG. U.S. PAT. OFF.

Radio frequency currents travel on the surface of a wire. Therefore, if surface conductivity is improved, the efficiency of the set will be increased. GEN-WIN Low Loss Tuners employ a primary of copper wire with an electrolytic silver surface, which tests have proven to be a far better conductor than any other metal. The GEN-WIN Low Loss Tuner is the only radio instrument incorporating this latest low resistance silver plated wire.



Circular of the Bureau of Standards
Radio Instruments and Measurements

Wire	Resistance per foot at 20°C.
Aluminum	1.68
Copper, standard	1.724
Copper, silver-plated	1.773
Gold	2.44
Steel	7
Brass	7.8
Phosphor	10
Iron	11.8
Ordinary silver, 10 per cent	20

New York Papers Say—

"Results were obtained that were actually a surprise. As the first since the silver was so great it attracted newspaper at least a block distant. To determine whether this exceptional result was due to some 'trick' the last of the conductors were examined by another laboratory and the results were the same. Electricity and results were good. Since selectivity and response as found in hand, it should be no surprise if this tuner has GEN-WIN's name for itself as a step ahead of the standard reputation for distance reception."

It makes Coast to Coast reception possible.

GEN-WIN Low Loss Tuner

marks a step in the advance of the design of Radio Tuners. Previously the lowest loss tuners were made of heavy copper wire wound so as to be self supporting. This kept dielectric losses low but did not take radio frequency resistance into consideration. The GEN-WIN Low Loss Tuner goes a step farther. It also reduces series resistance by using an aperiodic primary of special silver plated copper wire. Condenser tuned secondary and self supporting spider web feed back as well as of the latest low-loss design. A GEN-WIN Low Loss Tuner will enable you to build the most efficient regenerative set ever designed, both for DX and local reception. They are unconditionally guaranteed!




Pat. App. for

\$7.00

FREE With each Tuner we furnish free a complete set of detailed blue-prints (full size panel pattern, instrument layout, picture wiring diagram) for the GEN-WIN Low Loss Tuner set. Sold separately for 50c. All sets with each Tuner. Write for descriptive circular. Dept. H-4-22.

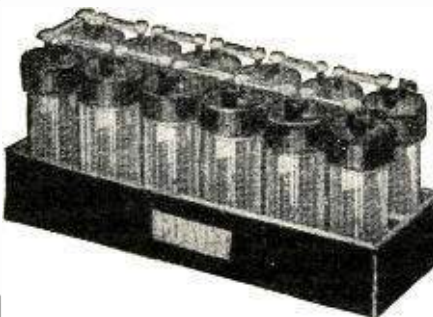GENERAL RADIO WINDING CO.
214 Fulton St., New York



To get the best results from your Radio Set, use Storage "B" Batteries.


Main Storage B Batteries

have 15 years of battery experience back of them. They are the best you can buy—insist on them. They increase reception, are re-chargeable from your lamp socket (with charger), and will soon save their cost. Write for circular today. Good dealers investigate.

MAIN RADIO BATTERIES, 7016 Euclid Ave., Cleveland, Ohio

Insert your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Experimenter Publishing Co., 55 Park Place, N. Y. C.

Only 127 Motors

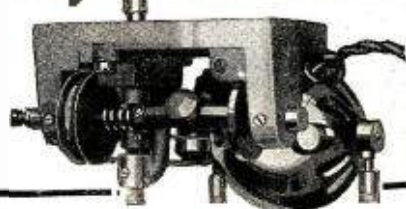

Left at \$10 Each

Ideal for home-made phonographs, experimental purposes and combination PHONOGRAPH-RADIO sets.

We have 127 small motors which are greatly underpriced for quick clearance. You will never again equal this low price, which this lot is sold.

They are universal motors, 110 volts, 60 cycle single phase, complete with turntable and lead socket for immediate use. 3400 R. P. M. Motor has 1" pulley with diameter 5/8" flat belt. Housed in highly polished, nickel-plated shell.

Don't lose out on this remarkable offer. Order your motor today. Tomorrow may be too late. **DO IT NOW!** Price \$10.00 f. o. b. Sugar, Illinois.

Exclusive Dealer

Steger & Sons Piano Manufacturing Co.

Dept. 48, Great Building CHICAGO, ILLINOIS

NATIONAL VELVET VERNIER DIALS

The Dial With The Velvet Finish

Prices:
3-inch \$3
4-inch \$2.50

FOR PRECISION TUNING
No backlash. Assembled by 11 hand workers. It's Just What You Want for a Radio!

NATIONAL COMPANY
Engineers and Manufacturers
414 Franklin St. Cambridge, Mass.

PATENTS

Hand Books on Patents, Trade Marks, etc., sent free. Over 28 years of experience, efficient service, and fair dealing assure fullest value and protection to the applicant. The Scientific American should be read by all inventors.

MUNN & CO.

617 Westcott Building, New York
Toronto, Ont., Canada, Pa.
Scientific American Bldg., Washington, D.C.
Times Bldg., 585 Market St., San Francisco, Cal.
Van Ness Bldg., Los Angeles, Cal.

solution that experiment later proves true and which would never be reached otherwise! I marked especially the wave surface on two plates close together. Perhaps this form of wave will be useful. Will mathematics ever lead us to an explanation as to a theory of the final or semi-final nature of matter and force? I don't believe that any system we have now will. Something radically different must be invented. I want to see a model of molecular action.

"My mathematical training this year I find already of the greatest practical value. Without it and every bit of it I could not read these books leading up to Maxwell. I want more and higher. Then I can expect to deal intelligently with light and wave phenomena along which lines I see lies the great future of electrical advance. Those who know, instead, dynamic construction and manipulation will soon be out of a job along lines of their training. And then they must learn again and start anew; the leaders and those to employ and reap benefits will be those who know rather a higher theory of waves and oscillations; and a transmission by these means of intelligence and power. So in this training I am already cutting loose and relying on the correctness of my own aim. Should I prove wrong I will be far behind and it will go hard for not knowing better my engineering. But I risk all on the cast of the die. I aim at Tesla. If I reach that I am a long way ahead. If I fail and seek elsewhere, what good chance have I? Especially after another year. But I shall not miss. I shall go on cutting orthodox lines towards my unique aim. The years will prove the soundness of my judgment."

This outburst seems to have filled him with further ambition, for the following day he applied himself with the utmost care to his experiments saying that he was entirely too careless in his work and must cultivate more precision.

He became so zealous in his work that he curbed every moment consumed in the mere business of getting a living. He and another student decided that the "Prom Bank" idea would go well at the Spring regatta and proceeded accordingly. They prepared the forms, sold the advertising and attempted to peddle the books. It meant more hard labor and time taken from his beloved experiments. He deplored the incursion of this "side line" upon his studies and "the time taken from his life." The only reason he considered it was because he planned on making enough money through the scheme to allow him to continue his experiments and study through the summer instead of working at something outside.

The venture was a miserable failure, however. Only a very small part of the books found buyers and the result was that DeForest soon felt the ire of his creditors. As soon as the accounts were balanced and the printers found that he did not have enough money to pay them, they went straight to the sheriff's office. It was only by wheedling and promises that he kept out of the hands of the law. He was forced to make a couple of quick loans from friends to pay off the most urgent of the debts.

With the financial failure of this venture, he was thrust back again into the old familiar dependency over money. He was called to New York for a completion of the business. He paid a call to Tesla in the hope of securing work for the summer as a computer, on the strength of his mathematical work. The great man received him, told him that he could take several of the sons of wealth at a remuneration to him (Tesla) of \$10,000 a year, but he refused, preferring, rather, to take the man who was in earnest and loved his work. He was extremely friendly in his reception of DeForest, but deplored the fact that he had a full staff

Poly Plug

Positive contact always maintained



The tension slot is the reason — a feature found only in Poly Plug. Permits the phone cords to be pulled and jarred without disturbing the contact a bit. The plug you have been wanting for.

It's genuine Bakelite too.

At your dealer or direct on receipt of **\$1.00** per 100.

75c "1000 ft."

Polymet Mfg. Corp.
70-74 Lafayette St., New York.

FURNESS BERMUDA LINE

(Bermuda Gov't's Official Cruise Line)

BERMUDA

Playground of Eternal Springtime

(Average Yearly Temperature of 70°)
Only Two Days From New York

Sailings Twice Weekly
From New York, Wed. & Sat.



Tickets good on either
Steamer, insuring unexcelled
express service, safety
and via Palatial new Twin-
Screw Out-fitting Steam-
ers.

S. S. "FORT VICTORIA" S. S. "FORT ST. GEORGE"

Modern ships—no passengers—no boats
swimming, tennis, sailing, fishing, horse racing,
skiing, riding, etc.

ST. GEORGE HOTEL, Bermuda. Beautifully situated,
furnished in the latest style, and service. Magnificent
view of harbor.

WCS' ROUTES

Delightful Cruises to the Isles of the Caribbean Sea.
For illustrated booklet on Bermuda, St. George, Barbados,
St. John, Antigua, visit

FURNESS BERMUDA LINE

24 Broadway St., N. Y., or Any Local Tourist Agent

QUALITY CABINETS

—Priced Exceptionally Low

Because We Sell Direct To You

No radio cabinet in the market compares with our
"Style A" model, designed for beauty and high
quality. And the low simplicity of their style, during
light from the maker. Cabinet colors and are for
yourself. Various cases, black, white, mahogany, etc.
cabinets in the market. Nickel-plated brass handles.
Built to equal any cabinet.

Size	Unfinished	Finished
12x12	\$1.95	\$2.95
12x18	2.10	3.15
12x24	2.25	3.30
12x30	2.40	3.45
12x36	2.55	3.60
12x42	2.70	3.75
12x48	2.85	3.90

The "Brother" is made in a small, neat, British
manufactured and unexcelled. It is built to last.
Cabinet is made of wood, or metal, or plastic, or
other material. The cabinet is made of wood, or metal,
or plastic, or other material. The cabinet is made of wood,
or metal, or plastic, or other material.

A. HALL, MICHIGAN, 75 Murray Street, New York

for the summer, but would try to make a place for him the following year. Lee wrote of the visit in glowing terms.

Seeing more clearly than ever his need for immediate funds he went back again to his inventing. The bicycle crane was at its height so he looked about for some invention which could be applied to it. He decided upon a system of hydraulic drive. A flexible tube was substituted for the chain drive. Filled with a liquid, oil preferably, the pistons operated rollers which compressed the tube, thus creating a pressure. At the rear, a stream set of rollers was attached to the wheel and was forced to revolve by the pressure in the tube. He sent the idea after working it out completely, to one or two companies in America. When they refused it he submitted it to an English firm. The idea was good except that the wear and tear to which the tube would be constantly subjected would cause it to wear out in a short time. Again he was disappointed, for the English firm pointed out the deficiency of the device and DeForest immediately saw it.


A few days following the disastrous rejection brought the close of the collegiate year. Always a happy time, with the constant stream of school activities, his disappointment at the defeat was alleviated and he slipped back into his old ways, enjoying the graduation events and continuing with deep interest his studies in electronics. He continued them all that summer.

ASTRONOMICAL WORK

A few weeks after the termination of the term he was given a place in the astronomical observatory taking photographs of shooting stars or meteors. This position gave him several weeks work and he lived a very merry, since the actual attention needed for the business at hand was not so great as to take him apart from his beloved speculations. When he was not employed with the stars the local gas company gave him work reading meters. All during the summer he continued his reading, and covered, apart from his regular text books a work by Poincaré on Oscillations, a volume by Sir Oliver Lodge dealing with the "Modern Science" and all the current scientific literature in the periodicals. One of these later was an extremely learned treatise upon the modern theory of the ether and vortex rings. Of this he said "My very soul is inflamed with desire, and burns with respectable zeal for scientific research. I must learn these truths. I must master the secrets of the search, for I am myself with the methods by which the evidence is found, probe deeply into these new fields which fascinate beyond all else."

"I shall learn to weigh an atom and circumnavigate a vortex ring—shall guess its shape and invent the few primeval knots and interwindings that make up the several elements—shall postulate the causes of the attraction and dare to carry back to the ultimate (the particle) and the final force (the impact) and dare not speak of affinity as such. For that our whole experience will not allow. I shall play how gold and silver may be interchanged, and reveal the reason for the universal course of energy, and produce the last and final destination. *Constitution, Electricity, Thought, Life, God.* These notions must be analyzed."

The summer drifted on into the following school year without the slightest ripple in DeForest's affairs. He studied all the time. The routine of lectures and matriculation were simply slight changes in the day's routine. He had continued some of his laboratory work during the vacation, so early in the second of his post graduate years he plunged into Herli's experiments. It was on October 11, 1909 that he began them. From that moment on, his interest, already at a high pitch, increased. Of the beginning of this work he wrote "Through-

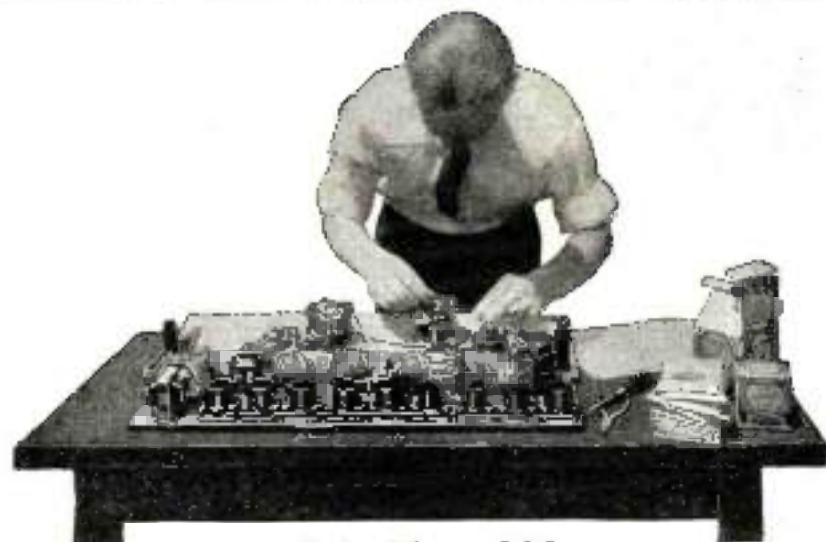

It's Easy!!!

Simply take a screwdriver and a pair of pliers—no soldering—assemble and wire your set in 2 hours with

THE RICHARDSON "Kan't-Go-Wrong" Wiring System

(Protected by copyright and patents pending).

You get Wires and Prints with each Kit—then

1. Paste picture prints on baseboard and back of panel.
2. Put every instrument on its picture.
3. Follow numbered system with the tagged and numbered wires.

Large Kit—Everything for a complete 9-tube Superheterodyne Set with push-pull audio (except accessories) fits in a standard Neutrodyne cabinet 7" x 26" \$95.00

Small Kit—Converts your Neutrodyne into a Superheterodyne and contains:

- | | |
|---|----------------|
| 1 Richardson Oscillo-Coupler (Nat. Freq.) | \$5.00 |
| 1 Richardson Tuned Transfer (12,000 meters) | 6.50 |
| 3 Richardson R. F. Transformers (12,000 meters) | 25.50 |
| | \$40.00 |

If your dealer cannot supply you, order direct from the factory.

RICHARDSON RADIO, INC.

Factory: 45-51 Lispenard St., New York City

Phone Canal 0100

5000
RADIO DEALERS
buy from
HUDSON-ROSS
123 W. Madison St. Chicago
Send for dealers' discount.

RADIO ENCYCLOPEDIA
FREE
MORWALK RADIO CORP.
1444 3d 66 READE ST., NEW YORK

PATENTS
O. L. PARKER
Formerly Member
Examining Corps,
U. S. Patent Office
PATENT LAWYER
1424 14th St., Wash., D. C.
Patents, Trade Marks, Copyrights, Patent Litigation
Handbook for Inventors, "How to Succeed in Inventing and Selling Inventions," and up-to-date

PATENTS
If you have an invention and desire to secure a patent, send for our Free Invention Book. HOW TO GET YOUR PATENT. Tells you Trade Method, air, and gives an outline and description for securing all the patent law details.
RANDOLPH & CO.
Dept. 459 Washington, D. C.

Insert your copy reaching you each month. Subscribe to Radio News \$2.00 a year. Experiment Publishing Co., 53 Park Plaza, N. Y. C.

BIGGEST VALUES EVER KNOWN Like New—5 Year Guarantee

Only \$2.00 Down 30 Days FREE TRIAL

You can have from \$33.00 to \$94.00 on the price of a new typewriter, and from \$34.00 to \$65.00 on the price of a rebuilt machine. If you buy a genuine LINCOLN Typewriter!

Genuine Self Starting Remington No. 10, \$38.95

Genuine Master Model ROYAL No. 10, \$49.95

Genuine Silent Smith L.C. SMITH No. 8, \$49.95
(Model No. 142 25)

Genuine Latest Model Underwood No. 4, \$49.95

Extremely like new. Guaranteed for five years. Spindle service for many years. All standard models, well known for dependability. Satisfactory guarantee of money refunded. 30 days' free trial. Write for full details. A popular willow.

Out Prices On All Standard Models

LINCOLN TYPEWRITER COMPANY

Radio's Leading Independent Typewriter Store

Dept. 16C 370 Broadway, New York City

Jiffy Blow Torch

Makes Your Connections Reception-Tight!

Building a one tube "flyer" or Super-Heterodyne? Jiffy Blow Torch is just the thing you need. You know the value of good soldering! Jiffy is on the job to give it to you.

Jiffy Blow Torch is self-blowing, lights instantly and burns with a blue, hot flame. Complete with heavy duty soldering iron, solder, non-corrosive flux and all accessories, \$2.50

At your dealer's or direct

Apex Stamping Company

Dept. 26 Riverdale, Ill.

"Make Your Marriage A Success"



Booths will heart you all you life if you marry strong and are physically fit. You know that exercise time cannot last. Vitality—energy are not lost with age. But your husband will believe you to be fit. It is a crime to waste his life and wreck his happiness. It is a crime to waste his life and wreck his happiness. It is a crime to waste his life and wreck his happiness.

STRONGFORTH—The new Science of Health. Prescribes will all have in relation your 5 major Powers, and Menstrual and Pituitary. Married and Paraphrased. A. B. Strongfort.

SEND FOR MY FREE BOOK "Promotion and Conservation of Health, Strength and Mental Energy"

including a life plan, loss of life for success, etc. It is a real life plan and a life plan. Send for it first. Name: LIONEL STRONGFORT

Physical and Health Specialist
Dept. 1880 Newark, New Jersey

out this work the most important part of it shall be my own observations of original phenomena and investigations which I may follow up. Sometimes it is fascinating—most of the time. Of course there is always an element of deadness due to the souring of profit—on me in which he seems to take delight."

He continued to follow out Hertz's work for more than two months until he had covered that work completely. It was during the latter part of these investigations, while he was doing some work with resonator wires at night that he was almost forced out of laboratory work entirely. The generator he was using was inadequate and Prof. Hertz knew it. On the night in question there was a lecture, illustrated with stereopticon views being given in another of the college buildings while DeForest was carrying on his experiments. During the course of the lecture something went wrong with the stereopticon lantern and the fuse was blown. No one at the lecture knew where to find the offending safety device and the lecture had to be terminated. Prof. Hertz at once offered the explanation that DeForest had drawn too much current and overloaded the line, blowing the fuse. He acted accordingly, going to the laboratory to prove the correctness of the assumption. On arriving there he forgot to look for profit when he found a number of nails driven into an old work table for suspending the wires of the resonator. He flew into a rage—a rage which had been gathering for months. He told DeForest that this "conclusively proved his total inability for research work," and to betake himself elsewhere to carry on his future laboratory work. As DeForest expressed it in later years: "That audience was dismissed by candle light, and I was dismissed by day light, next morning."


There was an alternative. An interview with one of the professors in the University post graduate school. Prof. "Buffalo" Wright gave him the use of a part of Stannard laboratory whence he moved his apparatus and carried out the remainder of his work.

THE winter moved on toward spring and DeForest moved closer to his goal. But with the opening of the weather there came the historic incident of the blowing up of the Maine and the attendant difficulties with Spain.

Always a hectic high-spirited person, extremely patriotic, the autumn between the sinking of the Maine, the investigations and the notes and the actual declaration of war, were for DeForest weeks of disorganization, arguments, quarrels, excitement and frenzy. One day he was fully decided to enlist at the first opportunity. The next he could not console himself to thrust all his hard earned knowledge upon the altar of Cuba's freedom. But as the time passed and the feeling grew more and more intense, the spirit of his ancestors found its place in his character. He settled the point with his mother and prepared to enlist in the Yale Battery.

Chance again played her false and he was too late by one man to be given a place in the company. But having decided that the war could possibly last no longer than six months and having assured himself that he could make up the time lost to his studies, he would not be hampered by the mere fact that he could not get into the company of his choice. Cuba had to be freed and he must help. When the Battery took train at New Haven for the upcountry camp a few miles out of town, DeForest, with a number of other aspirants, went with them as a camp follower.

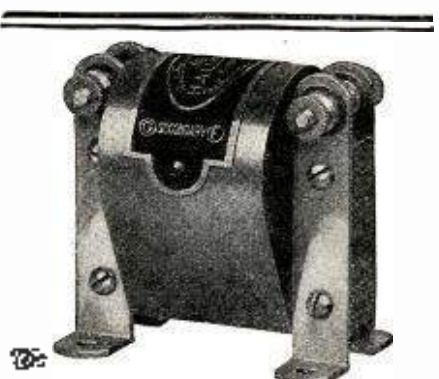For a couple of weeks he lived in hams and under bay stacks, eating with the soldiers




Halldorson Audio Frequency Transformer

Gives clear mellow tone, large volume and undistorted reception over the whole range of audio frequencies. It is neat and compact, the product of the highest technical skill—guaranteed to give satisfaction. Write for literature.

Price: Ratio 4:1 \$4.00
Ratio 2:1 4.75
Ratio 6:1 4.50

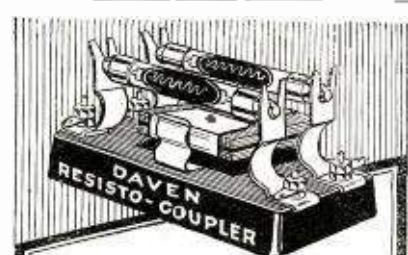THE HALLDORSON COMPANY
1772 Wilcox Avenue, Chicago



Imitation is the Sincerest Flattery

—and is irresistible with so fine and worthy a product. But an imitation rarely satisfies.

The discriminating ear will resist upon the original and only RESISTO-COUPLER. Price \$1.25

Sold everywhere

Get from your dealer. The Daven "RESISTO-COUPLER" by 2nd Daven. A practical hand-book on Resonance Coupled Amplification.

Price 25 cents.

DAVEN RADIO

"Resistor Specialist"

Newark New Jersey

SCIENTIFIC FIXED CRYSTAL DETECTOR BEST BY TEST

Price, \$1.50

Manufactured by SCIENTIFIC RESEARCH LABORATORIES, 502 N. Howard Street, Baltimore, Md.

If your dealer cannot supply you, order direct.



DEALERS

WE CAN SAVE YOU MONEY! Standard Guaranteed Lines. Send for latest Discount Book on Quality Radio Apparatus.

RADIO MATERIAL SUPPLY COMPANY
32 N. Wells St. Dept. 110 Chicago

and hoping for a place in the Battery. Tired of waiting, after a time, he decided to join the Connecticut National Guard. On May 18, 1898 he was mustered into the service of the United States of America as a private, first class. Later he became bugler with, as he said, "a horse to ride, two red stripes on my blue pants and no guard duty, hooray."

During his stay in camp he wrote long treatises on the war, its inefficiency and the rottenness of his own luck in getting no nearer the action than Long Island Sound. His company stayed in the original camp for the entire term of the fighting. Patriotism blossomed in him and became one of his strongest emotions.

The arduous, rough life of the army camp did him a deal of good physically. After the one sickness in his second year, he had never recovered full health on account of the large amount of work he was carrying and the scant chance for proper exercise. He was kept so busy with drill and the routine of army life that very little record of any sort is left which would be interesting to the reader.

Early in the following September the troops were returned to New Haven on furlough subject to call. Shortly after, they were mustered out. His back pay, given him at the time, allowed him to start his work again with a clean financial record. At last he was completely out of debt, due to the army pay and a gift from an old friend of his father.

With the return to his work he heaved a great sigh, dusted off his books, looked around the laboratory making plans for immediate experiments, selected his subject for the Ph.D. thesis and within three days was back into the harness as though nothing had happened. Indeed a record.

The fall of the year was spent in work of the most intensive sort—he was compelled to review in turn each of his last year's subjects completely forgotten during his five months in camp; Prof. Gibbs' Thermodynamics, Maxwell and higher mathematics, and pass a final exam in each in sequence. This all in addition to his new and difficult lecture courses. Never before or since, says DeForest, has he worked so steadily, uninterruptedly, for so many hours a week, week after week, month after month, as during the last year at Yale. By the New Year (1899) he was in the midst of his work on the thesis, was carrying out a great many investigations on his own account in the field of electric oscillations and Hertzian waves.

Time passed faster and faster as he came within hailing distance of his final college achievement, his Ph. D. degree. Work piled up and the strain constantly increased since the back work left undone through his enlistment in the army was not discharged until well after the first of the year. But when these tasks were finally off his mind, there was so much of the new that no respite afforded. He had time to think of little else save the eternal grind of reading, lectures and experiments. Nevertheless we still find long dissertations, philosophical and literary in his faithfully kept diaries.

Cold Weather Aids Radio Transmission

(Continued from page 904)

giving signals sharp by a radio compass, even in hurricanes, when long wave compass bearings are usually free from errors.

When cold waves subsided at the end of January, uniform transmission conditions were not restored, but an unstable condition persisted throughout the milder weather of February and March. The signals frequently fluctuated from high to normal vol-



A MICADON —its the condenser

The Micadon is the standard fixed condenser of radio! Extremely accurate because only the very best materials are used and because Dubilier condenser craftsmen assemble and inspect them. Simple to install because equipped with extension tabs for soldering and eyelets for set-screw assembly. Different capacities for different requirements. More than 90% of all sets made—by manufacturers and amateurs—use Dubilier Micadons. The preference of all these fans and experts has made Dubilier Micadons the standard.

Sold by all good Dealers

Dubilier

CONDENSER AND RADIO CORPORATION



Be a Motion Picture Photographer

Start in 1924 a week. Not plan enables you quickly to secure films at home. Rent 2 film cameras. Also obtainable in commercial, Radio Portulans and News Photographs.

CAMERA FREE

Stream Pictures in Professional 16mm Camera. Rent 2 film cameras. Also obtainable in commercial, Radio Portulans and News Photographs.



B-METAL, makes a lead bag in its made into a radio circuit and gives you way to utilize. Your dealer will accommodate you.

B-METAL
REPAIRING CO.
1119 S. 325 W. 10th Ave.
Detroit, Mich.

New — New — New
POCKET RADIO LOG BOOK
With pages for 36 stations. Indexed for each series.
IMITATION LEATHER COVER
Best present in making of 25 cents.
DEALERS WRITE FOR PROPOSITION
Radio News made of heavy black cardboard, 50c offhand.
THE FOX COMPANY
Dept. B, 247 So. Broadway, Los Angeles, Calif.

Perpetual Radio Fuse \$2.50
Bills in 1924 by two also four tubes with 1000 ohm resistor in each circuit, according to our instructions. KLEIN ELECTRONIC Transmitters, complete set including this set.
ULTA STROBOSCOPE Co., set of three.....\$10.00
Doublier Ray, set of three.....\$17.00
PEAKERS and JIBBERS we have an attractive series of illustrations.
THE STANLEY RADIO COMPANY, Manufacturing
2907 Leslie Street
Cleveland, Ohio

Insert your copy reaching you each month. Subscribe to Radio News—\$2.50 a year.
Experimenters Publishing Co., 51 Park Place, N. Y. C.

Standard KITS

ULTRADYNE Kit this new! containing 3 time "A" ultra-oscillator, 5 time "C" ultra-former, 2 low loss tuning coils, 1 low loss oscillator coil, 1 screen for ion couple, 4 matched fixed condensers.....\$32.00

INSTRUCTION BOOK.....\$3.50

SHAMROCK 2 Way REFLEX Kit, complete with ready for assembly.....\$34.00

FADA KRON-JONES NEUTRODYNE Kit, complete with 100% parts including parts including parts including parts including parts.....\$44.00

WONKITE NEUTRODYNE Kit, complete with 100% parts including parts including parts including parts.....\$70.00

ELCA 2 Way DUD-REFLEX Kit, complete with 100% parts including parts including parts including parts.....\$44.00

FRESHMAN MASTERPIECE - the new "Jumbo" Kit, complete with 100% parts including parts including parts including parts.....\$44.00

ATWATER KRON-JONES Kit, complete with 100% parts including parts including parts including parts.....\$44.00

GENWA COGNACAY Kit, complete with 100% parts including parts including parts including parts.....\$44.00

NOTE: THE DURELL BUYING DEPT. CAN OBTAIN FOR YOU PRAGMATICALLY ANY RADIO EQUIPMENT.

10% cash discount off above list prices when cash payments made.

MEMORANDUM SENT PREPAID

Send to Post Office or Railway mail order address New York City.

NOTE: THE DURELL BUYING DEPT. CAN OBTAIN FOR YOU PRAGMATICALLY ANY RADIO EQUIPMENT.

THE DURELL COMPANY
98 PARK PL.
N.Y.C.

AMPLEX GRID-DENSER

More Distance!

WATCH the DX stations come in the moment you replace your front end with GRID-DENSERS. A turn of the knob and you have the extra capacity for your set. That's the secret of the GRID-DENSER.

When you use the Amplex Grid-Denser and Grid-Denser GRID-DENSER by all circuits there is a marked increase in the capacity of your set. The Grid-Denser is a simple and effective device which will increase the capacity of your set.

FREE—Hook-up Booklet RN 12
AMPLEX INSTRUMENT LABS.
60 W. 17th St., N. Y. C.



Better than a fixed condenser

Big Savings



CATALOG FREE

Standard Parts of Quality

Save big money on standard parts and complete sets. Fast quality and prompt service guaranteed. Send for free catalog today.

GREAT LAKES RADIO CO.
205 N. LA SALLE ST.
CHICAGO, Dept. C-12

as your copy reaching you each month to RADIO NEWS — \$2.50 a year. Publisher Publishing Co., 33 Park Pl., N.Y.C.

ues, through apparently no connection with the weather. After March 12 the irregularities disappeared.

Observations on other long wave stations indicated that these large variations do not occur at a distance of 31 miles, but are large between 155 and 180 miles, and again decrease between 248 and 434 miles.

No definite explanation of this phenomenon has been found, although the cause is believed to be atmospheric. The connections with the coil waves suggest that either the part of the atmosphere concerned with the signal variations lies much below the Heaviside layer, between 50 and 62 miles or that weather phenomena are correlated with atmospheric action at much greater heights than has been supposed.

How Your Ear Helps Out Your Loud Speaker

(Continued from page 919)

trial filter which would cut off either the upper or the lower end of the scale at will. One man sang "ah" at a pitch corresponding to 145 cycles per second. While an observer listened, the filter operator began to cut off the lower end of the pitch scale. As more and more frequencies were blotted out the pitch remained unchanged, but the quality grew more and more, until with all tones cut out below 1,500 cycles the sound was merely a noise.

THE EAR AND THE PIANO

Results with the piano were impressive. When the C key (129 cycle) was struck there was a small change in quality when all below 250 cycles was cut off; when all below 500 cycles was cut off the tone was metallic; when all below 1,500 cycles was eliminated the tone was clanging. Yet through it all the pitch remained unchanged.

For the violin, clarinet and organ pipe the results were the same.

What had happened? All energy below a certain pitch had been suppressed, yet a note in that range was heard. What is the explanation?


When you strike a piano key you send off air waves whose frequency is that to which the string is tuned. This note is called the fundamental. Also you send off waves at twice, three times, four times, etc., that frequency. These are called the first, second, third, etc., harmonics. In the case of the C note on the piano (129 cycles) there are at least 10 harmonics. The number and relative loudness of these harmonics give the characteristic tone of the instrument by which we can tell a piano from a clarinet or a violin. They also make the difference between a \$20,000 Stradivarius and a cigar-box fiddle. And they make it possible for your ear to re-create the tones your loud speaker does not give out. Suppose the fundamental and the first two harmonics of the piano note C, are suppressed. We have eight or more harmonics left and from them the ear makes up a tone whose pitch is that of the missing fundamental. The tone doesn't sound like the original.

WHIMS OF TRANSMISSION

Of course, some orchestral instruments are transmitted by wire and radio better than others. In general, the higher toned instruments sound more like-like. Deep-toned ones, like the piano or organ and kettle drums, fare the worst.

Since the piano has so many over-tones, it is logical that cutting them off at the upper end would have quite an effect on the quality or naturalness of the transmission. This is true in practice; observers reported that cutting off the sixth and higher harmonics killed the brilliance characteristic of a fine piano. Curiously, a male voice is in-

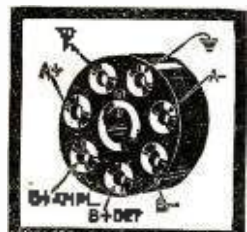Jones MULTI-PLUGS are supplied for panel mounting (see cut at right). Ear bracket mounting (see cut below) or for attaching to binding posts of any set (see cut at bottom of advertisement). Panel mounting type, complete with 8 foot cable, \$4.



Bracket mounting type, complete \$4.50

One Pull


One Pull (see cut at right) is a simple device which allows you to connect your set to any of the many different types of headphones without the need of a switch. It is a simple device which allows you to connect your set to any of the many different types of headphones without the need of a switch.

Jones MULTI-PLUG THE STANDARD SET CONNECTOR

Nothing else like it. Another group to remove. Set not with after. (see cut at right) is a simple device which allows you to connect your set to any of the many different types of headphones without the need of a switch. It is a simple device which allows you to connect your set to any of the many different types of headphones without the need of a switch.



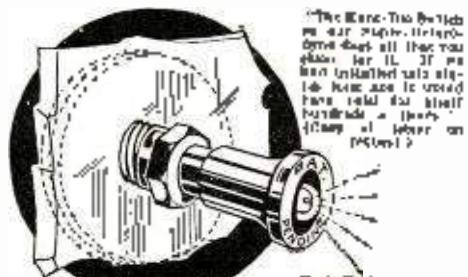From 400 to 700 HOWARD B. JONES 614 So. Canal St. Chicago



Push-Pull "A" type, 300 ohm input

YOUR MONEY BACK IF YOU BLOW A TUBE

When you buy a Kant-Blo, you get a money back guarantee. If you blow a tube, you get your money back. This is a simple device which allows you to connect your set to any of the many different types of headphones without the need of a switch.

Kant-Blo SIGNAL Lights on any Short Circuit

Only one Kant-Blo needed to protect any number of sets of any kind of radio tubes. This is a simple device which allows you to connect your set to any of the many different types of headphones without the need of a switch.

CANJO-KRAMER CO., Inc.
400 FIFTH AVENUE
NEW YORK, N. Y.
Telephone Murray 3-3525
Sole Distributors: Amer. Radio Company

YOUR CRYSTAL SET

will work 400 to 3000 miles if made by my plans. No tubes or batteries. Copyrighted plans \$1.00. Satisfied customers everywhere. Particulars free.

LEON LAMBERT
395 Eastman Bldg. Wichita, Kansas

Secure your copy reaching you each month. Subscribe to RADIO NEWS — \$2.50 a year. Experimenter Publishing Co., 33 Park Pl., N.Y.C.

ness more than a female voice by cutting off the unwanted frequencies above the same point, the richness of a man's voice comes from the presence of harmonics, while the soft notes from a woman's throat indicate the lack of harmonics in the region cut off by the filter.

Perfectly intelligible speech can be transmitted in which tones ranging from 500 to 2,500 cycles only are employed, but in order to obtain naturalness of effect comparable to that of the original, the range must be extended at both ends to include 100 cycles and 3,000 cycles. If music also is to be transmitted, the range must still be further extended to 5,000 cycles or more. To include so long a range requires close attention to the receiving apparatus, and the tendency for carelessly designed microphones, transformers, lines, etc., is to cut off both ends of the range.

In order to satisfy a radio audience that is growing more and more critical, it is necessary to transmit music with such naturalness that the listener can close his eyes and forget that he is not in the studio or concert hall. In other words, a great deal of work is being done in which he would care to hear it if he were free to choose his own program with respect to the source of sound.

SOME REVERBERATIONS NECESSARY

In the arrangement of a broadcast studio program which gives no reverberation is just as bad as one giving too much. It is generally recognized that a bare room is undesirable, as the reverberations cause one note or syllable to follow even into the next, producing an unpleasant timbre of sound; but it is a very common error to cover the walls, floor and ceiling of the studio as completely as possible with sound absorbing material, cutting off all echo and making the music sound "dead." This condition also makes it very difficult for a singer or vocalist to keep on the key, as they are accustomed to getting the push of each note from the reverberation of the preceding one.

When, as is often the case, the program is presented in an assembly room or concert hall, it is obviously impossible to change the acoustic properties of the room. The best solution of the problem is then in properly locating the microphone transmitter. When a symphony concert is broadcast, the best place for the microphone has been found to be from 30 to 50 feet in front of the orchestra and 10 or 20 feet from the ceiling. This location picks up the sound of the orchestra as a whole, and does not catch too much reverberation or incidental noise from the audience. It is not desirable to scatter several microphones through the orchestra, as with this arrangement the notes from some of the instruments will be transmitted with greater intensity than that from others, and the balance of the ensemble will be lost.

VARY AMPLIFICATION

Some one of the difficulty of artistically transmitting a program by radio is given by the fact that in one selection by a large orchestra, the volume of sound produced may be 100,000 times greater at one time than at another. As no broadcasting equipment has yet been devised which will handle such a range of intensities, it is necessary to vary the amount of amplification given the current from the microphone so that the sending apparatus will not be overloaded. This adjustment is made at the amplifier associated with the microphone, and calls for the greatest skill and care and the assistance of testing and recording instruments of extreme precision. A "volume indicator" bridged across the wires from the microphone follows accurately the strength of the current which is being delivered, and the operator varies the amplification so

"B-T for Mine— For a Radio Good Time"

Says W. Phillips of St. Louis, on Sept. 3rd, 1924, and adds:

"I am absolutely sold on the B-T tuner and condenser. I enclose a list of stations in all parts of the country to which I listened on the evening of Labor Day. I was indeed surprised to hear KGO at this time of the year, using only one stage of audio and no beat-planner. Had the family not arrived, I could have put them on the loud speaker."

He is one of thousands who have known B-T products for a long time and excellence and used them with the satisfaction found only in quality.

Read this from Kansas City, Sept. 11th, 1924:


"As an engineer and electrician using radio as a hobby, I have used dozens of radio sets, but none of the B-T variety. I have just built a well known direct and pure condenser set the first with which I was able to get a hot standard wire K-C was on the air. The first words anything I have ever used."—N. A. R. 3615 Irving Ave.

He means the original B-T tuner, designed two years before the magazines began talking "low losses." "It had the goods." It is still good thousands will use no other.

And here's a Radio Magazine Editor:

"I recently visited, using a loud speaker and two stages of audio, we brought in practically over a year of work and at 2:10 a. m. started on KGO 1270 and held it until 1:05 with full volume. Such stations as Dallas and Springfield, Mass., came in easily without interference from the powerful Chicago stations. These stations have been brought in a party, including KGO, showing that they were not accidents. Saturday evening, with Chicago stations on full blast, mostly the better stations were logged during the attempt to make a record."

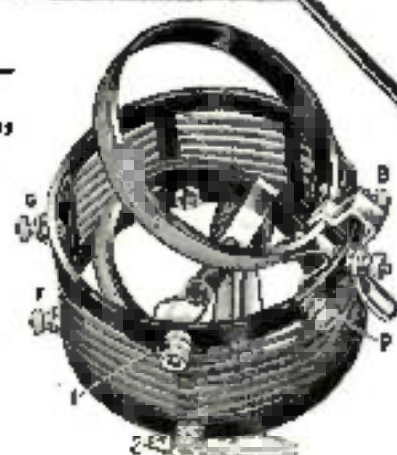He's talking about 1924 and the products pictured here.



The "B-T" is the first Low Loss Short Wave Tuner. Type SW covers 50 to 150 meters with a B-T 11-plate Type L Condenser. Type B covers 200 to 565. No caps in either case and price is

\$5.00

150 m.m. 1 plate...	\$4.25
250 m.m. 11 plates...	4.50
350 m.m. 23 plates...	5.00
500 m.m. 35 plates...	6.50



Want to know more?

Our circulars will tell you. Ask your dealer or drop us a line.

*We build good parts for
those not rich enough
to afford poor ones*

Bremer-Tully Mfg. Co.
Canal & Harrison Sts., Chicago

FREE Send your name and we will send you without obligation 100-page Radio Bargain Catalog
Liberty Mail Order House
Dept. 6912 104 Liberty St., N.Y.C.

REFLEX
Erie—Acme—Harkness
Dealers: Send for Discounts
HUDSON-ROSS
123 W. Madison St. Chicago

ELGIN SUPER-REINARTZ
The 2nd Major Export
2LO LONDON, ENGLAND
ONE TUBE
Send Stamp for Descriptive Circular
ELGIN RADIO SUPPLY CO.
207 E. Chicago Street, Elgin, Ill.

LUDWIG HOMMEL & CO.
Ludwig Hommel & Company
carry complete stocks of the most reliable radio apparatus.
Franklin Delmonico

Secure your copy reaching you each month. Subscribe to Radio News—\$2.50 a year.
Experimenter Publishing Co., 35 Park Place, N. Y. C.

THE SUPER-HETERODYNE

WILL BE YOUR EVENTUAL RECEIVER

**C-7 A LONG DISTANCE
CONCERT RECEIVER**



THE ROLLS ROYCE OF RECEPTION

THE super-heterodyne method of reception is used extensively by commercial radio companies and the armies and navies of the world, when the requirements are reception over extremely long distances without interference from nearby stations.

WE specialize in this type of receiver and after making exhaustive tests find the circuits and parts designed by the **EXPERIMENTER'S INFORMATION SERVICE** to be the best known in the art today. None of the so-called "new circuits" or modifications of standard receivers ever approaches the efficiency of a regenerative super-heterodyne employing a local oscillator. Good results can be obtained only when using laboratory apparatus and building according to naval engineering standards.

BELOW are listed models that have proven 100% satisfactory in the hands of advanced radio experimenters and navies as well:

MODEL C-7 Improved Regenerative Super-Heterodyne.
MODEL C Standard Long Super-Heterodyne.
MODEL N Antenna Adapter For Model C.
MODEL J 2-Range R. F. Amplifier for Model C.

All material we furnish is endorsed and recommended by the designers.
Immediate shipments can be made from stock.

WRITE TODAY FOR INFORMATION ON THE UNIT YOU ARE INTERESTED IN

NORDEN, HAUCK & COMPANY, Engineers

Office and Laboratories

1617 Chestnut Street

Philadelphia, Pennsylvania



Superior!

SUPERB
AUDIO TRANSFORMER
NOW IT'S SHIELDED!

The Superior Audio Frequency Transformer is now completely shielded—absolute protection against damage to the coil while mounting. Can be used with any amplifying tube with excellent results. Brings out the deep bass notes of the piano and the high, shrill treble of the violin better than any other transformer.

\$6.00 1 1/2 to 1
5 to 1

At good dealers everywhere.
Write for interesting literature.

FORD MICA CO., Inc.

33 East 8th Street

New York

DISTRIBUTORS

Wetmore-Savage
Boston


The Buckley-Robson Co.
Chicago

Coast Radio Supply Co.
San Francisco

Estelco Radio Co.
Bloomfield, N. J.

Radio, Limited
Montreal, Can.

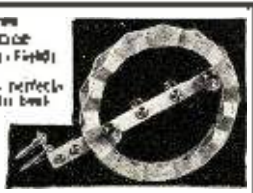New — 1925 — Type
Chubb Inductance
Concentrated Magnetics Field
Patent Pending
Complete coil unit with perfect
and shielded for use in best
resonant circuits.
These Radio
Components with
JAMES RAY
Patent 22
Mfg. Co.



SOLDERALL

Guaranty Metal Solder in Pure Form
Gives TO WIRE OR BAR SOLDER

Every Electrical
Connection needs
Solderall for perfect reception
25¢
L.S. BRACH MFG. CO. NEWARK, N.J.

that off tones will be audible to the listener and the extremely loud tones will not overtax the capacity of the apparatus.

RECEIVING TROUBLES

Receiving sets are found in so many varieties that no generalizations are practicable. Some of the most common sources of trouble, however, are these. Getting good results with a receiving set is largely a matter of arranging the various pieces of apparatus with a proper understanding of their characteristics. Transformers have been the cause of considerable trouble, although when the correct types are used satisfactory operation is obtained. Head-sets, amplifiers and loud speakers of correct design will also tend to prevent the distortion which too commonly characterizes the output of an amateur's outfit.

With the broadcasting apparatus now available, practically perfect transmission can be obtained, although with most of the loud speakers now on the market it is not possible to take the fullest advantage of this high class material. Recent scientific research, however, based on the science of acoustics as well as of electricity, is producing apparatus which will satisfy even the most critical.

A De Luxe Amateur Station

(Continued from page 928)

plifiers insure complete modulation with any type of microphone. During the past season a standard Western Electric "broadcasting" microphone and input amplifier was used for phone work and extremely high grade modulation was obtained.

Plate supply is obtained from a bank of Willard storage cells totalling 550 volts, or from an Esco motor-generator capable of delivering 1,500 volts to the tubes. An efficient filter system consisting of two 10-microfarad condenser banks and a total inductance of 70 henries produces a pure D.C. plate potential when the generator is in operation.

Power to run the plate supply motor-generator is obtained from a 5-K.W. gasoline driven lighting generator installed in a separate building.

The radio room switchboard controls the generator output, chargers for the six filament batteries, and the high voltage Willard cells.

In order to keep vibration at a minimum, the motor-generator is mounted on a heavy section of concrete matting, which in turn is located on a concrete support extending into the ground.

Filament and plate voltmeters are located on a small panel fastened above the transmitter. Suspended beneath this panel, which also holds the spare 50's, is a General Radio wavemeter. This provides an unusually clever method of maintaining a constant check on the operating wave-length. The wavemeter and the inductance of the transmitter are about 1 1/2 feet apart, and by merely turning the wavemeter dial an accurate reading is made possible. As the meter is in exactly the same position throughout the summer, any difference in the output of the set is instantly noticed.

The receiving equipment is the unusual feature of the station. There are 21 complete sets, ranging from an eight tube Super-Heterodyne to one tube receivers, in operation during the camp season. All amateur code work is copied on a home-made low-loss receiver. Head-phones are very seldom used, as practically all DX can be received with sufficient intensity to operate the Western Electric or the Magnavox loud speakers. Stations in every district, and in England, have been logged by this method nearly every evening, and it is apparently easier

to copy through summer static with a speaker three with hot plug.

Two power amplifiers, a Western Electric, and a Magnavox, step up signal strength to a degree great enough for loud speaker operation, and a Control tone connected across the amplifier reduces tube noise and takes the edge from static. Practically silent amplification is thus secured.

The QSL card of the station is quite original and is very cleverly arranged. The station description is printed within the figure of a crow in outline. A large numeral two in the center of the card completes the pictorial arrangement of the station's call. As a further take-off on the call the tubes are classified as quart bottles and pint bottles—meaning, of course, 50-watt and five-watt tubes respectively.

The operator at 2COW, Wm. S. Halstead, is well known to most amateurs because of his activities at old 2LH and at the Haverford College station 10VN, 32G and WANQ, where he is traffic manager of the Radio Club, and the Intercollegiate Radio League. His own station, old 2LH, now dismantled, was one of the leading amateur stations in the East and was awarded first prize several years ago by Radio News.

A Short Wave Adapter for the Broadcast Receiver

(Continued from page 925)

The socket is of the panel mounting type and has a shock-absorbing attachment. This latter feature is not absolutely necessary but is desirable since working at the high frequencies for which the adapter is designed, stability is both elusive and of the greatest importance. A UV-199 tube is used because of its low internal capacity. In making the connections to the socket flexible wire is used. Bus bar is suitable for the remainder of the set, but since its stiffness might pass on a measure of outside vibration, its use is prohibited in the socket leads.

For laying out the panel, pass a center line through the panel and drill the center line for the condenser shafts on this line. The condensers are spaced seven inches apart. The variable resistance and filament control switch may be placed as convenient. The lay-out depicted in the illustrations is good and may as well be followed.

If care is taken the coils may be attached directly to the rear of the condensers as shown. This is by far the best method and should be followed. The heavy wire of which the coils are wound is sufficient to support them and the advantage of short leads is gained, which advantage is extremely important in short wave work. No appreciable losses are incurred by mounting the coils close to the condensers because of the small amount of metal used in their construction. The coils are mounted at an angle of approximately 60 degrees so as to minimize the coupling between them. They are placed so that the condenser plates are out in their magnetic field.

The variable resistance having a range from one-half to 10 megohms, is of the commercial carbon compression type. No rheostat is used in the filament circuit since the tube is oscillating continuously while the set is in operation. An amperage may be employed for the protection of the tube.

As shown in the wiring diagram, the frames of the variable condensers are grounded. This is extremely important as any condenser used in the set must be constructed with the plates insulated from the frame and the frame so constructed that it may be separately grounded. This feature must be included in order that the body capacity effect of the operator becomes



LITERALLY thousands of people have come to know the joys of perfect radio reception through the Ferbend Wave Trap. Testimonials from all parts of the world continue to pour in, unsolicited, from those who have equipped their set with this marvelous instrument.

You, too, will find it the shortest, easiest, and—best of all—the least expensive route to clear, undistorted reception—without interference. Never reduces, but merely always increases volume. You can make your set selective to the point of perfection by simply adding a Ferbend Wave Trap. It will absolutely cut out any interfering station, no matter how loud, how close by or how troublesome. So why pay \$50.00 to \$200.00 extra for increased selectivity when you can buy it for \$8.50?

Guaranteed to free you any interfering station. The Ferbend Wave Trap is designed and manufactured complete by us after years of careful experimenting. It is not to be confused with imitations, hastily assembled shops, ordinary goods. This price is \$4.50. Shipments are made direct from C. O. D., plus a few cents postage. If you prefer, you can send your order in full with order, and we will ship postage prepaid. Clip and mail the COUPON today!

FERBEND ELECTRIC CO.

24 E. South Water Street

CHICAGO, ILL.



FERBEND Wave Trap

Always look for the Trade Mark A is your guarantee and the only one. The only one that will give you the best results. The only one that will give you the best results. The only one that will give you the best results.

- FERBEND ELECTRIC CO.
24 E. South Water St. Chicago, Ill.
Satisfaction Money refunded
- ☐ WAVE TRAP, Special package, 8 in. mounting, \$4.50, plus 10c. post. (No. 28-35)
 - ☐ WAVE TRAP, Special package, 10 in. mounting, \$5.00, plus 10c. post. (No. 28-35)
 - ☐ FREE BROCHURE on Radio News

Name ..
Address ..
City .. State ..

Learn Electricity in 12 Weeks

COYNE

EARN \$10 TO \$20 A WEEK

Electricity the Big Pay Field. Fascinating work. The only ELECTRICITY course in the practical—simple. You can make money on your own. No experience necessary. You can learn to work on all electrical appliances. Free course in 12 weeks. Electricity paid for you. Write today for more information. Write for course for FREE. Write for course for FREE. Write for course for FREE.

COYNE ELECTRICAL SCHOOL, Dept. 254-B
2320-2325 W. Madison St., Chicago, Ill.

DON'T MISS HALF THE MUSIC!

An unusual precision sound every note in the world. Coming from a small horn, every note is clear and loud. Every note is clear and loud. Every note is clear and loud.

MADONIA CLEAR SPEAKERS

Introduce a new melody to the human ear—because the clear, rich tones from which these speakers are made is many times louder than most. (100%) loud, clear, and clear. (100%) loud, clear, and clear. (100%) loud, clear, and clear.



Insure your copy reaching you each month. Subscribe to Radio News—\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



Book No. 1

Stand with full de-
scribing 1147 Radio
sets. Hundreds of home
built sets. One that
could easily have been
corrected. The E. I.
Company has a new
book that will
help you avoid all the
common mistakes and
building your Radio
set.


PRICE 25c



Book No. 2

The man who wants
to build sets should
read this book. It is
the most complete
and practical book
on the subject. It
gives the principles
of construction and
the practical details
of building.


PRICE 25c

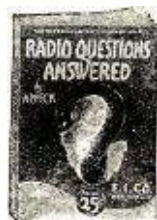

Book No. 3

Question No. 1—What
is Radio? This is a
complete book on the
subject. It gives the
principles of radio
and the practical details
of building a radio
set.

PRICE 25c

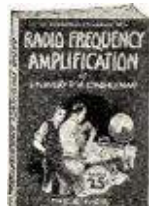

Book No. 4

Discover how to
amplify radio
signals. This book
gives the principles
of radio frequency
amplification and the
practical details of
building a radio set.


PRICE 25c



Book No. 5

Don't struggle in the
dark. This book
gives the principles
of tuning a radio set
and the practical details
of building a radio set.

PRICE 25c

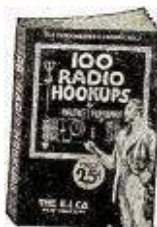

Book No. 7

No better book for
your work. This
book gives the principles
of radio and the
practical details of
building a radio set.

PRICE 25c

IN EVERY HOME

A Radio Well Understood

Complete satisfaction from any radio outfit is usually based on the operator's knowledge of the fundamentals of operation.

The E. I. Co. books, as shown here, are expressly written, by radio experts, for the man who wants to understand his radio receiving set. The important points are all covered and fully explained in simple, everyday language.

Each book consists of 64 pages bound with stiff board covers and handsomely printed in colors. Their handy pocket size enables you to keep them ready at all times.

READ THE DESCRIPTIONS OF THE BOOKS SHOWN HERE. PICK OUT THE BOOKS YOU NEED OR IF YOU DO NOT SEE JUST WHAT YOU WANT WRITE FOR OUR FREE LIST OF PUBLICATIONS.

ON SALE
AT ALL RADIO STORES
AND NEWSSTANDS

Each



Prepaid

The E. I. Company

Sales Agents


The Consrad Company
233 Fulton Street New York City

Consrad

RADIO'S FOREMOST PUBLISHERS—Everything in Books, Patterns and Diagrams

Everyone who
wants a radio set
should know the
principles of
radio. The E. I.
Company has a new
book that will
help you avoid all the
common mistakes and
building your Radio
set.

PRICE 25c

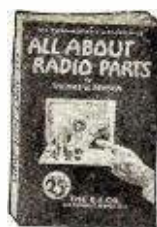

Book No. 8

The Vacuum Tube is
a marvelous piece of
mechanics. A short
study of it will
show you the
principles of its
operation. This
book gives the
principles of its
operation.


PRICE 25c



Book No. 9

Everyone knows the
vacuum tube. But
how does it work?
This book gives the
principles of its
operation and the
practical details of
building a radio set.


PRICE 25c

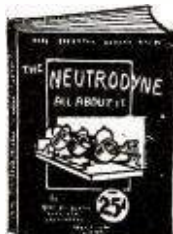

Book No. 10

The Neutrodyne is a
new type of radio
circuit. It gives the
principles of its
operation and the
practical details of
building a radio set.


PRICE 25c

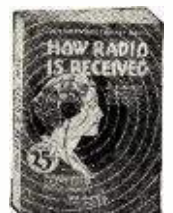

Book No. 11

Everyone who
wants a radio set
should know the
principles of radio
reception. This
book gives the
principles of its
operation and the
practical details of
building a radio set.


PRICE 25c

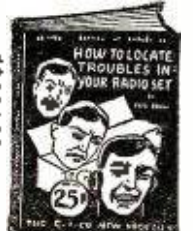

Book No. 12


Just off the press.
This book gives the
principles of locating
troubles in a radio
set. It gives the
principles of its
operation and the
practical details of
building a radio set.

PRICE 25c

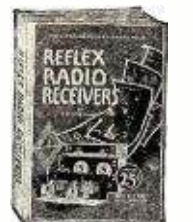

Book No. 13

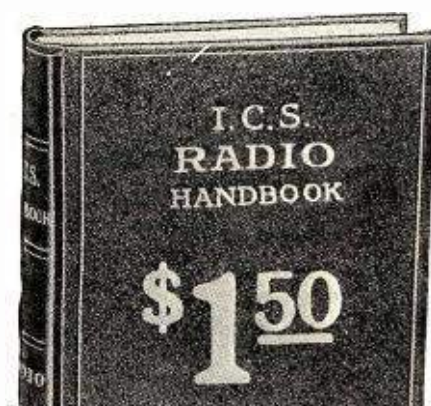Insure your copy reaching you each month. Subscribe to Radio News—
\$2.50 a year. Experimenter Publishing Co., 53 Park Place, N. Y. C.



Every Question ANSWERED for only \$1.50

At last you have under one cover a
Complete Radio Handbook
New Leatheroid Edition

Compiled by HARVEY F. DART, E.E., formerly with
the Western Electric Co., and U. S. Army Institute
of Radio. Technically edited by P. H. DODGE
514 PAGES

NO MORE need you turn from book to
book, hoping to find what you want.
It is all here, in 514 pages crammed full
of every possible radio detail. Written in
plain language, by engineers for laymen.
Clears up the mysteries, tells you what you
want to know.

IT EXPLAINS: Electrical terms
and circuits, antennas, batteries,
generators and motors, electron
(vacuum) tubes, every receiving
hook-up, radio and audio frequency
amplification, broadcast and com-
mercial transmitters and receivers,
super-regeneration, codes, license
rules, etc.

Under one cover. Yes, it is all in one
volume of 514 pages of clear type with
hundreds of diagrams and illustrations.
Takes the place of eleven or more spe-
cialized texts, each costing from two to ten
times the cost of this single book.

Send \$1.50 today and get this 514-page
I.C.S. Radio Handbook—the biggest value in
radio to-day. Money back if not satisfied.

TEAR OUT HERE

International Communications Company
Inc. 2321-L, Broadway, New York

I enclose \$1.50. Please send me—postpaid—
the 514-page I.C.S. Radio Handbook. It
is understood that if I am not entirely satis-
fied I may return the book within ten days
and you will refund my money.

Name.....

Address.....

Please have it sent to me at the
above address.

The Greatest Radio Tube Set on the earth for the money

"THE J.A.H.C."—Range 1000 miles. Beautiful
Panel Cabinet, size 24 1/2 inches. Equal to
sets costing many times more.
Agents making \$25 to \$50 a day selling this
magnificent Radio.

Sample
Priced \$10.00 Looks
Like \$50

DISTRIBUTORS WANTED

International Radio Co., Dept. RN
52 W. 42d St. New York City

One year copy teaching you each month
in RADIO NEWS—\$2.50 a year.
Publishing Co., 37 Park Pl., N.Y.C.

to the uninitiated, like an unsurmountable
problem, it is really quite simple.

In working out such a control system, it
must be considered that the present signal
system utilizes the two rails to carry direct
current as supplied from a storage battery,
to actuate the signal mechanism. This cur-
rent flow is quite small, being about one
half volt at from 250 to 300 milliamperes.
When no train or other metallic obstruction
is in the particular track section protected
by the usual signal lights, the lights are
normally dark. However, if a train enters
the preceding section, approaching the
signal, the effect of its wheels and axles
short-circuiting the rails causes the power
light to show, dependent of course upon the
conditions in the block thus protected.
Obviously, then, any control system which
utilizes the tracks to carry an electric cur-
rent will experience difficulty in preventing a
short circuit of the rails by the control
wiring, thus rendering the block system
practically useless. It, therefore, develops
that a current of some characteristic which
will not cause such a condition be used.
Radio frequency currents solve this problem
admirably, for they may be fed into the
track through an ordinary fixed condenser,
passing through it easily, whereas the direct
current used in the signal mechanism is
effectively blocked by a condenser. Further
precautions to keep the radio frequency en-
ergy from entering any signal equipment
are taken by inserting proper radio fre-
quency chokes in the direct current wiring.

Feeding radio frequency current into the
rails may sound very simple, but it never-
theless presents a number of complications.
Using a vacuum tube oscillator, connected to
be the most efficient producer of radio fre-
quency currents, makes it essential that a
comparatively high voltage be fed into the
tracks, even though the current be kept low.
When it is considered that with the latest
type of railroad tie, which is zinc-treated,
a resistance of but about 1/2 ohm per section
(1,000 to 3,000 feet) exists between rails,
it is a difficult proposition to keep the re-
latively high voltage from leaking. Radio
frequency will follow the two rails for a
distance that presents less resistance than
that between rails, but once the stretch of
track increases its resistance, as it is bound
to do with length, the energy naturally fol-
lowing the easiest path returns across the
ties to the other rail, rendering the energy
useless beyond the leakage point. Such a
path has been found to be but a few hundred
feet from the point where the energy is fed
into the rails, whereas it is essential that a
good bit of the initial energy reach the ex-
treme end of the block, sometimes 5,000
feet distant. Leakage conditions are almost
double during rainy weather or whenever
the ties are covered with moisture. This
makes it essential that practically double the
required energy be available in the rails
during dry weather to take care of the wet
condition.

After considerable exhaustive experiment-
al work had been conducted, it was finally
determined to use one or both rails, as ex-
perimental work proved most desirable, and
a wired circuit carried on poles along the
right-of-way. Any leakage effects, steady
or varying with weather conditions, would
then present no obstacle to the radio fre-
quency energy. Tests made with this sys-
tem established the fact that it was easily
possible to get about the same energy at the
extreme end of the block as at the entrance
point, and accordingly, experiments are
being conducted on this score.

Once the proper value of radio frequency
current is established, and maintained in the
rails, it requires only for a suitable loop
pick-up device to be installed on the loco-
motive, with the pick-up loop in inductive
relation to the rail or axle, as found most
desirable. The current thus induced in the

What Makes Metallic DURHAM Fixed or Variable Grid Leaks Noiseless?

CIRCUIT noises are caused by uncontrollable
resistance changes—unavoidable in the
old style leaks. Carbon, graphite, India ink,
pencil marks—all vary greatly with tempera-
ture and atmospheric changes. Metals alone
remain constant.

DURHAM Fixed Metallic Grid Leaks are the
only truly noiseless. A case metal deposited
on glass has its resistance value fixed for all
time. Noise is impossible.



DURHAM Variable Metallic Grid
Leak—in 3 equal—have a permanent
range of the value marked. Constant
variation is by smooth sliding glass set.
For any particular wiring, operation or
application see the DURHAM Grid Leak.

DURHAM Metallic Grid Leaks will fit
your present holders. But for new
sets, the new DURHAM base has
more convenient—plain, condenser
clip, or double for resonant amplifiers.

Prices:—

Fixed, 28 pins

10¢ + 75¢

Variable

3 ranges, 75¢

Models

30¢ + 40¢



All about Resistance Amplifiers—75¢

Build a distribution amplifier. Parts for any
range can be had from one good transformer. Com-
plete detailed instructions booklet, 50¢. All your
dealer's or postpaid.

Subscriptions: Circulars

DURHAM & CO., Inc.
1930 Market St., Philadelphia

BUILD-UP

MICA CONDENSER

Patent Pending



Insure high efficiency and the
Build-Up feature enables the
operator to obtain any definite
capacity from .00025 to .001
by simply adding extra plates
of copper and mica to the
Build-Up base.

Each alternate copper and
mica plate has a capacity of
approximately .00025 Mfd.

Build-Up Mica Condensers
of the following capacities,
each assembled complete in
cabinet:

.00025 Mfd.	File Price	40¢
.0005 Mfd.	File Price	50¢
.001 Mfd.	File Price	55¢
.002 Mfd.	File Price	60¢
.005 Mfd.	File Price	65¢
.01 Mfd.	File Price	70¢
.02 Mfd.	File Price	75¢

Extra envelope containing 20 copper and
mica plates, or sufficient to build up a condenser
from .00025 to .006, has price 25¢.

Table showing required number of plates
needed for any capacity is furnished with each
condenser.

Ask your dealer—or order direct.

CHAS. SCHINDLER

1401 W. University Ave., Toledo, Ohio

DEALERS SAVE MONEY

By Ordering from Our Bargain
Catalog of Nationally Advertised
Radio Goods, Write for It Today!
AMERICAN RADIO CO.
Dept. A 6 WEST 14th ST. KANSAS CITY, MO.

pick-up coil is carried to two third circuits employing a variable condenser and a sensitive relay, capable of operating on minute values of current $\frac{1}{2}$ milliamperes or so. The relay obviously, upon closing, equalizes any desired electrical circuit.

In actual practice, radio frequency energy of a wave-length of, say, 1000 ft., will be pumped into the track when the oscillations are started by applying proper plate and filament potentials to the vacuum tube oscillator. This will be started and stopped by an additional contact on the present signal relay mechanism, so that the train control current is 'in' into the rails only when the block signals are in circuit for that particular block. This prevents the constant use of current by maintaining the oscillator always in a condition of oscillation.

Such 10,000-meter waves, following the rail, are picked up by the loop placed in inductive relation thereto, and actuate the relay in the circuit that is tuned for 10,000 meters. Upon closing, this relay will cause a light (green or "clear") for purposes of illustration) to light in a miniature signal tower in the engine cab. The engineer then knows the traffic conditions ahead of him, and the train is left entirely within his control.

Should the main signal light, beside the track, show yellow, or "caution", however, a 12,000-meter wave would be pumped into the rail and activate the other tuned circuit, which has been adjusted to resonance, lighting a yellow ("caution") signal in the cab indicator, and through additional equipment, warning a speed control governor, automatically reducing the speed of the train to a predetermined speed of say, 30 miles an hour. This is done without the engineer making a move.

Suppose, however, a "danger" condition exists, and a red light shows beside the track. In this case, the oscillator is not energized, and no radio frequency current enters the rails. Both relays in the cab being upon contacts are engaged, which light a red signal in the cab indicator, and apply the brakes, slowing the train to a permissive speed of 10 or 15 miles an hour, or bringing it to a complete stop as the governor may be set at the signal.

Obviously, then, as no enemy produces the danger indication, the failure of the control system, such as the destruction of a tube, the interruption of the circuit, or the rails short circuited by some object, would also produce the same identical danger condition aboard the locomotive. The great value here, though, lies in the fact that regardless of whether the engineer is alert and on the job, or whether a sudden attack of heart trouble has left him without life, the train is perfectly controlled in harmony with the traffic conditions ahead.

Many little difficulties have been encountered; for instance, the effect of the train moving through the block producing a constant change of wave-length was found necessary to overcome. This was done by the use of an intermediate circuit, capacity coupled to a Hartley oscillator, and inductively coupled to the track. This appeared to give the tube the same action substantially, as the impulse type of spark radio transmitter; the "antenna" (rail) circuit oscillated at its own natural frequency, regardless of what the oscillator was doing. Incidentally, the same circuit, applied to a vacuum tube radio telegraph transmitter, produced remarkable results and the writer intends to investigate this further.

Continuous train control seems to offer a solution to the great question of 100 per cent protection to the traveling public. Hundreds of wrecks have been investigated by those interested in train control work, and in each and every instance it was found that the human element somewhere, had been

Enjoy Radio Without Noise

Thousands of Radio Fans are enjoying Radio without noise.

You can, too.

No longer do you have to be annoyed and have the joy of your radio set spoiled because of hissing, sizzling and other discordant noises.

The Ray-dio "B" Storage Battery—the most remarkable development since radio became general—eliminates the causes of these noises and makes constant retuning unnecessary.

Enjoy your radio 100 per cent.

Write at once for full details which tell about the greatest radio battery ever made.

Jordan Battery Co.
Ypsilanti, Mich.

Dept. 1

R^{RIGGS}_{RECTIFIER} Model C

Price: \$10.00

Franklin D. Roosevelt
Quincy House, 100 Madison Avenue
New York 17, N. Y.
JULIUS ROSENBERG CO.

Page 324

பிழைப்பு, பிழை

DEALERS

WE CAN SAVE YOU MONEY!
Standard Guaranteed Loans. Send in loan
Discount Book on Quality Radio Apparatus.

RADIO MATERIAL SUPPLY COMPANY
11 N. Wabash St. Dept. 117 Chicago

RADIO FANS

Frank D. Payne, RADIO AUTHORITY,
Sons:

"The only initial war to determine if we can take full control of America is by taking it all at once."

YOU NEED THIS

**POCKET
VOLT METER**

WOLFE LYN .50

Heat Absorption at surface of roof
If your house can't handle this
and energy costs too much, you

Decker's and Johnson's, Ser. 100-2-122174 is identified
also list of police logs: telling a story with a 2000-01

CHARTERED BY E. D. JACKSON & COMPANY
Bank of America, N.Y. & Co., Inc. 100 Wall Street, New York, N.Y.

The Standard Super-Heterodyne

Build It Yourself With This

SUPER PATTERN



The Consrad Method

As illustrated above, "Consrad" patterns are the simplest ever originated. You have blueprints, full size, and an instruction book to follow. You cannot go wrong. Write for our full list of publications on reflex, crystal and tube hookups.

All Patterns are complete with blueprints and instruction pamphlet.

Write for our Free Catalogue of Modern Radio Hookup Patterns and Radio Books.



THE simplest, greatest and most revolutionary Radio Pattern ever designed. The complete Super-Heterodyne as shown above can be built with this pattern by anyone. The secret of the marvelous simplicity is the gigantic blueprint that are drawn the full size of the super-heterodyne itself. The blueprint at the working diagram measuring 19½" x 44" as drawn by a professional engineer, every conceivable measurement is given right on the pattern so that you need not measure a single wire.

The Blueprint of the panel layout is made up so that all you need to do is to lay it flat on the panel and then take a pencil and carefully trace each hole as shown because the blueprint measuring 19½" x 44" is the exact size of the panel required.

Then extra comes a 16 page booklet, size 8" x 12", the most complete booklet of this kind ever made up. It describes every little detail, shows you how to proceed in building. What parts are necessary, how to set them up and lastly how to operate them.

The price of the complete pattern, comprising two blueprints, size 19½" x 44" and a 16 page booklet size 8" x 12" and enclosed in an extra heavy cardboard box printed handily in two colors is only \$1.00.

Here is the most wonderful opportunity for every radio amateur to have the finest set yet designed for radio receiving.

GET YOUR ORDER IN EARLY OR SEE YOUR DEALER TODAY

ON SALE AT ALL RADIO AND NEWS DEALERS

Price \$1.00 Prepaid

or Direct from Us

The CONSRAD COMPANY
233 Fulton Street New York City

Consrad

RADIO'S FOREMOST PUBLISHERS—Everything in Books, Patterns and Diagrams

broadcast stations, bringing the total to 1001; the removal of the marine sparks on 300 meters from the broadcast band, and the designation of 600 meters for calling and distress calls only, clearing the air program of code interference. A re-classification of broadcasters and the transfer of all Class C stations from 360 meters, improves the situation further, while the re-zoning of the country into six zones will further aid broadcast operation. This will provide a separate zone for the New England States, including New York City and part of New Jersey. Zone Two will comprise the remainder of the Atlantic states, Pennsylvania, West Virginia, and the western part of New York. Zone Three, Michigan, Ohio, Illinois, Kentucky, Tennessee, West Georgia, Alabama and Mississippi; the Central States are divided horizontally, the southern states forming Zone Four, and the northern, Zone Five; all the Pacific States with Idaho, Utah and Arizona, constitute the Sixth zone. When assigning experimental stations high power licenses, the Department intends to use this system and in assigning new Class I station waves.

Marine communications will be handled on 660, 730, 875 and 706 meters, giving the ships five channels instead of two, also removing coast-wise interference and congestion. Amateurs retain substantially the same wave bands as heretofore, but benefit by low wavelengths assigned temporarily by the Department recently; all of which assures the amateurs an increase in channels over what they had a year ago, and permits greater latitude in 24-hour operation.

The conference voted not to interfere with broadcast programs, discouraging censorship definitely. The conferees found that simultaneous broadcasting of national events is practical over a large area and believes that nation-wide broadcasting by interconnecting stations deserves encouragement.


Additional funds for the administration of matters radio were urged of Congress in a special plea of the whole Conference.

Hiram Percy Maxim, President of the American Radio Relay League, reported as chairman of the subcommittee on amateur problems. It was recommended by this committee that the use of receiving sets capable of radiating be discouraged for use on the short wave relay broadcast band.

In order to eliminate as far as possible the interference from amateur transmitting sets, it was recommended that, except in case of transmitters using coil antennas or loops, of transmitters using roof antennae or loops, radiating system or a device producing an equivalent effect be required in all amateur transmitters. All of the amateur bands shall be open to telegraphic communication by tubes or devices producing similar effects, except those utilizing forms of I.C.W. obtained by mechanical intervention on radio frequency circuits. A band of 170 to 180 meters was assigned non-exclusively to amateur radio telephone and I.C.W. stations which employ apparatus in which one of the radio frequency circuits is mechanically interrupted. This keeps those types of amateur transmitting sets which are capable of producing the greatest amount of interference well within the largest amateur band.

Previous to his remarks, Secretary Hoover had been thanked personally for his service to radio science, on motion of Earle C. Anthony, of California, who said: "Mr. Hoover has practically given up his time day and night to this work, and it shows the interest of our Secretary in radio. I would, therefore, like to call for a vote of thanks to Mr. Hoover for his personal interest." The motion was seconded and carried with applause.

CELORON

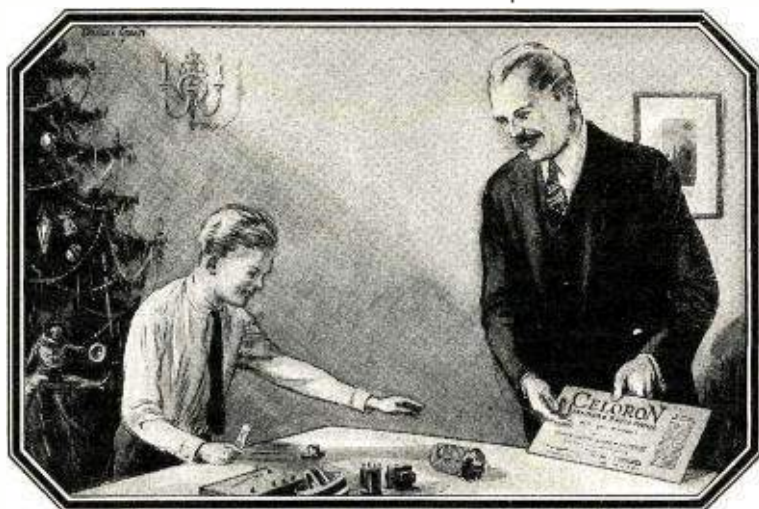

"Gee, dad, that's a peach!"

CHRISTMAS morning—and with it gifts that make the radio fan's heart skip a beat or two. There are cubes, batteries, a tuning coil and beside them a beautiful, glossy-black panel. The best part about the panel is that it is a Celoron panel.

Dad used his old bean when he selected a Celoron panel. He picked Celoron because it is a bakelite panel and furnishes the insulation that delicate instruments need to give the best results. He knows that it doesn't pay to skimp in buying a panel.

Celoron has high dielectric strength and it is practically indestructible. You can drill, tap, saw and bore a Celoron panel without fear of its chipping or cracking. It is not affected by atmospheric changes, and it never softens, warps or buckles.

You can buy Celoron in black or mahogany finishes. These never lose their luster or become discolored. They improve with age.

Celoron has been tested and approved by the U. S. Navy, the U. S. Signal Corps, by leading radio manufacturers, and by thousands of radio fans all over the country.

Ask your dealer to show you his assortment of Celoron bakelite panels.

CELORON A Bakelite Panel

Diamond State Fibre Company
Bridgeport, Pa., and Chicago, Ill.
Branches in Principal Cities
Toronto, Canada London, England

Send for FREE booklets

We have prepared two interesting booklets, "Getting the Right Hook-up with Celoron" and "Vulcanwood—the New Cabinet Material," which contain many valuable suggestions for building and operating a radio set. Send for your copies now. They are free.

Diamond State Fibre Co., Bridgeport, Pa.
Please send me without charge copies of "Getting the Right Hook-up with Celoron" and "Vulcanwood—the New Cabinet Material."

My radio dealer's name is

Name


Address

"Lighting Fixtures"
READY TO HANG
(Direct from Manufacturer)
Completely wired incandescent lighting
and all fixtures No. 30.
(Just off the Press)
Special Proposition to Dealers
ERIE FIXTURE SUPPLY CO.
STATION B ERIE, PA.

Write for complete illustrated FREE Catalog of
PARAGON
Reg. U.S. Pat. Off.
RADIO PRODUCTS
ADAMS-MORGAN CO.
1 Ards Place Upper Merishdale N. J.

KESTER Radio SOLDER
(Rosin-Core)
If your dealer cannot supply you
send us 25c in postage
CHICAGO SOLDER COMPANY
CHICAGO, U. S. A.

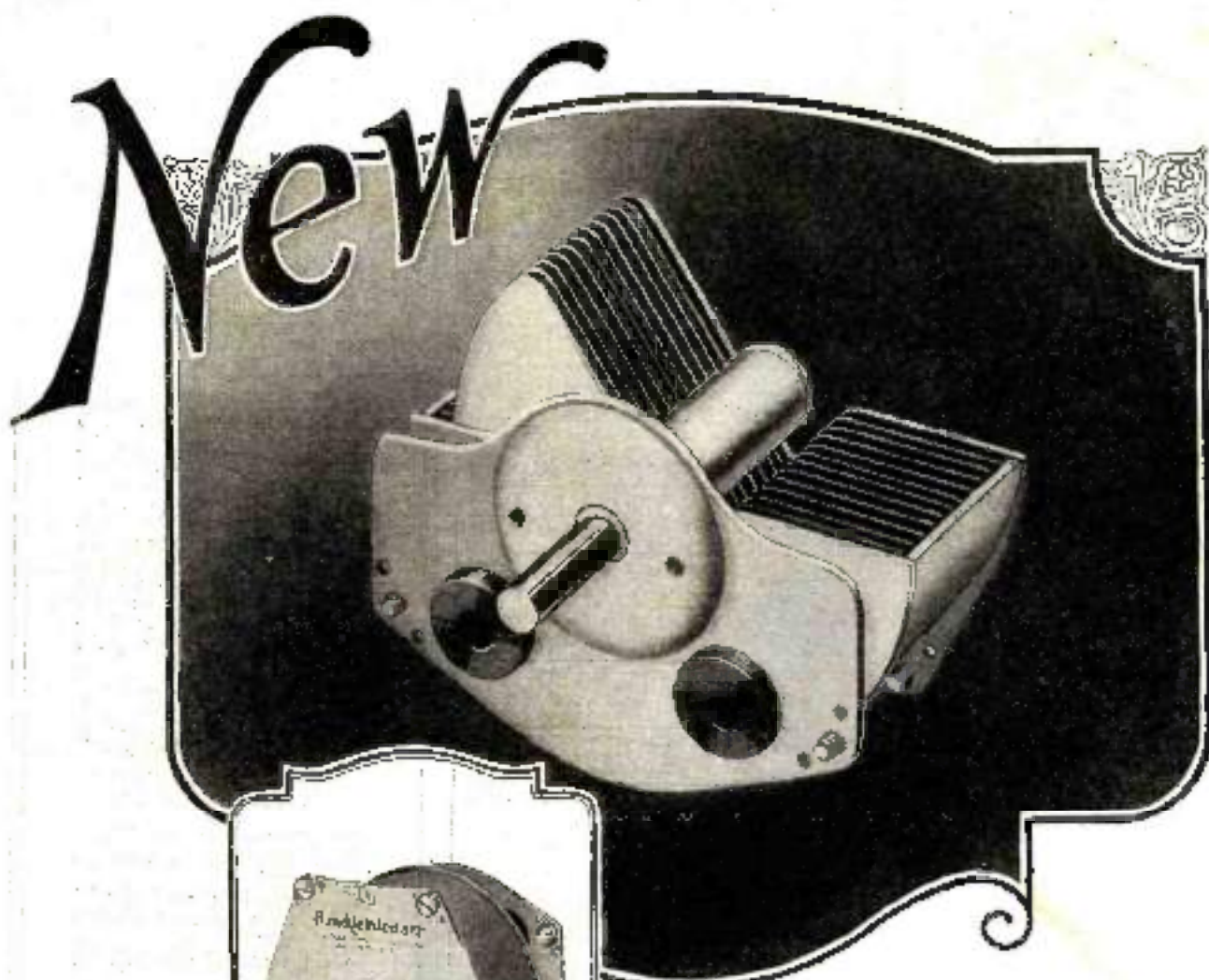INSIDE-AERIAL
DISTANCE-SELECTIVE-NO-T-A-LOOP
NOT AFFECTED BY WIND, RAIN, SNOW OR LIGHTNING
CERTIFICATE OF APPROVAL by one of the leading Radio Laboratories
PRICE 5 PORTLAND IN 1/2 IN. and 1/4 IN. SIZES
Write for details and prices
UNITED STATES SIGNAL CO. Dept. 4 432, CHICAGO



The Bradleydenser

PERFECT VARIABLE CONDENSER

Brass Plates—Grounded Rotor—Low Loss

PERFECTION to the last detail! Even the unique bearing of the new Bradleydenser is a marked improvement over the older types. The rugged brass plates, the grounded rotor construction, and the new detachable dust shield are other details that serve to increase the high-frequency efficiency of the Bradleydenser. Exhaustive laboratory tests reveal exceptional improvements in efficiency. In fact, the Bradleydenser sets a new low record for losses. It tunes the weakest oscillations with the least energy loss, and, therefore, increases the range of any set. There are many other new and striking features of the Bradleydenser. Our new literature explains them, fully. Send for our latest bulletin on the Bradleydenser today.

Standard Capacities

0.00025 M-F . . .	\$4.50
0.0005 M-F . . .	5.00
0.001 M-F . . .	6.00

Furnished without vernier plates, only.

Allen-Bradley Co.

Electric Controlling Apparatus

287
Greenfield
Ave.



Milwaukee,
Wis.

Standard Carton

The Bradleydenser is sold in the well-known Allen-Bradley checkered box by all leading radio dealers and jobbers.

Baltimore
Birmingham
Boston

Buffalo
Chicago
Cincinnati

Cleveland
Denver
Detroit

Knoxville
Los Angeles
New York

Philadelphia
Pittsburgh
Saint Louis

St. Paul
San Francisco
Seattle


THE PERIODICAL PRESS, NEW YORK



The New Bradleystat

A Remarkable Achievement

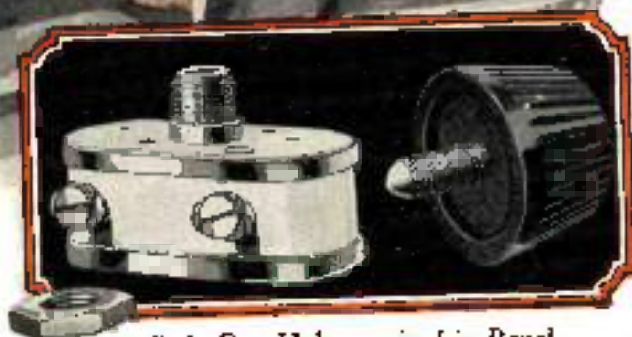Many refinements are embodied in the new Bradleystat. The graphite disc controls are enclosed in a smaller container; two terminals suffice for ALL poles; a new mounting simplifies installation, the knob is of a daintier pattern. And the new, stepless, control of the old Bradleystat remains unchanged. Such a combination of advantages can be found in no other element thereof.



Only One Hole required in Panel

Every radio set can be improved by substituting the new Allen-Bradley radio devices.



Ask your radio dealer about the new Allen-Bradley line

A DISTINCTLY new and valuable contribution to radio! That is the verdict of all radio engineers and designers who have seen the new Allen-Bradley radio devices and have witnessed their amazing performance. The new "one-hole mounting," which replaces the older clip mounting, makes for marvelous compactness and simplicity of installation. The new Bradleystat, Bradleyleak and Bradleyohm require only a 11/16-inch space behind the panel, and the Bradleyometer only 7/8-inch. Thus, the new models can replace inferior wire rheostats and potentiometers without disturbing the arrangement of the set. Our new literature is ready. Send for it, today!

Allen-Bradley Co.
Electric Controlling Apparatus

287
Greenfield
Ave.



Milwaukee,
Wis.

Baltimore
Birmingham
Boston

Buffalo
Chicago
Cincinnati

Cleveland
Denver
Detroit

Kansas City
Los Angeles
New York

Philadelphia
Pittsburgh
St. Louis

San Paul
San Francisco
Seattle



"Are those Tubes Genuine?"

All Radiotrons Now
Reduced to \$4.00

It isn't a genuine WD-11
unless it's a Radiotron.
It isn't a genuine WD-12
unless it's a Radiotron.
It isn't a genuine UV-199
unless it's a Radiotron.
It isn't a genuine UV-200
unless it's a Radiotron.
It isn't a genuine UV-201-a
unless it's a Radiotron.

The question is heard at every radio counter: "Is it a genuine Radiotron?" Almost every dependable manufacturer uses genuine Radiotrons in his sets. Everyone who builds his own knows enough about radio to know that nothing else but the genuine will do. And the man who replaces used-up tubes in his set knows that to get the same performance, he must have the same tubes—genuine Radiotrons only. So everybody asks "Is it genuine?" And asks to see the marks that prove it—the name "Radiotron" and the "RCA" mark.



This symbol of
quality is your
protection.

Radio Corporation of America

233 Broadway, New York

Sales Office

10 So. La Salle St., Chicago, Ill.

433 California St., San Francisco, Cal.

Radiotron

REG. U. S. PAT. OFF.